



**Department of Computer Science
Faculty of Computing
UNIVERSITI TEKNOLOGI MALAYSIA**

SUBJECT NAME: **DIGITAL LOGIC**
SUBJECT CODE: **SECR1013**
SEMESTER: **1**
LAB TITLE: **LAB 1: COMBINATIONAL LOGIC**

GROUP MEMBER : **1. Name: HARCHANA A/P ARULAPPAN**
Email: harchana@graduate.utm.my
2. Name: NASRUL AMIN BIN AB HADI
Email: nasrulamin@graduate.utm.my

SUBMITTED DATE: 29 / 11 / 2021

COMMENTS:

MARKS:

Lab # 1



**Department of Computer Science
Faculty of Computing
UNIVERSITI TEKNOLOGI MALAYSIA**

SUBJECT : SCSR1013 DIGITAL LOGIC

SESSION/SEM : 01 / SEM 1

LAB 1 : COMBINATIONAL LOGIC

NAME 1 : HARCHANA A/P ARVLAPPAN (A21EC0028)

NAME 2 : NASRVL AMIN BIN AB. HADI (A21EC0099)



DATE : 27 NOVEMBER 2021

REMARKS :


MARKS:

D. Preliminary Work

1. Draw a symbol, determine the IC number and produce a truth table for the following gate.
  
<u>AND</u>	<u>NAND</u>																																				
Symbol:	Symbol:																																				
																																					
IC Number: 7408	IC Number: 7400																																				
Truth Table 1	Truth Table 2																																				
<table border="1" style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th colspan="2" style="text-align: center;">Input</th><th style="text-align: center;">Output</th></tr> <tr> <th style="text-align: center;">A</th><th style="text-align: center;">B</th><th style="text-align: center;">F</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	Input		Output	A	B	F	0	0	0	0	1	0	1	0	0	1	1	1	<table border="1" style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th colspan="2" style="text-align: center;">Input</th><th style="text-align: center;">Output</th></tr> <tr> <th style="text-align: center;">A</th><th style="text-align: center;">B</th><th style="text-align: center;">F</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	Input		Output	A	B	F	0	0	1	0	1	1	1	0	1	1	1	0
Input		Output																																			
A	B	F																																			
0	0	0																																			
0	1	0																																			
1	0	0																																			
1	1	1																																			
Input		Output																																			
A	B	F																																			
0	0	1																																			
0	1	1																																			
1	0	1																																			
1	1	0																																			

 
2. Complete the truth table for the following circuit.



Truth Table 3

A	B	C	F
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

 3. Write the Boolean expression for output C, D and F the following circuit.



$$C = A\bar{B}$$

$$D = \bar{A}B$$

$$F = (A\bar{B}) + (\bar{A}B)$$

4. Complete the truth table for the circuit in (3) based on the Boolean expression produced for C, D and F.

Truth Table 4


A	B	C	D	F
0	0	0	0	0
0	1	0	1	1
1	0	1	0	1
1	1	0	0	0

E. Laboratory Work

Part 1

1. Construct Circuit 1 on the breadboard. Connect all inputs (A, B) to a switches and output F to LEDs.

Truth Table 5

 

Circuit 1

Input		Output
A	B	F
0	0	0
0	1	0
1	0	0
1	1	1



Fully Completed


Partially Completed

Checked by: _____

Part 2

3. Construct Circuit 2 on the breadboard. Connect all inputs (A, B) to a switches and output C and F to LEDs.

Truth Table 6

 

Circuit 2

A	B	C	F
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

4. Test Circuit 2; fill in Truth Table 6, for the circuit response to all possible input combinations.

5. Compare Truth Table 6 to Truth Table 2. What conclusion can you make?

Both of the truth table have the same output. If all or any of the input are Low, then the output is high. If all of the input are high, then the output is Low.




Fully Completed

Partially Completed

Checked by: _____

Part 3

 6. Construct circuit 3 on the breadboard. Connect all inputs (A, B) to a switches and output C, D and F to LEDs.



Truth Table 7

A	B	C	D	F
0	0	0	0	0
0	1	0	1	1
1	0	1	0	1
1	1	0	0	0

Circuit 3

7. Test Circuit 3; fill in Truth Table 7 for the circuit outputs (C, D, and F) for all possible input combinations.

8. What single gate does Circuit 3 represent?

XOR Gate ,



Fully
Completed

Partially
Completed

Checked by: _____