



Department of Computer Science
Faculty of Computing
UNIVERSITI TEKNOLOGI MALAYSIA

SUBJECT NAME: DIGITAL LOGIC

SUBJECT CODE: SECR1013-01

SEMESTER: 2021/2022

LAB TITLE: LAB 1: COMBINATIONAL LOGIC

GROUP MEMBER : 1. Name: NOOR HANNANI SYAMIMI BINTI MOHD SUFFIAN

Email: noorhannanisyamimi@graduate.utm.my

2. Name: THUVAARITHA SIVARAJAH

Email: thuvaaritha@graduate.utm.my

SUBMITTED DATE: _____


COMMENTS:

MARKS:


Lab # 1

D. Preliminary Work

1. Draw a symbol, determine the IC number and produce a truth table for the following gate.
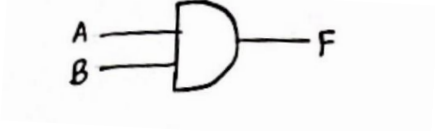
<u>AND</u>	<u>NAND</u>																																				
Symbol: 	Symbol: 																																				
IC Number: 7408	IC Number: 7400																																				
Truth Table 1	Truth Table 2																																				
<table border="1"><thead><tr><th colspan="2">Input</th><th>Output</th></tr><tr><th>A</th><th>B</th><th>F</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></tbody></table>	Input		Output	A	B	F	0	0	0	0	1	0	1	0	0	1	1	1	<table border="1"><thead><tr><th colspan="2">Input</th><th>Output</th></tr><tr><th>A</th><th>B</th><th>F</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></tbody></table>	Input		Output	A	B	F	0	0	1	0	1	1	1	0	1	1	1	0
Input		Output																																			
A	B	F																																			
0	0	0																																			
0	1	0																																			
1	0	0																																			
1	1	1																																			
Input		Output																																			
A	B	F																																			
0	0	1																																			
0	1	1																																			
1	0	1																																			
1	1	0																																			

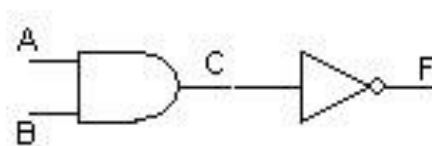
2. Complete the truth table for the following circuit.



Truth Table 3

A	B	C	D
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

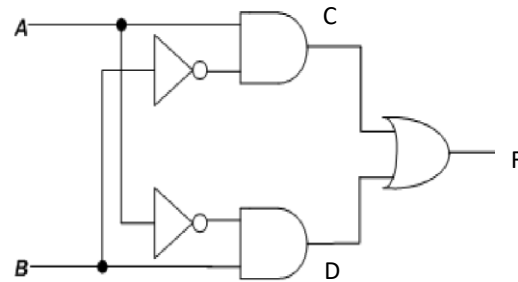3. Write the Boolean expression for output C, D and F in the following circuit.



$$C = A\bar{B}$$

$$D = \bar{A}B$$

$$F = A\bar{B} + \bar{A}B$$

4. Complete the truth table for the circuit in (3) based on the Boolean expression produced for C, D and F.

Truth Table 4

A	B	C	D	F
0	0	0	0	0
0	1	0	1	1
1	0	1	0	1
1	1	0	0	0

E. Laboratory Work

Part 1

1. Construct Circuit 1 on the breadboard. Connect all inputs (A, B) to a switch and output F to LEDs.



Truth Table 5

Input		Output
A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

2. Test circuit 1 and fill in Truth Table 5 for the circuit response to all possible input combinations. The Truth Table 5 should match the Truth Table 1 prepared in the Preliminary Work.



Fully
Completed

☐


Partially
Completed

☐

Checked by: _____

Part 2

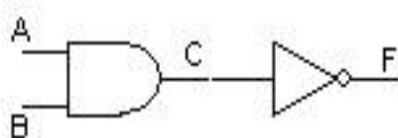3. Construct Circuit 2 on the breadboard. Connect all inputs (A, B) to a switch and output F to LEDs.



Truth Table 6

A	B	C	F
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

4. Test Circuit 2, fill in Truth Table 6, for the circuit response to all possible input combinations.
5. Compare Truth Table 6 to Truth Table 2. What conclusion can you make?

Truth Table 6 matches Truth Table 2. Both logic circuits are equivalent.



Fully
Completed

☐


Partially
Completed

☐

Checked by: _____

Part 3

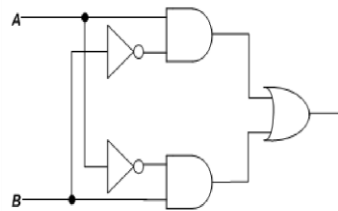6. Construct circuit 3 on the breadboard. Connect all inputs (A, B) to a switch and output C, D and F to LEDs.



Truth Table 7

A	B	C	D	F
0	0	0	0	0
0	1	0	1	1
1	0	1	0	1
1	1	0	0	0

7. Test Circuit 3, fill in Truth Table 7 for the circuit outputs (C, D and F) for all possible input combinations.
8. What single gate does Circuit 3 represent?

XOR Gate



Fully
Completed

☐

Partially
Completed

☐

Checked by: _____