



**UTM**  
UNIVERSITI TEKNOLOGI MALAYSIA

*M. Afendi M. Piah, PhD*

[www.utm.my](http://www.utm.my)

# Circuit Theory (SKEE 1023)

**Assoc. Prof. Dr. Mohamed Afendi Mohamed Piah**

**Institute of High Voltage & High Current  
Faculty of Electrical Engineering, UTM**

## Circuit Theory

### Topics

- ❖ **Basic Laws:** Ohm's law; Nodes, Branches and Loops; Kirchhoff's Law; Series-parallel resistors; Voltage and Current Division.

# Circuit Theory

## Basic Laws

**Ohm's law** states that the voltage  $v$  across a resistor is directly proportional to the current  $i$  flowing through the resistor.

The **resistance**  $R$  of an element denotes its ability to resist the flow of electric current, it is measured in ohms ( $\Omega$ )

Ohm's  
Law


$$I = \frac{V}{R}$$

Electric current = Voltage / Resistance


Value of  $R$  can range from zero to infinity, which are the two extreme possible values of  $R$  ( $0$  and  $\infty$ ).



# Circuit Theory

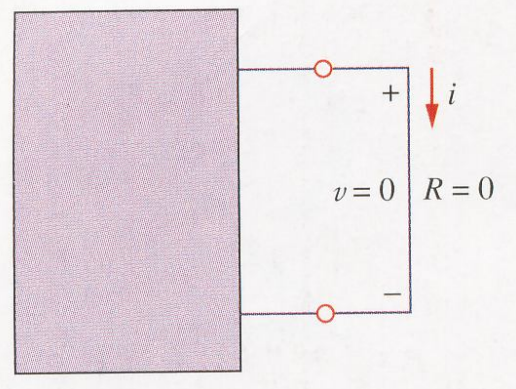

short  
circuit

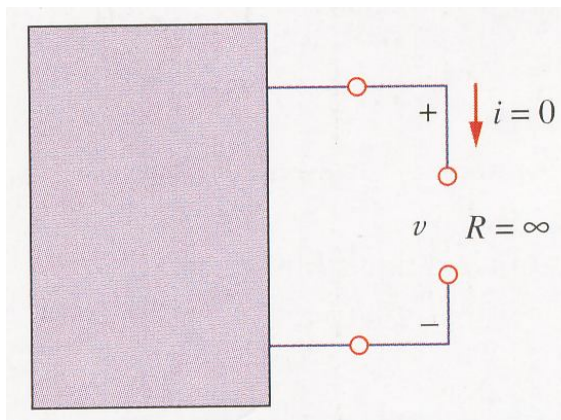

open  
circuit

- A short circuit is a circuit element with resistance approaching zero.
- An open circuit is a circuit element with resistance approaching infinity.
- The reciprocal of resistance, known as *conductance* and denoted by  $G$ ;

$$G = \frac{1}{R} = \frac{i}{v}$$

- Conductance is the ability of an element to conduct electric current; it is measured in mhos or siemens (S).




# Circuit Theory

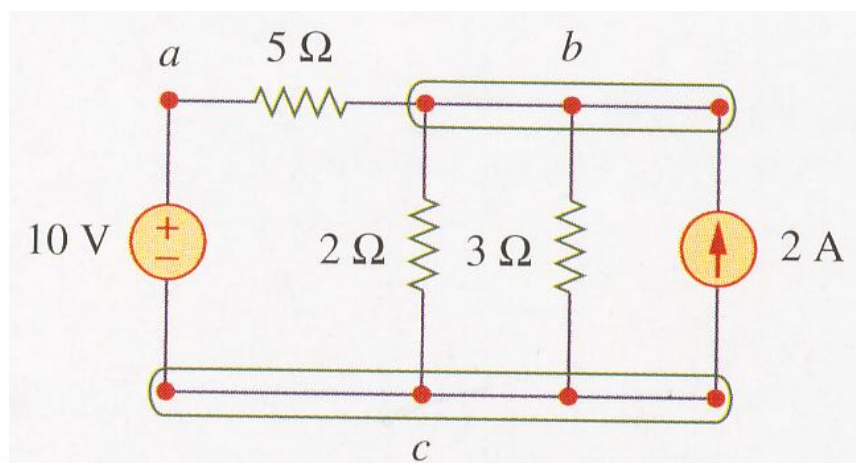
## Nodes, Branches and Loops

To understand some basic concepts of network topology. A **network** – as an interconnection of elements/devices. A **circuit** is a network providing one or more closed path.

- ❑ A **branch** represents a single element such as voltage/current source or a resistor.
- ❑ A **node** is the point of connection between two or more branches.
- ❑ A **loop** is any closed path in a circuit.



# Circuit Theory

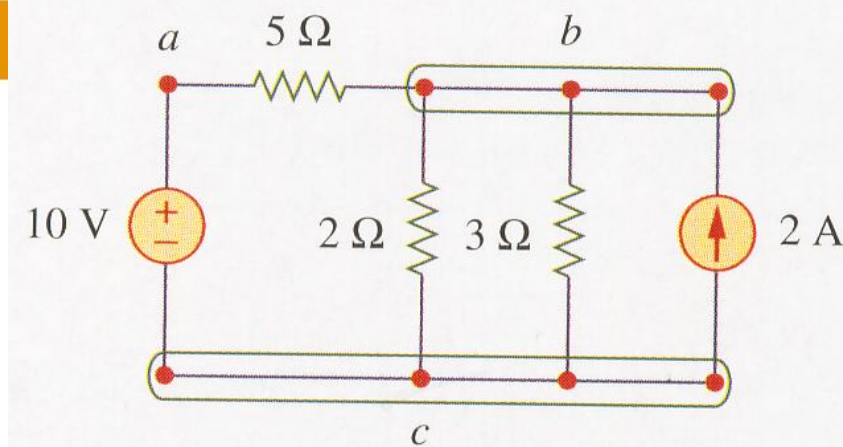


Fundamental theorem of network topology:

$$b = l + n - 1$$

$b$  : branches

$n$  : nodes


$l$  : independent loops

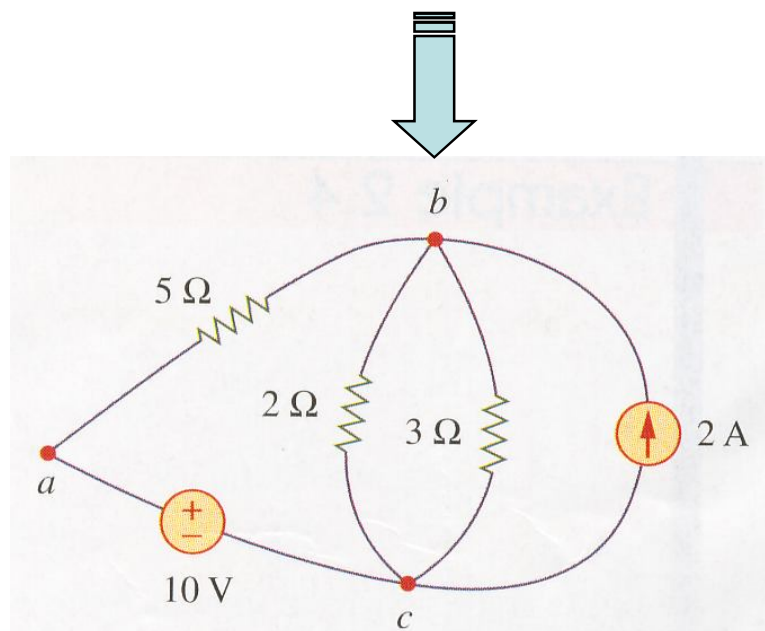

# Circuit Theory

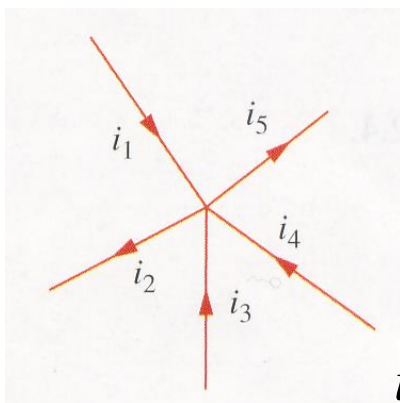
## Kirchhoff's Laws

- Introduced in 1847 by the German physicist Gustav Robert Kirchhoff (1824-1887). The laws are formally known as Kirchhoff's current law (KCL) and Kirchhoff's voltage law (KVL).
- Kirchhoff's current law (KCL)** states that the algebraic sum of currents entering a node (or a closed boundary) is zero.



$$i_1 + i_3 + i_4 = i_2 + i_5$$

$$\sum_{n=1}^N i_n = 0$$

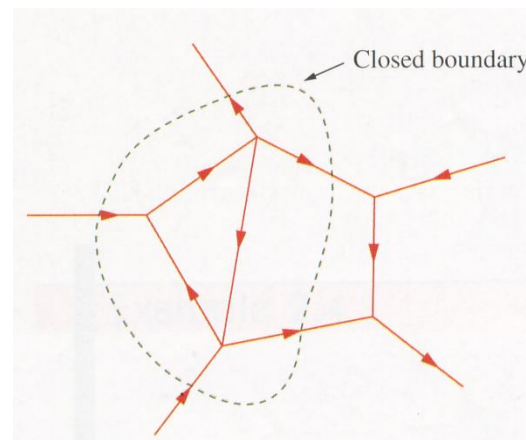

The sum of the currents entering a node is equal to the sum of the currents leaving the node.

# Circuit Theory


## Kirchhoff's Laws

- Kirchhoff's voltage law (KVL) states that the algebraic sum of all voltages around a closed path (or loop) is zero.

$$\sum_{m=1}^M v_m = 0$$

$$-v_1 + v_2 + v_3 - v_4 + v_5 = 0$$
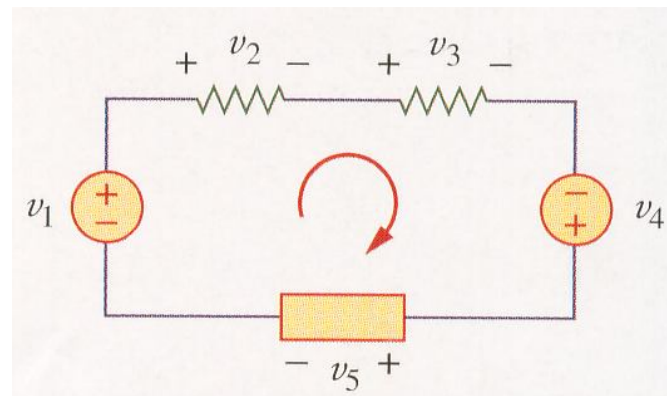
$$\therefore v_2 + v_3 + v_5 = v_1 + v_4$$



Sum of voltage drops = Sum of voltage rises




# Circuit Theory
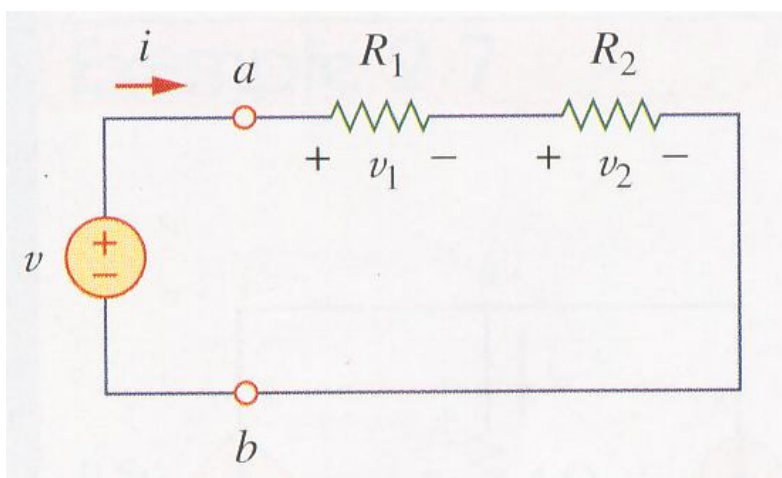
## Series Resistors and Voltage Division

- ❑ The **equivalent resistance** of any number of resistors **connected in series** is the sum of the individual resistances
- ❑ For N resistors in series, then;

$$R_{eq} = R_1 + R_2 + \dots + R_N = \sum_{n=1}^N R_n$$



$$v_1 = \frac{R_1}{R_1 + R_2} v ; \quad v_2 = \frac{R_2}{R_1 + R_2} v$$

For N resistors in series;

$$v_n = \frac{R_n}{R_1 + R_2 + \dots + R_N} v$$

**Principle of voltage division**

## Circuit Theory

### Parallel Resistors and Current Division

- The **equivalent resistance** of two parallel resistors is equal to the product of their resistances divided by their sum.

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} ; \quad R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

- For the circuit with  $N$  resistors in parallel.

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$


in terms of conductance ( $G$ );

$$G_{eq} = G_1 + G_2 + G_3 + \dots + G_N$$

The equivalent conductance of resistors connected in parallel is the sum of their individual conductances.

# Circuit Theory
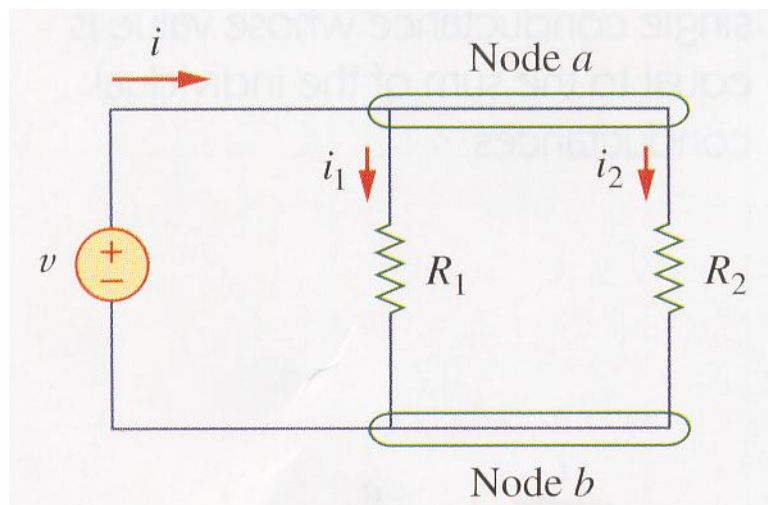
## Parallel Resistors and Current Division



$$i_1 = \frac{R_2}{R_1 + R_2} i ; \quad i_2 = \frac{R_1}{R_1 + R_2} i$$

*Principle of current division*



- If a current divider has  $N$  conductors ( $G_1, G_2, \dots, G_N$ ) in parallel with the source current  $i$ , the  $n$ th conductor ( $G_n$ ) will have current;

$$i_n = \frac{G_n}{G_1 + G_2 + \dots + G_N} i$$


# Circuit Theory
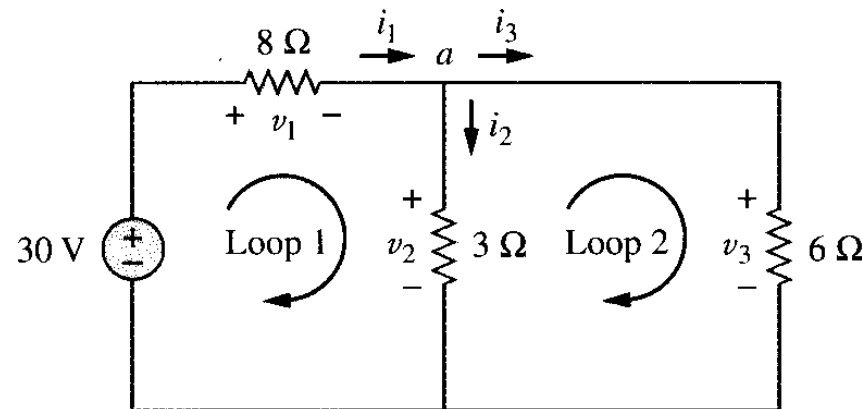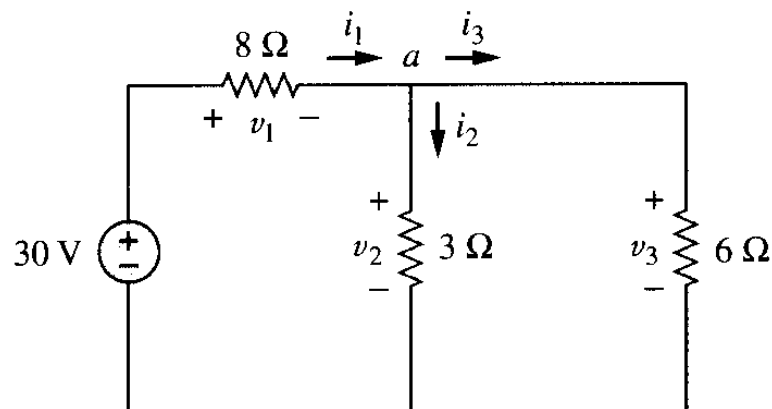
## Examples and Problems

- Find currents and voltages in the circuit below.




- Find  $v_o$  and  $i_o$ .

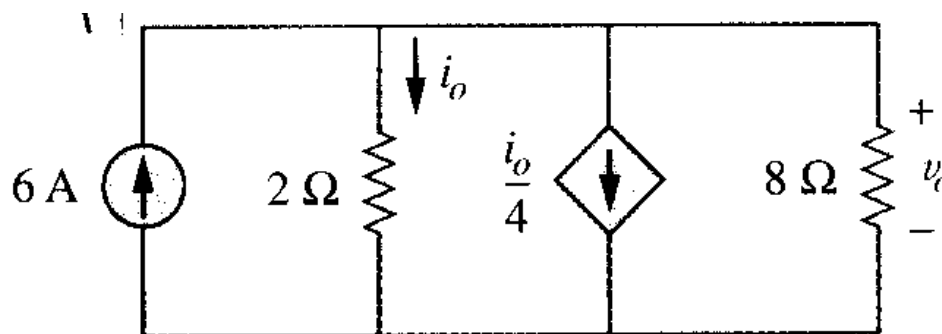




## Circuit Theory

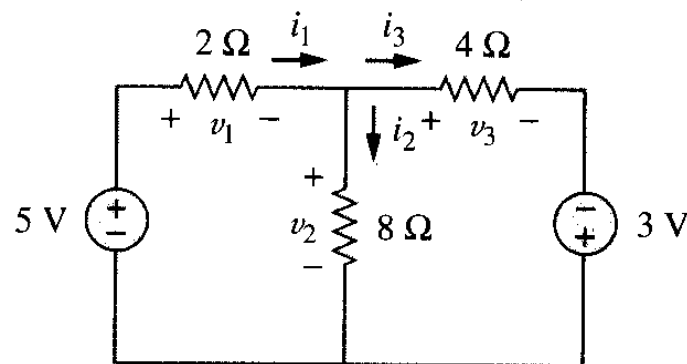3. Find currents and voltages in the circuit below.



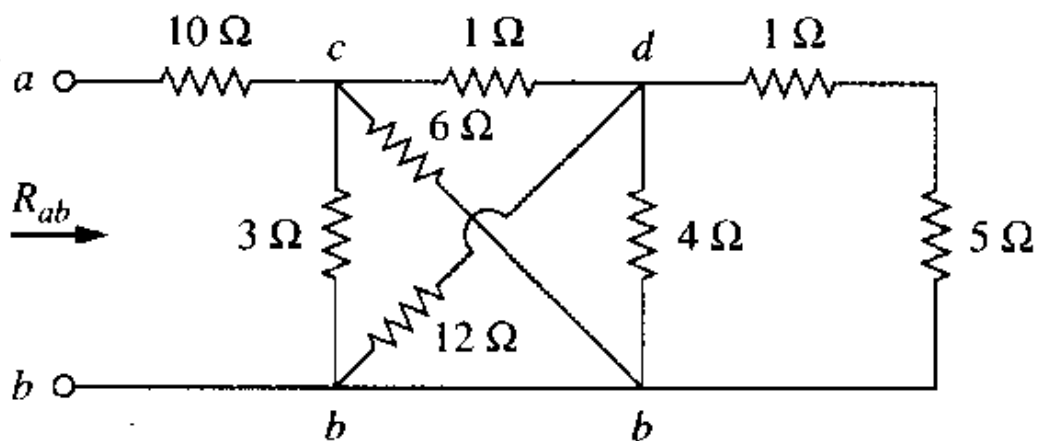4. Calculate the equivalent resistance  $R_{ab}$ .








## Circuit Theory

5. Find  $R_{ab}$ .

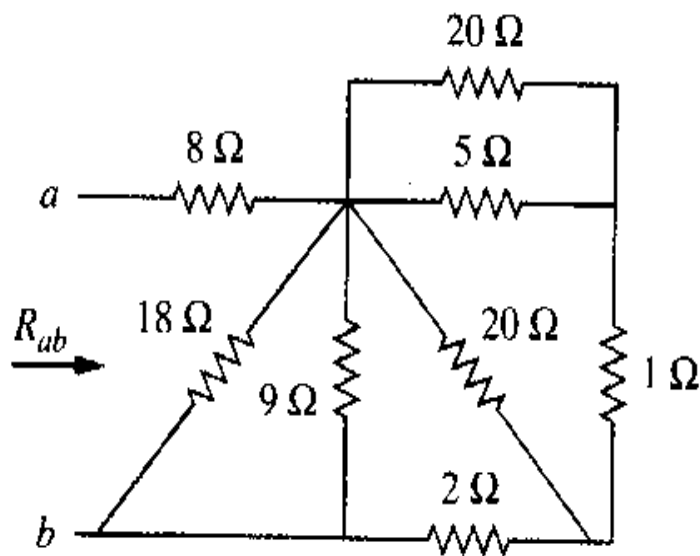

## Circuit Theory

6. Find  $v_1$  and  $v_2$  in the circuit shown in Fig. 2.43. Also calculate  $i_1$  and  $i_2$  and the power dissipated in the  $12\text{-}\Omega$  and  $40\text{-}\Omega$  resistors.

**Answer:**  $v_1 = 5\text{ V}$ ,  $i_1 = 416.7\text{ mA}$ ,  $p_1 = 2.083\text{ W}$ ,  $v_2 = 10\text{ V}$ ,  $i_2 = 250\text{ mA}$ ,  $p_2 = 2.5\text{ W}$ .

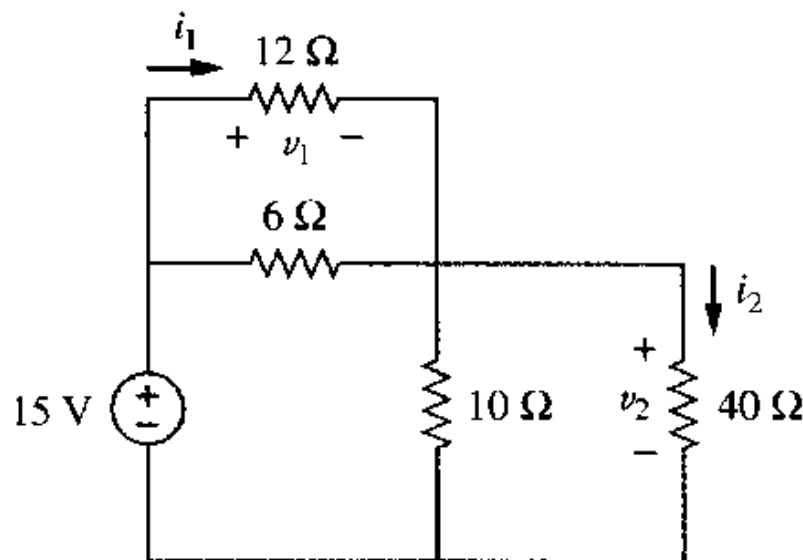


Fig 2.43

## Circuit Theory

7. For the circuit shown in Fig. 2.45, find: (a)  $v_1$  and  $v_2$ , (b) the power dissipated in the 3-k $\Omega$  and 20-k $\Omega$  resistors, and (c) the power supplied by the current source.

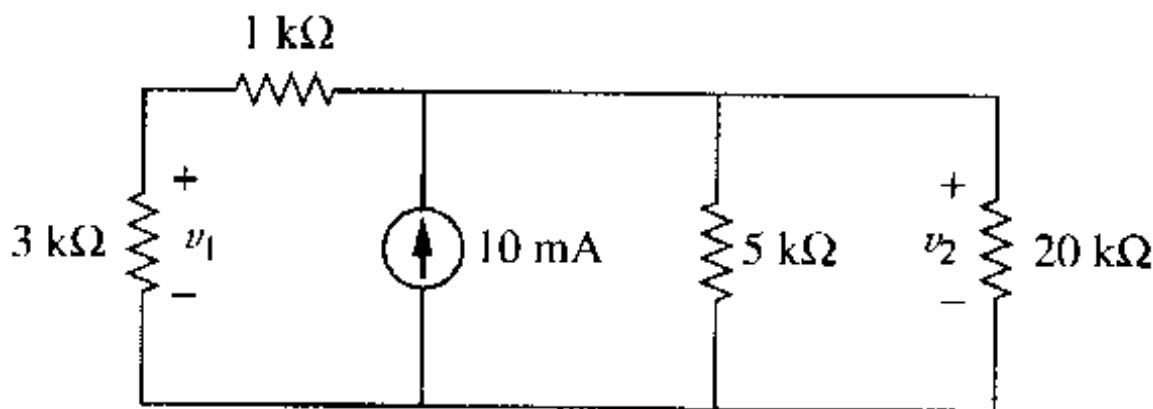




Fig. 2.45

**Answer:** (a) 15 V, 20 V, (b) 75 mW, 20 mW, (c) 200 mW.



# Circuit Theory
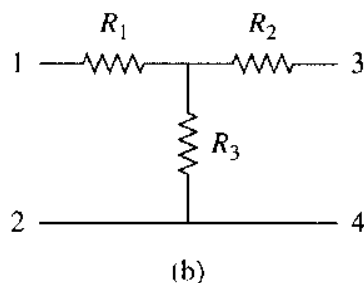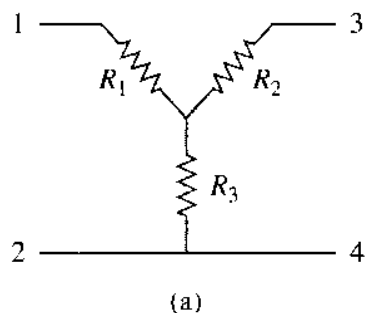
## Wye-Delta Transformations

- Situations often arise in circuit analysis when the resistors are neither in parallel nor in series.
- Two types of network, i.e. **wye** and **delta**.



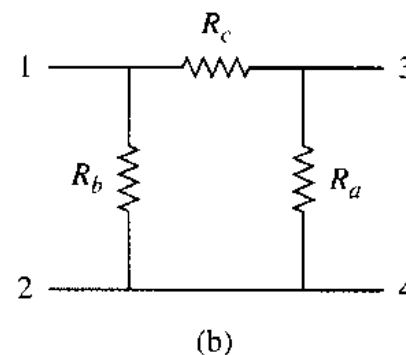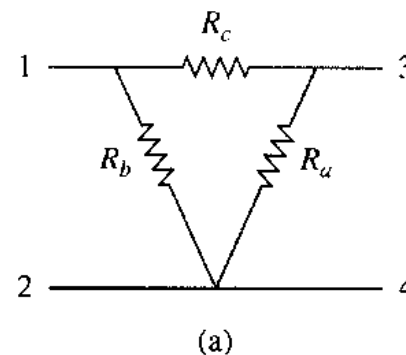Two forms of the same network: (a) Y, (b) T.



Two forms of the same network: (a)  $\Delta$ , (b)  $\Pi$ .



## Circuit Theory

### Delta to Wye (star) Conversion

$$R_{12}(Y) = R_1 + R_3 \quad \text{and} \quad R_{12}(\Delta) = R_b // (R_a + R_c)$$

Setting  $R_{12}(Y) = R_{12}(\Delta)$ , gives;

$$R_{12} = R_1 + R_3 = \frac{R_b(R_a + R_c)}{R_a + R_b + R_c}$$

Similarly;

$$R_{13} = R_1 + R_2 = \frac{R_c(R_a + R_b)}{R_a + R_b + R_c}$$

$$R_{34} = R_2 + R_3 = \frac{R_a(R_b + R_c)}{R_a + R_b + R_c}$$

Therefore;

$$R_1 - R_2 = \frac{R_c(R_b - R_a)}{R_a + R_b + R_c}$$






## Circuit Theory

Finally, for delta to Y (star) conversion;

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$
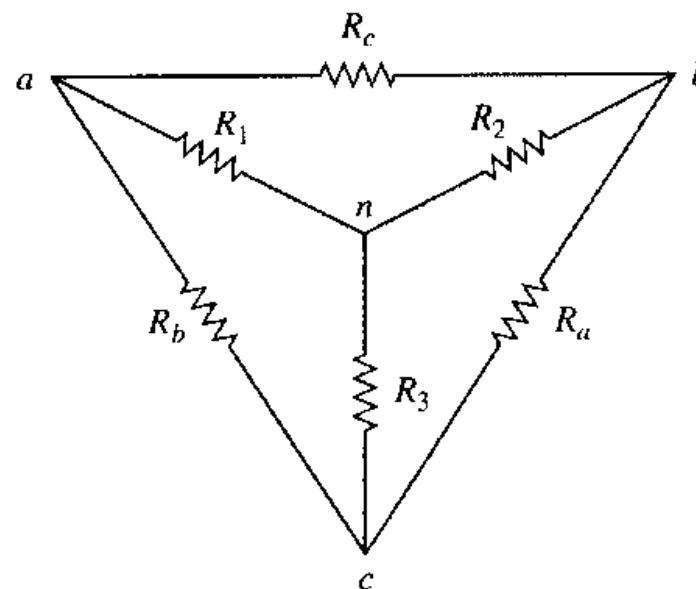
$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$



Each resistor in the Y network is the product of the resistors in the two adjacent  $\Delta$  branches, divided by the sum of the three  $\Delta$  resistors.

# Circuit Theory


## Wye (star) to Delta Conversion

By using the equations of  $R_1, R_2$  &  $R_3$ ;

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_a R_b R_c (R_a + R_b + R_c)}{(R_a + R_b + R_c)^2}$$

$$= \frac{R_a R_b R_c}{R_a + R_b + R_c}$$

Therefore;

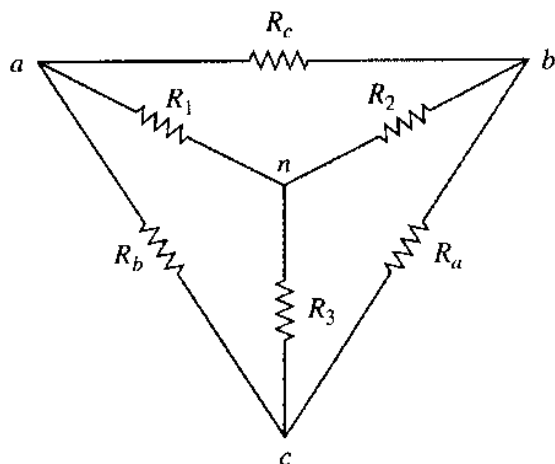

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

Each resistor in the  $\Delta$  network is the sum of all possible products of Y resistors taken two at a time, divided by the opposite Y resistor.

# Circuit Theory

The Y and  $\Delta$  networks are said to be *balanced* when.

$$R_1 = R_2 = R_3 = R_Y, \text{ and } R_a = R_b = R_c = R_{\Delta}$$


Under these conditions, conversion formulas become

$$R_Y = \frac{R_{\Delta}}{3}, \text{ or } R_{\Delta} = 3R_Y$$

## Problem


For the bridge network shown in the figure, find  $R_{ab}$  and  $i$ .

Ans: 40 $\Omega$ , 2.5A

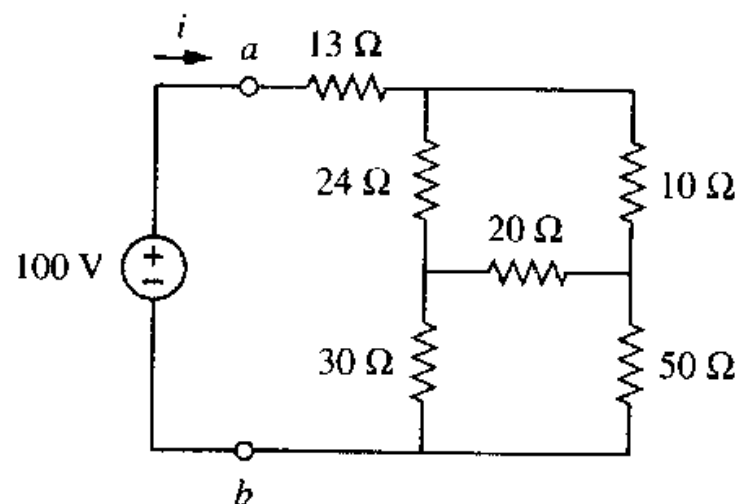

# Circuit Theory

## Source Transformations

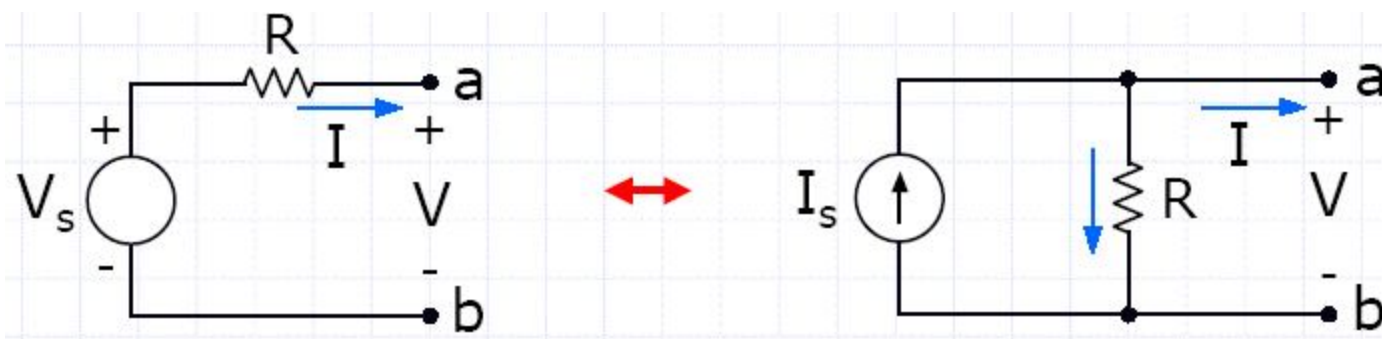

- If the two networks are equivalent with respect to terminals ab, then  $V$  and  $I$  must be identical for both networks. Thus,

$$V_s = I_s R, \text{ or } I_s = \frac{V_s}{R}$$

# Circuit Theory

## Problem

By using the method of source transformations, find  $v_x$ .

