



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

M. Afendi M. Piah, PhD

www.utm.my

Circuit Theory (SKEE 1023)

Assoc. Prof. Dr. Mohamed Afendi Mohamed Piah

**Institute of High Voltage & High Current
Faculty of Electrical Engineering, UTM**



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

www.utm.my

M. Afendi M. Piah, PhD

Circuit Theory

Topics

- ❖ Linearity Property, Superposition, Source Transformation, Thevenin and Norton Theorem.



Circuit Theory

Linearity Property

- Linearity is the property of an element describing a linear relationship between cause and effect.
- Combination of both homogeneity (scaling) property and the additivity property.
- E.g. Resistor is a linear element because the voltage-current relationship satisfies both the homogeneity and the additivity properties.
- A linear circuit consists of only linear elements, linear dependent source and independent sources.

Circuit Theory

Linearity Property

Example 4.1

Solution:

Applying KVL to the two loops, we obtain

$$12i_1 - 4i_2 + v_s = 0$$

$$-4i_1 + 16i_2 - 3v_x - v_s = 0$$

But $v_x = 2i_1$. Equation (4.1.2) becomes

$$-10i_1 + 16i_2 - v_s = 0$$

Adding Eqs. (4.1.1) and (4.1.3) yields

$$2i_1 + 12i_2 = 0 \Rightarrow i_1 = -6i_2$$

Substituting this in Eq. (4.1.1), we get

$$-76i_2 + v_s = 0 \Rightarrow i_2 = \frac{v_s}{76}$$


When $v_s = 12$ V,

$$I_o = i_2 = \frac{12}{76} \text{ A}$$

When $v_s = 24$ V,

$$I_o = i_2 = \frac{24}{76} \text{ A}$$

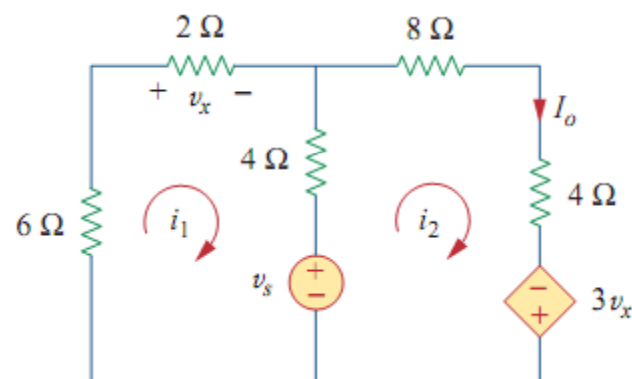showing that when the source value is doubled, I_o doubles.





Circuit Theory

Superposition Theorem

- The voltage across (or current through) an element in a linear circuit is the algebraic sum of the voltages across (or currents through) that element due to each independent source acting alone.
- Combination of both **homogeneity (scaling)** property and the **additivity** property. Applicable to linear circuit only.
- One of the method to solve the circuit with two or more independent sources.
- The number of analysis depend on how many independent sources does the circuit has.



Circuit Theory

Superposition Theorem

Steps to apply Superposition theorem/principle.

1. Choose one independent source and eliminate (turn-off) the effect of other independent sources. [*Voltage source* \Rightarrow short-circuit ; *Current source* \Rightarrow open-circuit]
2. Start the analysis using any circuit analysis methods/techniques and theorems. [KCL, KVL, nodal/mesh analysis, etc]
3. Start the analysis using any circuit analysis methods/techniques and theorems. [KCL, KVL, nodal/mesh analysis, etc]
4. Combine/add-ups all the value of each element for all separated analysis.



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

www.utm.my

M. Afendi M. Piah, PhD

Circuit Theory

Superposition Theorem

- This technique does **not allow to find power** at any separated circuit.
- This technique has one major disadvantage; it may very likely **involve more work**.
- However superposition does help reduce a complex circuit to a simpler circuit.
- Combine/add-ups all the value of each element for all separated analysis.

Circuit Theory

Superposition Theorem

Problem 4.1:

Using the superposition theorem, find v_o in the circuit of Fig. P4.1. (Ans: 6 V)

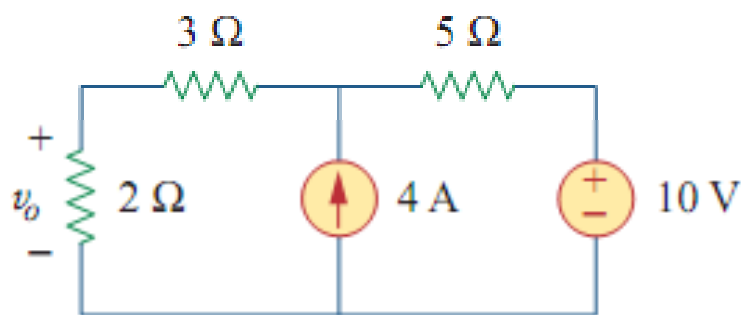



Fig. P4.1

Circuit Theory

Superposition Theorem

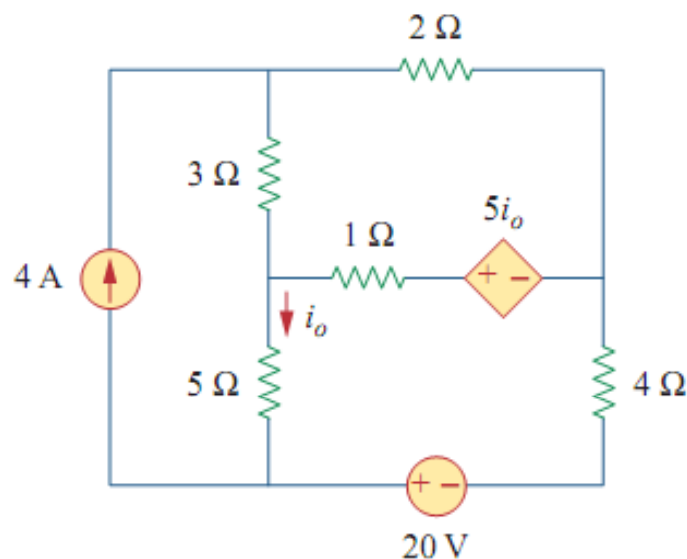Example 4.2:

Find i_o in the circuit using superposition theorem.






Circuit Theory

Superposition Theorem


The circuit involves a dependent source, which must be left intact. The i_o is given by;

$$i_o = i_o' + i_o''$$

How to find i_o' ?

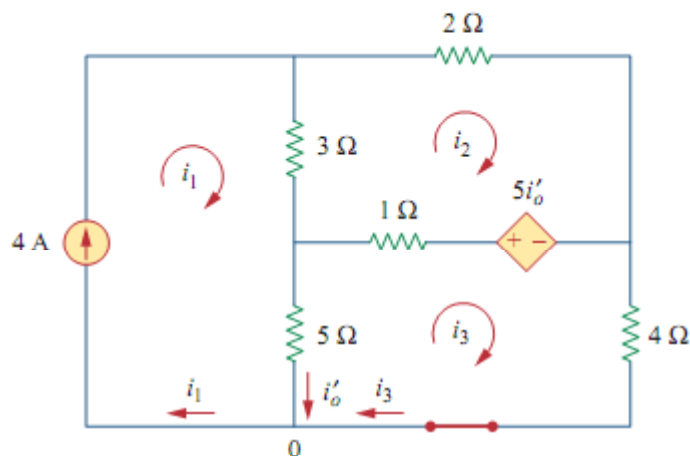

How to find i_o'' ?

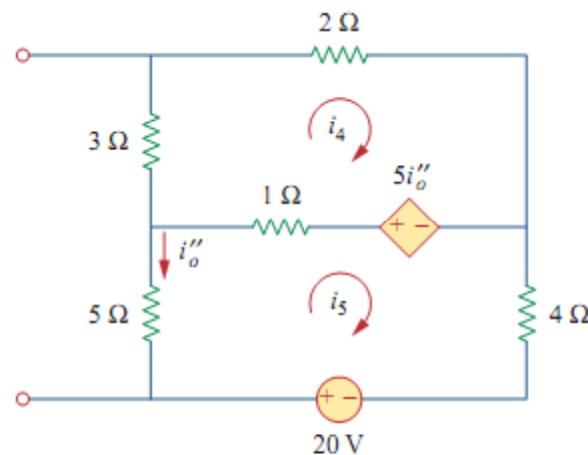

Circuit Theory

Superposition Theorem

Problem 4.2:

Use superposition to find v_x in the circuit of Fig. P4.2. (Ans: 25 V)


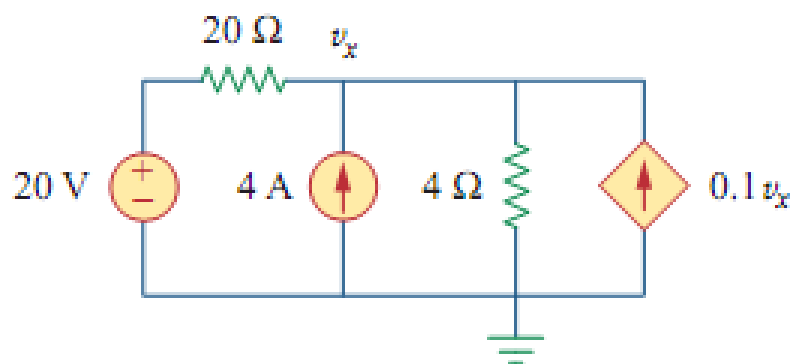
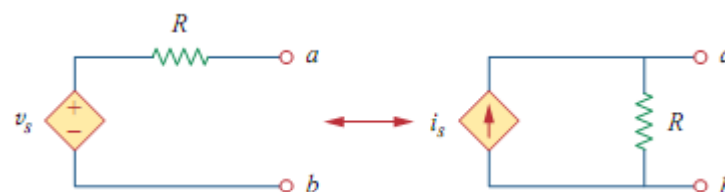


Fig. P4.2

Circuit Theory

Source Transformation

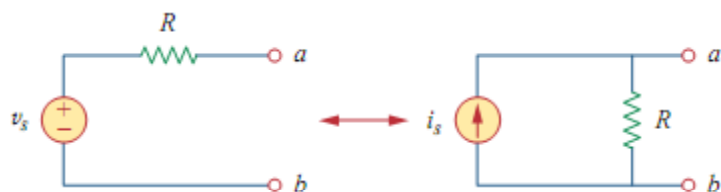- A source transformation is the process of replacing a voltage source V_s in series with a resistor R by a current source I_s in parallel with a resistor R , or vice versa.




$$v_s = i_s R \quad \text{or} \quad i_s = \frac{v_s}{R}$$



Circuit Theory

Thevenin's Theorem

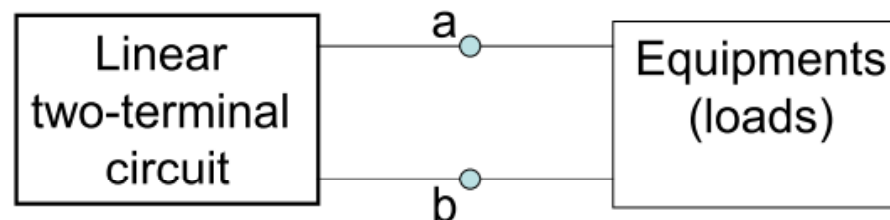
- Objective : To simplify the circuit.
- Provides a technique by which the fixed part of the circuit is replaced by an equivalent circuit.
- Developed in 1883 by M. Leon Thevenin (1857–1926), a French telegraph engineer.
- When the load are varies, all the variables (voltage & current) inside the linear circuit would also varies, thus the analysis has to be done again.




Circuit Theory

Thevenin's Theorem

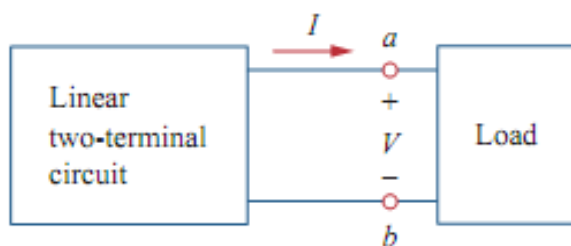- Thevenin's theorem states that a linear 2-terminal circuit can be replaced by an **equivalent circuit** consisting of a **voltage source** V_{Th} in series with a **resistor** R_{Th} .



(a)

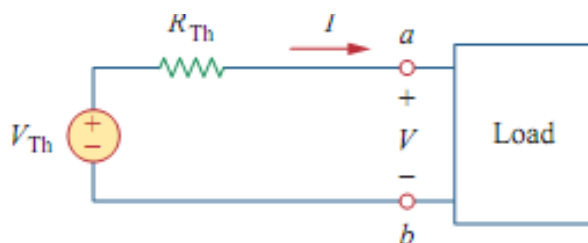

(b)


- ❖ V_{Th} is the **open-circuit voltage** at the terminals, and R_{Th} is the **input or equivalent resistance** at the terminals when the independent sources are turned off.
- ❖ It is easy to find the **open-circuit voltage** (v_{oc}) and **short-circuit current** (i_{sc}) at terminal a-b through experimental method.
- ❖ Thus, $V_{Th} = v_{oc}$ and $R_{Th} = v_{oc}/i_{sc}$




Circuit Theory

Thevenin's Theorem

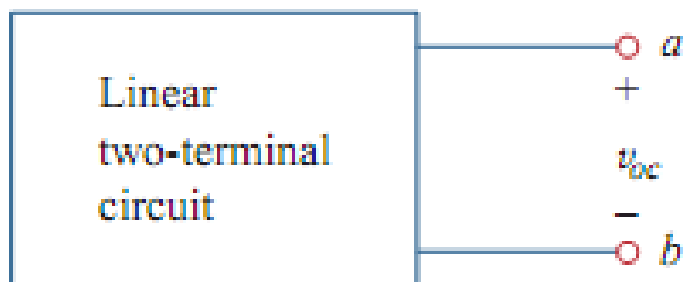- How to find V_{Th} (Thevenin voltage) and R_{Th} (Thevenin resistance)?



$$V_{Th} = v_{oc}$$

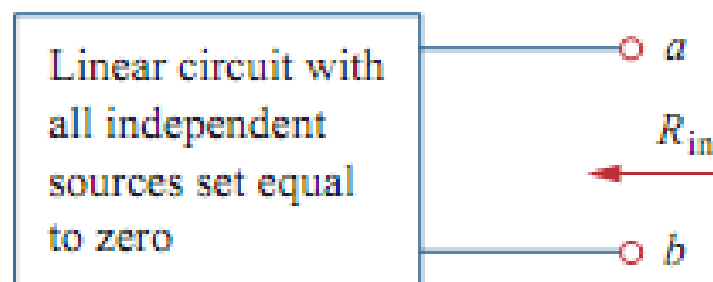

$$R_{Th} = R_{in}$$

Circuit Theory

Thevenin's Theorem

- ❑ A linear circuit without dependent source.
 1. Find v_{oc} across the two terminal (either using mesh/nodal, etc). The Thevenin voltage (V_{Th}) is equal to v_{oc} .
 2. Simply turn off all the independent sources.
 3. Find the equivalent resistance (R_{eq}) between the two terminal. The Thevenin resistor (R_{Th}) is equal to the R_{eq} .

Circuit Theory

Thevenin's Theorem



□ A linear circuit with dependent source

1. Find v_{oc} across the two terminal (either using mesh/nodal, etc). The Thevenin voltage (V_{Th}) is equal to v_{oc} .
2. Simply turn off all the independent sources. The dependent sources should remain intact/unchanged.
3. Inject a voltage source (v_o) OR current source (i_o) across the two terminal. Then determine current supplied by voltage source OR voltage across the current source.
4. The value of $R_{Th} = v_o/i_o$

Circuit Theory

Thevenin's Theorem

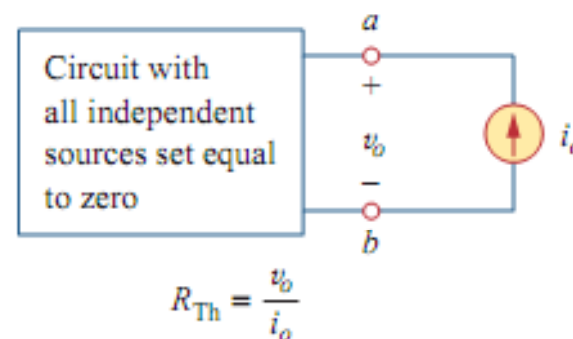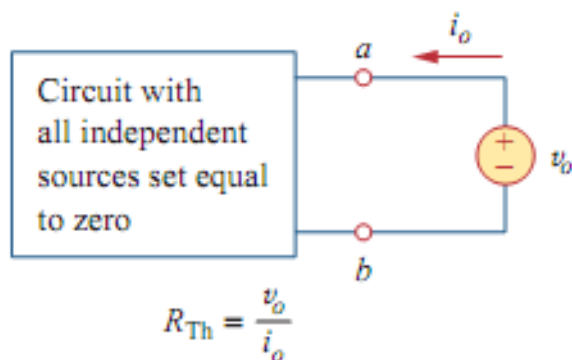- ❖ Finding R_{Th} when circuit has dependent sources.





- We may assume any value of v_o and i_o . For example, we may use $v_o = 1V$ or $i_o = 1A$, or even use unspecified values of v_o or i_o .

Circuit Theory

Thevenin's Theorem

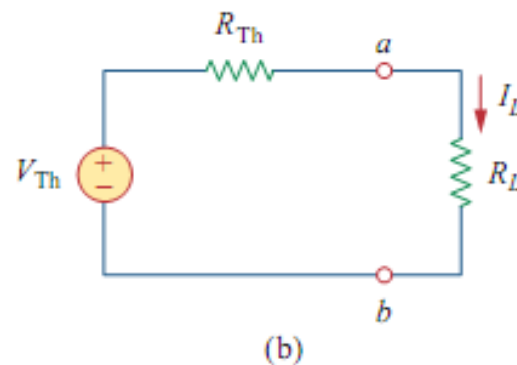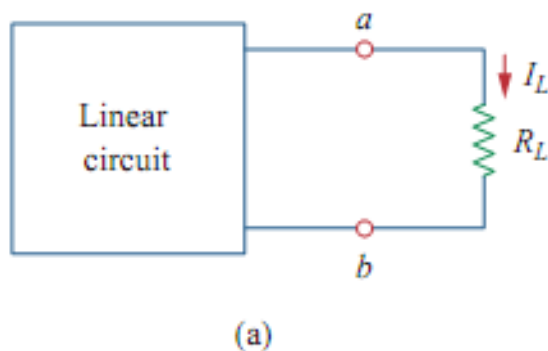- ❖ A circuit with a load: (a) original circuit, (b) Thevenin equivalent



$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

$$V_L = R_L I_L = \frac{R_L}{R_{Th} + R_L} V_{Th}$$

Circuit Theory

Thevenin's Theorem

Example 4.3:

Find the Thevenin equivalent circuit of the circuit shown in Fig. E4.3, to the left of the terminals $a-b$. Then find the current through $R_L = 6, 16$ and 36Ω .

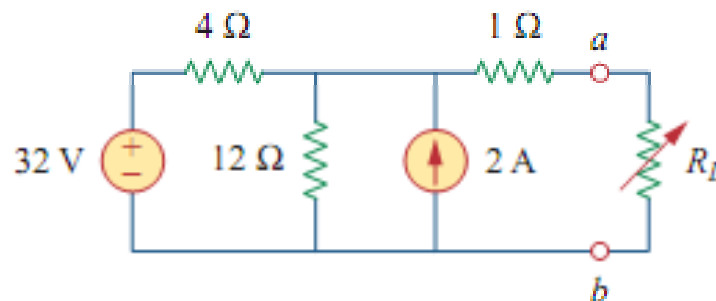


Fig. E4.3

Circuit Theory

Thevenin's Theorem

Example 4.4:

Find the Thevenin equivalent circuit of the circuit in Fig. E4.4 at terminals a - b .

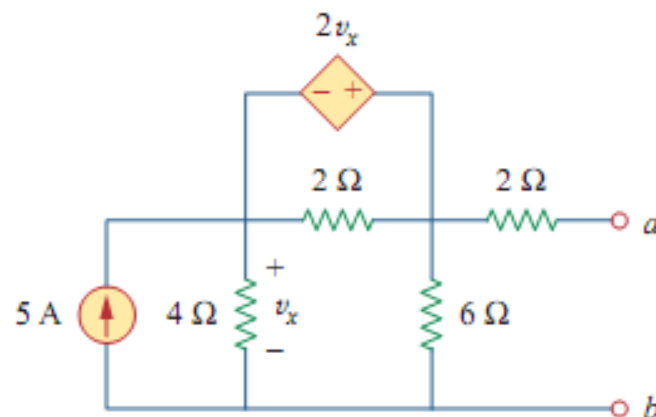



Fig. E4.4

Circuit Theory


Thevenin's Theorem

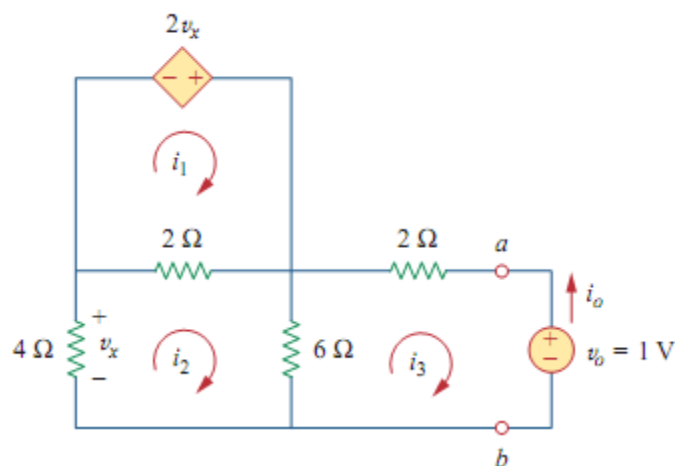Example 4.4 (cont.):

Finding R_{Th} and V_{Th} at terminals $a-b$.



Finding R_{Th}

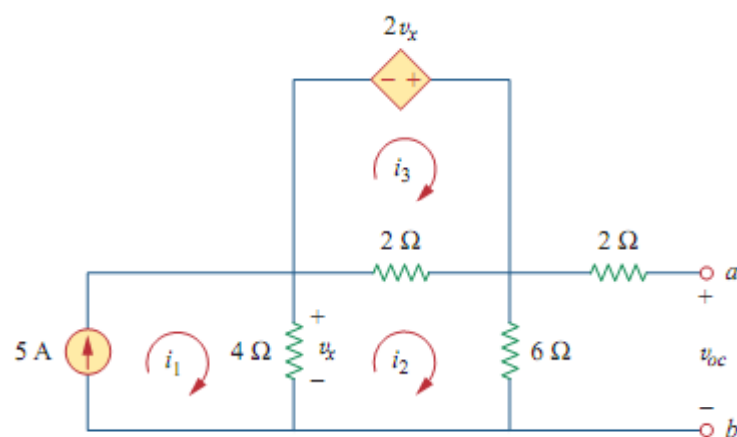


Finding V_{Th}


Circuit Theory

Norton's Theorem

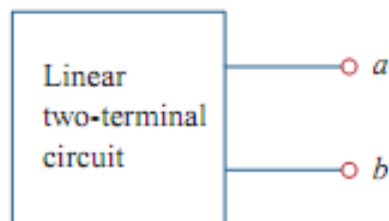- Similar with Thevenin's theorem.
- Proposed by E.L. Norton (1926), an American engineer at Bell Telephone Laboratories.
- Norton's theorem states that a linear two-terminal circuit can be replaced by an **equivalent circuit** consisting of a **current source** (I_N) in parallel with a **resistor**, R_N .



Original circuit

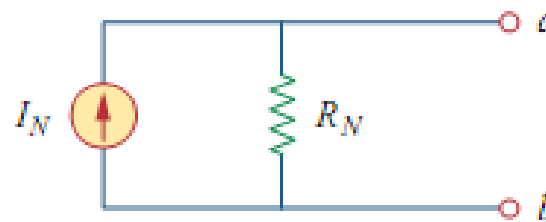

Norton equivalent circuit

Circuit Theory

Norton's Theorem

- I_N is the **short-circuit current (i_{sc})** through the terminals and R_N is the **input or equivalent resistance** at the terminals when the independent sources are turned off.
- Method to find R_N is same with $R_{Th} \Rightarrow R_N = R_{Th}$
- By using “Source Transformation” method, the conversion between Thevenin and Norton theorems are possible.
- Correlation between Thevenin and Norton parameters are given as follows;

$$I_N = \frac{V_{Th}}{R_{Th}}; \quad V_{Th} = v_{oc} \quad \text{and} \quad I_N = i_{sc}$$
$$R_{Th} = \frac{v_{oc}}{i_{sc}} = R_N$$

Circuit Theory

Norton's Theorem

Example 4.5 :

Find the Norton equivalent circuit of the circuit of Fig. E4.5.

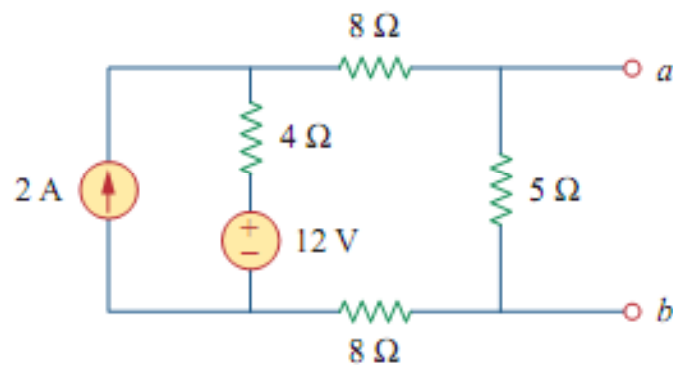





Fig. E4.5



Circuit Theory

Norton's Theorem

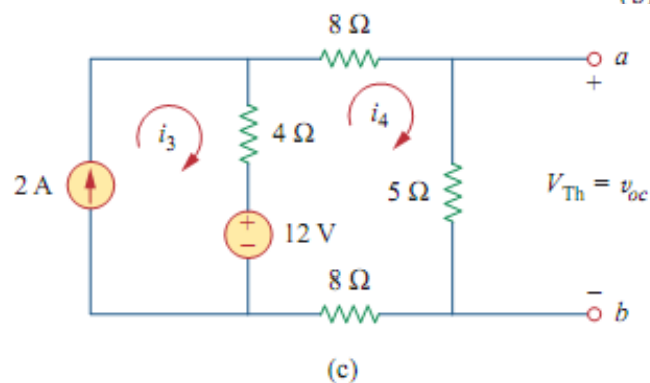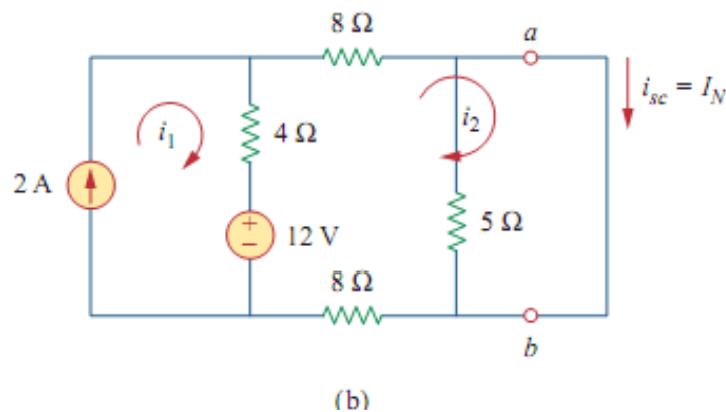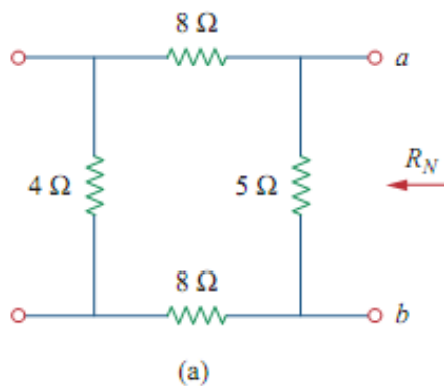Finding (a) R_N , (b) $I_N = i_{sc}$, (c) $V_{Th} = v_{oc}$.



Circuit Theory

Norton's Theorem

Problem 4.3:

Find the Norton equivalent circuit of the circuit in Fig. P4.3 at terminals a - b .

(Ans: $R_N = 1 \Omega$, $I_N = 10 \text{ A}$)


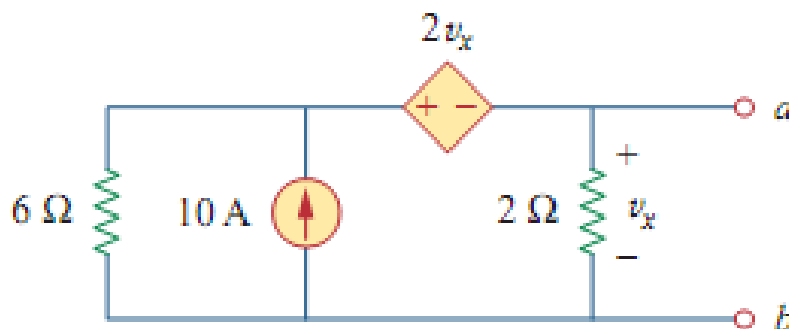


Fig. P4.3

Circuit Theory

Maximum Power Transfer

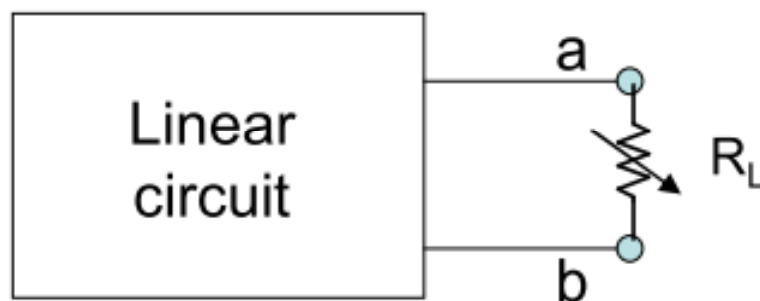
- A circuit is purposely designed to suit the demand of the loads (*in terms of voltage/current/power*).
- If the load (resistive load) is variable, then **what is the maximum power** that can be transferred to the load?



Circuit Theory

Maximum Power Transfer

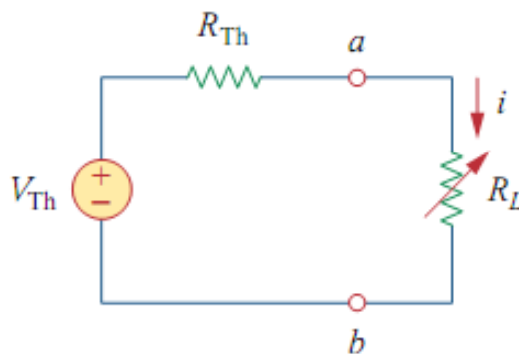- **Thevenin equivalent** is useful in finding the maximum power that the linear circuit can deliver to a load.




- Power absorbed by the load;

$$p = i^2 R_L = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$

Circuit Theory

Maximum Power Transfer

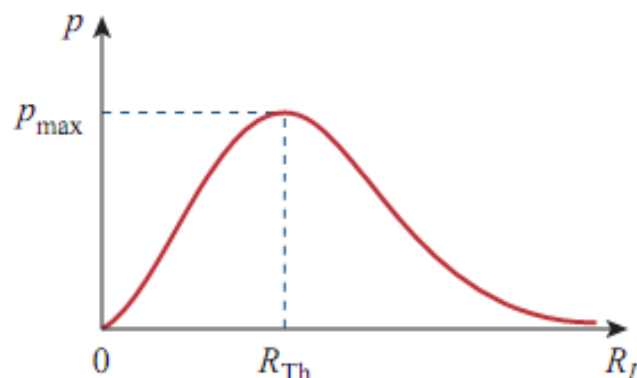- By varying the load resistance R_L , the power delivered to the load varies as sketched in figure below;



- **Maximum power** is transferred to the load when the load resistance equals the Thevenin resistance as seen from the load ($R_L = R_{Th}$)

Circuit Theory

Maximum Power Transfer

Example 4.6 :

Find the value of R_L for maximum power transfer in the circuit of Fig. E4.6.
Find maximum power. (Ans: $R_L = 9 \Omega$, 13.44 W)

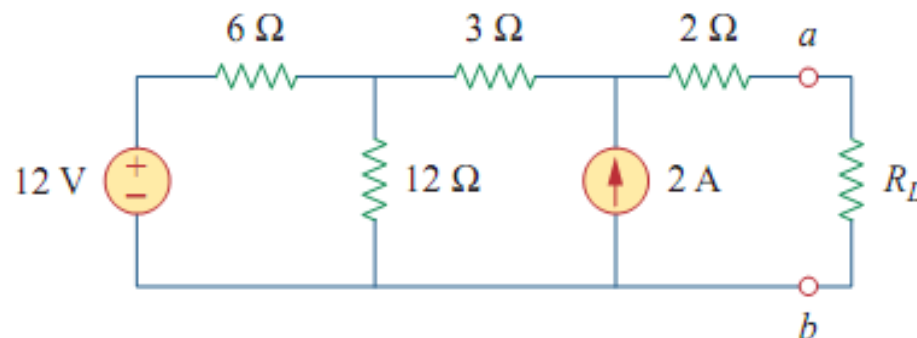


Fig. E4.6