



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

M. Afendi M. Piah, PhD

www.utm.my

Circuit Theory (SKEE 1023)

Assoc. Prof. Dr. Mohamed Afendi Mohamed Piah

**Institute of High Voltage & High Current
Faculty of Electrical Engineering, UTM**



Operational Amplifiers

Topics

- ❖ Operational Amplifiers, Ideal Op Amp, Inverting Amplifier, Noninverting Amplifier, Summing Amplifier, Difference Amplifier, Cascaded Op Amp Circuits.

Operational Amplifiers

Introduction



- The operational amplifier (**op amp**) is an electronic unit that behaves like a voltage-controlled voltage source.
- An op amp can sum signals, amplify a signal, integrate it or differentiate it.
- An op amp is **an active circuit element** designed to perform mathematical operations of addition, subtraction, multiplication, division, differentiation and integration.
- The op amp is an electronic device consisting of a complex arrangement of resistors, transistors, capacitors, and diodes.



Operational Amplifiers


Introduction

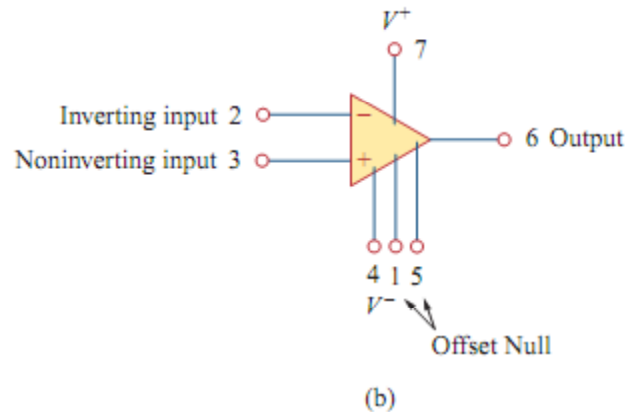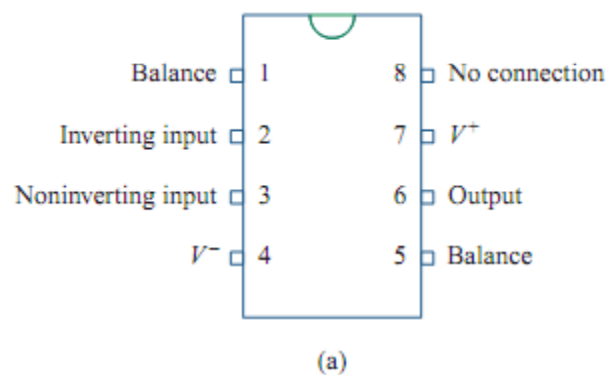- ✓ A typical op amp: (a) pin configuration, (b) circuit symbol.




Operational Amplifiers

Introduction

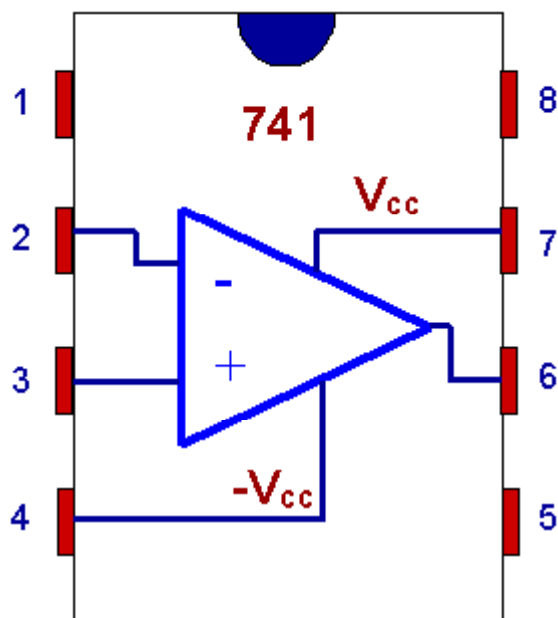

✓ Powering the op amp

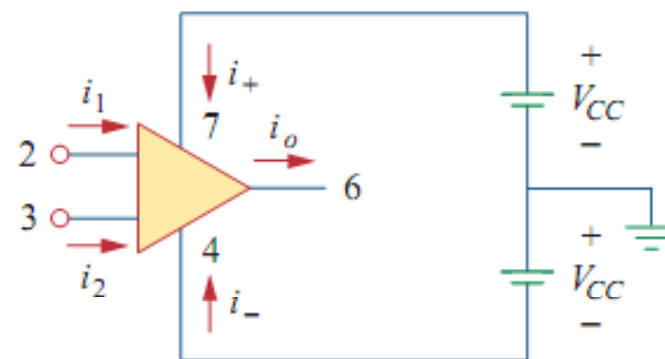


$$i_o = i_1 + i_2 + i_+ + i_-$$

Operational Amplifiers

Introduction

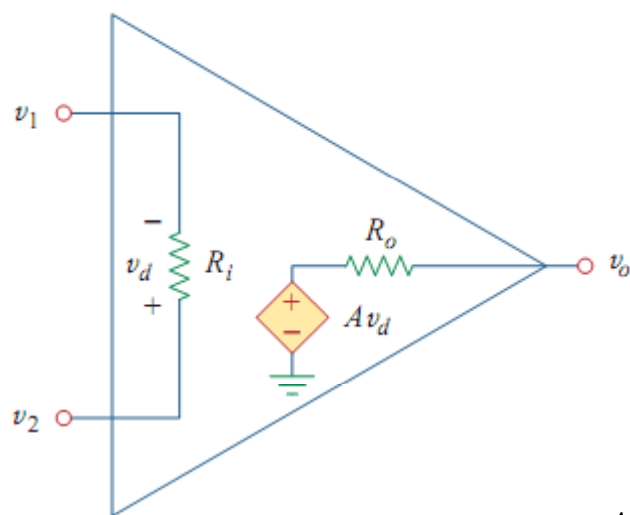- ✓ Equivalent circuit of the non-ideal op amp



The differential input voltage, v_d ;

$$v_d = v_2 - v_1$$

- ✓ Op amp senses the difference between the two inputs, multiplies it by the gain A , and causes the resulting output.


$$v_o = Av_d = A(v_2 - v_1)$$

A : open - loop voltage gain

Operational Amplifiers

Introduction

- The concept of feedback is crucial to understanding of op amp circuits.
- **Negative feedback** is achieved when the output is fed back to the inverting terminal of the op amp.
- The ratio of the output voltage to the input voltage is called the **closed-loop gain**, $\Rightarrow (v_o / v_s)$
- A practical limitation of the op amp is that the magnitude of its output voltage cannot exceed $|V_{CC}|$.

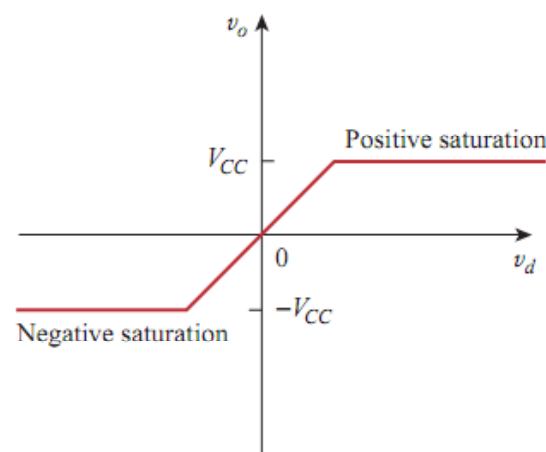

Operational Amplifiers

✓ Some applications of op amp


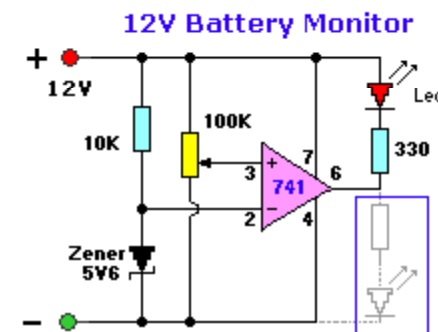
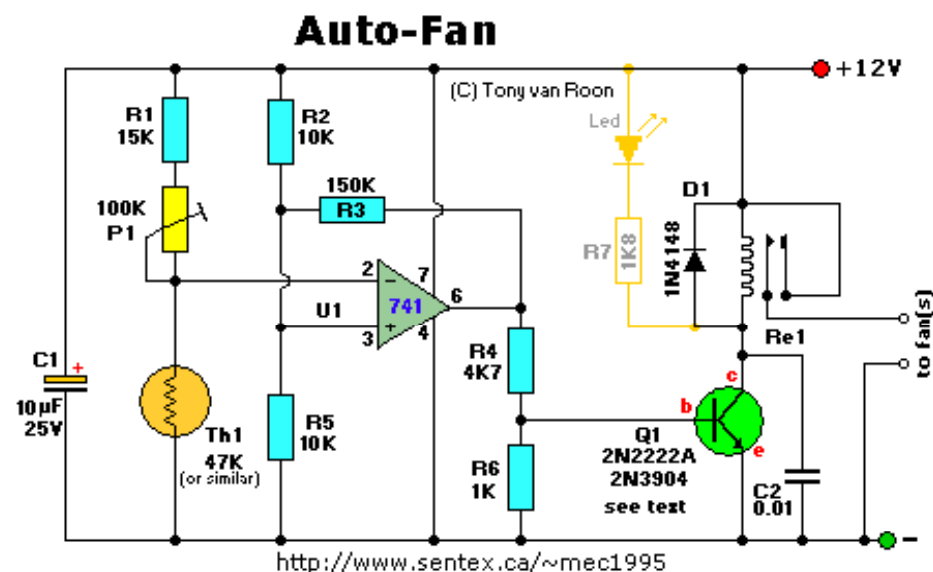


Fig. 14

Smart Continuity Tester

http://www.uoguelph.ca/~antoon

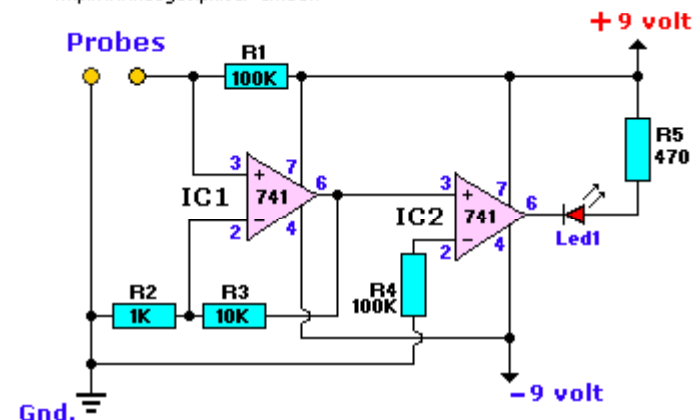


Gnd., +9V, and -9V NEEDS to be connected or the circuit will **NOT** work!

Operational Amplifiers

Ideal Op Amp

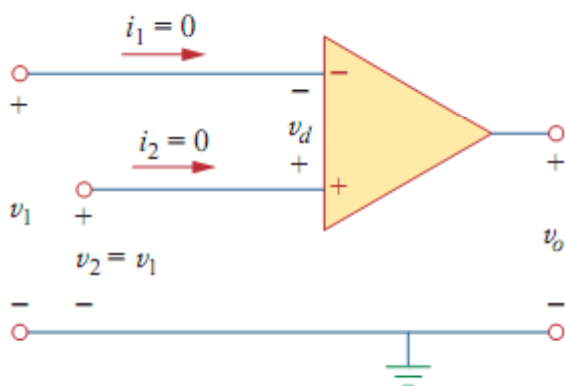- An **ideal op amp** is an amplifier with infinite open-loop gain, infinite input resistance, and zero output resistance.
- Two important characteristics of the ideal op amp are:
 - The currents into both input terminals are zero.
 - The voltage across the input terminals is equal to zero



$$i_1 = 0; \quad i_2 = 0$$


$$v_d = v_2 - v_1 = 0$$

$$v_1 = v_2$$

Operational Amplifiers

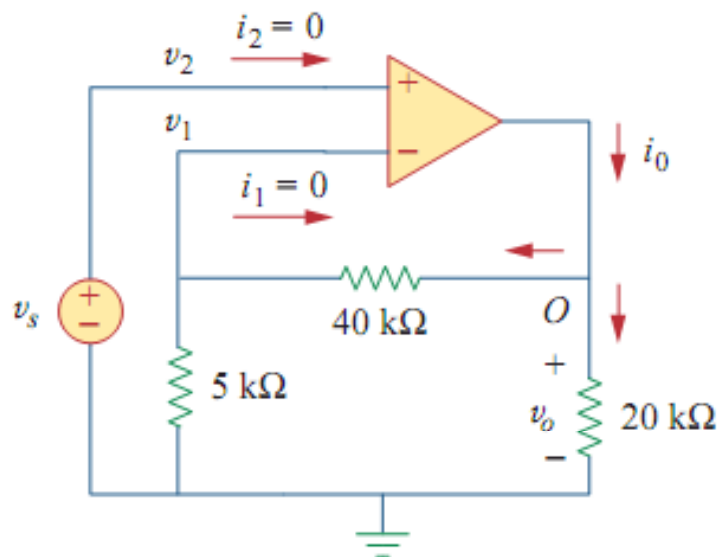Example 1


Calculate the closed-loop gain (v_o / v_s). Find i_o when $v_s = 1V$.



Operational Amplifiers

Inverting Op Amp

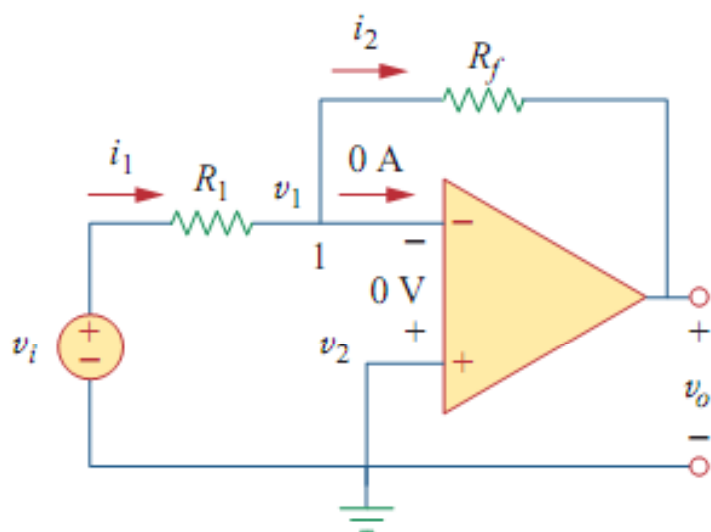- ✓ v_i is connected to the inverting input through R_1 , and the feedback resistor R_f is connected between the inverting input and output



$$i_1 = i_2 \Rightarrow \frac{v_i - v_1}{R_1} = \frac{v_1 - v_o}{R_f}$$

$v_1 = v_2 = 0$ for an ideal op amp.

Noninverting terminal is grounded, hence


$$\frac{v_i}{R_1} = -\frac{v_o}{R_f}$$

Operational Amplifiers

Inverting Op Amp

$$\text{Voltage gain, } A_v = \frac{v_o}{v_i} = -\frac{R_f}{R_1}$$

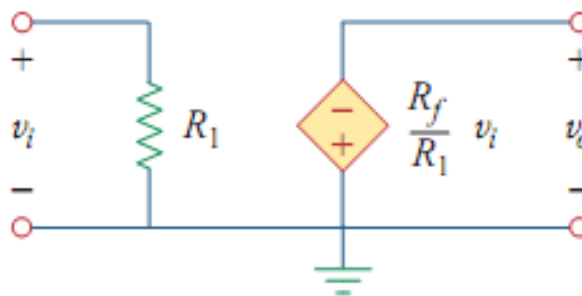
- An inverting amplifier reverses the polarity of the input signal while amplifying it.
- The gain depends only on the external elements connected to the op amp.
- Equivalent circuit for the inverting amplifier;



Operational Amplifiers

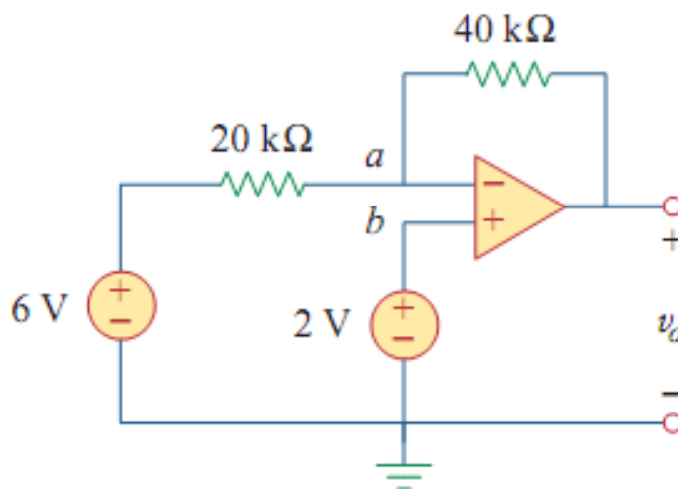Example 2


Determine v_o in the op amp circuit below.




Operational Amplifiers

Practice Problem 1

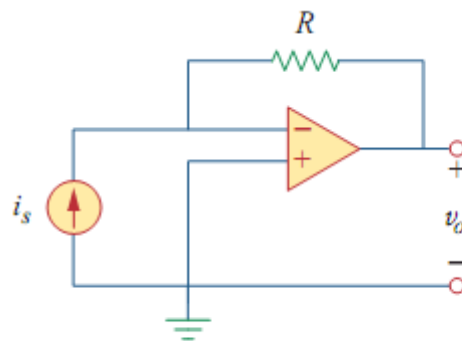Find v_o / i_s for the current-to-voltage converter circuits as shown below.



(a)

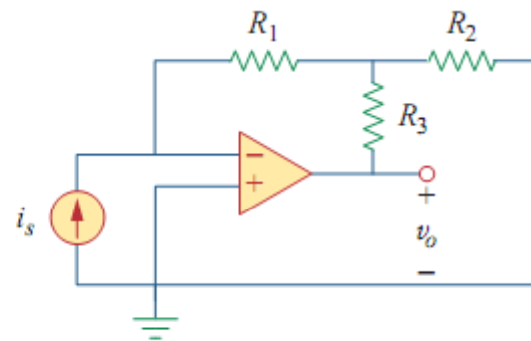

(b)


Answers:

$$(a) \frac{v_o}{i_s} = -R; \quad (b) \frac{v_o}{i_s} = -R_1 \left(1 + \frac{R_3}{R_1} + \frac{R_3}{R_2} \right)$$

Operational Amplifiers

Noninverting Op Amp

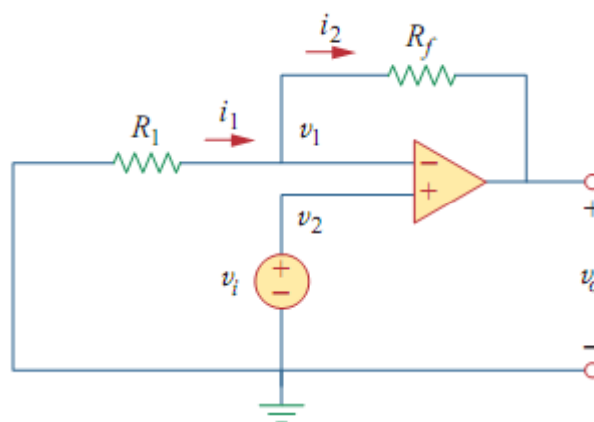- Input voltage v_i is applied directly at the noninverting input terminal, and R_1 is connected between the ground and the inverting terminal.



$$\text{Voltage gain, } A_v = \frac{v_o}{v_i} = \left(1 + \frac{R_f}{R_1} \right)$$




Operational Amplifiers

Noninverting Op Amp


- A noninverting amplifier is an op amp circuit designed to provide a positive voltage gain.
- Gain depends only on the external resistors.
- If $R_f = 0$ (short-circuit) or $R_1 = \infty$ (open-circuit) or both, the gain becomes 1; \Rightarrow called a **voltage follower** (or unity gain amplifier).
- This voltage follower circuit has a very high input impedance and is therefore useful as an **intermediate-stage (or buffer) amplifier** to isolate one circuit from another.

Operational Amplifiers

Noninverting Op Amp

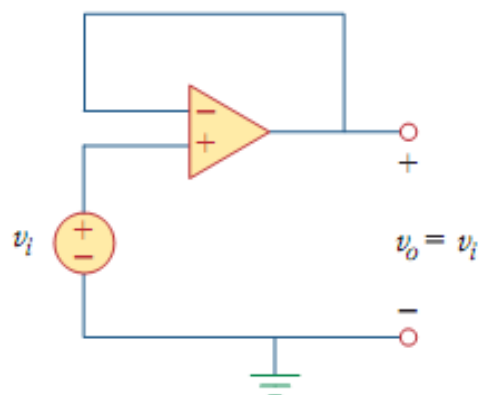

The voltage follower

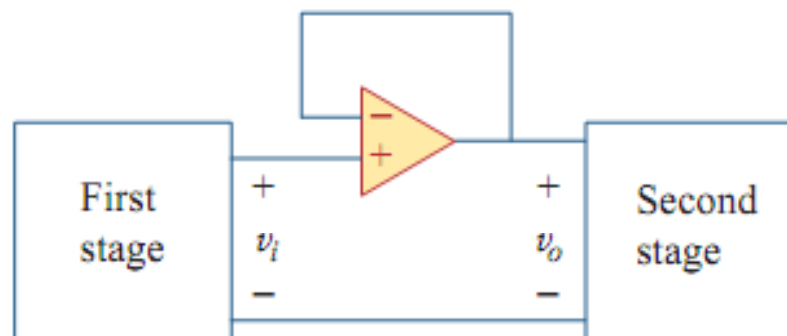

A voltage follower used to isolate two cascaded stages of a circuit

Operational Amplifiers

Example 3

For the op amp circuit in Fig E3, calculate the output voltage v_o .


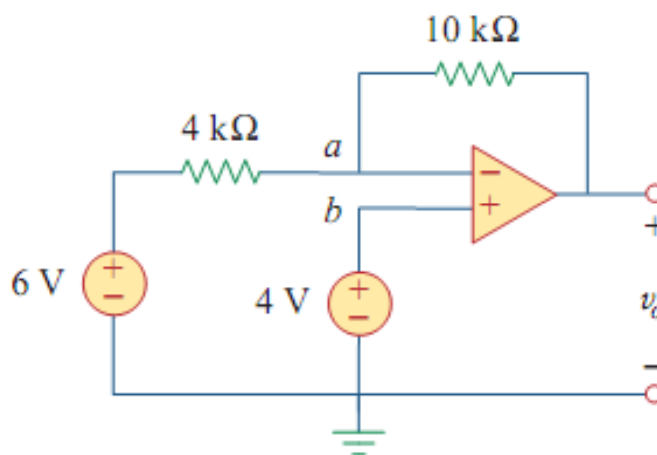


Fig E3

Operational Amplifiers

Practice Problem 2

Calculate v_o in the circuit of Fig. P2.

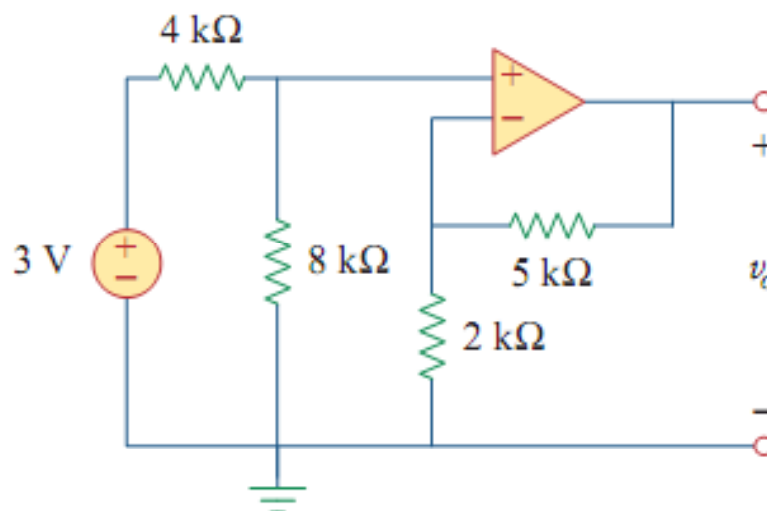


Answers: 7V

Operational Amplifiers

Summing Amplifier

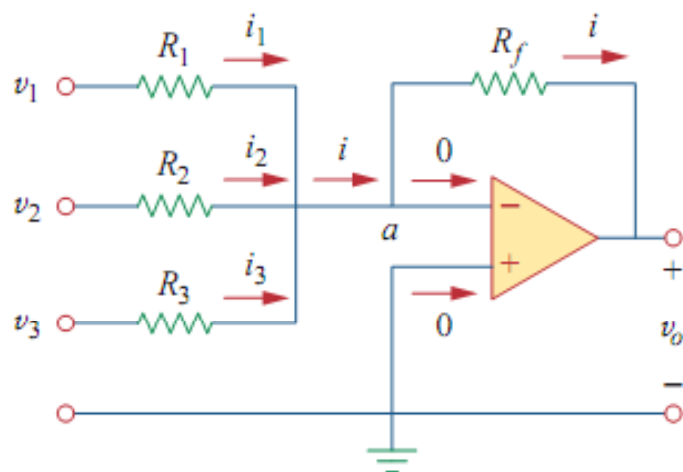- A summing amplifier is an op amp circuit that combines several inputs and produces an output that is the weighted sum of the inputs.



Also called *summer*

$$i = i_1 + i_2 + i_3$$

$$i_1 = \frac{v_1 - v_a}{R_1}, \quad i_2 = \frac{v_2 - v_a}{R_2}$$

$$i_3 = \frac{v_3 - v_a}{R_3}, \quad i = \frac{v_a - v_o}{R_f}$$

$$v_o = - \left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3 \right)$$

Operational Amplifiers

Practice Problem 3

Find v_o and i_o in the op amp circuit of Fig. P3.

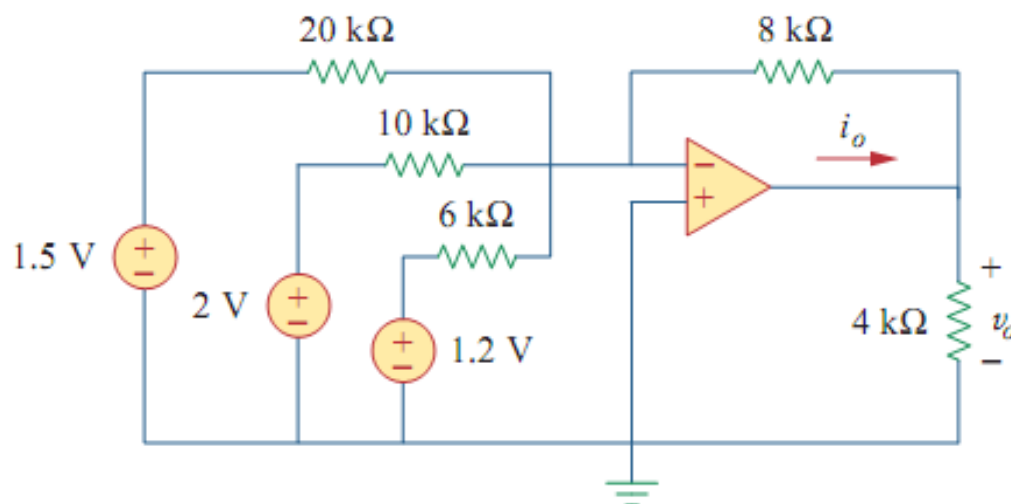



Fig. P3

Answers: -3.8V, -1.425mA

Operational Amplifiers

Difference Amplifier

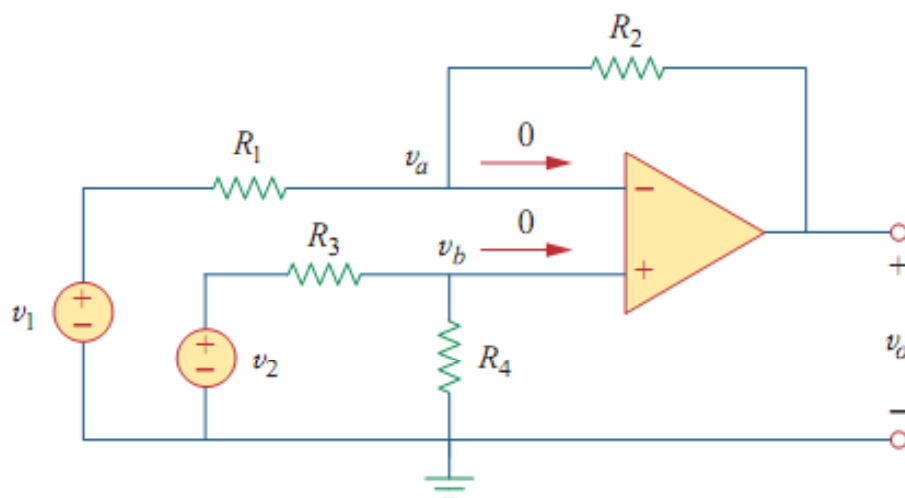- A difference amplifier is a device that amplifies the difference between two inputs but rejects any signals common to the two inputs.



KCL at node a;

$$v_o = \left(\frac{R_2}{R_1} + 1 \right) v_a - \frac{R_2}{R_1} v_1$$

KCL at node b;

$$v_b = \frac{R_4}{R_3 + R_4} v_2$$

Operational Amplifiers

Difference Amplifier

Since $v_a = v_b$, therefore ;

$$v_o = \frac{R_2 (1 + R_1 / R_2)}{R_1 (1 + R_3 / R_4)} v_2 - \frac{R_2}{R_1} v_1$$

- Since a difference amplifier must reject a signal common to the two inputs. \therefore amplifier must have the property $v_o = 0$ when $v_1 = v_2$.

This property exists when,

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}; \Rightarrow v_o = \frac{R_2}{R_1} (v_2 - v_1)$$

If $R_2 = R_1$ & $R_3 = R_4$;

diff. amp becomes a *subtractor*

$$\Rightarrow v_o = v_2 - v_1$$

Operational Amplifiers

Practice Problem 4

Obtain i_o in the instrumentation amplifier circuit of Fig. P4.

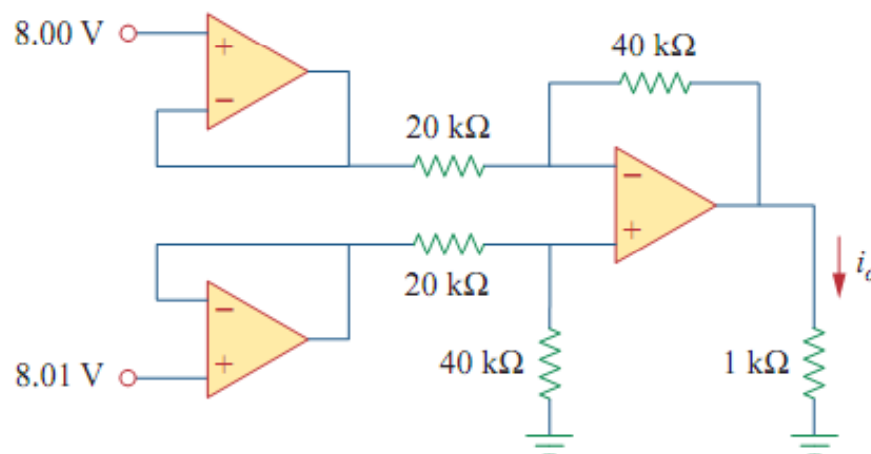


Fig. P4

Answers: $20 \mu\text{A}$

Operational Amplifiers


Cascaded Op Amp Circuits

- A cascade connection is a **head-to-tail arrangement** of two or more op amp circuits such that the output of one is the input of the next.
- When op amp circuits are cascaded, **each circuit in the string** is called **a stage**; the original input signal is increased by the gain of the individual stage.
- Can be cascaded without changing input-output relationships.
- The overall gain of the cascaded connection is the product of the gains of the individual op amp circuits; **$A = A_1 A_2 A_3$**
- Care must be exercised in the design of an actual op amp circuit to ensure that the load due to the next stage in the cascade does not saturate the op amp.

Operational Amplifiers

Cascaded Op Amp Circuits

A three-stage cascaded connection

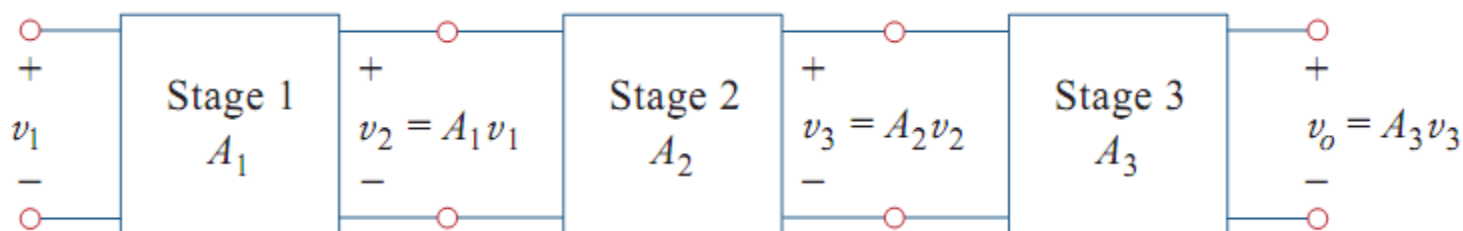

$$v_2 = A_1 v_1 ; \quad v_3 = A_2 v_2 ; \quad v_o = A_3 v_3$$

$$v_o = A_3 A_2 v_2 = A_3 A_2 A_1 v_1$$

$$\therefore \frac{v_o}{v_1} = A = A_1 A_2 A_3$$

Operational Amplifiers

Example 4

Find v_o and i_o in the circuit in Fig E4.

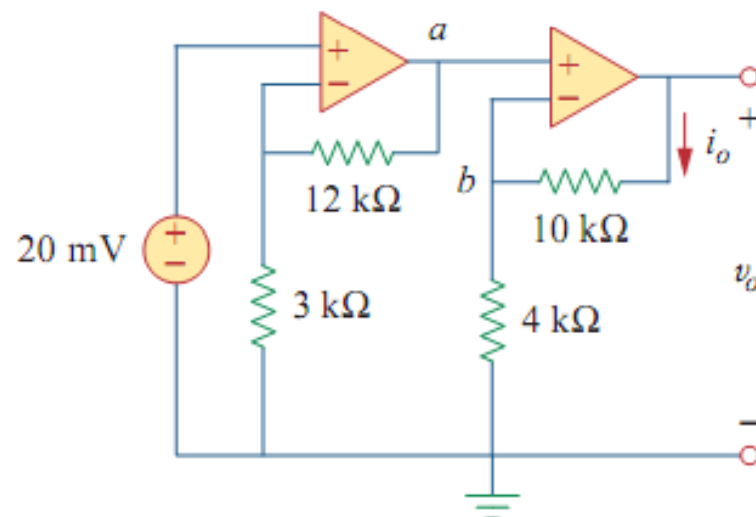


Fig E4

Operational Amplifiers

Practice Problem 5

Determine v_o and i_o in the op amp circuit in Fig. P5.

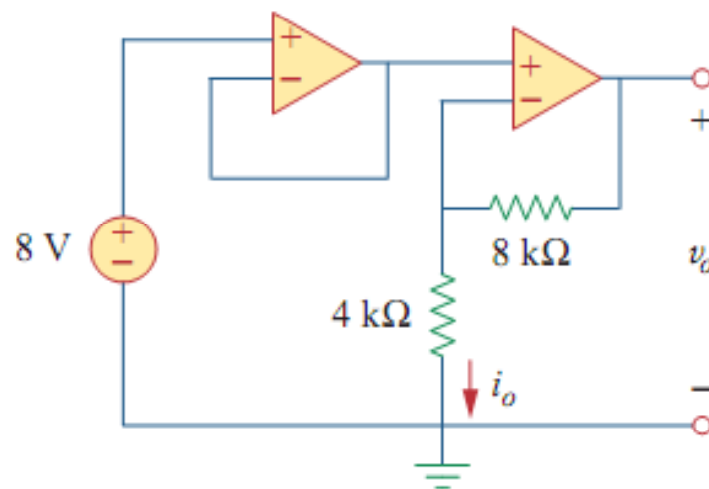


Fig. P5

Answers: 24 V, 2 mA