

CHAPTER 2

P.P.2.1 $i = V/R = 110/12 = \underline{9.167 \text{ A}}$

P.P.2.2 (a) $v = iR = 2 \text{ mA}[10 \text{ kohms}] = \underline{20 \text{ V}}$

(b) $G = 1/R = 1/10 \text{ kohms} = \underline{100 \mu\text{S}}$

(c) $p = vi = 20 \text{ volts}[2 \text{ mA}] = \underline{40 \text{ mW}}$

P.P.2.3 $p = vi$ which leads to $i = p/v = [20 \cos^2(t) \text{ mW}]/[10\cos(t) \text{ mA}]$

or $i = \underline{2\cos(t) \text{ mA}}$

$R = v/i = 10\cos(t)\text{V}/2\cos(t)\text{mA} = \underline{5 \text{ k}\Omega}$

P.P.2.4 5 branches and 3 nodes. The 1 ohm and 2 ohm resistors are in parallel. The 4 ohm resistor and the 10 volt source are also in parallel.

P.P.2.5 Applying KVL to the loop we get:

$-10 + 4i - 8 + 2i = 0$ which leads to $i = 3\text{A}$

$v_1 = 4i = \underline{12\text{V}}$ and $v_2 = -2i = \underline{-6\text{V}}$

P.P.2.6 Applying KVL to the loop we get:

$-35 + 10i + 2v_x + 5i = 0$

But, $v_x = 10i$ and $v_0 = -5i$. Hence,


$-35 + 10i + 20i + 5i = 0$ which leads to $i = 1\text{A}$.

Thus, $v_x = \underline{10\text{V}}$ and $v_0 = \underline{-5\text{V}}$

P.P.2.7 Applying KCL, $6 = i_0 + [i_0/4] + [v_0/8]$, but $i_0 = v_0/2$

Which leads to: $6 = (v_0/2) + (v_0/8) + (v_0/8)$ thus, $v_0 = \underline{8V}$ and $i_0 = \underline{4A}$

P.P.2.8

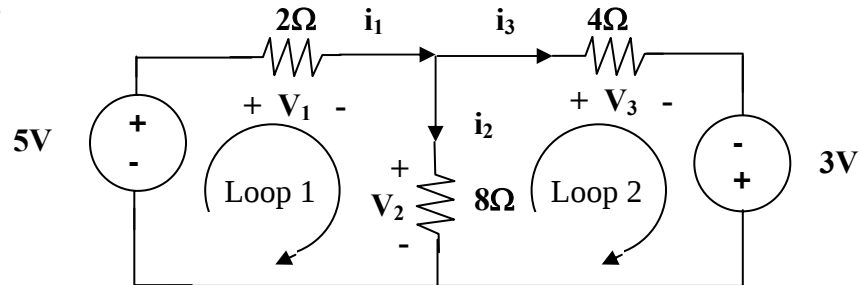

At the top node, $i_1 = i_2 + i_3$ (1)

For loop 1 $-5 + V_1 + V_2 = 0$
or $V_1 = 5 - V_2$ (2)

For loop 2 $-V_2 + V_3 - 3 = 0$
or $V_3 = V_2 + 3$ (3)

Using (1) and Ohm's law, we get

$$(V_1/2) = (V_2/8) + (V_3/4)$$


and now using (2) and (3) in the above yields

$$[(5 - V_2)/2] = (V_2/8) + (V_2 + 3)/4$$

or $V_2 = \underline{2V}$

$V_1 = 5 - V_2 = \underline{3V}$, $V_3 = 2 + 3 = \underline{5V}$, $i_1 = (5 - 2)/2 = \underline{1.5A}$,
 $i_2 = \underline{250 mA}$, $i_3 = \underline{1.25A}$


P.P.2.9

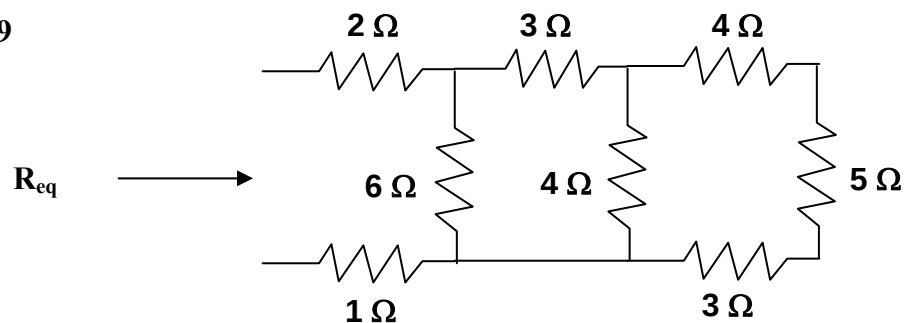

Combining the 4 ohm, 5 ohm, and 3ohm resistors in series gives $4+3+5 = 12$.


But, 4 in parallel with 12 produces $[4 \times 12] / [4 + 12] = 48/16 = 3\text{ohm}$.

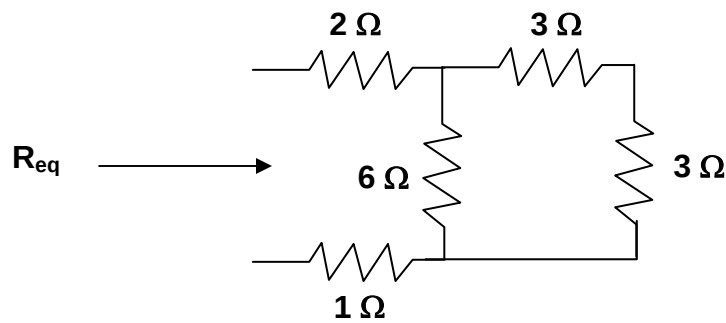So that the equivalent circuit is shown below.




Thus, $R_{eq} = 1 + 2 + [6 \times 6] / [6 + 6] = \underline{6\ \Omega}$

P.P.2.10

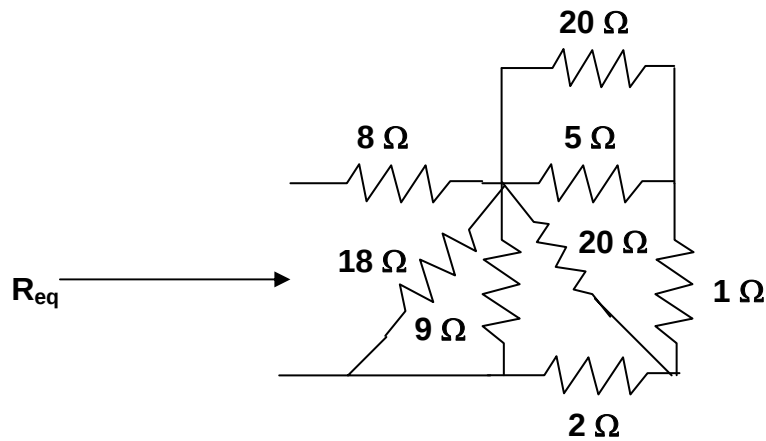


Combining the 9 ohm resistor and the 18 ohm resistor yields $[9 \times 18] / [9 + 18] = 6\text{ ohms}$.

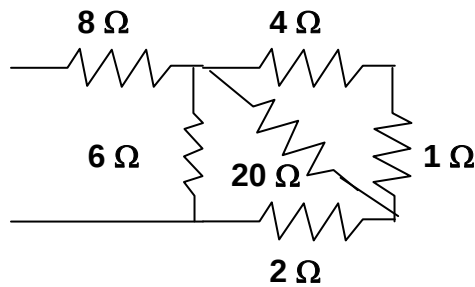Combining the 5 ohm and the 20 ohm resistors in parallel produces $[5 \times 20 / (5 + 20)] = 4$ ohms. We now have the following circuit:



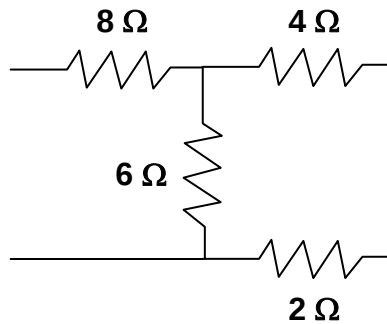
The 4 ohm and 1 ohm resistors can be combined into a 5 ohm resistor in parallel with a 20 ohm resistor. This will result in $[5 \times 20 / (5 + 20)] = 4$ ohms and the circuit shown below:



The 4 ohm and 2 ohm resistors are in series and can be replaced by a 6 ohm resistor. This gives a 6 ohm resistor in parallel with a 6 ohm resistor, $[6 \times 6 / (6 + 6)] = 3$ ohms. We now have a 3 ohm resistor in series with an 8 ohm resistor or $3 + 8 = 11$ ohms. Therefore:


$$R_{eq} = \underline{\underline{11 \text{ ohms}}}$$

P.P. 2.11

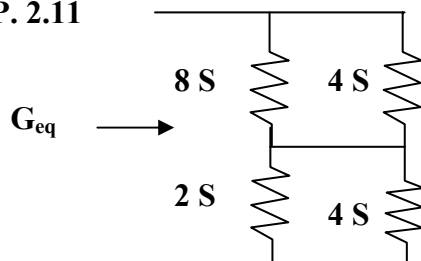


$$8 \parallel 4 = 8 + 4 = 12 \text{ S}$$

$$2 \parallel 4 = 2 + 4 = 6 \text{ S}$$

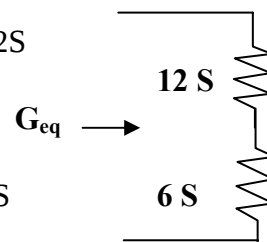

$$12 \text{ S in series with } 6 \text{ S} = \{12 \times 6 / (12 + 6)\} = 4 \text{ or: } G_{eq} = \underline{\underline{4 \text{ S}}}$$

P.P.2.12

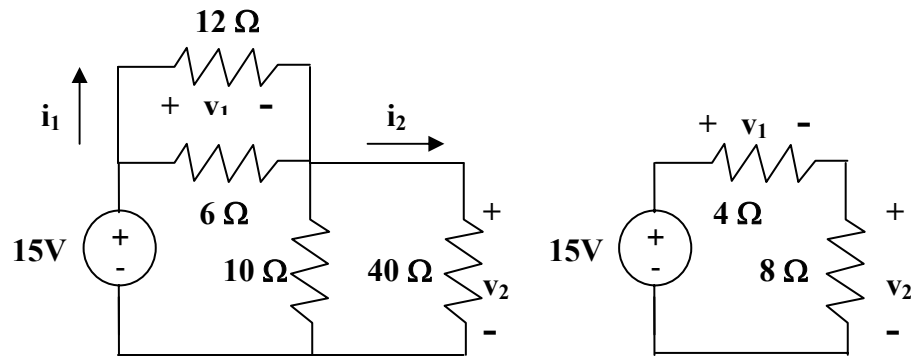

$$6 \parallel 12 = [6 \times 12 / (6 + 12)] = 4 \text{ ohm} \quad \text{and} \quad 10 \parallel 40 = [10 \times 40 / (10 + 40)] = 8 \text{ ohm}.$$


Using voltage division we get:

$$v_1 = [4 / (4 + 8)] (15) = \underline{\mathbf{5 \text{ volts}}}, \quad v_2 = [8 / 12] (15) = \underline{\mathbf{10 \text{ volts}}}$$

$$i_1 = v_1 / 12 = 5 / 12 = \underline{\mathbf{416.7 \text{ mA}}}, \quad i_2 = v_2 / 40 = 10 / 40 = \underline{\mathbf{250 \text{ mA}}}$$

$$P_1 = v_1 i_1 = 5 \times 5 / 12 = \underline{\mathbf{2.083 \text{ watts}}}, \quad P_2 = v_2 i_2 = 10 \times 0.25 = \underline{\mathbf{2.5 \text{ watts}}}$$

P.P.2.13

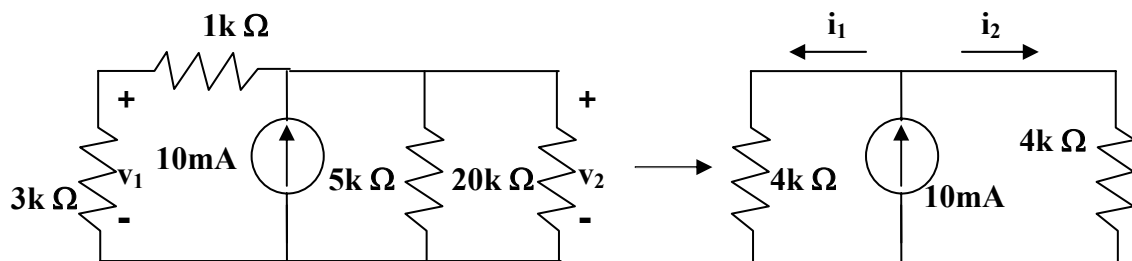

Using current division, $i_1 = i_2 = (10 \text{ mA})(4 \text{ kohm} / (4 \text{ kohm} + 4 \text{ kohm})) = 5 \text{ mA}$

$$(a) \quad v_1 = (3 \text{ kohm})(5 \text{ mA}) = \underline{\mathbf{15 \text{ volts}}}$$

$$v_2 = (4 \text{ kohm})(5 \text{ mA}) = \underline{\mathbf{20 \text{ volts}}}$$

$$(b) \quad \text{For the } 3\text{k ohm resistor, } P_1 = v_1 \times i_1 = 15 \times 5 = \underline{\mathbf{75 \text{ mw}}}$$

$$\text{For the } 20\text{k ohm resistor, } P_2 = (v_2)^2 / 20\text{k} = \underline{\mathbf{20 \text{ mw}}}$$

$$(c) \quad \text{The total power supplied by the current source is equal to:}$$

$$P = v_2 \times 10 \text{ mA} = 20 \times 10 = \underline{\mathbf{200 \text{ mw}}}$$

P.P.2.14


$$R_a = [R_1 R_2 + R_2 R_3 + R_3 R_1] / R_1 = [10 \times 20 + 20 \times 40 + 40 \times 10] / 10 = \underline{140 \text{ ohms}}$$

$$R_b = [R_1 R_2 + R_2 R_3 + R_3 R_1] / R_2 = 1400 / 20 = \underline{70 \text{ ohms}}$$

$$R_c = [R_1 R_2 + R_2 R_3 + R_3 R_1] / R_3 = 1400 / 40 = \underline{35 \text{ ohms}}$$

P.P.2.15

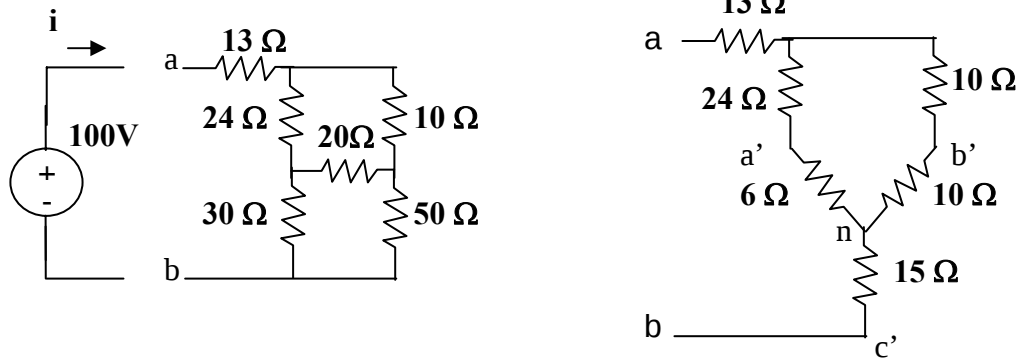We first find the equivalent resistance, R . We convert the delta sub-network to a wye connected form as shown below:



$$R_{a'n} = 20 \times 30 / [20 + 30 + 50] = 6 \text{ ohms}, R_{b'n} = 20 \times 50 / 100 = 10 \text{ ohms}$$

$$R_{c'n} = 30 \times 50 / 100 = 15 \text{ ohms.}$$

$$\text{Thus, } R_{ab} = 13 + (24 + 6) \parallel (10 + 10) + 15 = 28 + 30 \times 20 / (30 + 20) = \underline{40 \text{ ohms.}}$$

$$i = 100 / R_{ab} = 100 / 40 = \underline{2.5 \text{ amps}}$$

P.P.2.16

For the parallel case, $v = v_0 = 110 \text{ volts.}$

$$p = vi \implies i = p/v = 40/110 = \underline{364 \text{ mA}}$$

For the series case, $v = v_0/N = 110/10 = 11 \text{ volts}$

$$i = p/v = 40/11 = \underline{3.64 \text{ amps}}$$

P.P.2.17

We use equation (2.61)

$$(a) \quad R_1 = 50 \times 10^{-3} / (1 - 10^{-3}) = 0.05/999 = \underline{50 \text{ m}\Omega \text{ (shunt)}}$$

$$(b) \quad R_2 = 50 \times 10^{-3} / (100 \times 10^{-3} - 10^{-3}) = 50/99 = \underline{505 \text{ m}\Omega \text{ (shunt)}}$$

$$(c) \quad R_3 = 50 \times 10^{-3} / (10 \times 10^{-3} - 10^{-3}) = 50/9 = \underline{5.556 \Omega \text{ (shunt)}}$$