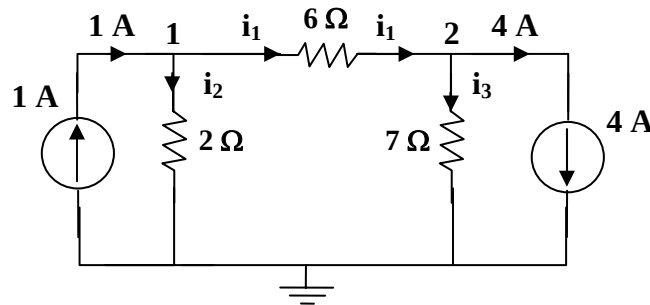


CHAPTER 3**P.P.3.1**

At node 1,

$$1 = i_1 + i_2 \longrightarrow 1 = \frac{v_1 - v_2}{6} + \frac{v_1 - 0}{2}$$

$$\text{or } 6 = 4v_1 - v_2 \quad (1)$$


At node 2,

$$i_1 = 4 + i_3 \longrightarrow \frac{v_1 - v_2}{6} = 4 + \frac{v_2 - 0}{7}$$

$$\text{or } 168 = 7v_1 - 13v_2 \quad (2)$$

Solving (1) and (2) gives

$$v_1 = \underline{-2 \text{ V}}, v_2 = \underline{-14 \text{ V}}$$

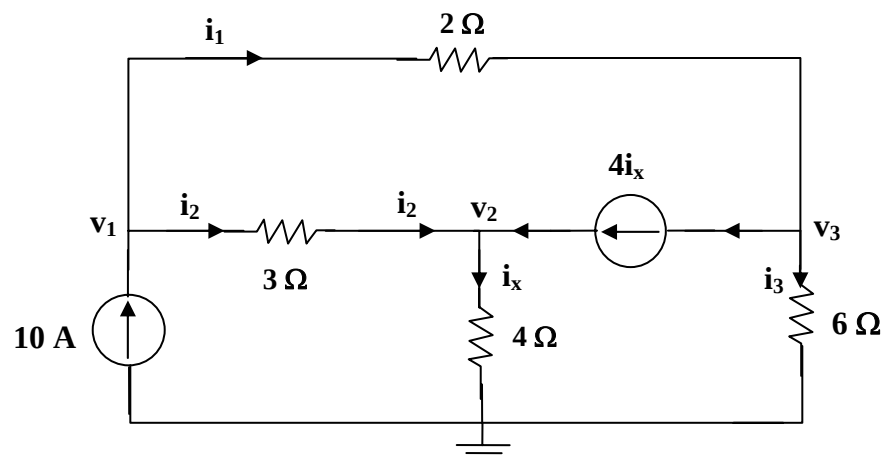P.P.3.2

At node 1,

$$10 = i_1 + i_2 = \frac{v_1 - v_3}{2} + \frac{v_1 - v_2}{3}$$

$$\text{or } 60 = 5v_1 - 2v_2 - 3v_3 \quad (1)$$

At node 2,

$$i_2 + 4i_x = i_x \longrightarrow \frac{v_1 - v_2}{3} + 3\frac{v_2}{4} = 0$$

$$\text{or } 4v_1 + 5v_2 = 0 \quad (2)$$

At node 3,



$$i_1 = i_3 + 4i_x \longrightarrow \frac{v_1 - v_3}{2} = \frac{v_3 - 0}{6} + 4\frac{v_2}{4}$$

$$\text{or } -3v_1 + 6v_2 + 4v_3 = 0 \quad (3)$$

Solving (1) to (3) gives

$$v_1 = \underline{80 \text{ V}}, v_2 = \underline{-64 \text{ V}}, v_3 = \underline{156 \text{ V}}$$

P.P.3.3

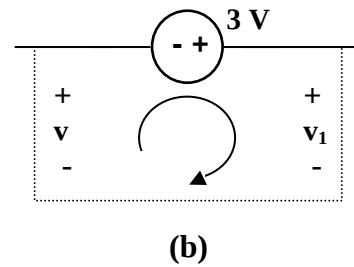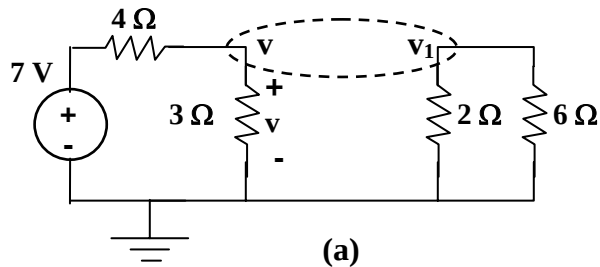

At the supernode in Fig. (a),

$$\frac{7 - v}{4} = \frac{v}{3} + \frac{v_1}{2} + \frac{v_1}{6}$$

$$\text{or } 21 = 7v + 8v_1 \quad (1)$$

Applying KVL to the loop in Fig. (b),

$$-v - 3 + v_1 = 0 \longrightarrow v_1 = v + 3 \quad (2)$$


Solving (1) and (2),

$$v = \underline{-200 \text{ mV}}$$


$$v_1 = v + 3 = 2.8, i_1 = \frac{v_1}{2} = 1.4$$

$$i_1 = \underline{1.4 \text{ A}}$$

P.P.3.4

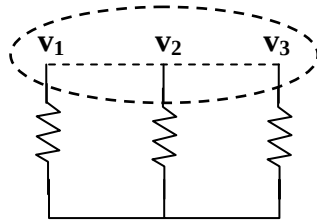

(a)

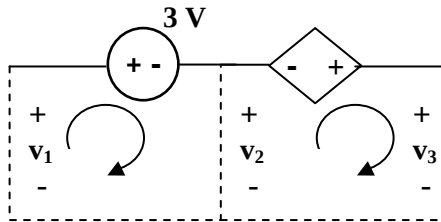

(b)

From Fig. (a),

$$\frac{v_1}{2} + \frac{v_2}{4} + \frac{v_3}{3} = 0 \longrightarrow 6v_1 + 3v_2 + 4v_3 = 0 \quad (1)$$

From Fig. (b),

$$-v_1 + 10 + v_2 = 0 \longrightarrow v_1 = v_2 + 10 \quad (2)$$

$$-v_2 - 5i + v_3 = 0 \longrightarrow v_3 = v_2 + 5i \quad (3)$$

Solving (1) to (3), we obtain

$$v_1 = \underline{3.043 \text{ V}}, v_2 = \underline{-6.956 \text{ V}}, v_3 = \underline{652.2 \text{ mV}}$$

P.P.3.5 We apply KVL to the two loops and obtain

$$-12 + 18i_1 - 12i_2 = 0 \longrightarrow 3i_1 - 2i_2 = 2 \quad (1)$$

$$8 + 24i_2 - 12i_1 = 0 \longrightarrow -3i_1 + 6i_2 = -2 \quad (2)$$

From (1) and (2) we get

$$i_1 = \underline{666.7 \text{ mA}}, i_2 = \underline{0 \text{ A}}$$

P.P.3.6 For mesh 1,

$$-20 + 6i_1 - 2i_2 - 4i_3 = 0 \longrightarrow 3i_1 - i_2 - 2i_3 = 10 \quad (1)$$

For mesh 2,

$$10i_2 - 2i_1 - 8i_3 - 10i_0 = 0 = -i_1 + 5i_2 - 9i_3 \quad (2)$$

But $i_0 = i_3$,

$$18i_3 - 4i_1 - 8i_2 = 0 \longrightarrow -2i_1 - 4i_2 + 9i_3 = 0 \quad (3)$$

From (1) to (3),

$$\begin{bmatrix} 3 & -1 & -2 \\ -1 & 5 & -9 \\ -2 & -4 & 9 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 3 & -1 & -2 \\ -1 & 5 & -9 \\ -2 & -4 & 9 \end{vmatrix} = 135 - 8 - 18 - 20 - 108 - 9 = -28$$

$$\Delta_1 = \begin{vmatrix} 10 & -1 & -2 \\ 0 & 5 & -9 \\ 0 & -4 & 9 \end{vmatrix} = 450 - 360 = 90$$



$$\Delta_2 = \begin{vmatrix} 3 & 10 & -2 \\ -1 & 0 & -9 \\ -2 & 0 & 9 \end{vmatrix} = 180 + 90 = 270$$

$$\Delta_3 = \begin{vmatrix} 3 & -1 & 10 \\ -1 & 5 & 0 \\ -2 & -4 & 0 \\ 3 & -1 & 10 \\ -1 & 5 & 0 \end{vmatrix} = 40 + 100 = 140$$

$$i_1 = \frac{\Delta_1}{\Delta} = \frac{90}{-28} = -3.214, i_2 = \frac{\Delta_2}{\Delta} = \frac{270}{-28} = -9.643, i_3 = \frac{\Delta_3}{\Delta} = \frac{140}{-28} = -5A$$

$$i_0 = i_3 = \underline{\underline{-5A}}$$

P.P.3.7

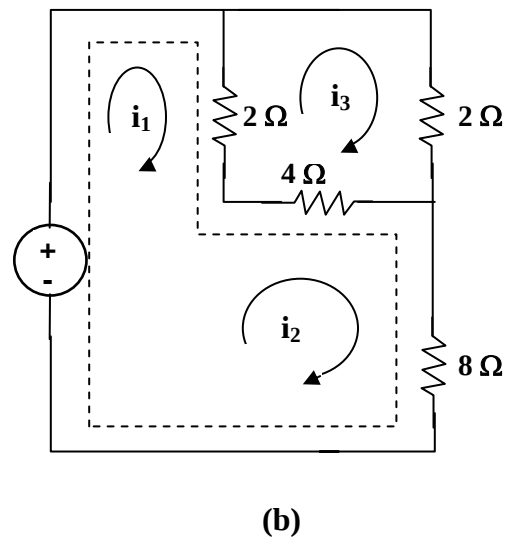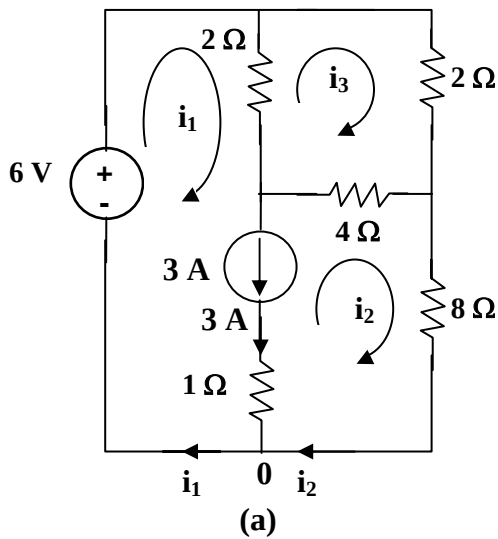

For the supermesh,

$$-6 + 2i_1 - 2i_3 + 12i_2 - 4i_3 = 0 \longrightarrow i_1 + 6i_2 - 3i_3 = 3 \quad (1)$$

For mesh 3,

$$8i_3 - 2i_1 - 4i_2 = 0 \longrightarrow -i_1 - 2i_2 + 4i_3 = 0 \quad (2)$$

At node 0 in Fig. (a),

$$i_1 = 3 + i_2 \longrightarrow i_1 - i_2 = 3$$

Solving (1) to (3) yields

$$i_1 = \underline{\underline{3.474A}}, i_2 = \underline{\underline{473.7 \text{ mA}}}, i_3 = \underline{\underline{1.1052A}}$$

P.P.3.8 $G_{11} = 1/(1) + 1/(10) + 1/(5) = 1.3$, $G_{12} = -1/(5) = -0.2$,
 $G_{33} = 1/(4) + 1 = 1.25$, $G_{44} = 1/(2) + 1/(4) = 0.75$,
 $G_{12} = -1/(5) = -0.2$, $G_{13} = -1$, $G_{14} = 0$,
 $G_{21} = -0.2$, $G_{23} = 0 = G_{26}$,
 $G_{31} = -1$, $G_{32} = 0$, $G_{34} = -1/4 = -0.25$,
 $G_{41} = 0$, $G_{42} = 0$, $G_{43} = 0.25$,
 $i_1 = 0$, $i_2 = 2 - 1 = 1$, $i_3 = -1$, $i_4 = 3$.

Hence,

$$\begin{bmatrix} 1.3 & -0.2 & -1 & 0 \\ -0.2 & 0.2 & 0 & 0 \\ -1 & 0 & 1.25 & -0.25 \\ 0 & 0 & -0.25 & 0.75 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 3 \\ -1 \\ 3 \end{bmatrix}$$


P.P.3.9 $R_{11} = 50 + 40 + 80 = 170$, $R_{22} = 40 + 30 + 10 = 80$,
 $R_{33} = 30 + 20 = 50$, $R_{44} = 10 + 80 = 90$,
 $R_{55} = 20 + 60 = 80$, $R_{12} = -40$, $R_{13} = 0$, $R_{14} = -80$,
 $R_{15} = 0$, $R_{21} = -40$, $R_{23} = -30$, $R_{24} = -10$, $R_{25} = 0$,
 $R_{31} = 0$, $R_{32} = -30$, $R_{34} = 0$, $R_{35} = -20$,
 $R_{41} = -80$, $R_{42} = -10$, $R_{43} = 0$, $R_{45} = 0$,
 $R_{51} = 0$, $R_{52} = 0$, $R_{53} = -20$, $R_{54} = 0$,
 $v_1 = 24$, $v_2 = 0$, $v_3 = -12$, $v_4 = 10$, $v_5 = -10$

Hence the mesh-current equations are

$$\begin{bmatrix} 170 & -40 & 0 & -80 & 0 \\ -40 & 80 & -30 & -10 & 0 \\ 0 & -30 & 50 & 0 & -20 \\ -80 & -10 & 0 & 90 & 0 \\ 0 & 0 & -20 & 0 & 80 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = \begin{bmatrix} 24 \\ 0 \\ -12 \\ 10 \\ -10 \end{bmatrix}$$


P.P.3.10 The schematic is shown below. It is saved and simulated by selecting Analysis/Simulate. The results are shown on the viewpoints:
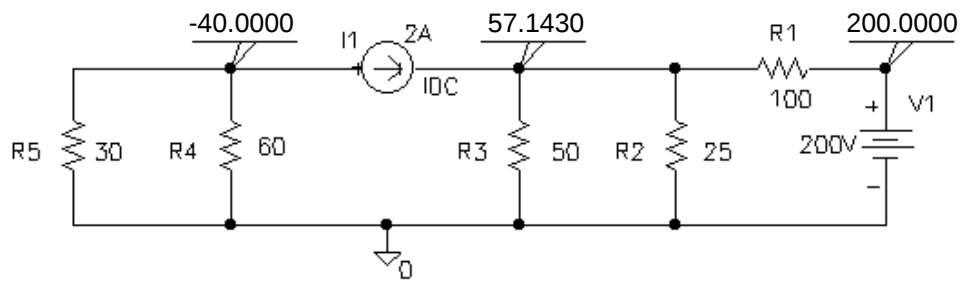
$$v_1 = \underline{-40 \text{ V}}, v_2 = \underline{57.14 \text{ V}}, v_3 = \underline{200 \text{ V}}$$



P.P.3.11 The schematic is shown below. After saving it, it is simulated by choosing Analysis/Simulate. The results are shown on the IPROBES.
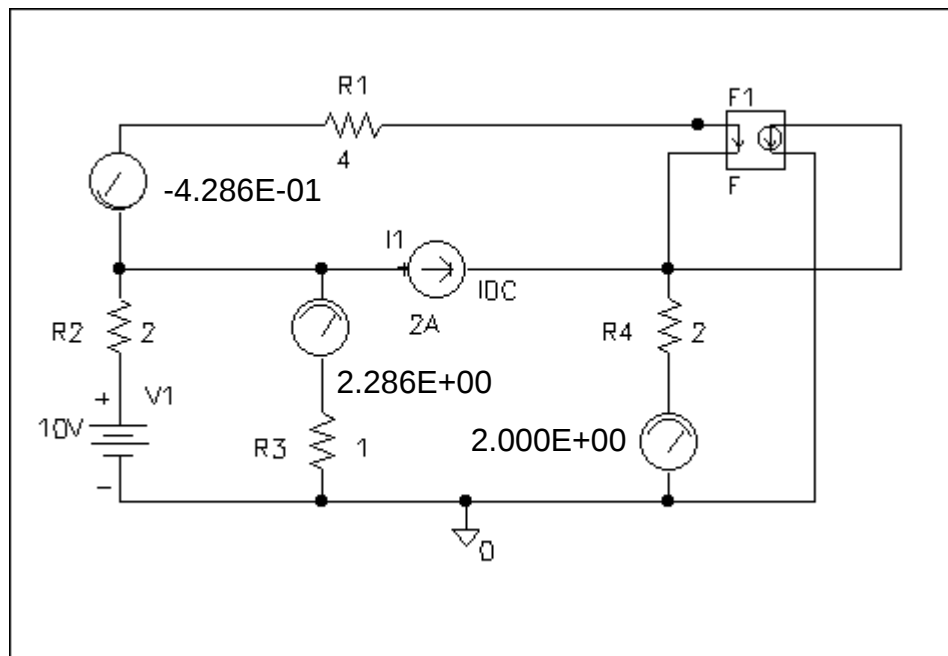
$$i_1 = \underline{-428.6 \text{ mA}}, i_2 = \underline{2.286 \text{ A}}, i_3 = \underline{2 \text{ A}}$$



P.P.3.12 For the input loop,

$$-5 + 10 \times 10^3 I_B + V_{BE} + V_0 = 0 \quad (1)$$

For the outer loop,

$$-V_0 - V_{CE} - 500 I_0 + 12 = 0 \quad (2)$$

But $V_0 = 200 I_E \quad (3)$

Also $I_C = \beta I_B = 100 I_B, \alpha = \beta/(1 + \beta) = 100/(101)$

$$I_C = \alpha I_E \longrightarrow I_E = I_C/(\alpha) = \beta I_B/(\alpha)$$

$$I_E = 100 (101/(100)) I_B = 101 I_B \quad (4)$$

From (1), (3) and (4),

$$10,000 I_B + 200(101) I_B = 5 - V_{BE}$$

$$I_B = \frac{5 - 0.7}{10,000 + 20,000} = 142.38 \mu A$$


$$V_0 = 200 I_E = 20,000 I_B = \underline{\underline{2.876 \text{ V}}}$$

From (2),

$$V_{CE} = 12 - V_0 - 500 I_C = 9.124 - 500 \times 100 \times 142.38 \times 10^{-6}$$

$$V_{CE} = \underline{\underline{1.984 \text{ V} \text{ {often, this is rounded to 2.0 volts}}}}$$

P.P.3.13

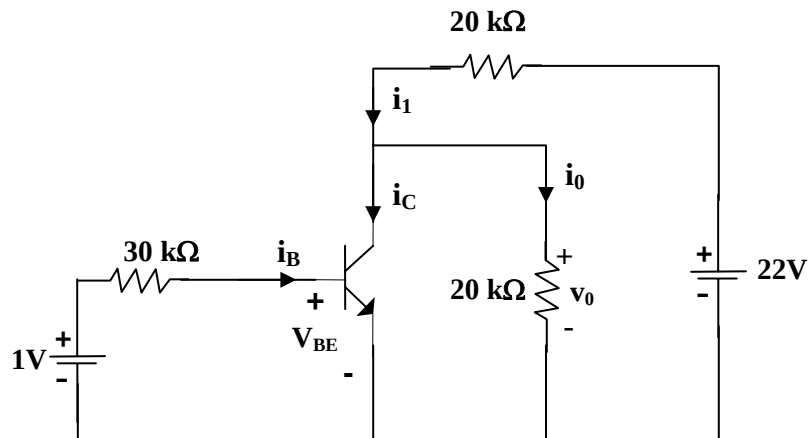

First of all, it should be noted that the circuit in the textbook should have a 22V source on the right hand side rather than the 10 V source.

$$i_B = \frac{1 - 0.7}{30k} = 10\mu A, \quad i_C = \beta i_B = 0.8 \text{ mA}$$

$$i_1 = i_C + i_0 \quad (1)$$

$$\text{Also,} \quad -20ki_0 - 20ki_1 + 22 = 0 \longrightarrow i_1 = 1.1 \text{ mA} - i_0 \quad (2)$$

Equating (1) and (2),

$$1.1\text{mA} - i_0 = 0.8 \text{ mA} + i_0 \longrightarrow i_0 = \underline{\underline{150 \mu A}}$$

$$v_0 = 20 ki_0 = 20 \times 0.15 = \underline{\underline{3 \text{ V}}}$$