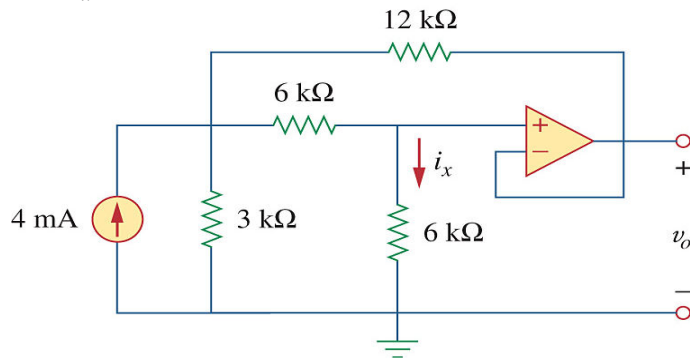


SKEE 1023 CIRCUIT THEORY
SECTION 13
TUTORIAL 6: Operational Amplifier


1. Problem 5.31

Find i_x




2. Problem 5.32

Find i_x and v_o

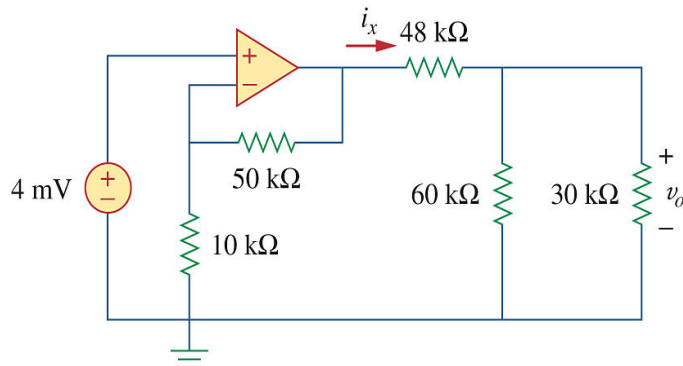


3. Problem 5.40

Find v_o in terms of v_1 , v_2 , and v_3

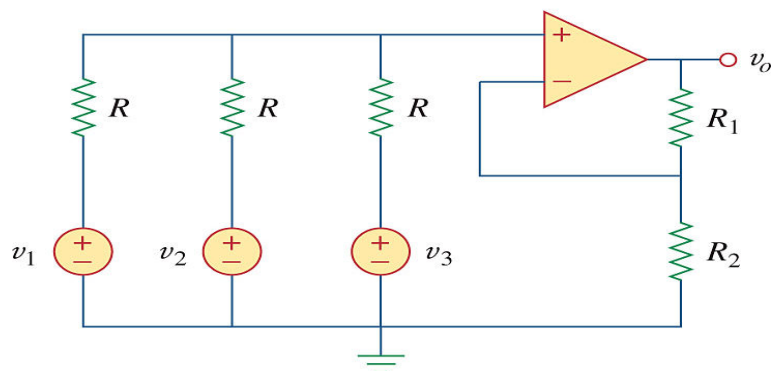


4. Problem 5.57

Find v_o

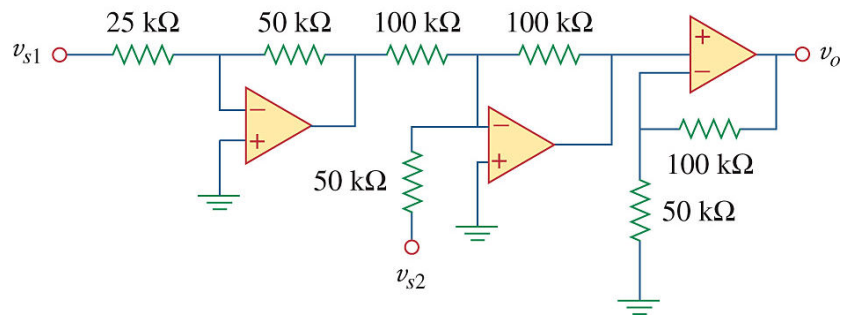

5. Problem 5.60

Calculate v_o/v_i

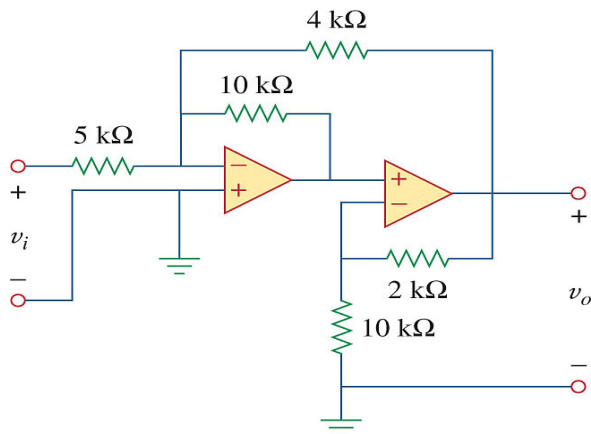

6. Problem 5.71 (Assignment group F)

Determine v_o

