

**SKEE 1023 CIRCUIT THEORY**  
**SECTION 13**  
**TUTORIAL 7: AC CIRCUITS**

1. Problem 9.5


Given  $v_1 = 20 \sin(\omega t + 60^\circ)$  and  $v_2 = 60 \cos(\omega t - 10^\circ)$ , determine the phase angle between the two sinusoids and which one lags the other

2. Problem 9.17

Two voltages  $v_1$  and  $v_2$  appear in series so that their sum is  $v = v_1 + v_2$ . If  $v_1 = 10 \cos(50t - \pi/3)$  V and  $v_2 = 12 \cos(50t + 30^\circ)$  V. Find  $v$ .


3. Problem 10.3

Determine  $v_o$

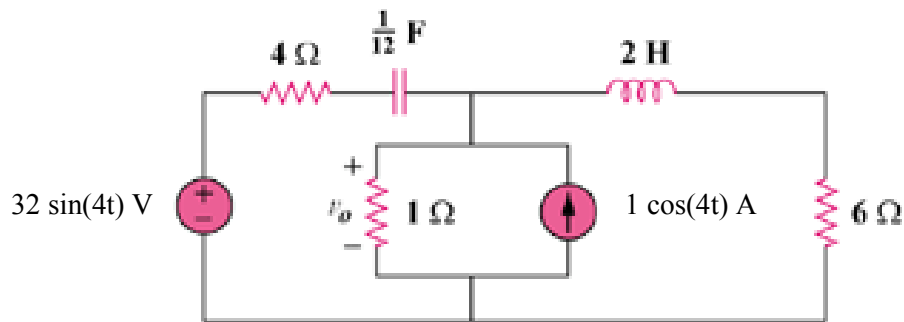

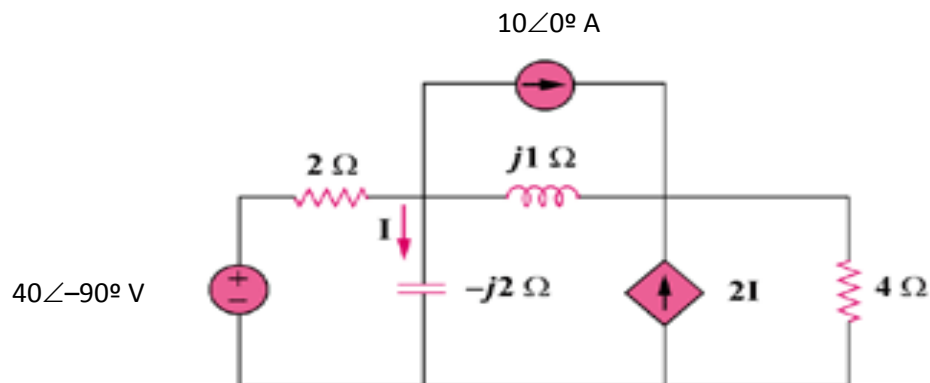
4. Problem 10.15

Solve for the current  $\mathbf{I}$  using nodal analysis.



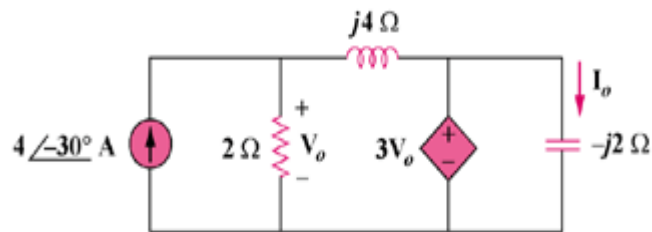
5. Problem 10.32

Determine  $V_o$  and  $I_o$  mesh analysis.




6. Problem 10.48

Find  $i_o$  using superposition.

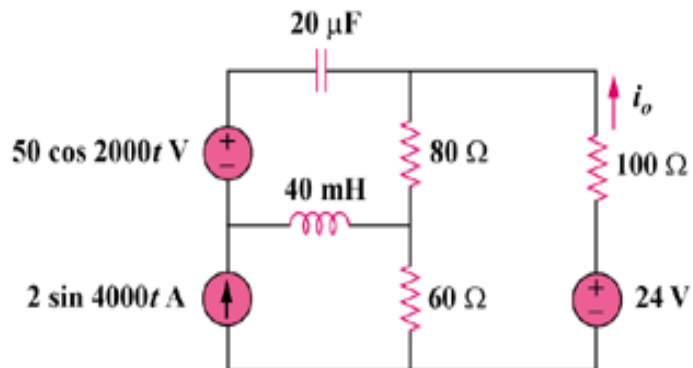

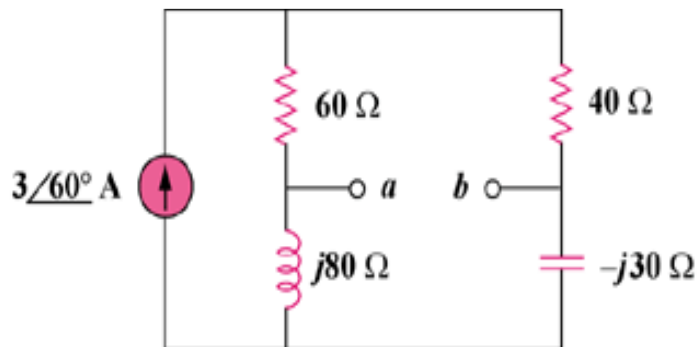7. Problem 10.64

Find the Norton equivalent circuit at terminals  $a-b$ .




8. Problem 9.90 (Assignment group G)

An industrial coil is modeled as a series combination of an inductance  $L$  and resistance  $R$ . Since an ac voltmeter measures only the magnitude of a sinusoid, the following measurements are taken at 60 Hz when the circuit operates in the steady state:

$$|V_s| = 145\text{V}, \quad |V_1| = 50\text{V}, \quad |V_o| = 110\text{V}$$

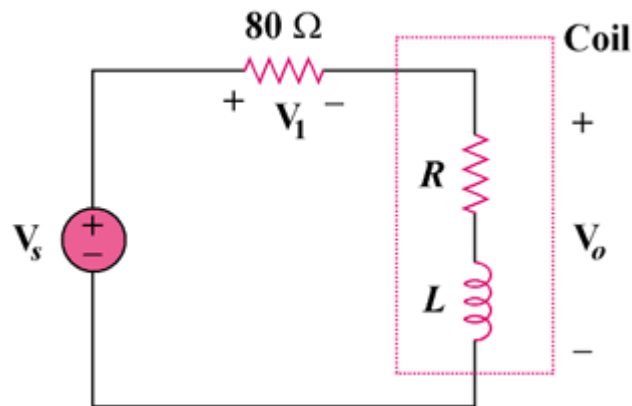Use these measurements to determine the values of  $L$  and  $R$ .



9. Problem 10.75 (Assignment group H)

Find the closed-loop gain and phase shift of the output voltage with respect to the input voltage if  $C_1 = C_2 = 1\text{ nF}$ ,  $R_1 = R_2 = 100\text{ k}\Omega$ ,  $R_3 = 20\text{ k}\Omega$ ,  $R_4 = 40\text{ k}\Omega$ , and  $\omega = 2000\text{ rad/s}$ .

