


AC CIRCUITS

Sinusoids & phasors; Impedance & Admittance;
Kirchhoff's Law in Frequency Domain

SINUSOIDS

- ▶ A sinusoid is a signal that has the form of the sine or cosine function.
- ▶ A sinusoidal current is called alternating current (ac). It reverses at regular time intervals and has alternately positive and negative values
- ▶ AC circuits are circuits driven by sinusoidal current or voltages.

Sinusoids

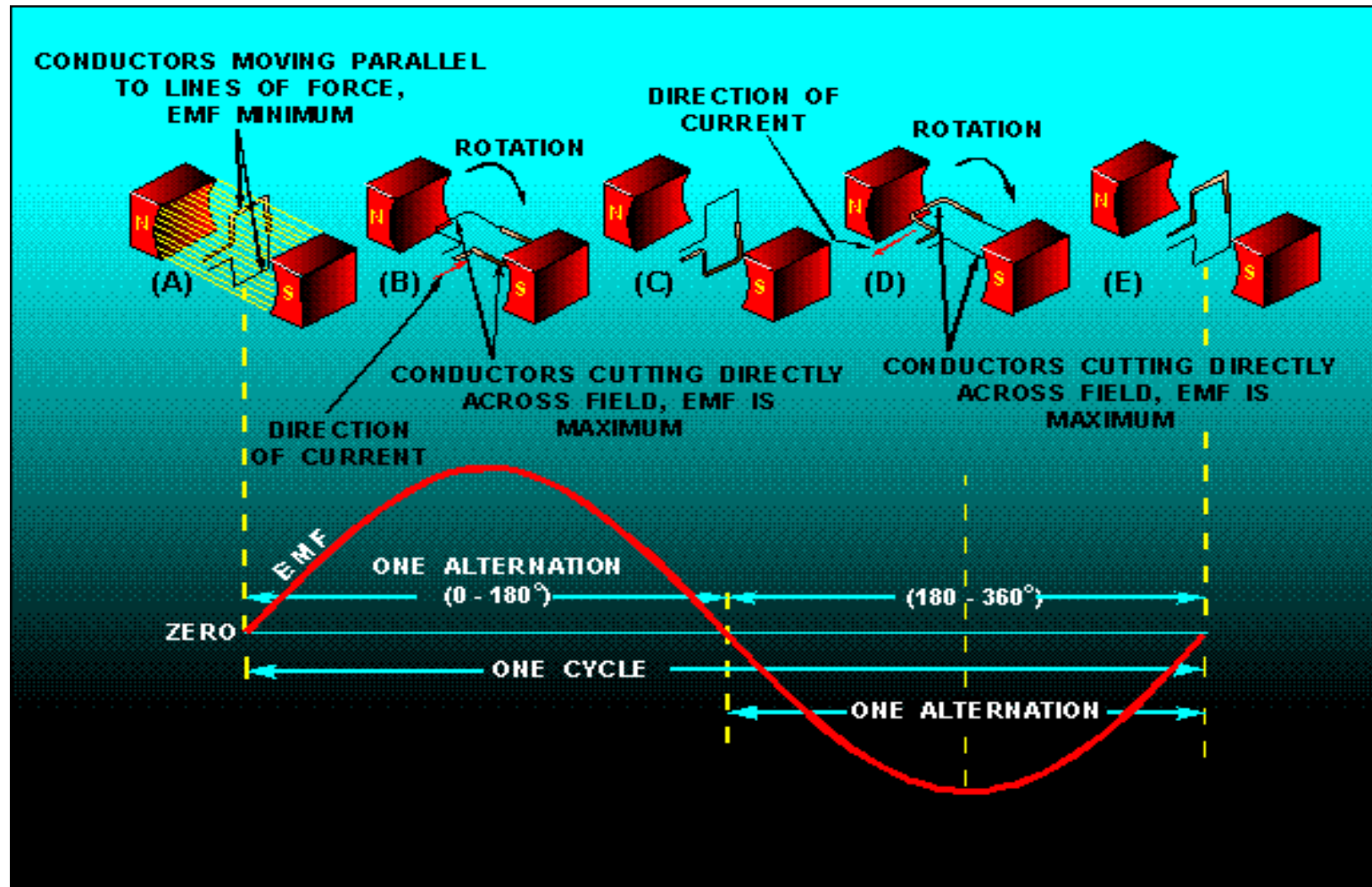

Sinusoids

- ▶ Considering a sinusoidal voltage,

$$v(t) = V_m \sin \omega t$$


where

V_m = the amplitude of the sinusoid


ω = the angular frequency in radians/s

ωt = the argument of the sinusoid

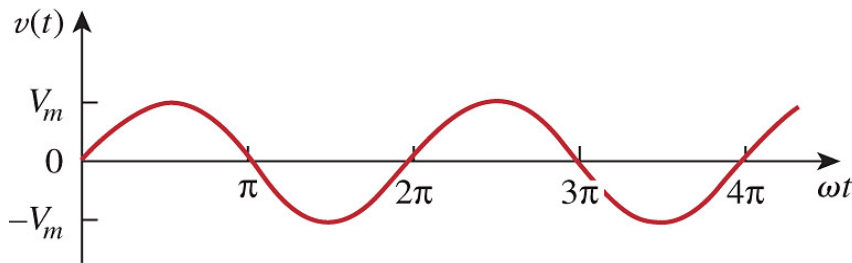Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



(a)

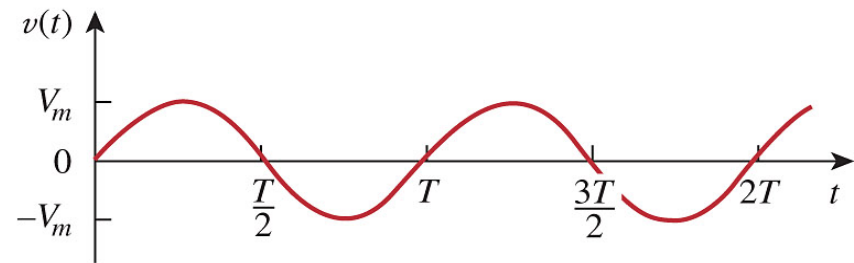

(b)

$$\omega T = 2\pi$$

$$T = \frac{2\pi}{\omega}$$

Sinusoids

A periodic function is one that satisfies $v(t) = v(t + nT)$, for all t and for all integers n

$$f = \frac{1}{T}$$

f is in Hertz (Hz)

$$\omega = 2\pi f$$

ω is in radians per second


Sinusoids

A more general expression for a sinusoid

$$v(t) = V_m \sin(\omega t + \phi)$$

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

ϕ = the phase

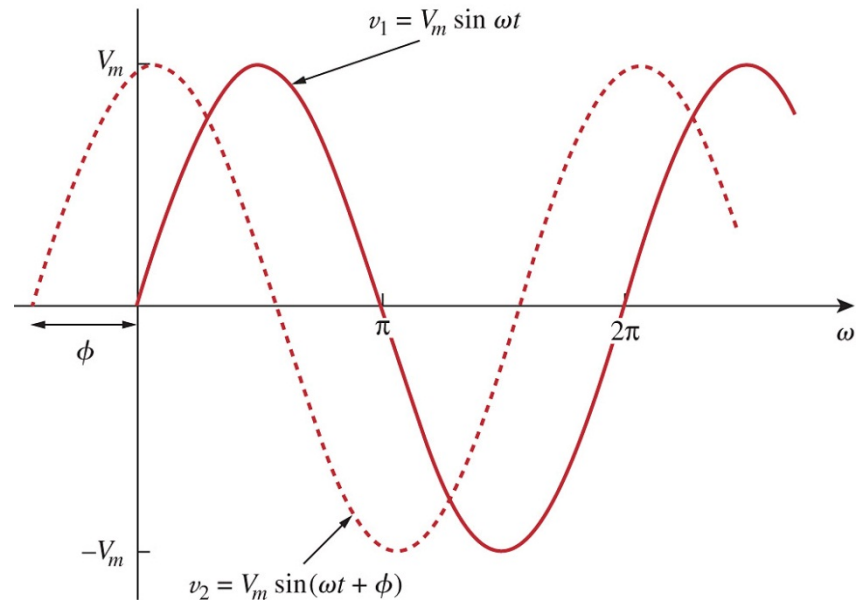

- Only two sinusoidal values with the same frequency can be compared by their amplitude and phase difference.
- If phase difference is zero, they are in phase; if phase difference is not zero, they are out of phase.

Sinusoids

- A sinusoid can be expressed in either sine or cosine form.
- When comparing two sinusoids, it is better to express both as either sine or cosine with positive amplitudes.
- To achieve this, 2 approaches can be used:
 1. Trigonometric identities
 2. Graphical approach

$$\sin(A \pm B) = \sin A \cos B \pm \cos A \sin B$$

$$\cos(A \pm B) = \cos A \cos B \mp \sin A \sin B$$

$$\sin(\omega t \pm 180^\circ) = -\sin \omega t$$


$$\cos(\omega t \pm 180^\circ) = -\cos \omega t$$

$$\sin(\omega t \pm 90^\circ) = \pm \cos \omega t$$


$$\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$$

Sinusoids

Phase Relations

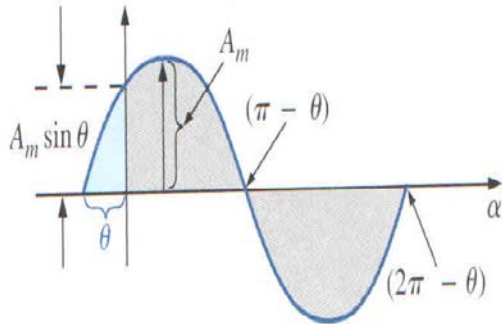

$$A_m \sin(\omega t + \theta)$$

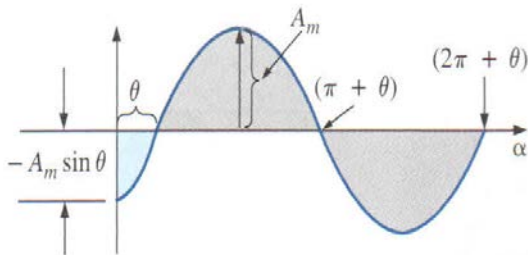

$$A_m \sin(\omega t - \theta)$$

Sinusoids

Practice Problem 9.1

Given the sinusoid $5 \sin(4\pi t - 60^\circ)$, calculate its amplitude, phase, angular frequency, period and frequency.

Practice Problem 9.2

Find the phase angle between $i_1 = -4 \sin(377t + 25^\circ)$ and $i_2 = 5 \cos(377t - 40^\circ)$. Does i_1 lead or lag i_2 ?

PHASORS

- ▶ A phasor is a complex number that represents the amplitude and phase of a sinusoid.
- ▶ It can be represented in one of the following three forms:

a. Rectangular $z = x + jy = r(\cos \phi + j \sin \phi)$


b. Polar $z = r \angle \phi$

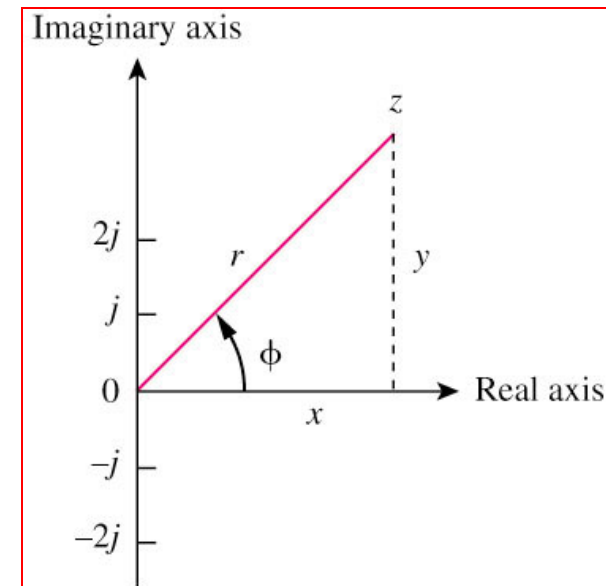c. Exponential



where

$$r = \sqrt{x^2 + y^2}$$
$$\phi = \tan^{-1} \frac{y}{x}$$



Phasors

Mathematic operation of complex number:

1. Addition

$$z_1 + z_2 = (x_1 + x_2) + j(y_1 + y_2)$$

2. Subtraction

$$z_1 - z_2 = (x_1 - x_2) + j(y_1 - y_2)$$

3. Multiplication

$$z_1 z_2 = r_1 r_2 \angle \phi_1 + \phi_2$$

4. Division

$$\frac{z_1}{z_2} = \frac{r_1}{r_2} \angle \phi_1 - \phi_2$$

5. Reciprocal

$$\frac{1}{z} = \frac{1}{r} \angle -\phi$$

6. Square root

$$\sqrt{z} = \sqrt{r} \angle \phi/2$$

7. Complex conjugate

$$z^* = x - jy = r \angle -\phi = r e^{-j\phi}$$

8. Euler's identity

$$e^{\pm j\phi} = \cos \phi \pm j \sin \phi$$

Phasors

- ▶ Transform a sinusoid to and from the time domain to the phasor domain:

$$v(t) = V_m \cos(\omega t + \phi) \longleftrightarrow V = V_m \angle \phi$$

(time domain)

(phasor domain)

- Amplitude and phase difference are two principal concerns in the study of voltage and current sinusoids.
- Phasor will be defined from the cosine function in all our proceeding study. If a voltage or current expression is in the form of a sine, it will be changed to a cosine by subtracting from the phase.

Phasors

Sinusoidal-Phasor Transformation

Time domain representation

$$V_m = \cos(\omega t + \phi)$$

$$V_m = \sin(\omega t + \phi)$$

$$I_m = \cos(\omega t + \phi)$$

$$I_m = \sin(\omega t + \phi)$$

Phasor domain representation

$$V_m \angle \phi$$

$$V_m \angle \phi - 90^\circ$$

$$I_m \angle \phi$$

$$I_m \angle \phi - 90^\circ$$

Phasors

The differences between $v(t)$ and V :

- ▶ $v(t)$ is instantaneous or time-domain representation
 V is the frequency or phasor-domain representation.
- ▶ $v(t)$ is time dependent, V is not.
- ▶ $v(t)$ is always real with no complex term, V is generally complex.

Note: Phasor analysis applies only when frequency is constant; when it is applied to two or more sinusoid signals only if they have the same frequency.

Phasors

Relationship between differential, integral operation in phasor listed as follow:

$$v(t) \longleftrightarrow V = V \angle \phi$$

$$\frac{dv}{dt} \longleftrightarrow j\omega V$$

$$\int v dt \longleftrightarrow \frac{V}{j\omega}$$

Phasors

Practice Problem 9.4

Express these sinusoids as phasors:

a. $v = 7 \cos(2t + 40^\circ) V$

b. $i = -4 \sin(10t + 10^\circ) A$

Practice Problem 9.5

Find the sinusoids corresponding to these phasors:

a. $V = -10 \angle 30^\circ V$

b. $j(5 - j12) A$

Practice Problem 9.6

If $v_1 = -10 \sin(\omega t - 30^\circ) V$ and $v_2 = 20 \cos(\omega t + 45^\circ) V$.

Find $v = v_1 + v_2$


Phasors

Practice Problem 9.7


Find the voltage $v(t)$ in a circuit described by the integrodifferential equation

$$2 \frac{dv}{dt} + 5v + 10 \int v dt = 50 \cos(5t - 30^\circ)$$

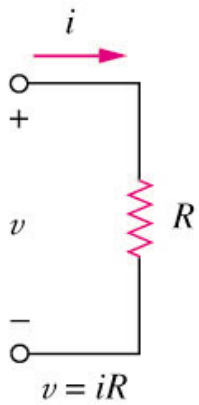
PHASORS RELATIONSHIPS FOR CIRCUIT ELEMENTS




(a)

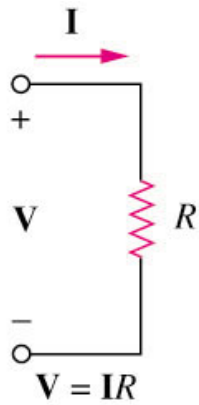


(b)

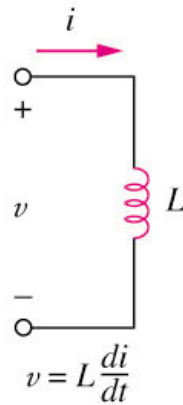


(a)

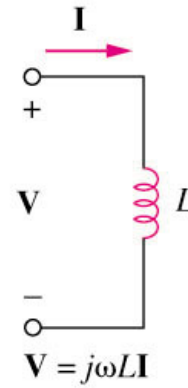




(b)

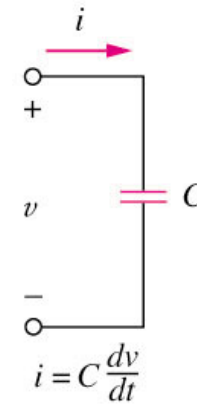

(a)

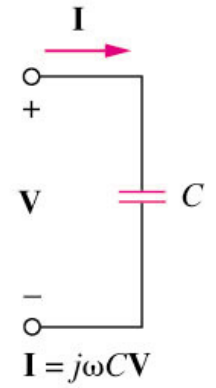

(b)

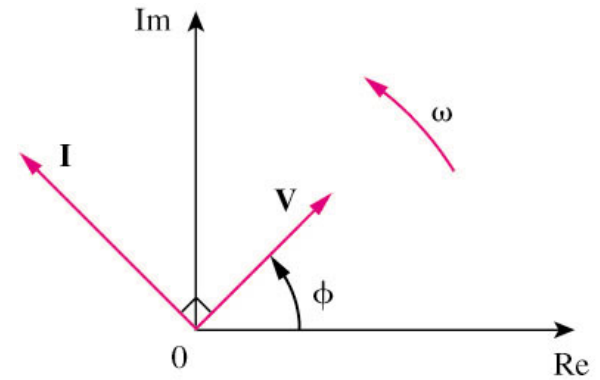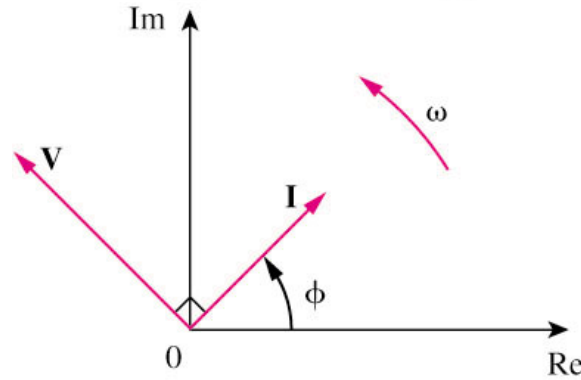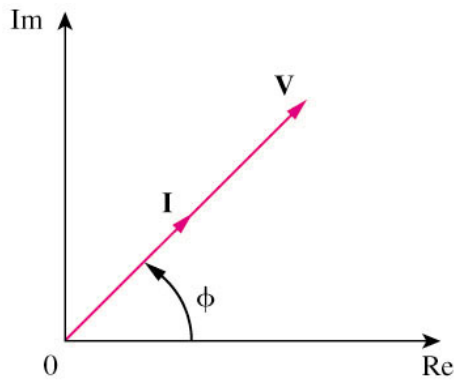

PHASORS RELATIONSHIPS FOR CIRCUIT ELEMENTS

Summary of voltage-current relationship

Element	Time domain	Frequency domain
R	$v = Ri$	$V = RI$
L	$v = L \frac{di}{dt}$	$V = j\omega LI$
C	$i = C \frac{dv}{dt}$	$V = \frac{I}{j\omega C}$

Phasors

Practice Problem 9.8

If $v = 10 \cos(100t + 30^\circ)$ is applied to a $50\mu F$ capacitor, calculate the current through the capacitor.

Example 9.8

The voltage $v = 12 \cos(60t + 45^\circ)$ is applied to a 0.1-H inductor. Find the steady-state current through the inductor.

Practice Problem 9.3

Evaluate the following complex numbers:

(a) $[(5 + j2)(-1 + j4) - 5\angle 60^\circ]^*$

(b) $\frac{10 + j5 + 3\angle 40^\circ}{-3 + j4} + 10\angle 30^\circ + j5$

IMPEDANCE & ADMITTANCE

- ▶ The impedance Z of a circuit is the ratio of the phasor voltage V to the phasor current I , measured in ohms Ω . It is a frequency-dependent quantity.
- ▶ It represents the opposition that the circuit exhibits to the flow of sinusoidal current.

$$Z = \frac{V}{I} = R + jX = |Z| \angle \theta$$

where $R = \text{Re } Z$ is the resistance and $X = \text{Im } Z$ is the reactance.

- ▶ The admittance Y is the reciprocal of impedance, measured in siemens (S).

$$Y = \frac{1}{Z} = \frac{I}{V} = G + jB$$

where $G = \text{Re } Y$ is the conductance and $B = \text{Im } Y$ is the susceptance.

Impedance & Admittance

Impedances and admittances of passive elements


Element	Impedance	Admittance
R	$Z = R$	$Y = \frac{1}{R}$
L	$Z = j\omega L$	$Y = \frac{1}{j\omega L}$
C	$Z = \frac{1}{j\omega C}$	$Y = j\omega C$

$Z = R + jX$ inductive/lagging (I lags V)

$Z = R - jX$ capacitive/leading (I leads V)


Impedance & Admittance

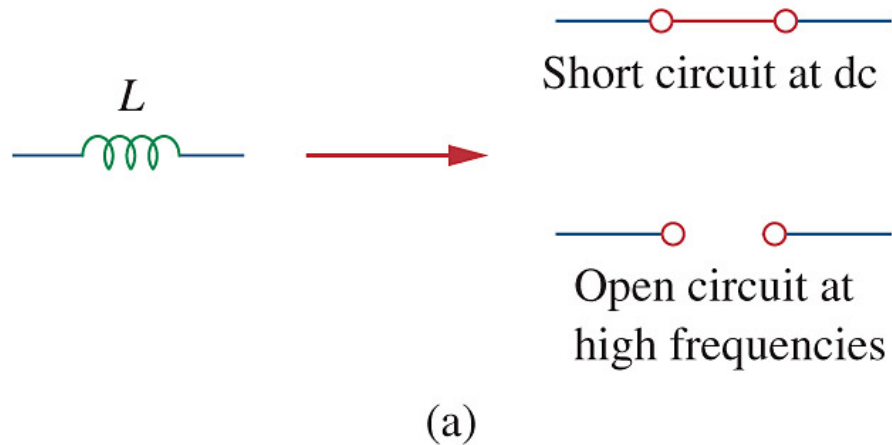Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



$$\omega = 0; Z = 0$$
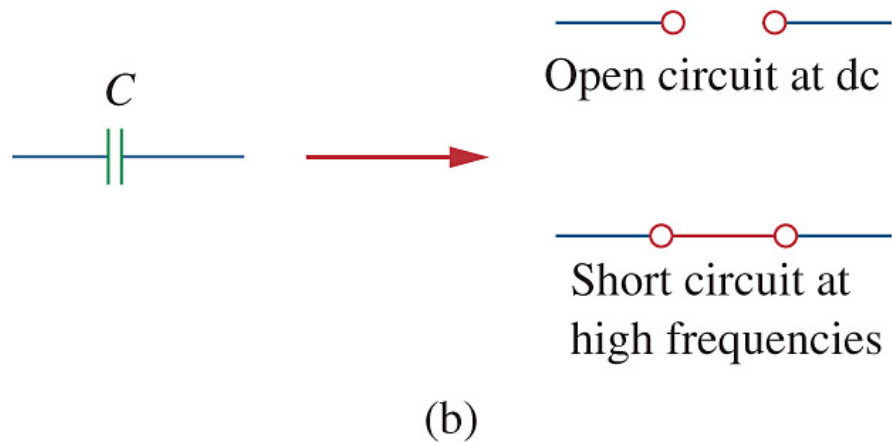
$$\omega \rightarrow \infty; Z \rightarrow \infty$$



$$\omega = 0; Z \rightarrow \infty$$


$$\omega \rightarrow \infty; Z = 0$$

Impedance & Admittance

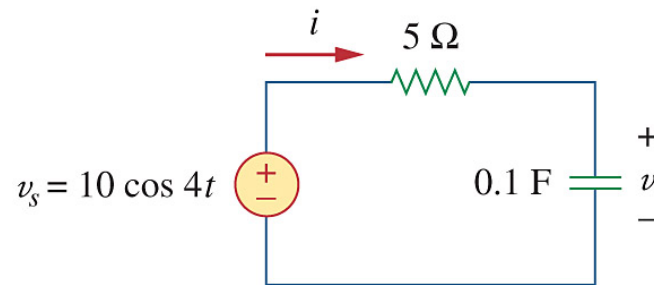Example 9.9

Find $v(t)$ and $i(t)$ in the circuit below:


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Practice Problem 9.9

Determine $v(t)$ and $i(t)$ in the circuit below:

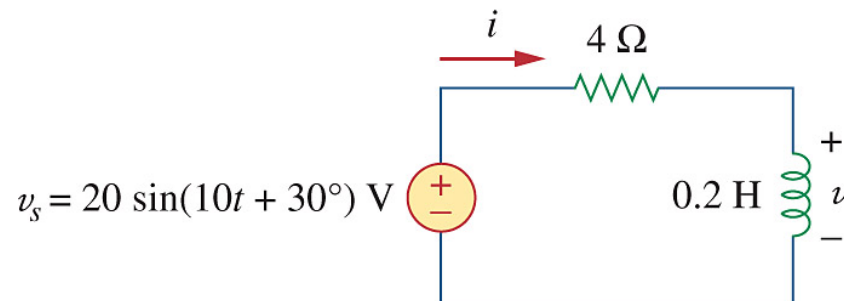Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




KIRCHHOFF'S LAWS IN THE FREQUENCY DOMAIN

- ▶ Both KVL and KCL are hold in the phasor domain (frequency domain).
- ▶ Variables to be handled are phasors, which are complex numbers.
- ▶ All the mathematical operations involved are now in complex domain.
- ▶ The following principles used for DC circuit analysis all apply to AC circuit:
 - a.voltage division
 - b.current division
 - c.circuit reduction
 - d.impedance equivalence
 - e.Y- Δ transformation

KIRCHHOFF'S LAWS IN THE FREQUENCY DOMAIN

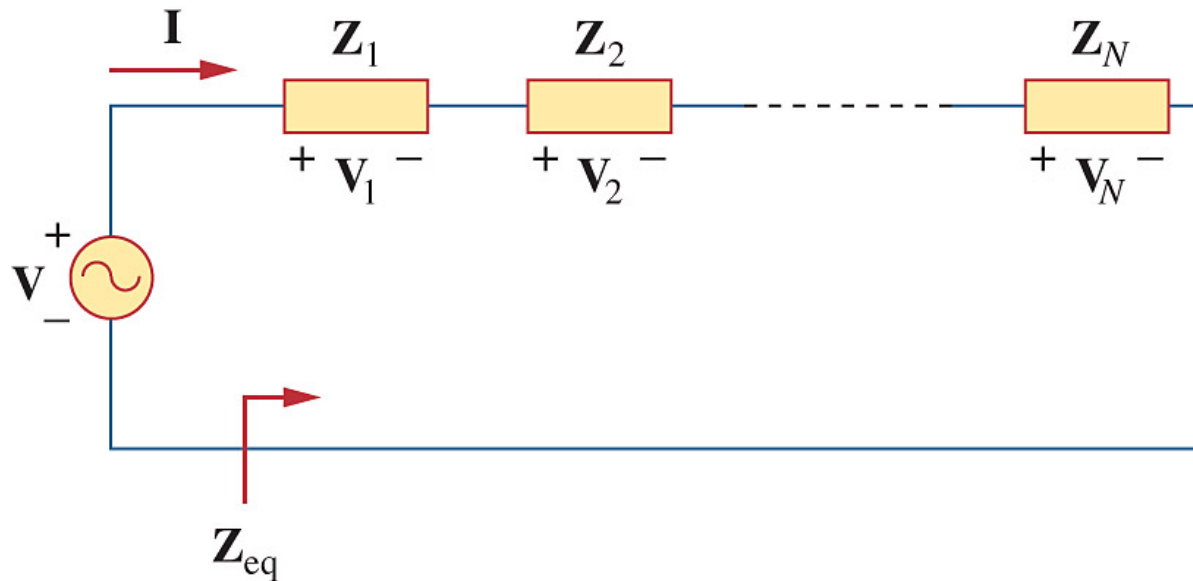
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



$$Z_{eq} = Z_1 + Z_2 + \dots + Z_N$$

KIRCHHOFF'S LAWS IN THE FREQUENCY DOMAIN

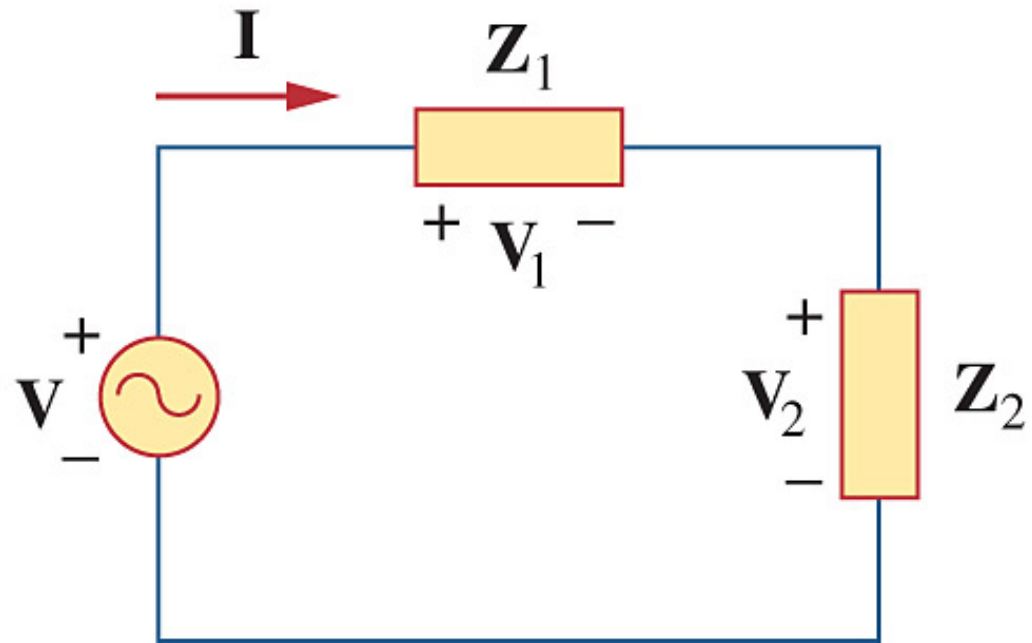Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




$$V_1 = \frac{Z_1}{Z_1 + Z_2} V$$

$$V_2 = \frac{Z_2}{Z_1 + Z_2} V$$

KIRCHHOFF'S LAWS IN THE FREQUENCY DOMAIN

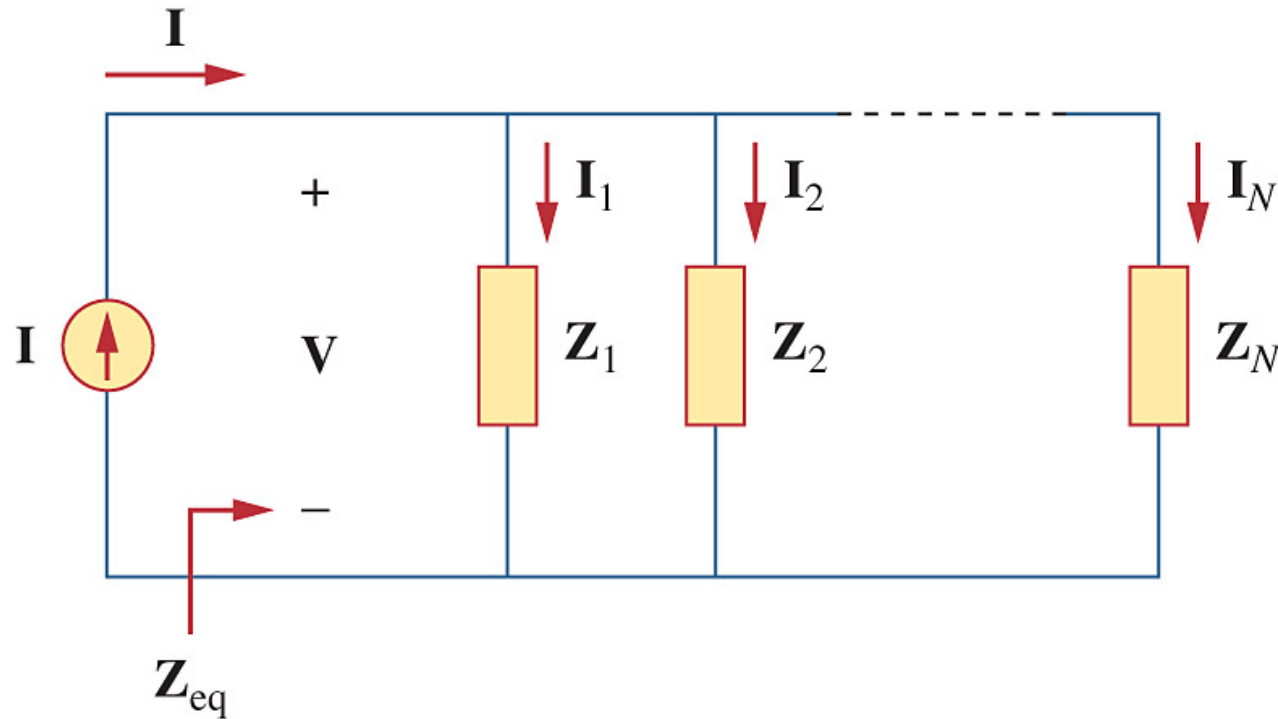Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




$$\frac{1}{Z_{eq}} = \frac{I}{V} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N}$$

$$Y_{eq} = Y_1 + Y_2 + \dots + Y_N$$

KIRCHHOFF'S LAWS IN THE FREQUENCY DOMAIN

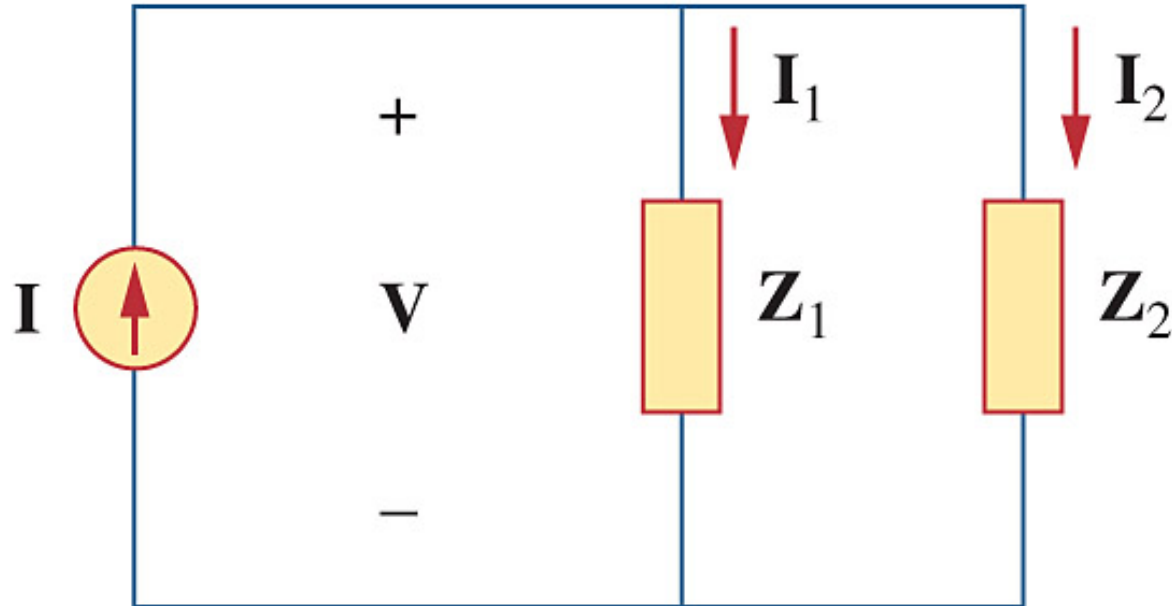Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




$$I_1 = \frac{Z_2}{Z_1 + Z_2} I$$

$$I_2 = \frac{Z_1}{Z_1 + Z_2} I$$

KIRCHHOFF'S LAWS IN THE FREQUENCY DOMAIN

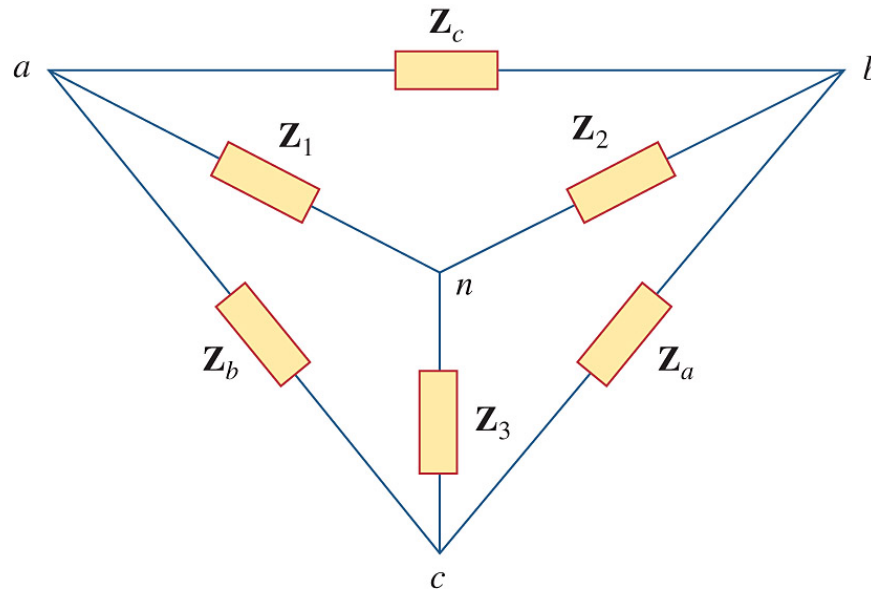Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



$$Z_a = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_1}$$

$$Z_b = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_2}$$

$$Z_c = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_3}$$

$$Z_1 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c}$$

$$Z_2 = \frac{Z_c Z_a}{Z_a + Z_b + Z_c}$$


$$Z_3 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c}$$

KIRCHHOFF'S LAWS IN THE FREQUENCY DOMAIN

Practice Problem 9.10

Determine the input impedance of the circuit below at $\omega = 10 \text{ rad/s}$

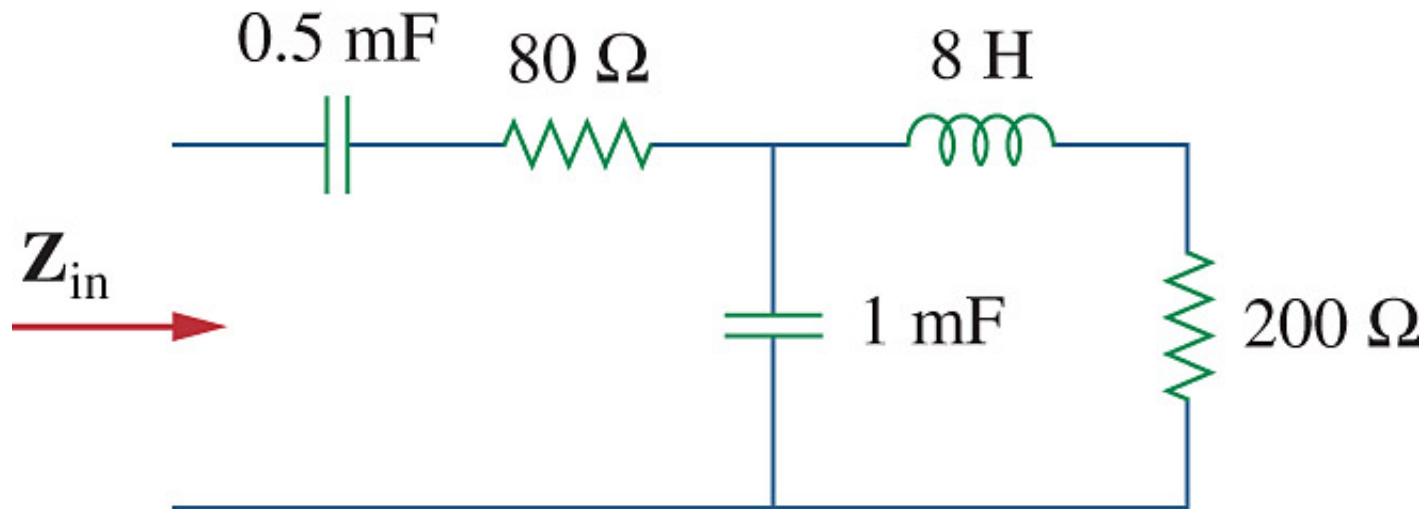Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




KIRCHHOFF'S LAWS IN THE FREQUENCY DOMAIN

Practice Problem 9.11

Calculate v_o in the circuit below:

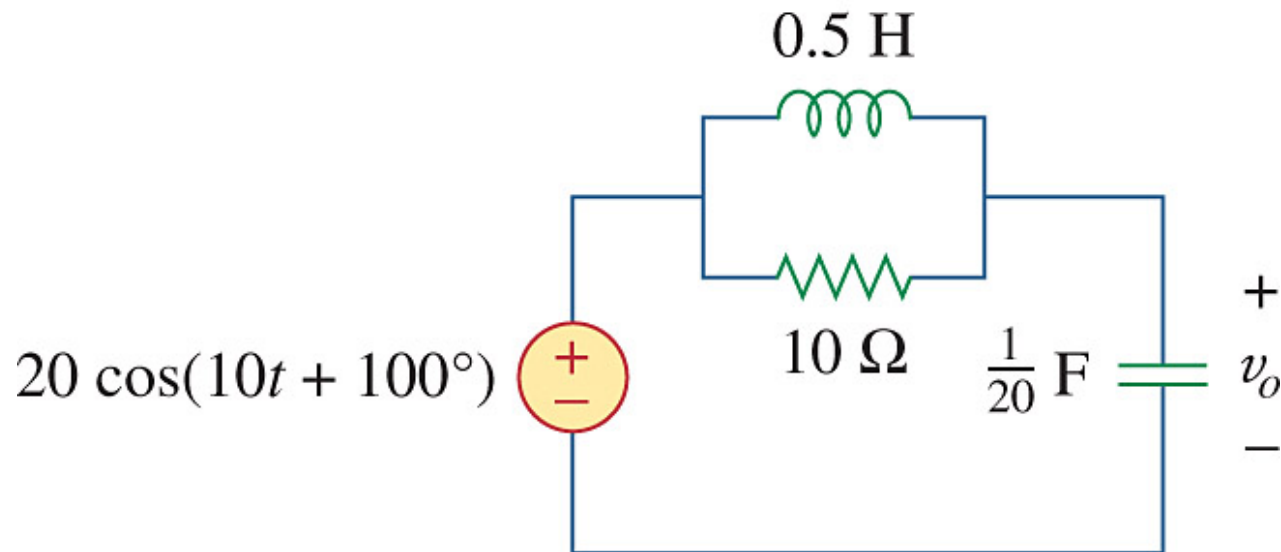Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




KIRCHHOFF'S LAWS IN THE FREQUENCY DOMAIN

Practice Problem 9.12

Find I in the circuit below:

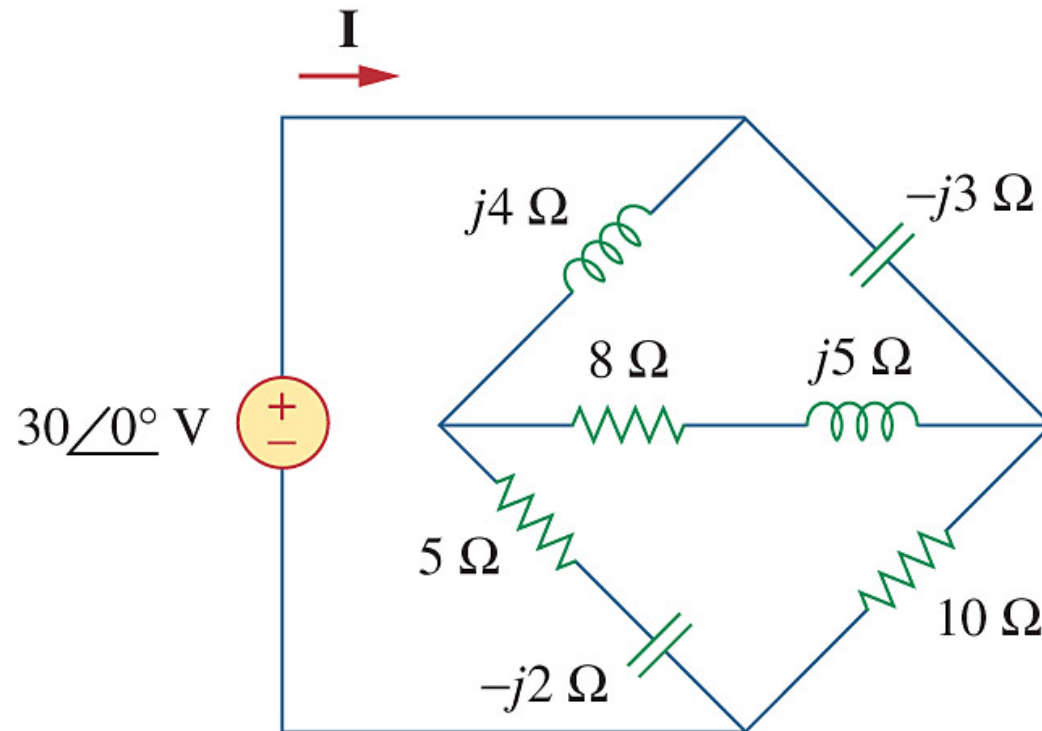Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



TUTORIALS (sinusoids)

Problem 9.6

For the following pairs of sinusoids, determine which one leads and by how much.

1. $v(t) = 10 \cos(4t - 60^\circ)$ and $i(t) = 4 \sin(4t + 50^\circ)$
2. (b) $v_1(t) = 4 \cos(377t + 10^\circ)$ and $v_2(t) = -20 \cos 377t$
3. (c) $x(t) = 13 \cos 2t + 5 \sin 2t$ and $y(t) = 15 \cos(2t - 11.8^\circ)$

TUTORIALS (Phasors)

1. Find the phasors corresponding to the following signals.
 - (a) $v(t) = 21 \cos(4t - 15^\circ) \text{ V}$
 - (b) $i(t) = -8 \sin(10t + 70^\circ) \text{ mA}$
 - (c) $v(t) = 120 \sin(10t - 50^\circ) \text{ V}$
 - (d) $i(t) = -60 \cos(30t + 10^\circ) \text{ mA}$

2. Using phasors, find:
 - (a) $3 \cos(20t + 10^\circ) - 5 \cos(20t - 30^\circ)$
 - (b) $40 \sin 50t + 30 \cos(50t - 45^\circ)$
 - (c) $20 \sin 400t + 10 \cos(400t + 60^\circ) - 5 \sin(400t - 20^\circ)$


3. Find $v(t)$ in the following integrodifferential equations using the phasor approach:
 - (a) $v(t) + \int v \, dt = 5 \cos(t + 45^\circ) \text{ V}$
 - (b) $\frac{dv}{dt} + 5v(t) + 4 \int v \, dt = 20 \sin(4t + 10^\circ) \text{ V}$

TUTORIALS (Impedance & Admittance)

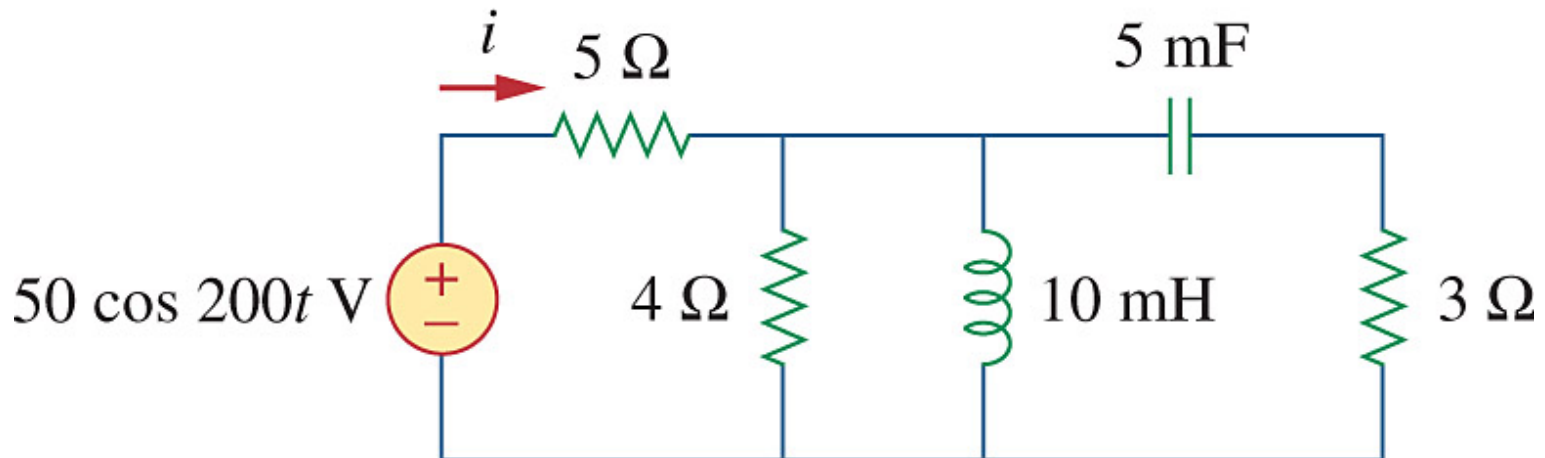Problem 9.44

Calculate $i(t)$ in the circuit below:

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




TUTORIALS (Impedance & Admittance)

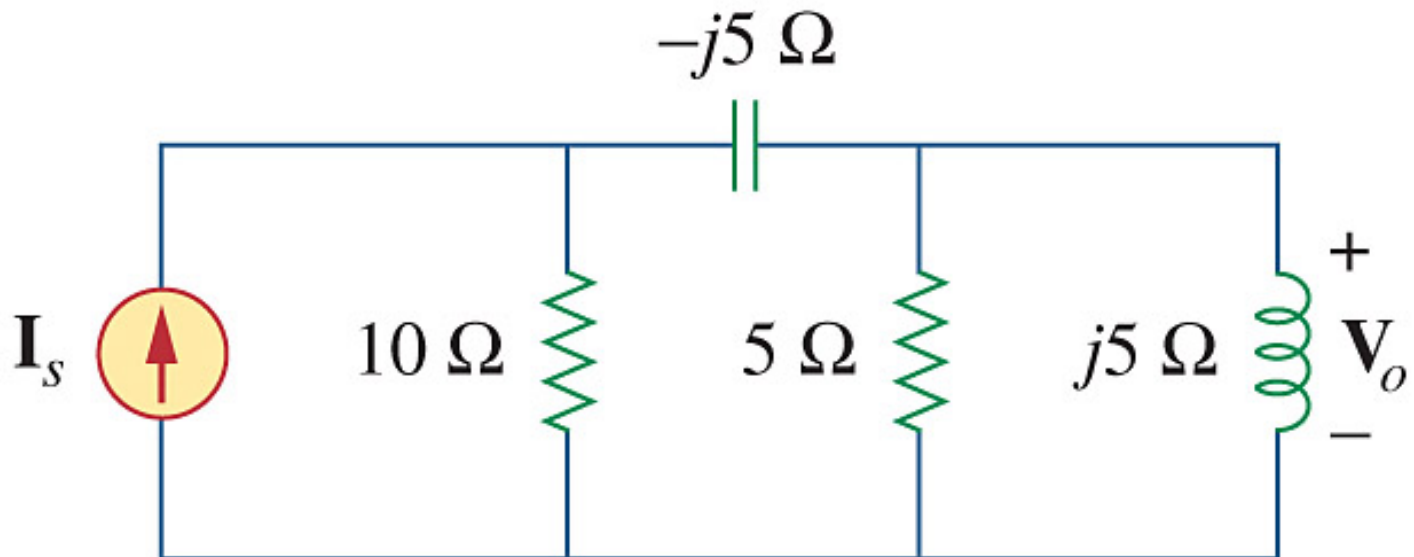Problem 9.52

If $V_o = 20\angle 45^\circ$ V in the circuit, find I_s :

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



TUTORIALS (Impedance & Admittance)

Problem 9.55*

Given $V_o = 8\angle 0^\circ$ V, find the Z . What are the elements are contained in Z ? Calculate the value of their resistances/reactances if the system frequency is 50 Hz.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

