


# AC CIRCUITS

Sinusoids and phasors

# SINUSOIDS

- ▶ A sinusoid is a signal that has the form of the sine or cosine function.
- ▶ A sinusoidal current is called alternating current (ac). It reverses at regular time intervals and has alternately positive and negative values
- ▶ AC circuits are circuits driven by sinusoidal current or voltages.

# Sinusoids

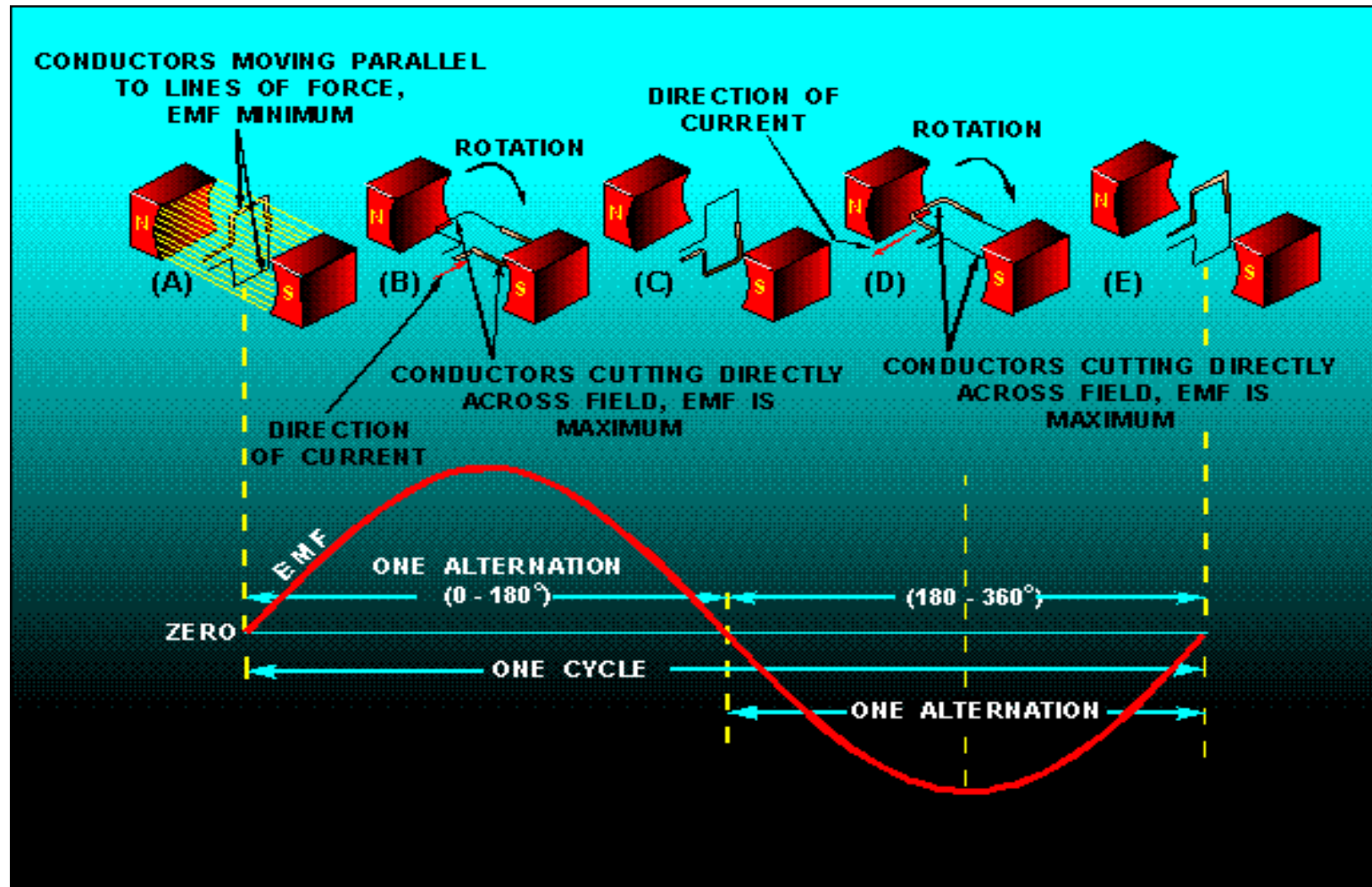

# Sinusoids

- ▶ Considering a sinusoidal voltage,

$$v(t) = V_m \sin \omega t$$


where

$V_m$  = the amplitude of the sinusoid


$\omega$  = the angular frequency in radians/s

$\omega t$  = the argument of the sinusoid

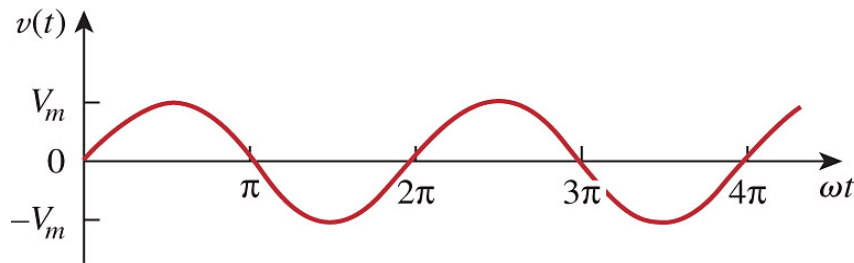Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



(a)

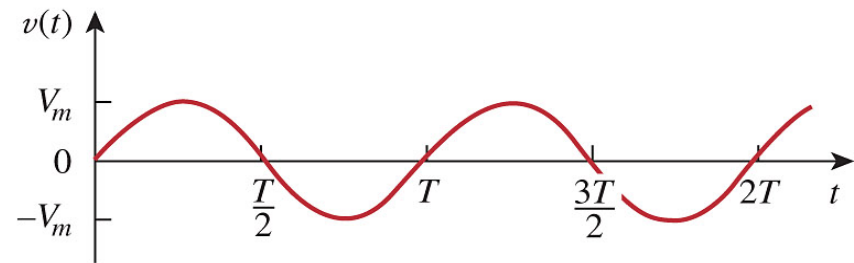

(b)

$$\omega T = 2\pi$$

$$T = \frac{2\pi}{\omega}$$

# Sinusoids

A periodic function is one that satisfies  $v(t) = v(t + nT)$ , for all  $t$  and for all integers  $n$

$$f = \frac{1}{T}$$

$f$  is in Hertz (Hz)

$$\omega = 2\pi f$$

$\omega$  is in radians per second


# Sinusoids

A more general expression for a sinusoid

$$v(t) = V_m \sin(\omega t + \phi)$$

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

$\phi$  = the phase

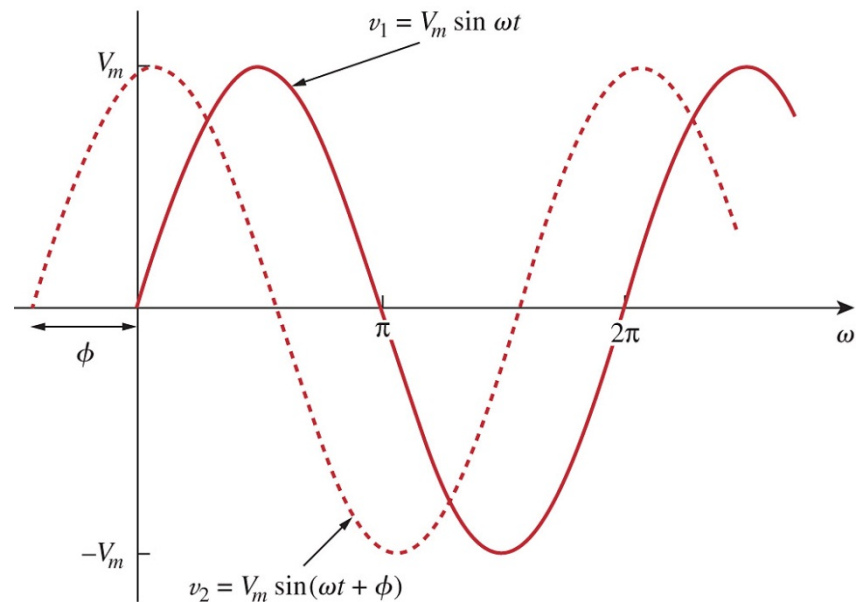

- Only two sinusoidal values with the same frequency can be compared by their amplitude and phase difference.
- If phase difference is zero, they are in phase; if phase difference is not zero, they are out of phase.

# Sinusoids

- A sinusoid can be expressed in either sine or cosine form.
- When comparing two sinusoids, it is better to express both as either sine or cosine with positive amplitudes.
- To achieve this, 2 approaches can be used:
  1. Trigonometric identities
  2. Graphical approach

$$\sin(A \pm B) = \sin A \cos B \pm \cos A \sin B$$

$$\cos(A \pm B) = \cos A \cos B \mp \sin A \sin B$$

$$\sin(\omega t \pm 180^\circ) = -\sin \omega t$$


$$\cos(\omega t \pm 180^\circ) = -\cos \omega t$$

$$\sin(\omega t \pm 90^\circ) = \pm \cos \omega t$$


$$\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$$

# Sinusoids

## Phase Relations

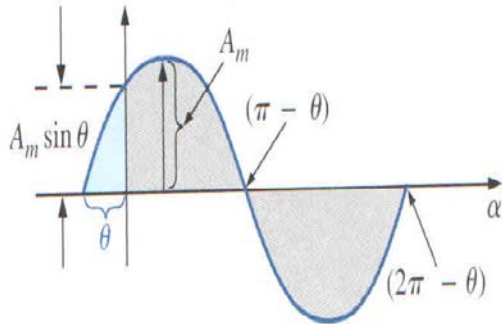

$$A_m \sin(\omega t + \theta)$$

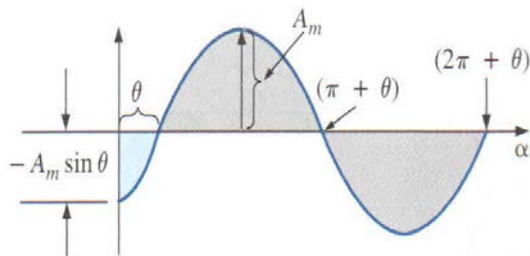

$$A_m \sin(\omega t - \theta)$$



# Sinusoids

## Practice Problem 9.1

Given the sinusoid  $5 \sin(4\pi t - 60^\circ)$ , calculate its amplitude, phase, angular frequency, period and frequency.

## Practice Problem 9.2

Find the phase angle between  $i_1 = -4 \sin(377t + 25^\circ)$  and  $i_2 = 5 \cos(377t - 40^\circ)$ . Does  $i_1$  lead or lag  $i_2$ ?

# PHASORS

- ▶ A phasor is a complex number that represents the amplitude and phase of a sinusoid.
- ▶ It can be represented in one of the following three forms:

a. Rectangular  $z = x + jy = r(\cos \phi + j \sin \phi)$


b. Polar  $z = r \angle \phi$

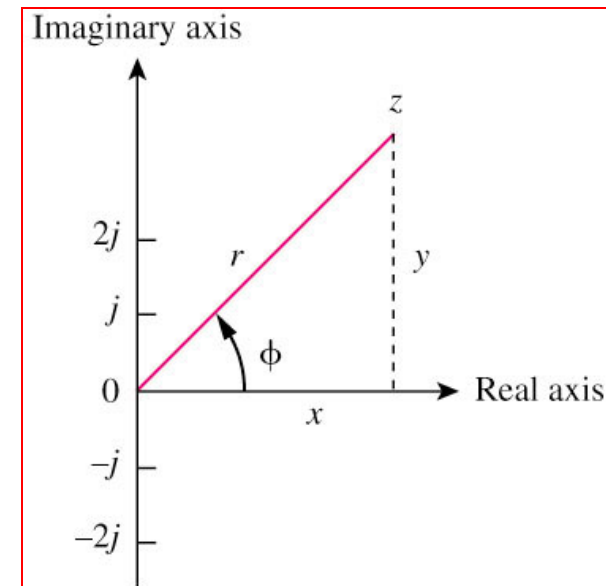c. Exponential



where

$$r = \sqrt{x^2 + y^2}$$
$$\phi = \tan^{-1} \frac{y}{x}$$



# Phasors

## Mathematic operation of complex number:

1. Addition

$$z_1 + z_2 = (x_1 + x_2) + j(y_1 + y_2)$$

2. Subtraction

$$z_1 - z_2 = (x_1 - x_2) + j(y_1 - y_2)$$

3. Multiplication

$$z_1 z_2 = r_1 r_2 \angle \phi_1 + \phi_2$$

4. Division

$$\frac{z_1}{z_2} = \frac{r_1}{r_2} \angle \phi_1 - \phi_2$$

5. Reciprocal

$$\frac{1}{z} = \frac{1}{r} \angle -\phi$$

6. Square root

$$\sqrt{z} = \sqrt{r} \angle \phi/2$$

7. Complex conjugate

$$z^* = x - jy = r \angle -\phi = r e^{-j\phi}$$

8. Euler's identity

$$e^{\pm j\phi} = \cos \phi \pm j \sin \phi$$

# Phasors

- ▶ Transform a sinusoid to and from the time domain to the phasor domain:

$$v(t) = V_m \cos(\omega t + \phi) \longleftrightarrow V = V_m \angle \phi$$

(time domain)

(phasor domain)

- Amplitude and phase difference are two principal concerns in the study of voltage and current sinusoids.
- Phasor will be defined from the cosine function in all our proceeding study. If a voltage or current expression is in the form of a sine, it will be changed to a cosine by subtracting from the phase.

# Phasors

## Sinusoidal-Phasor Transformation

Time domain representation

$$V_m = \cos(\omega t + \phi)$$

$$V_m = \sin(\omega t + \phi)$$

$$I_m = \cos(\omega t + \phi)$$

$$I_m = \sin(\omega t + \phi)$$

Phasor domain representation

$$V_m \angle \phi$$

$$V_m \angle \phi - 90^\circ$$

$$I_m \angle \phi$$

$$I_m \angle \phi - 90^\circ$$

# Phasors

## The differences between $v(t)$ and $V$ :

- ▶  $v(t)$  is instantaneous or time-domain representation  
 $V$  is the frequency or phasor-domain representation.
- ▶  $v(t)$  is time dependent,  $V$  is not.
- ▶  $v(t)$  is always real with no complex term,  $V$  is generally complex.

Note: Phasor analysis applies only when frequency is constant; when it is applied to two or more sinusoid signals only if they have the same frequency.

# Phasors

**Relationship between differential, integral operation in phasor listed as follow:**

$$v(t) \longleftrightarrow V = V \angle \phi$$

$$\frac{dv}{dt} \longleftrightarrow j\omega V$$

$$\int v dt \longleftrightarrow \frac{V}{j\omega}$$

# Phasors

## Practice Problem 9.4

Express these sinusoids as phasors:

a.  $v = 7 \cos(2t + 40^\circ) V$

b.  $i = -4 \sin(10t + 10^\circ) A$

## Practice Problem 9.5

Find the sinusoids corresponding to these phasors:

a.  $V = -10 \angle 30^\circ V$

b.  $j(5 - j12) A$

## Practice Problem 9.6

If  $v_1 = -10 \sin(\omega t - 30^\circ) V$  and  $v_2 = 20 \cos(\omega t + 45^\circ) V$ .

Find  $v = v_1 + v_2$




# Phasors

## Practice Problem 9.7


Find the voltage  $v(t)$  in a circuit described by the integrodifferential equation

$$2 \frac{dv}{dt} + 5v + 10 \int v dt = 50 \cos(5t - 30^\circ)$$

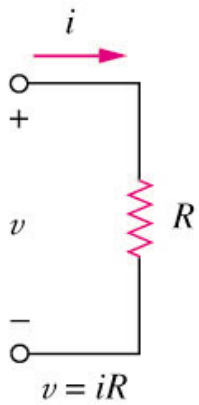
# PHASORS RELATIONSHIPS FOR CIRCUIT ELEMENTS




(a)

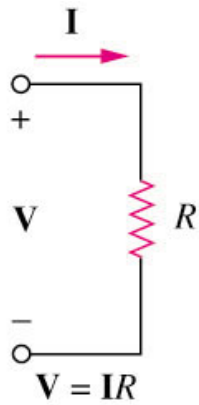


(b)

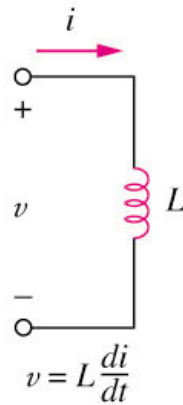


(a)

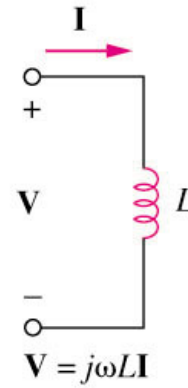




(b)

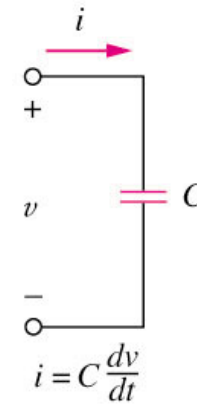

(a)

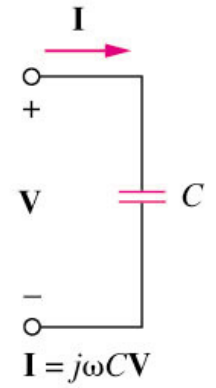

(b)

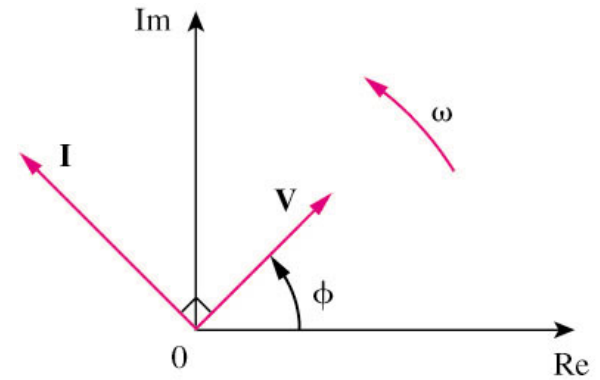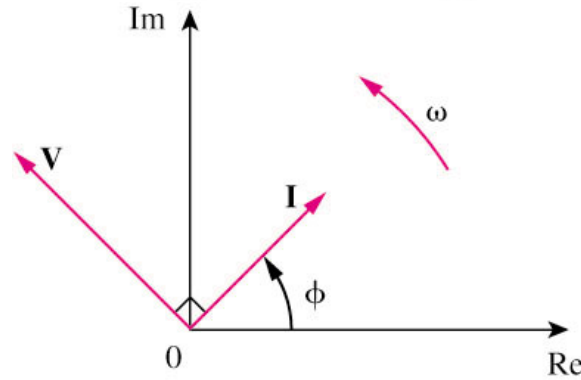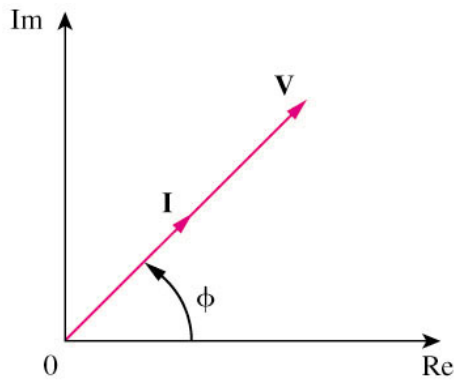

# PHASORS RELATIONSHIPS FOR CIRCUIT ELEMENTS

## Summary of voltage-current relationship

Element	Time domain	Frequency domain
R	$v = Ri$	$V = RI$
L	$v = L \frac{di}{dt}$	$V = j\omega LI$
C	$i = C \frac{dv}{dt}$	$V = \frac{I}{j\omega C}$

# Phasors

## Practice Problem 9.8

If  $v = 10 \cos(100t + 30^\circ)$  is applied to a  $50\mu F$  capacitor, calculate the current through the capacitor.

## Example 9.8

The voltage  $v = 12 \cos(60t + 45^\circ)$  is applied to a  $0.1\text{-H}$  inductor. Find the steady-state current through the inductor.

## Practice Problem 9.3

Evaluate the following complex numbers:

(a)  $[(5 + j2)(-1 + j4) - 5\angle 60^\circ]^*$

(b)  $\frac{10 + j5 + 3\angle 40^\circ}{-3 + j4} + 10\angle 30^\circ + j5$

# IMPEDANCE & ADMITTANCE

- ▶ The impedance  $Z$  of a circuit is the ratio of the phasor voltage  $V$  to the phasor current  $I$ , measured in ohms  $\Omega$ . It is a frequency-dependent quantity.
- ▶ It represents the opposition that the circuit exhibits to the flow of sinusoidal current.

$$Z = \frac{V}{I} = R + jX = |Z| \angle \theta$$

where  $R = \text{Re } Z$  is the resistance and  $X = \text{Im } Z$  is the reactance.

- ▶ The admittance  $Y$  is the reciprocal of impedance, measured in siemens (S).

$$Y = \frac{1}{Z} = \frac{I}{V} = G + jB$$

where  $G = \text{Re } Y$  is the conductance and  $B = \text{Im } Y$  is the susceptance.

# Impedance & Admittance

## Impedances and admittances of passive elements


Element	Impedance	Admittance
<b>R</b>	$Z = R$	$Y = \frac{1}{R}$
<b>L</b>	$Z = j\omega L$	$Y = \frac{1}{j\omega L}$
<b>C</b>	$Z = \frac{1}{j\omega C}$	$Y = j\omega C$

$Z = R + jX$  inductive/lagging ( $I$  lags  $V$ )

$Z = R - jX$  capacitive/leading ( $I$  leads  $V$ )

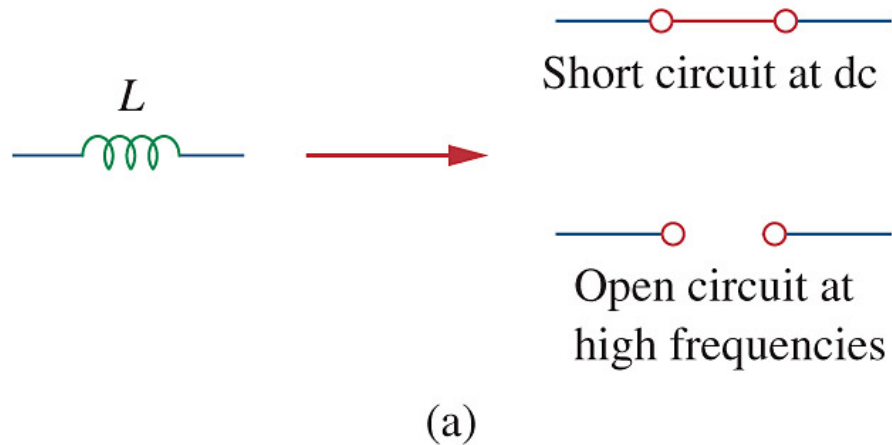
# Impedance & Admittance

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



$$\omega = 0; Z = 0$$
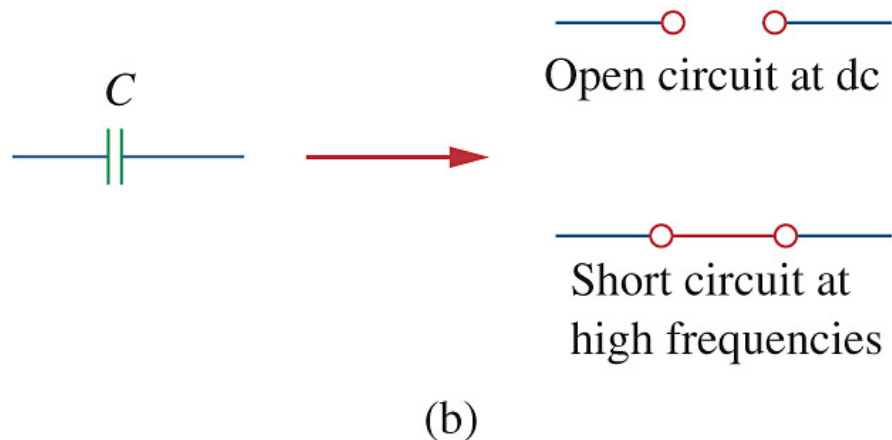
$$\omega \rightarrow \infty; Z \rightarrow \infty$$



$$\omega = 0; Z \rightarrow \infty$$


$$\omega \rightarrow \infty; Z = 0$$

# Impedance & Admittance
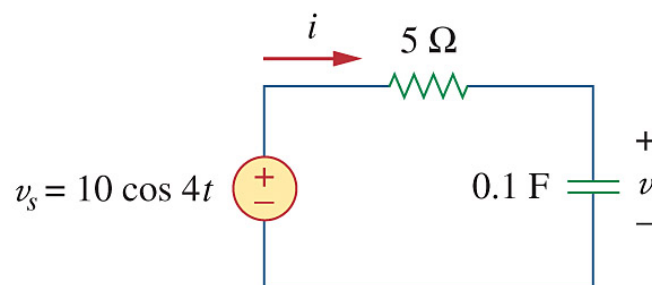
## Example 9.9

Find  $v(t)$  and  $i(t)$  in the circuit below:


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.


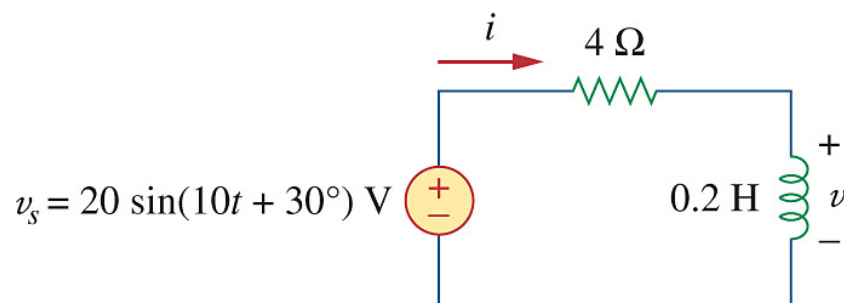
## Practice Problem 9.9

Determine  $v(t)$  and  $i(t)$  in the circuit below:

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.






# KIRCHHOFF'S LAWS IN THE FREQUENCY DOMAIN

- ▶ Both KVL and KCL are hold in the phasor domain (frequency domain).
- ▶ Variables to be handled are phasors, which are complex numbers.
- ▶ All the mathematical operations involved are now in complex domain.
- ▶ The following principles used for DC circuit analysis all apply to AC circuit:
  - a.voltage division
  - b.current division
  - c.circuit reduction
  - d.impedance equivalence
  - e.Y- $\Delta$  transformation
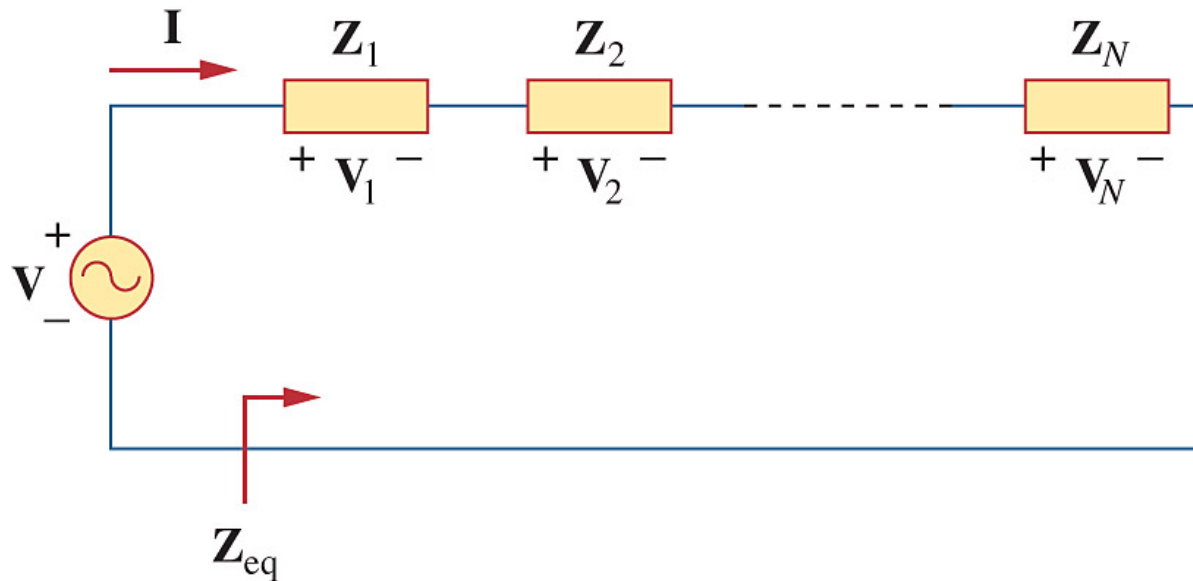
# KIRCHHOFF'S LAWS IN THE FREQUENCY DOMAIN


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



$$Z_{eq} = Z_1 + Z_2 + \dots + Z_N$$
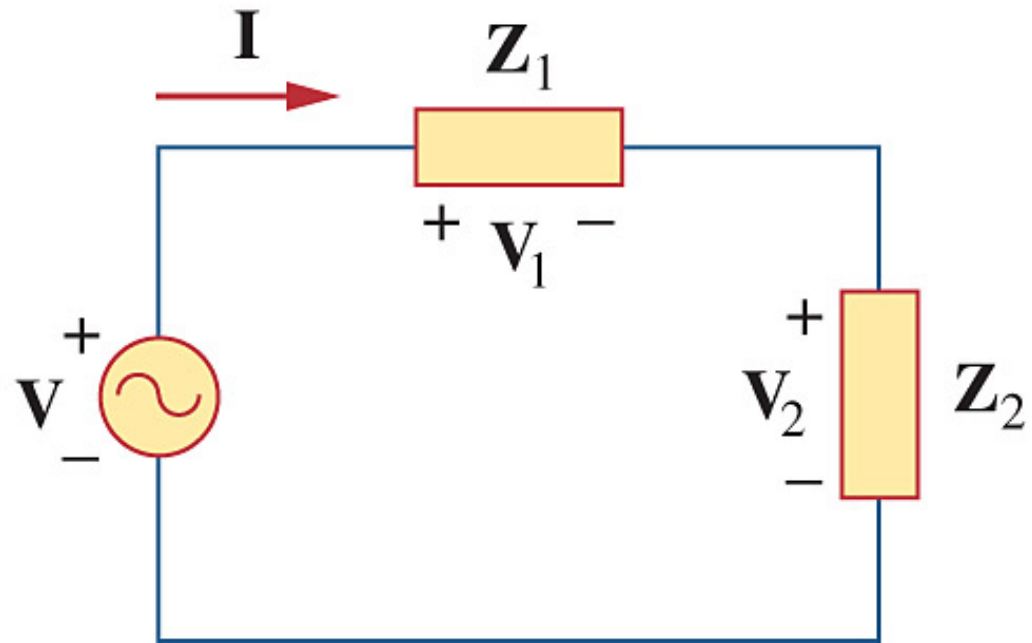
# KIRCHHOFF'S LAWS IN THE FREQUENCY DOMAIN

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




$$V_1 = \frac{Z_1}{Z_1 + Z_2} V$$

$$V_2 = \frac{Z_2}{Z_1 + Z_2} V$$
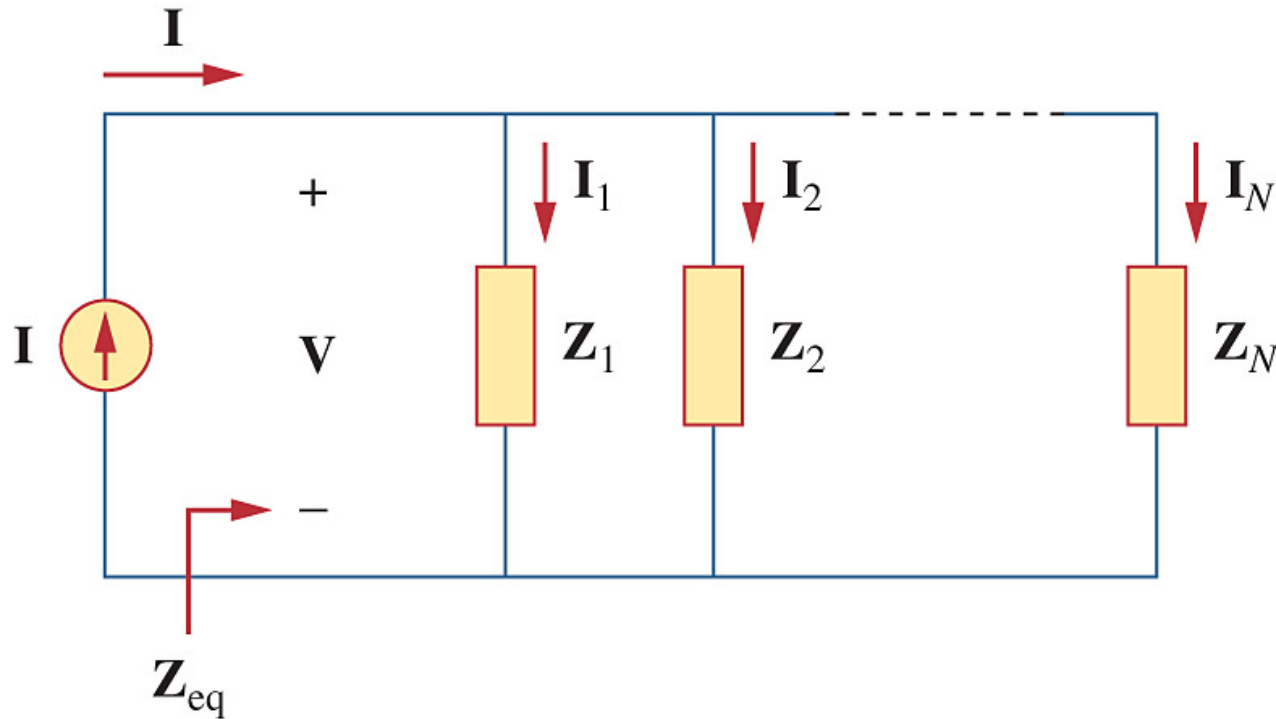
# KIRCHHOFF'S LAWS IN THE FREQUENCY DOMAIN

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




$$\frac{1}{Z_{eq}} = \frac{I}{V} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N}$$

$$Y_{eq} = Y_1 + Y_2 + \dots + Y_N$$
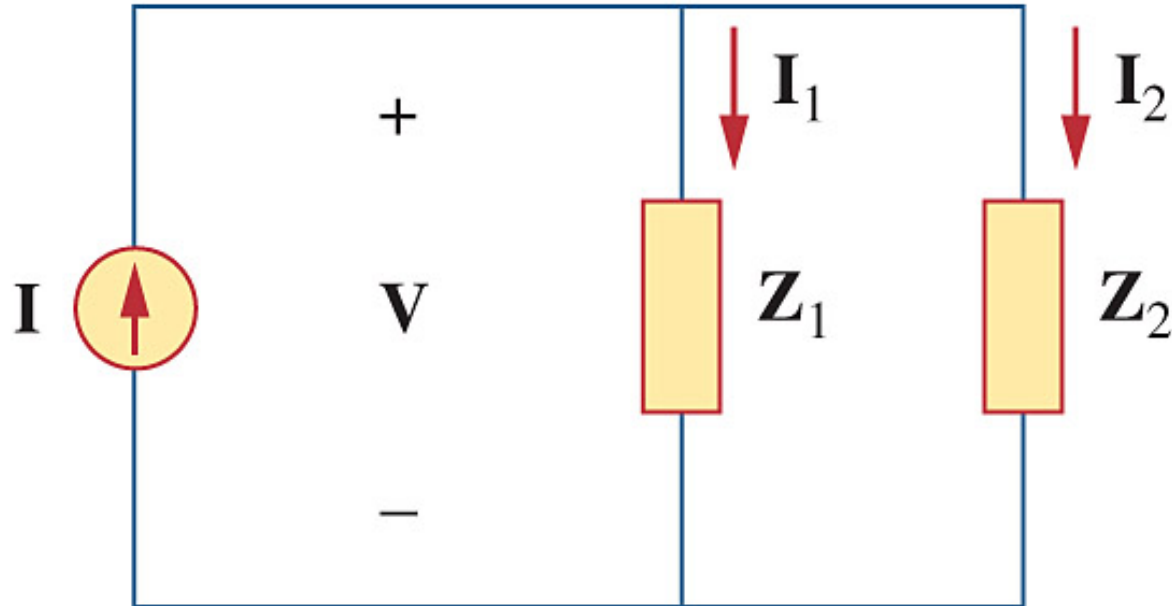
# KIRCHHOFF'S LAWS IN THE FREQUENCY DOMAIN

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




$$I_1 = \frac{Z_2}{Z_1 + Z_2} I$$

$$I_2 = \frac{Z_1}{Z_1 + Z_2} I$$
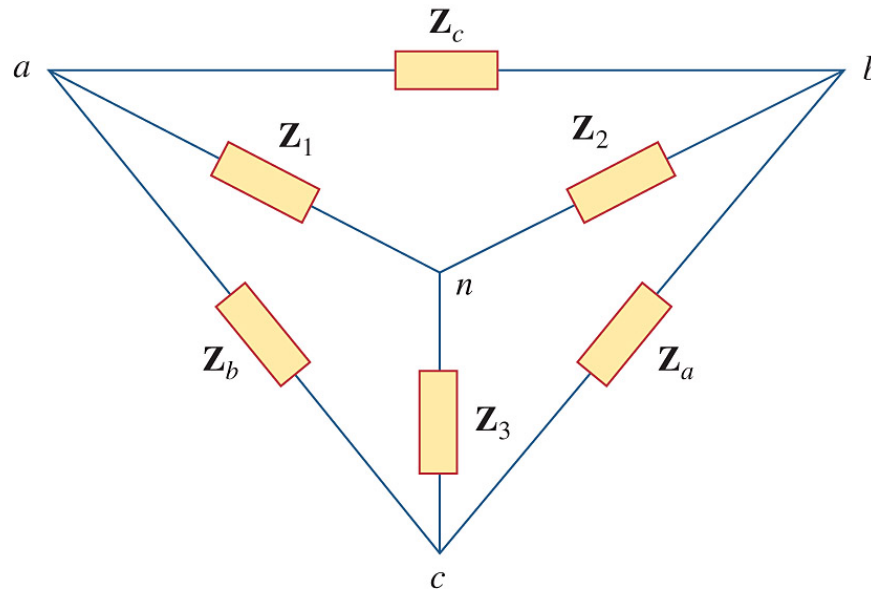
# KIRCHHOFF'S LAWS IN THE FREQUENCY DOMAIN

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



$$Z_a = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_1}$$

$$Z_b = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_2}$$

$$Z_c = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_3}$$

$$Z_1 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c}$$

$$Z_2 = \frac{Z_c Z_a}{Z_a + Z_b + Z_c}$$


$$Z_3 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c}$$

# KIRCHHOFF'S LAWS IN THE FREQUENCY DOMAIN
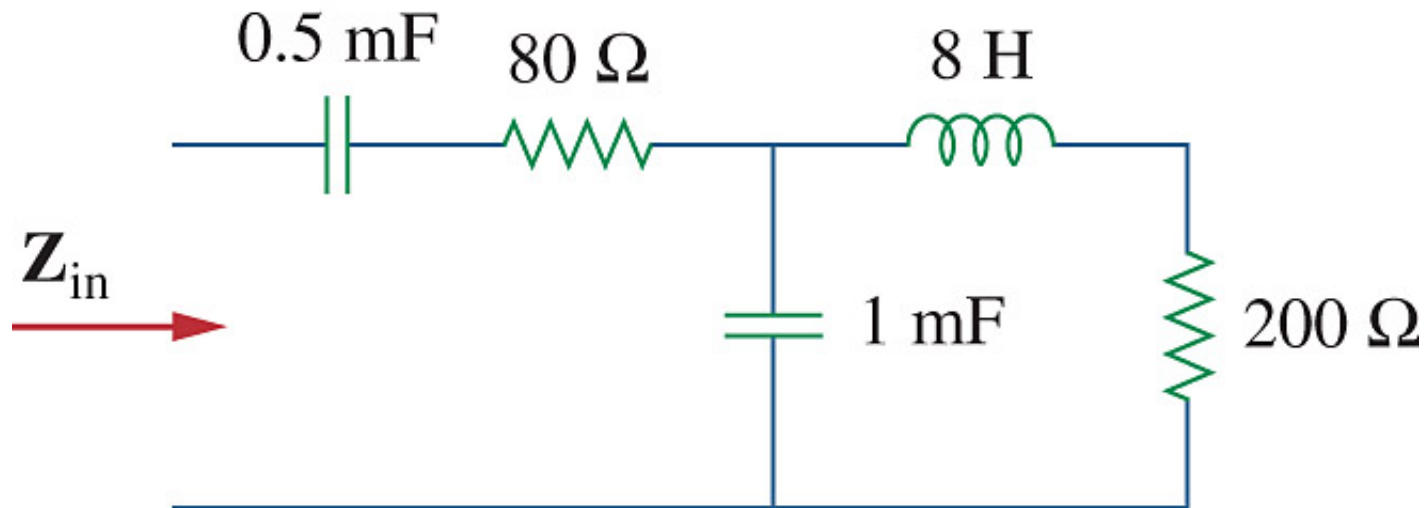
## Practice Problem 9.10

Determine the input impedance of the circuit below at  $\omega = 10 \text{ rad/s}$

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




# KIRCHHOFF'S LAWS IN THE FREQUENCY DOMAIN
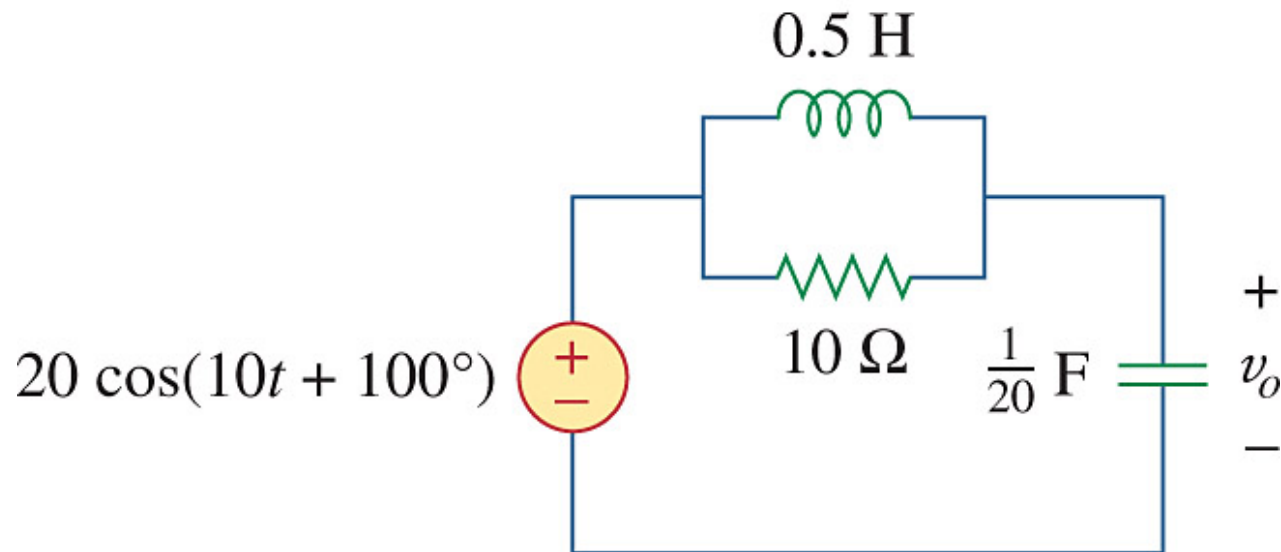
## Practice Problem 9.11

Calculate  $v_o$  in the circuit below:

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.






# KIRCHHOFF'S LAWS IN THE FREQUENCY DOMAIN
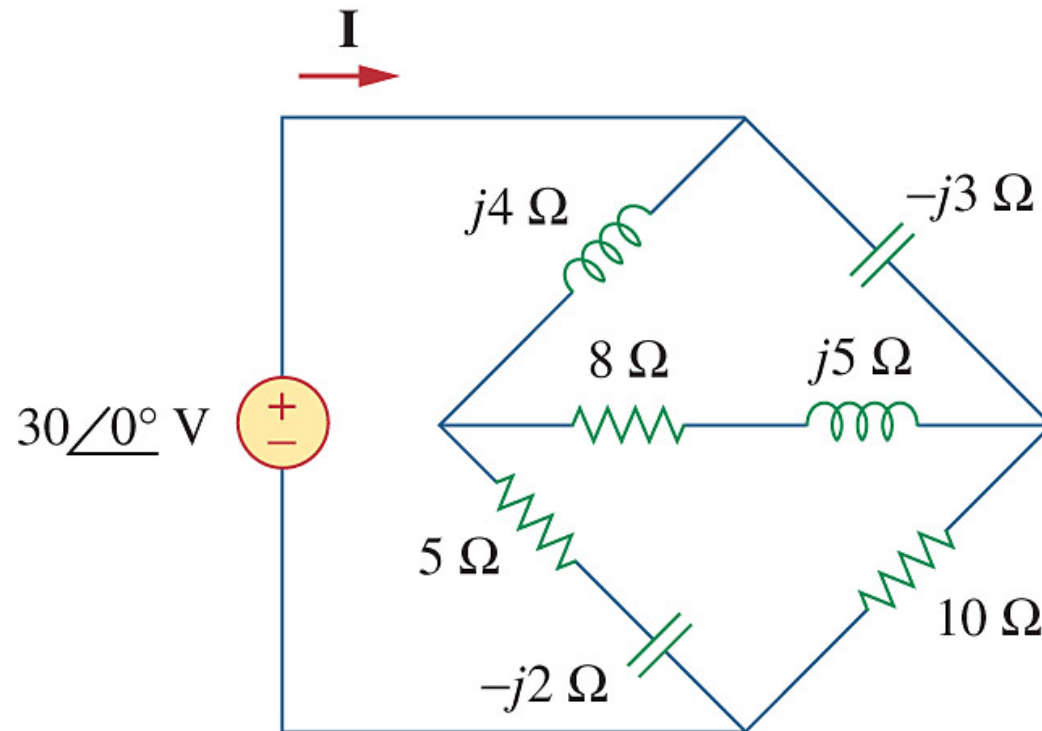
## Practice Problem 9.12

Find  $I$  in the circuit below:

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



## TUTORIALS (sinusoids)

### Problem 9.6

For the following pairs of sinusoids, determine which one leads and by how much.

1.  $v(t) = 10 \cos(4t - 60^\circ)$  and  $i(t) = 4 \sin(4t + 50^\circ)$
2. (b)  $v_1(t) = 4 \cos(377t + 10^\circ)$  and  $v_2(t) = -20 \cos 377t$
3. (c)  $x(t) = 13 \cos 2t + 5 \sin 2t$  and  $y(t) = 15 \cos(2t - 11.8^\circ)$

# TUTORIALS (Phasors)


1. Find the phasors corresponding to the following signals.
  - (a)  $v(t) = 21 \cos(4t - 15^\circ) \text{ V}$
  - (b)  $i(t) = -8 \sin(10t + 70^\circ) \text{ mA}$
  - (c)  $v(t) = 120 \sin(10t - 50^\circ) \text{ V}$
  - (d)  $i(t) = -60 \cos(30t + 10^\circ) \text{ mA}$
  
2. Using phasors, find:
  - (a)  $3 \cos(20t + 10^\circ) - 5 \cos(20t - 30^\circ)$
  - (b)  $40 \sin 50t + 30 \cos(50t - 45^\circ)$
  - (c)  $20 \sin 400t + 10 \cos(400t + 60^\circ) - 5 \sin(400t - 20^\circ)$
  
3. Find  $v(t)$  in the following integrodifferential equations using the phasor approach:
  - (a)  $v(t) + \int v dt = 5 \cos(t + 45^\circ) \text{ V}$
  - (b)  $\frac{dv}{dt} + 5v(t) + 4 \int v dt = 20 \sin(4t + 10^\circ) \text{ V}$

## TUTORIALS (Impedance & Admittance)
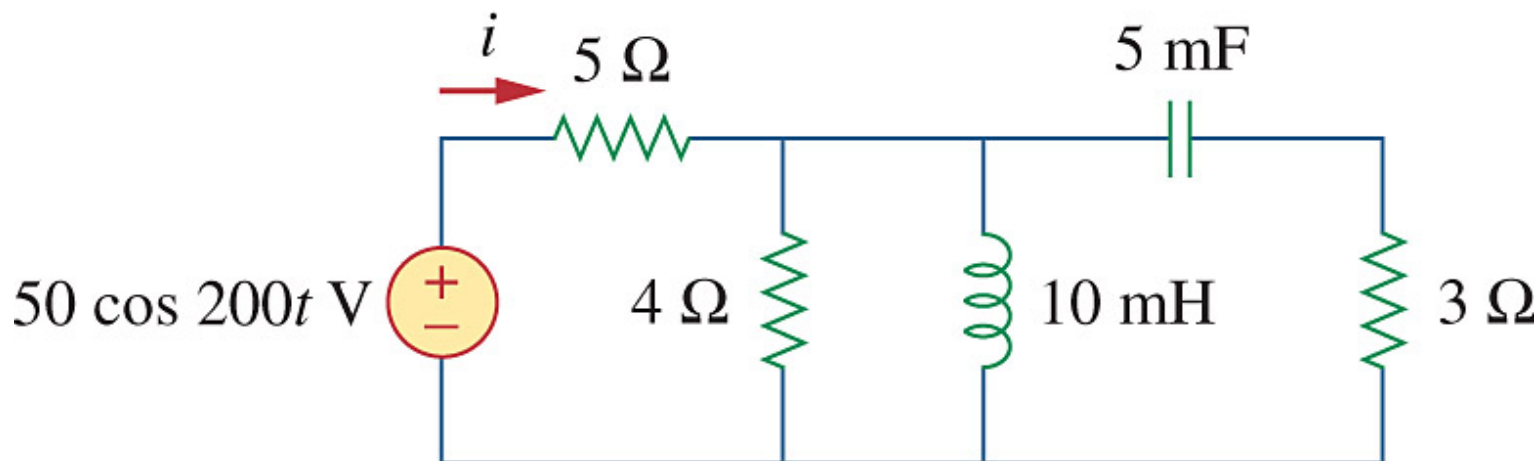
### Problem 9.44

Calculate  $i(t)$  in the circuit below:

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




## TUTORIALS (Impedance & Admittance)
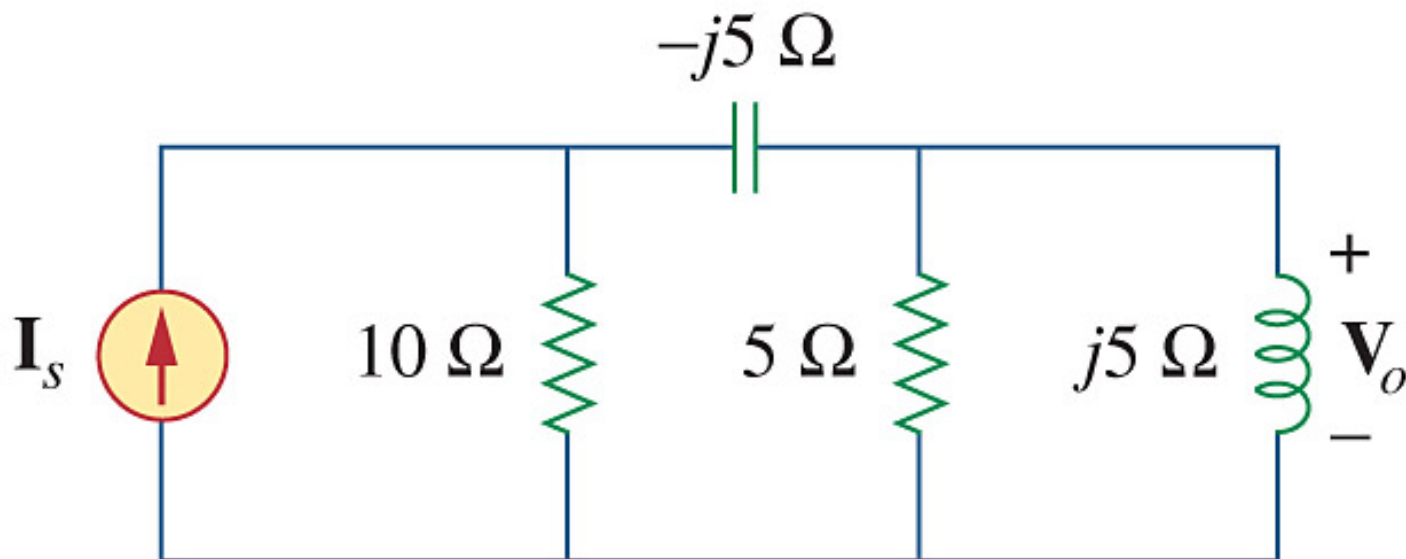
### Problem 9.52

If  $V_o = 20\angle 45^\circ$  V in the circuit, find  $I_s$ :

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




## TUTORIALS (Impedance & Admittance)
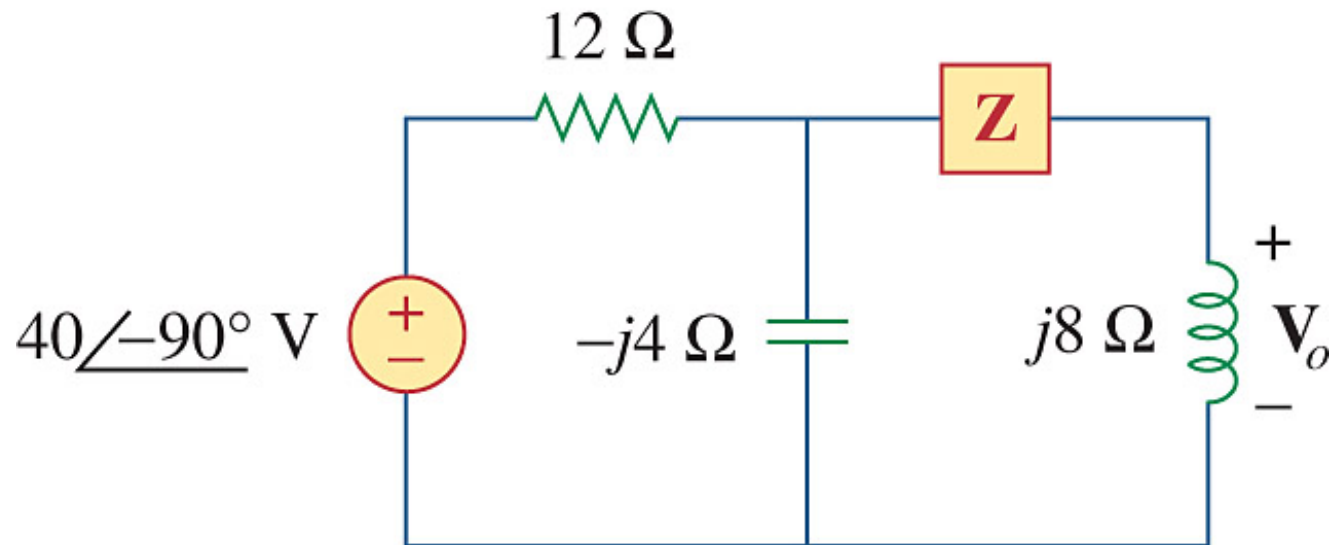
### Problem 9.55\*

Given  $V_o = 8\angle 0^\circ$  V, find the  $Z$ . What are the elements are contained in  $Z$ ? Calculate the value of their resistances/reactances if the system frequency is 50 Hz.


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



# Average & Effective (rms) Values
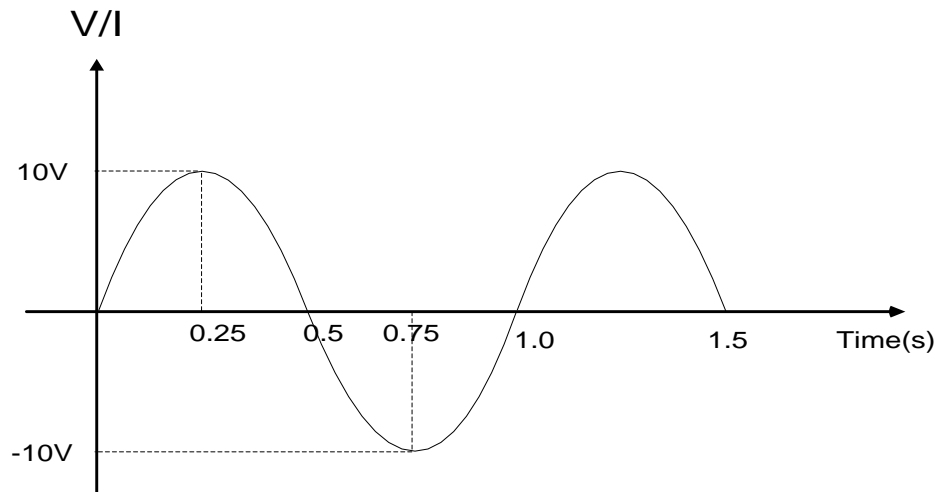
## Instantaneous Value

- Instantaneous value is magnitude value of waveform at one specific time.
- Symbol for Instantaneous value of voltage is  $v(t)$  and current is  $i(t)$ .
- Example of Instantaneous value for voltage is shown:



$$v(0.25) = 10V$$

$$v(0.5) = 0V$$

$$v(0.75) = -10V$$

$$v(1.0) = 0V$$

# Average & Effective (rms) Values

## Average Value

- Average value is average value for all instantaneous value in half or one complete waveform cycle.
- It can be calculate in two ways:
  1. Calculate the area under the graph:  
Average value =  $\frac{\text{area under the function in a period}}{\text{period}}$
  2. Use integral method

$$average\_value = \frac{1}{T} \int_0^T v(t) dt$$



# Average & Effective (rms) Values

## Average Value

- For example

Instantaneous power:

$$p(t) = v(t)i(t) = V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$

Average power:

$$P = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

# Average & Effective (rms) Values

## Effective value

- The most common method of specifying the amount of sine wave of voltage or current by relating it into dc voltage and current that will produce the same heat effect.
- It is called root means square value, rms
- The formula of effective value for sine wave waveform is

$$V_{rms} = \frac{v_m}{\sqrt{2}} = 0.7071v_m$$

where  $I_m$  &  $V_m$  are peak values

$$I_{rms} = \frac{i_m}{\sqrt{2}} = 0.7071i_m$$


# Phasor Diagram

- For example, if given a sine wave waveform


$$v(t) = V_m \cos(\omega t + \phi^0) V$$

- It can be represent by a phasor diagram

$$V = V_m \angle \phi^0$$

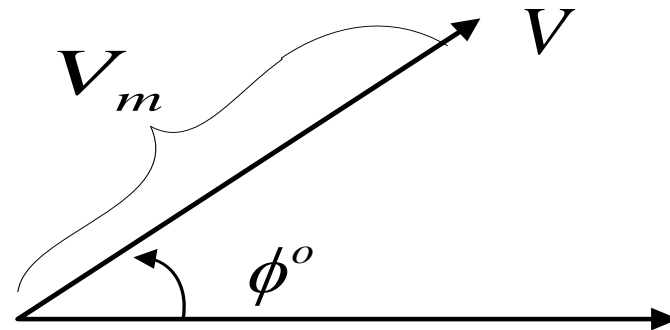

# Phasor Diagram

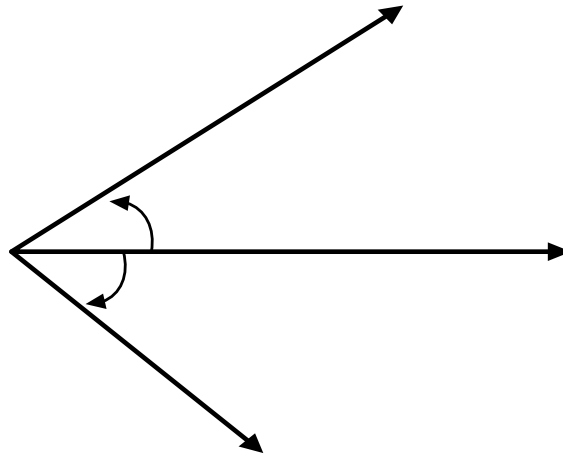

From the phase diagram above, it can be conclude that:

- i) I leading V for  $\theta^\circ$  degree or V lagging I for  $\theta^\circ$  degree
- ii) V leading V1 for  $\Phi^\circ$  degree or V1 lagging V for  $\Phi^\circ$  degree
- iii) I leading V1 for  $(\Phi^\circ + \theta^\circ)$  degree or V1 lagging I for  $(\Phi^\circ + \theta^\circ)$  degree

# Example

Given the circuit below, sketch the phasor diagram of  $V_S, V_R, V_L, V_C, I_S$ .

