



**UTM**  
UNIVERSITI TEKNOLOGI MALAYSIA

*M. Afendi M. Piah, PhD*

[www.utm.my](http://www.utm.my)

# Circuit Theory (SKEE 1023)

**Assoc. Prof. Dr. Mohamed Afendi Mohamed Piah**

**Institute of High Voltage & High Current  
Faculty of Electrical Engineering, UTM**



**UTM**  
UNIVERSITI TEKNOLOGI MALAYSIA

[www.utm.my](http://www.utm.my)

*M. Afendi M. Piah, PhD*

# Circuit Theory

## Topics

- ❖ Linearity Property, Superposition, Source Transformation, Thevenin and Norton Theorem.



# Circuit Theory

## Linearity Property

- Linearity is the property of an element describing a linear relationship between cause and effect.
- Combination of both homogeneity (scaling) property and the additivity property.
- E.g. Resistor is a linear element because the voltage-current relationship satisfies both the homogeneity and the additivity properties.
- A linear circuit consists of only linear elements, linear dependent source and independent sources.

# Circuit Theory

## Linearity Property

### Example 4.1

#### Solution:

Applying KVL to the two loops, we obtain

$$12i_1 - 4i_2 + v_s = 0$$

$$-4i_1 + 16i_2 - 3v_x - v_s = 0$$

But  $v_x = 2i_1$ . Equation (4.1.2) becomes

$$-10i_1 + 16i_2 - v_s = 0$$

Adding Eqs. (4.1.1) and (4.1.3) yields

$$2i_1 + 12i_2 = 0 \Rightarrow i_1 = -6i_2$$

Substituting this in Eq. (4.1.1), we get

$$-76i_2 + v_s = 0 \Rightarrow i_2 = \frac{v_s}{76}$$


When  $v_s = 12$  V,

$$I_o = i_2 = \frac{12}{76} \text{ A}$$

When  $v_s = 24$  V,

$$I_o = i_2 = \frac{24}{76} \text{ A}$$

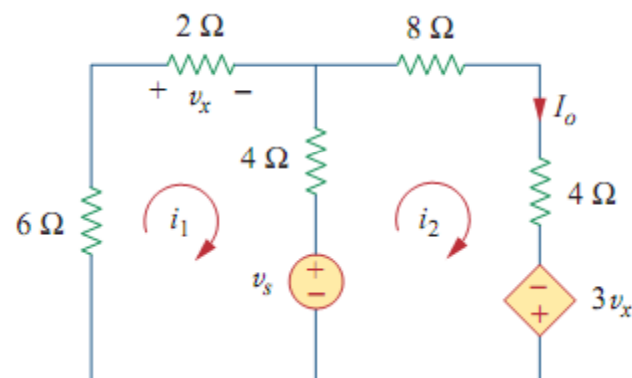showing that when the source value is doubled,  $I_o$  doubles.





# Circuit Theory

## Superposition Theorem

- The voltage across (or current through) an element in a linear circuit is the algebraic sum of the voltages across (or currents through) that element due to each independent source acting alone.
- Combination of both **homogeneity (scaling)** property and the **additivity** property. Applicable to linear circuit only.
- One of the method to solve the circuit with two or more independent sources.
- The number of analysis depend on how many independent sources does the circuit has.



# Circuit Theory

## Superposition Theorem

Steps to apply Superposition theorem/principle.

1. Choose one independent source and eliminate (turn-off) the effect of other independent sources. [*Voltage source*  $\Rightarrow$  short-circuit ; *Current source*  $\Rightarrow$  open-circuit]
2. Start the analysis using any circuit analysis methods/techniques and theorems. [KCL, KVL, nodal/mesh analysis, etc]
3. Start the analysis using any circuit analysis methods/techniques and theorems. [KCL, KVL, nodal/mesh analysis, etc]
4. Combine/add-ups all the value of each element for all separated analysis.



**UTM**  
UNIVERSITI TEKNOLOGI MALAYSIA

[www.utm.my](http://www.utm.my)

M. Afendi M. Piah, PhD

# Circuit Theory

## Superposition Theorem

- This technique does **not allow to find power** at any separated circuit.
- This technique has one major disadvantage; it may very likely **involve more work**.
- However superposition does help reduce a complex circuit to a simpler circuit.
- Combine/add-ups all the value of each element for all separated analysis.

# Circuit Theory

## Superposition Theorem

### Problem 4.1:

Using the superposition theorem, find  $v_o$  in the circuit of Fig. P4.1. (Ans: 6 V)

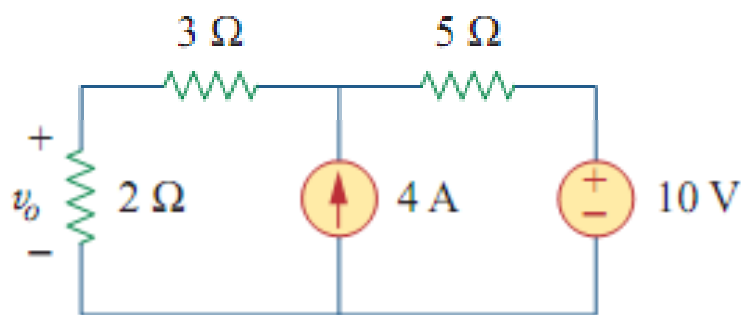



Fig. P4.1

# Circuit Theory

## Superposition Theorem

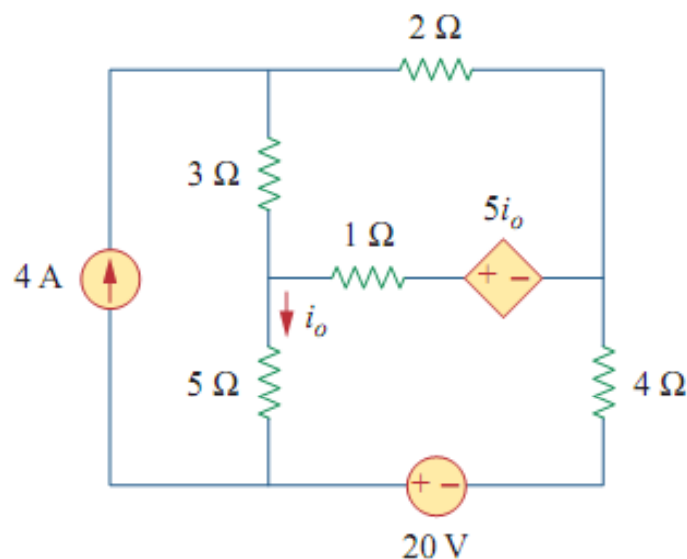Example 4.2:

Find  $i_o$  in the circuit using superposition theorem.






# Circuit Theory

## Superposition Theorem


The circuit involves a dependent source, which must be left intact. The  $i_o$  is given by;

$$i_o = i_o' + i_o''$$

How to find  $i_o'$  ?

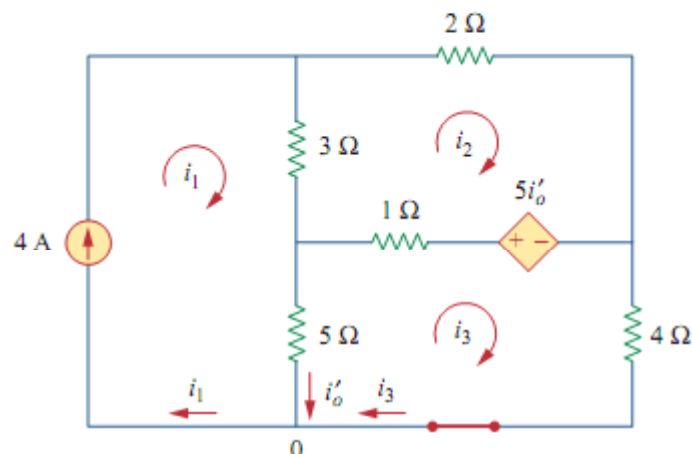

How to find  $i_o''$  ?

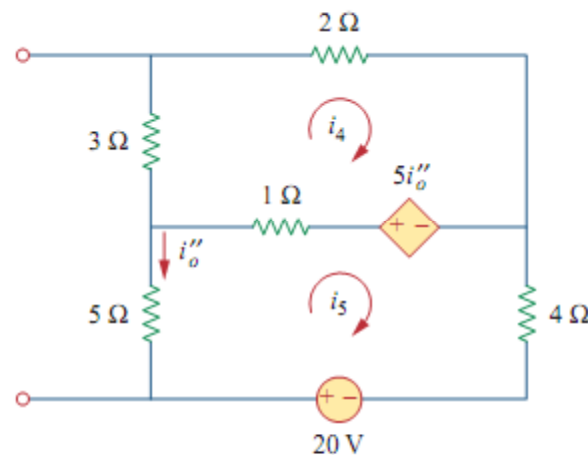

# Circuit Theory

## Superposition Theorem

### Problem 4.2:

Use superposition to find  $v_x$  in the circuit of Fig. P4.2. (Ans: 25 V)


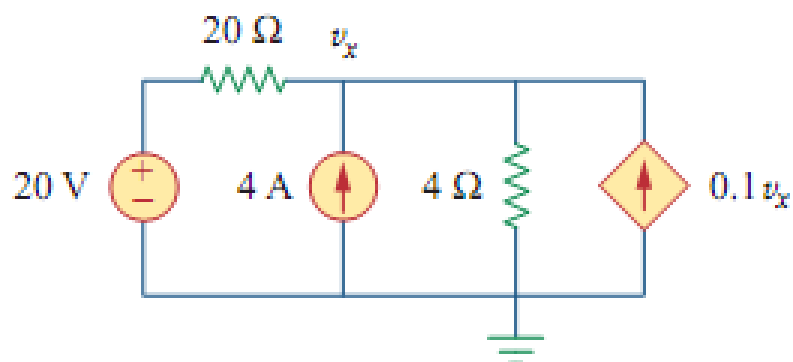
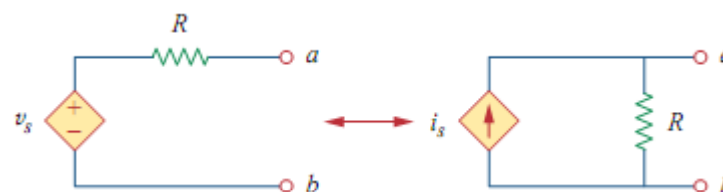


Fig. P4.2

# Circuit Theory
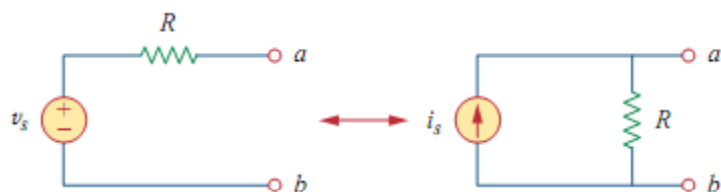
## Source Transformation

- A source transformation is the process of replacing a voltage source  $V_s$  in series with a resistor  $R$  by a current source  $I_s$  in parallel with a resistor  $R$ , or vice versa.




$$v_s = i_s R \quad \text{or} \quad i_s = \frac{v_s}{R}$$



# Circuit Theory
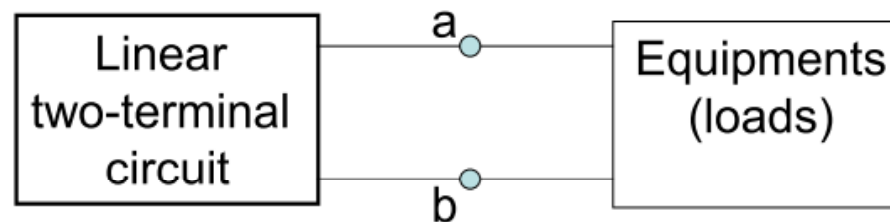
## Thevenin's Theorem


- Objective : To simplify the circuit.
- Provides a technique by which the fixed part of the circuit is replaced by an equivalent circuit.
- Developed in 1883 by M. Leon Thevenin (1857–1926), a French telegraph engineer.
- When the load are varies, all the variables (voltage & current) inside the linear circuit would also varies, thus the analysis has to be done again.




# Circuit Theory
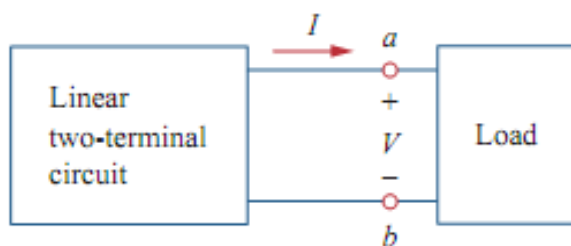
## Thevenin's Theorem

- Thevenin's theorem states that a linear 2-terminal circuit can be replaced by an **equivalent circuit** consisting of a **voltage source**  $V_{Th}$  in series with a **resistor**  $R_{Th}$ .



(a)

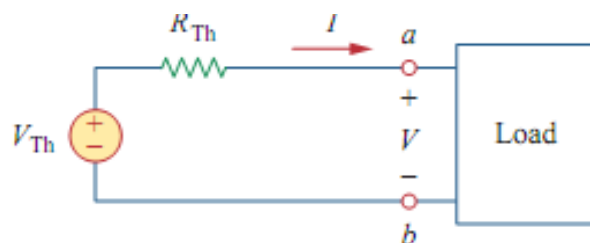

(b)


- ❖  $V_{Th}$  is the **open-circuit voltage** at the terminals, and  $R_{Th}$  is the **input or equivalent resistance** at the terminals when the independent sources are turned off.
- ❖ It is easy to find the **open-circuit voltage** ( $v_{oc}$ ) and **short-circuit current** ( $i_{sc}$ ) at terminal a-b through experimental method.
- ❖ Thus,  $V_{Th} = v_{oc}$  and  $R_{Th} = v_{oc}/i_{sc}$




# Circuit Theory
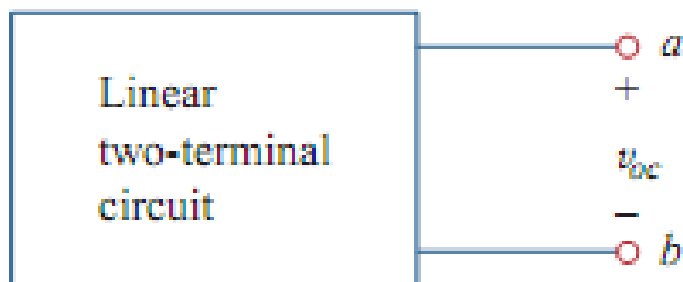
## Thevenin's Theorem

- How to find  $V_{Th}$  (Thevenin voltage) and  $R_{Th}$  (Thevenin resistance)?



$$V_{Th} = v_{oc}$$

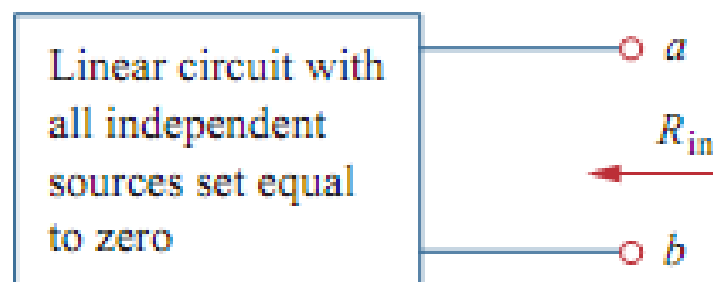

$$R_{Th} = R_{in}$$



# Circuit Theory

## Thevenin's Theorem

- ❑ A linear circuit without dependent source.
  1. Find  $v_{oc}$  across the two terminal (either using mesh/nodal, etc). The Thevenin voltage ( $V_{Th}$ ) is equal to  $v_{oc}$ .
  2. Simply turn off all the independent sources.
  3. Find the equivalent resistance ( $R_{eq}$ ) between the two terminal. The Thevenin resistor ( $R_{Th}$ ) is equal to the  $R_{eq}$ .

# Circuit Theory

## Thevenin's Theorem



### □ A linear circuit with dependent source

1. Find  $v_{oc}$  across the two terminal (either using mesh/nodal, etc). The Thevenin voltage ( $V_{Th}$ ) is equal to  $v_{oc}$ .
2. Simply turn off all the independent sources. The dependent sources should remain intact/unchanged.
3. Inject a voltage source ( $v_o$ ) OR current source ( $i_o$ ) across the two terminal. Then determine current supplied by voltage source OR voltage across the current source.
4. The value of  $R_{Th} = v_o/i_o$

# Circuit Theory
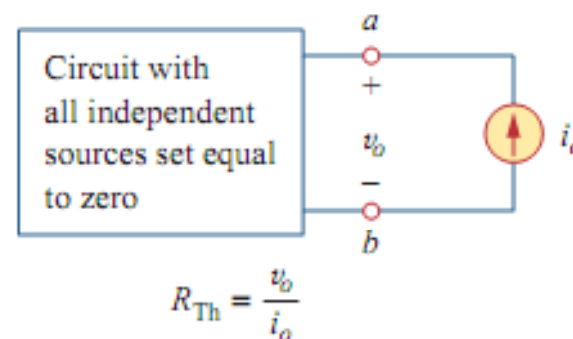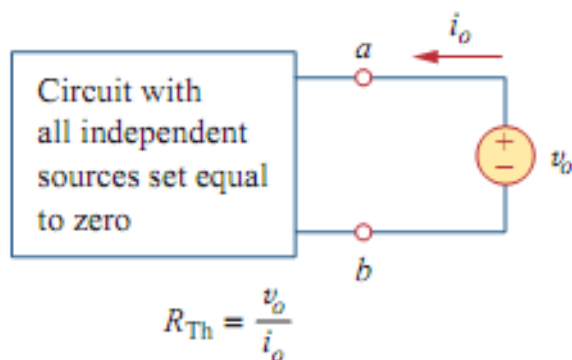
## Thevenin's Theorem

- ❖ Finding  $R_{Th}$  when circuit has dependent sources.





- We may assume any value of  $v_o$  and  $i_o$ . For example, we may use  $v_o = 1V$  or  $i_o = 1A$ , or even use unspecified values of  $v_o$  or  $i_o$ .

# Circuit Theory
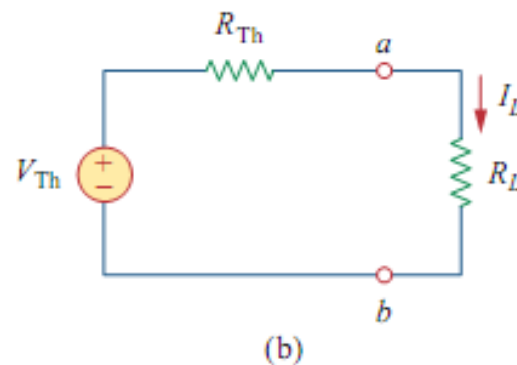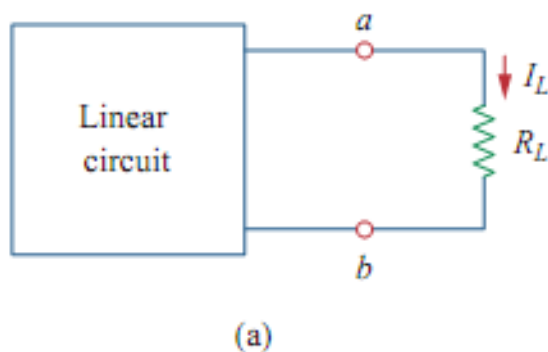
## Thevenin's Theorem

- ❖ A circuit with a load: (a) original circuit, (b) Thevenin equivalent



$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

$$V_L = R_L I_L = \frac{R_L}{R_{Th} + R_L} V_{Th}$$

# Circuit Theory

## Thevenin's Theorem

### Example 4.3:

Find the Thevenin equivalent circuit of the circuit shown in Fig. E4.3, to the left of the terminals  $a-b$ . Then find the current through  $R_L = 6, 16$  and  $36 \Omega$ .

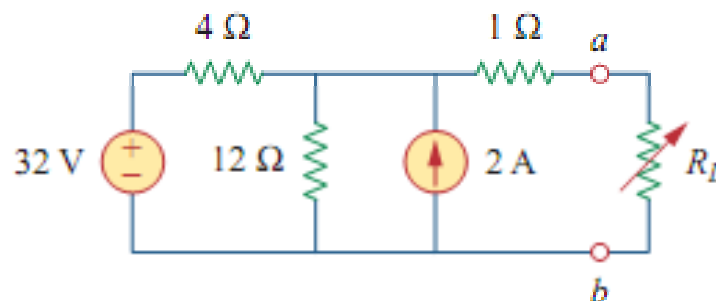


Fig. E4.3

# Circuit Theory

## Thevenin's Theorem

### Example 4.4:

Find the Thevenin equivalent circuit of the circuit in Fig. E4.4 at terminals  $a$ - $b$ .

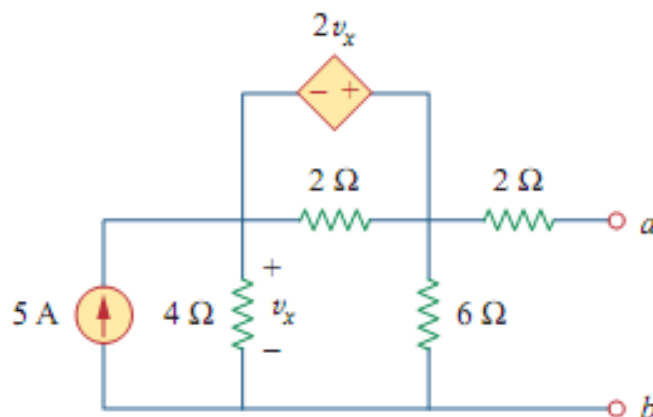



Fig. E4.4

# Circuit Theory


## Thevenin's Theorem

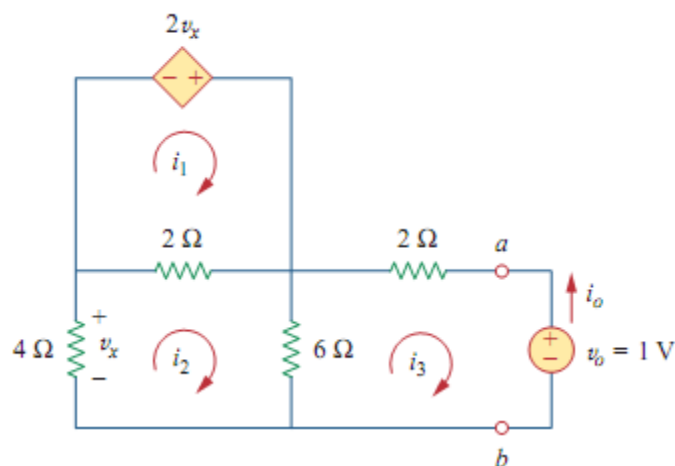Example 4.4 (cont.):

Finding  $R_{Th}$  and  $V_{Th}$  at terminals  $a-b$ .



Finding  $R_{Th}$

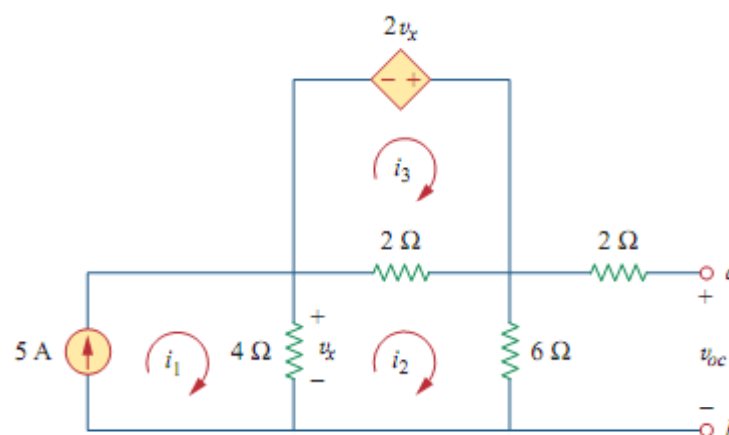


Finding  $V_{Th}$


# Circuit Theory
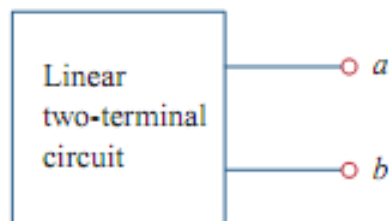
## Norton's Theorem

- Similar with Thevenin's theorem.
- Proposed by E.L. Norton (1926), an American engineer at Bell Telephone Laboratories.
- Norton's theorem states that a linear two-terminal circuit can be replaced by an **equivalent circuit** consisting of a **current source** ( $I_N$ ) in parallel with a **resistor**,  $R_N$ .



Original circuit

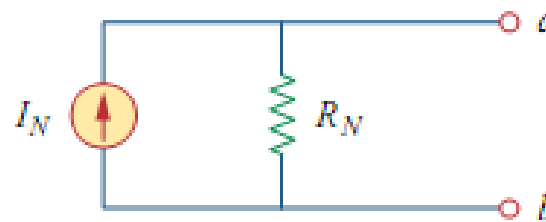

Norton equivalent circuit

# Circuit Theory

## Norton's Theorem

- $I_N$  is the **short-circuit current ( $i_{sc}$ )** through the terminals and  $R_N$  is the **input or equivalent resistance** at the terminals when the independent sources are turned off.
- Method to find  $R_N$  is same with  $R_{Th} \Rightarrow R_N = R_{Th}$
- By using “Source Transformation” method, the conversion between Thevenin and Norton theorems are possible.
- Correlation between Thevenin and Norton parameters are given as follows;

$$I_N = \frac{V_{Th}}{R_{Th}}; \quad V_{Th} = v_{oc} \quad \text{and} \quad I_N = i_{sc}$$
$$R_{Th} = \frac{v_{oc}}{i_{sc}} = R_N$$

# Circuit Theory

## Norton's Theorem

Example 4.5 :

Find the Norton equivalent circuit of the circuit of Fig. E4.5.

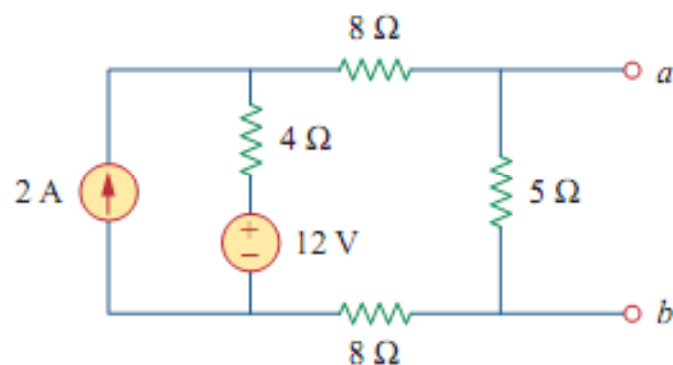





Fig. E4.5



# Circuit Theory
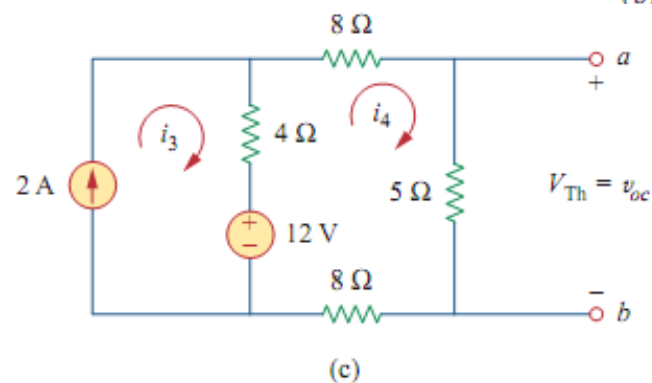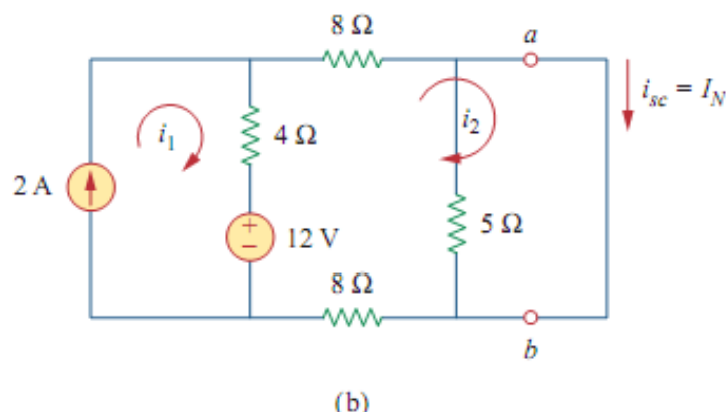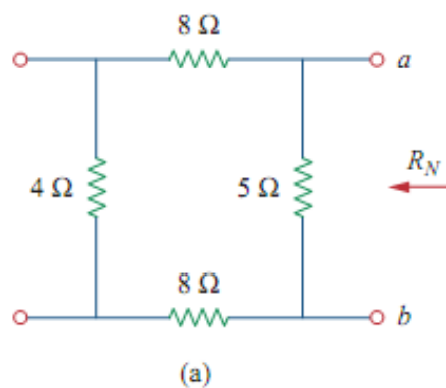
## Norton's Theorem

Finding (a)  $R_N$ , (b)  $I_N = i_{sc}$ , (c)  $V_{Th} = v_{oc}$ .



# Circuit Theory

## Norton's Theorem

### Problem 4.3:

Find the Norton equivalent circuit of the circuit in Fig. P4.3 at terminals  $a$ - $b$ .

(Ans:  $R_N = 1 \Omega$ ,  $I_N = 10 \text{ A}$ )

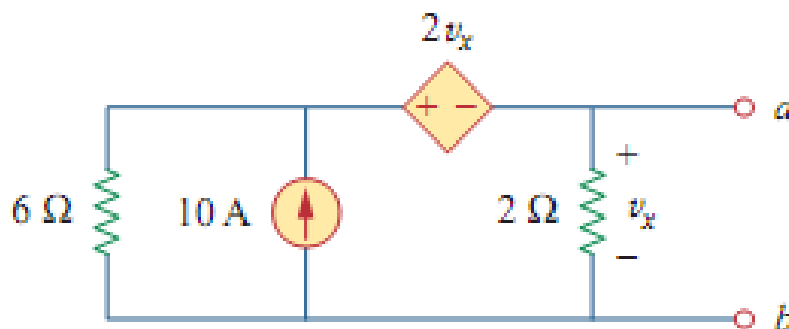


Fig. P4.3