



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

www.utm.my

SKEE 1043

Three Phase Systems

06/07/2009

INSPIRING CREATIVE AND INNOVATIVE MINDS



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

www.utm.my

Three Phase Systems

- A 3- Φ system is formed by 3*1- Φ systems, which are physically connected together for 3- Φ operation.
- To maintain constant power flow, the three single phase circuits must be operated with the same voltage and current magnitudes in each phase (circuit), with a relative phase angle of 120 electrical degrees apart.

06/07/2009

INSPIRING CREATIVE AND INNOVATIVE MINDS



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

www.utm.my

Three Phase Systems

Advantages of 3- Φ compared to 1- Φ system

- High efficiency
- For same power transfer at the transmission line, less conductor and hence lighter in weight
- Construction and maintenance minimum and therefore cheaper
- Starting characteristic and operation of 3- Φ equipment better/more stable than 1- Φ

06/07/2009

INSPIRING CREATIVE AND INNOVATIVE MINDS



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

www.utm.my

Three Phase Systems

Basic AC Generation Principle

When a conductor is placed in a magnetic field, if one of them is moved, an electromotive force (emf) will be induced in the conductor. This effect is called electromagnetic induction.

06/07/2009


INSPIRING CREATIVE AND INNOVATIVE MINDS



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

www.utm.my

Three Phase Systems

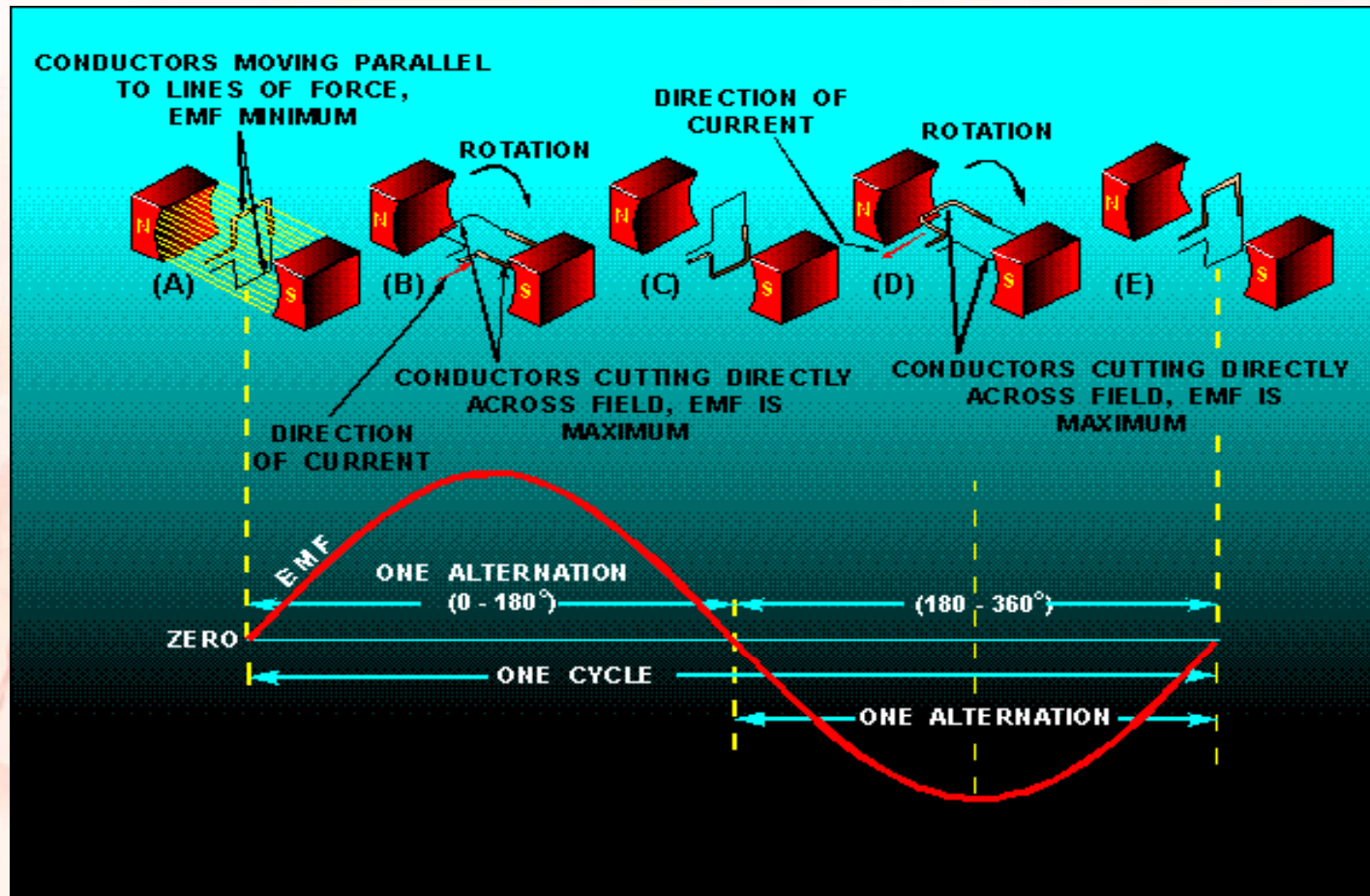

06/07/2009

INSPIRING CREATIVE AND INNOVATIVE MINDS






UTM
UNIVERSITI TEKNOLOGI MALAYSIA

www.utm.my

A simple three-phase two-pole generator

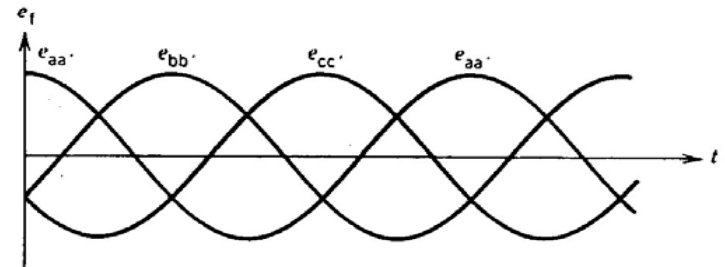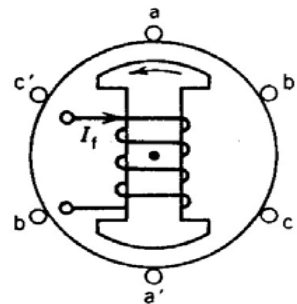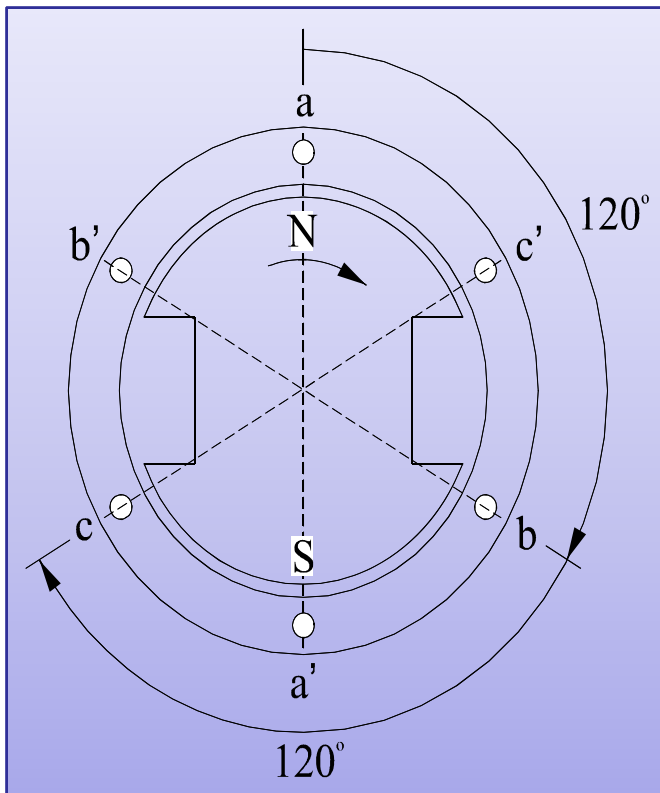Three separate windings or coils with terminals a-a', b-b' and c-c' are physically placed 120° apart around the stator.



06/07/2009


INSPIRING CREATIVE AND INNOVATIVE MINDS



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

www.utm.my

Emf Generated

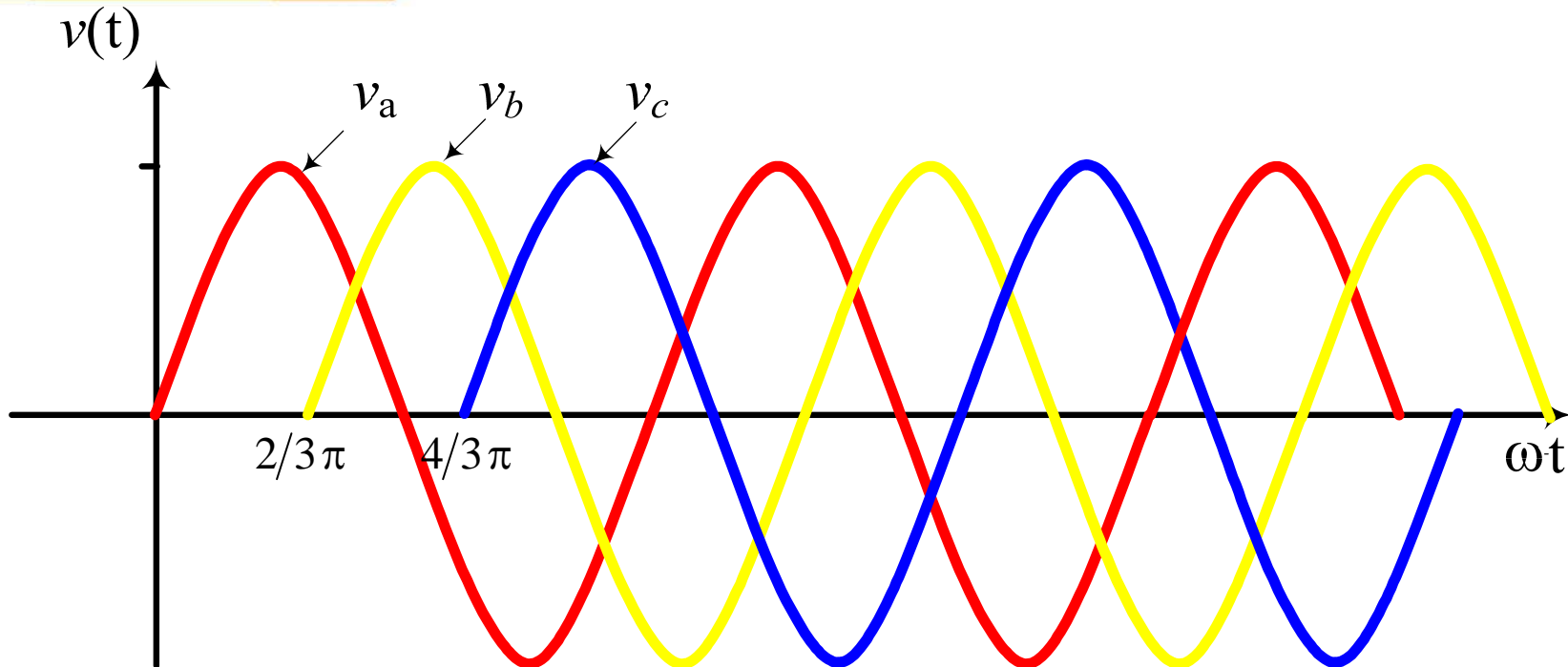

$$v_a = V_a \sin \omega t$$

$$v_b = V_b \sin (\omega t - 120^\circ)$$

$$v_c = V_c \sin (\omega t - 240^\circ) = V_c \sin (\omega t + 120^\circ)$$

$$V_a = V \angle 0^\circ$$

$$V_b = V \angle -120^\circ$$

$$V_c = V \angle -240^\circ = V \angle 120^\circ$$

06/07/2009


INSPIRING CREATIVE AND INNOVATIVE MINDS



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

www.utm.my

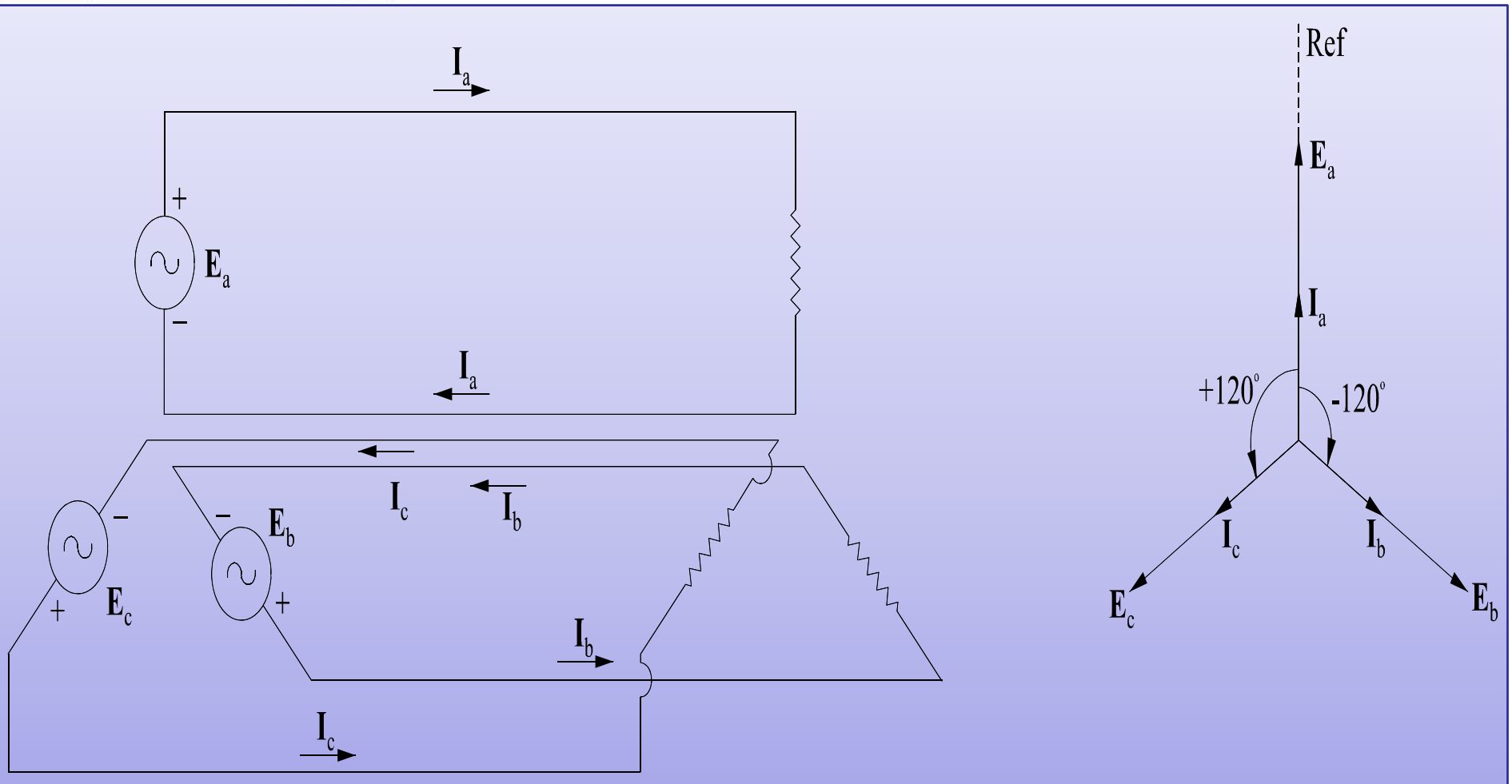A three phase system and its vector diagrams




06/07/2009

INSPIRING CREATIVE AND INNOVATIVE MINDS



Three Phase System-Phase Sequence

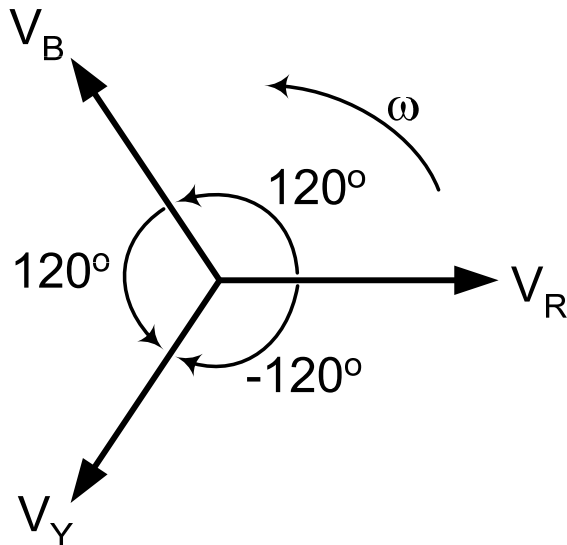- RYB or positive sequence, we describe the phase sequence as Red-Yellow-Blue
- V_R leads V_Y , which in turn leads V_B . This sequence is produced when the rotor rotates in the counterclockwise direction.



$$V_R = V_{R(rms)} \angle 0^\circ$$


$$V_Y = V_{Y(rms)} \angle -120^\circ$$

$$V_B = V_{B(rms)} \angle -240^\circ \\ = V_{B(rms)} \angle 120^\circ$$



Three Phase System-Phase Sequence

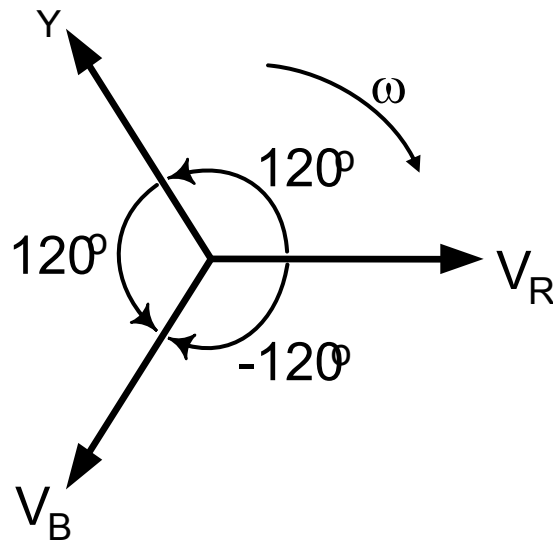- **RBV or negative sequence, we describe the phase sequence as Red-Blue-Yellow**
- V_R leads V_B , which in turn leads V_Y . This sequence is produced when the rotor rotates in the clockwise direction.



$$V_R = V_{R(rms)} \angle 0^\circ$$


$$V_B = V_{B(rms)} \angle -120^\circ$$

$$V_Y = V_{Y(rms)} \angle -240^\circ \\ = V_{Y(rms)} \angle 120^\circ$$

- **Remember in this subject all phasor systems rotate counter clockwise**




Three Phase System-Connections

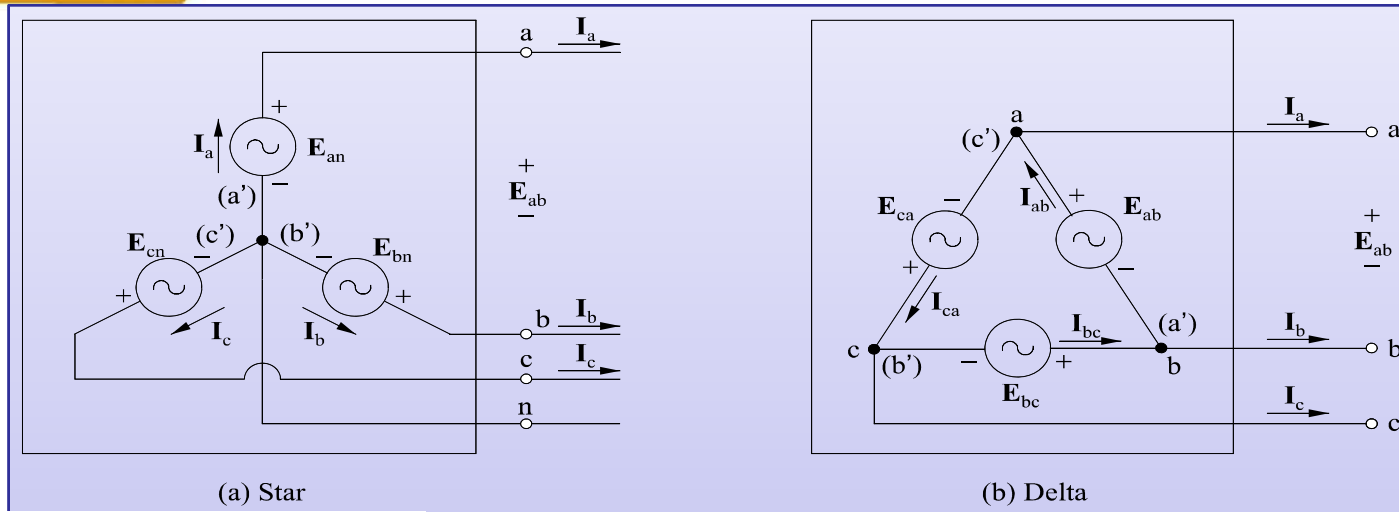

Star Connection (Y)

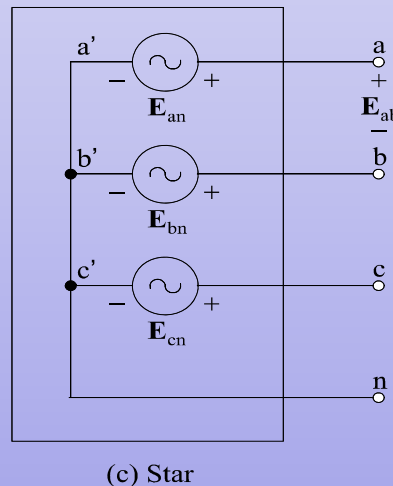- Usually is being used in system that need **high voltage** and **low current**
- There are two type of Y connection, i.e:
 - i) 3 wire star connection
 - ii) 4 wire star connection (3 live conductors and one neutral)



Delta Connection (Δ)


- Usually is being used in system that need **high line current** and **low phase current**.
- Connect all the conductor in **series**.
- No neutral line



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

www.utm.my

An example of three phase connections

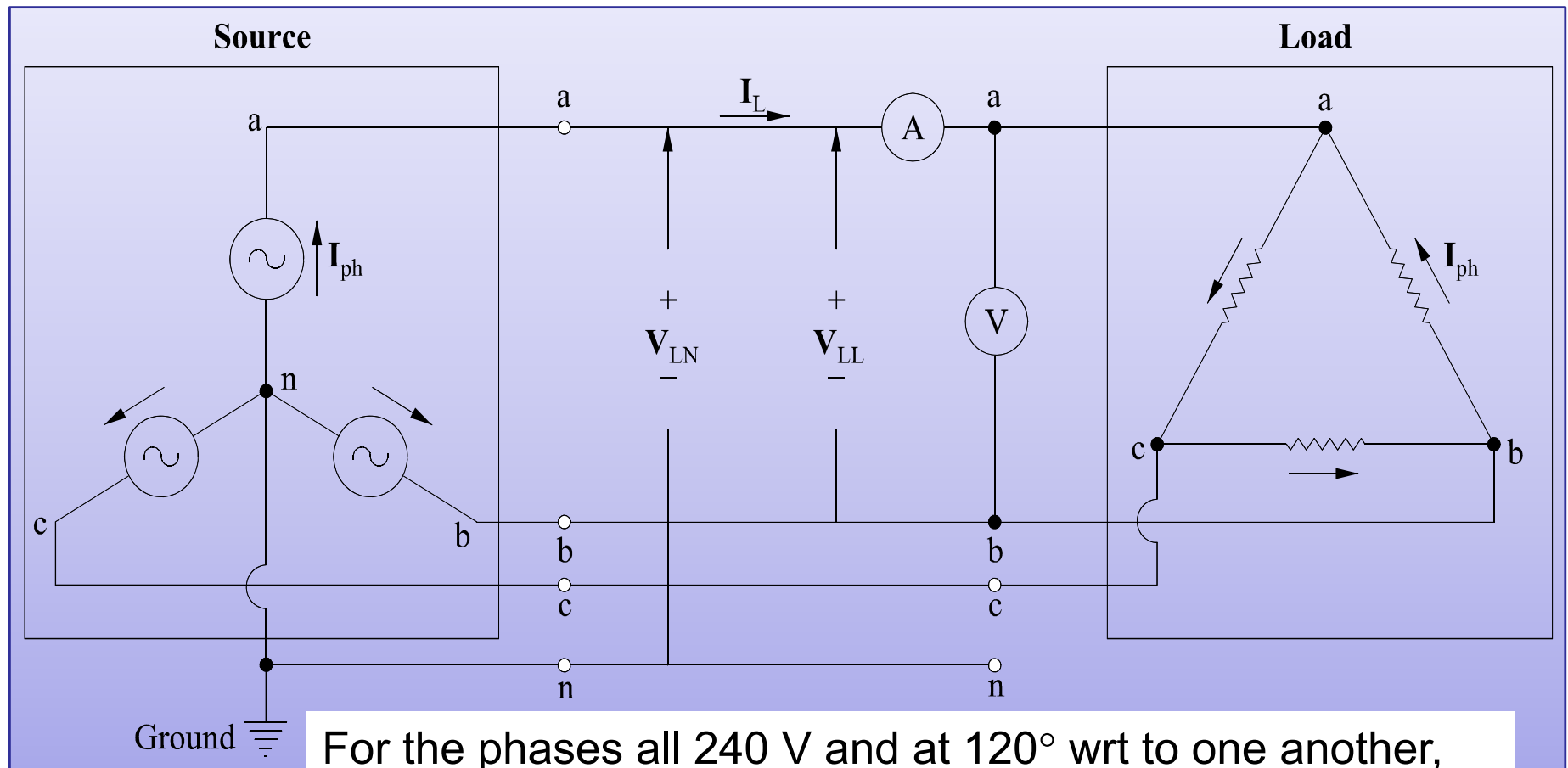

For the phases all 240 V and at 120° wrt to one another, the system is balanced if the 3 loads are equal

06/07/2009

INSPIRING CREATIVE AND INNOVATIVE MINDS



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

www.utm.my

Definitions

Commonly AC power is a three-phase (3- Φ) supply system as shown
The 240 Volts single phase supply is just one part of such a multiphase system


It is a common practice to use the following to specify the voltage and current ratings of the three phase devices:

- Voltage between external terminals
(**line-to-line voltage**): V_{LL}
- Current flowing in external lines
(**line current**): I_L

V_{LL} and I_L are called 'line' quantities.

The voltages and currents internal to the device are referred to as
'Phase' quantities
(e.g. phase-to-neutral voltage).

06/07/2009

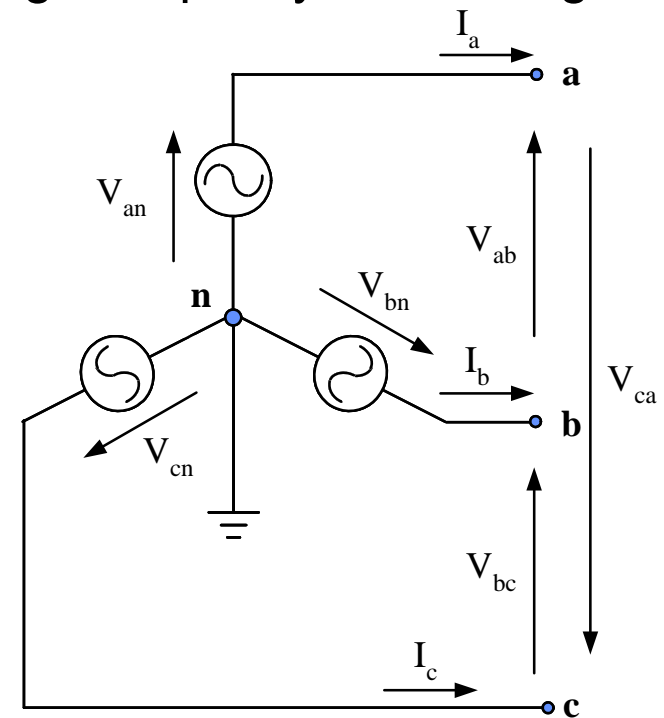



Relationship between voltages and currents

For balanced systems the relationships are:

Star connection


Reference voltage: V_{an}

Phase current = Line current = I_L

The voltage from one live conductor to another is called the **line-to-line** voltages or simply **line** voltages

- e.g. V_{ab} , V_{bc} , V_{ca}
- To calculate V_{ab} , (KVL)
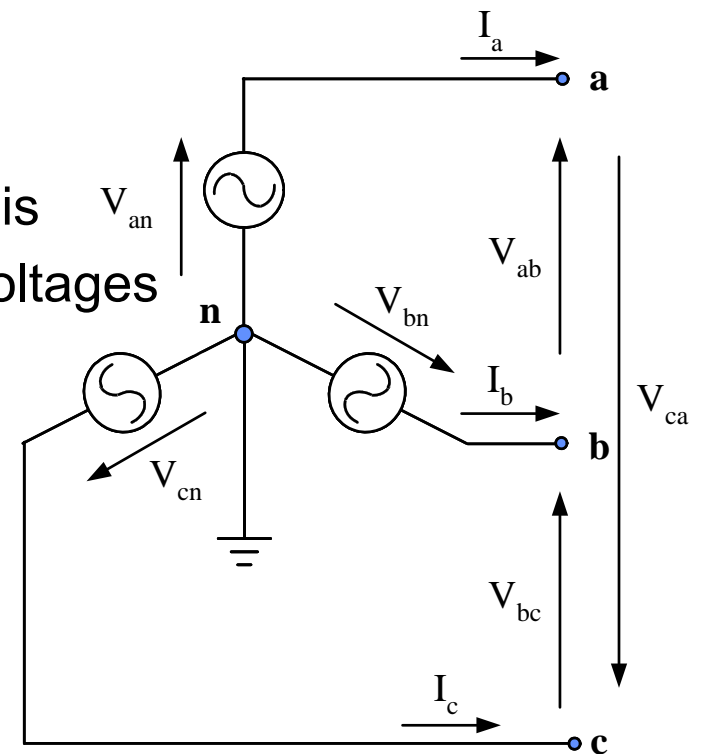
$$\begin{aligned} V_{ab} &= V_{an} - V_{bn} \\ &= V_{an} - V_{an} \angle -120^\circ \\ &= V_{an} (1 - (-0.5 - j0.866)) \\ &= \sqrt{3} V_{an} \angle 30^\circ V \end{aligned}$$



$$V_{an} + V_{bn} + V_{cn} = 0$$

In a perfectly balanced system

06/07/2009



Relationship between voltages and currents


- The following vector diagram shows the relationship between phase angles of the phase and line voltages
- The 120° phase shift also exists between each line voltage

$$V_{ab} = \sqrt{3} V_{an} \angle 30^\circ$$

$$V_{bc} = \sqrt{3} V_{bn} \angle -90^\circ$$

$$V_{ca} = \sqrt{3} V_{cn} \angle -210^\circ$$

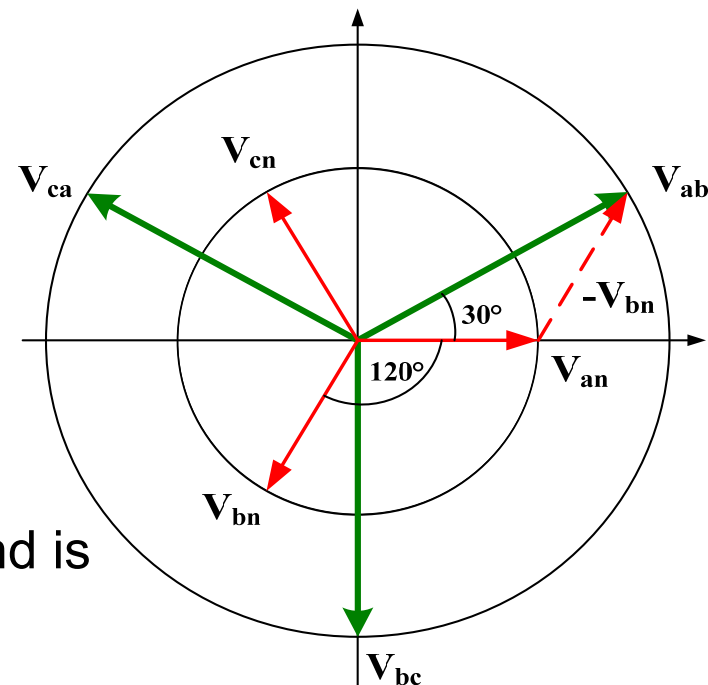Line voltage (V_L) has magnitude $\sqrt{3} V_P$ and is leading phase voltage (V_{PH}) with 30° .





Relationship between voltages and currents

For balanced systems the relationships are:

Delta connection:

Phase voltage = Line-to-Line Voltage = V_{LL}

$$I_{ab} = I_{ab} \angle 0^\circ = I_P \angle 0^\circ$$

$$I_{bc} = I_{bc} \angle -120^\circ = I_P \angle -120^\circ$$

$$I_{ca} = I_{ca} \angle 120^\circ = I_P \angle 120^\circ$$

KCL :


$$\Rightarrow I_a = I_{ab} - I_{ca}$$

$$= I_P \angle 0^\circ - I_P \angle 120^\circ$$

$$= I_P (1 - (-0.5 + j0.866))$$

$$= \sqrt{3} I_P \angle -30^\circ$$

06/07/2009

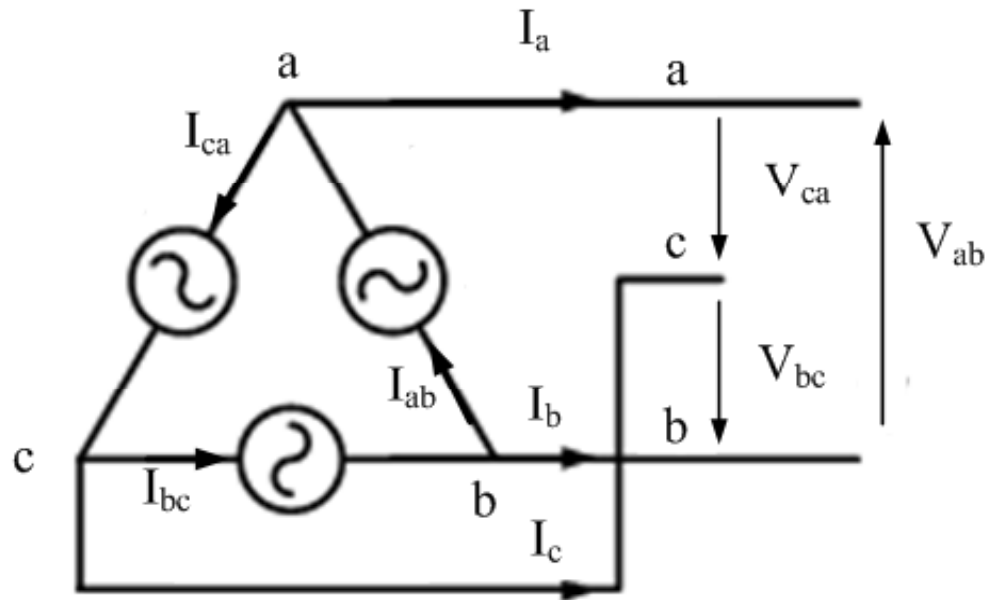




Relationship between voltages and currents

$$I_a = I_{ab} - I_{ca} = \sqrt{3} I_p \angle -30^\circ$$

$$I_b = I_{bc} - I_{ab} = \sqrt{3} I_p \angle -150^\circ$$



$$I_c = I_{ca} - I_{bc} = \sqrt{3} I_p \angle 90^\circ$$

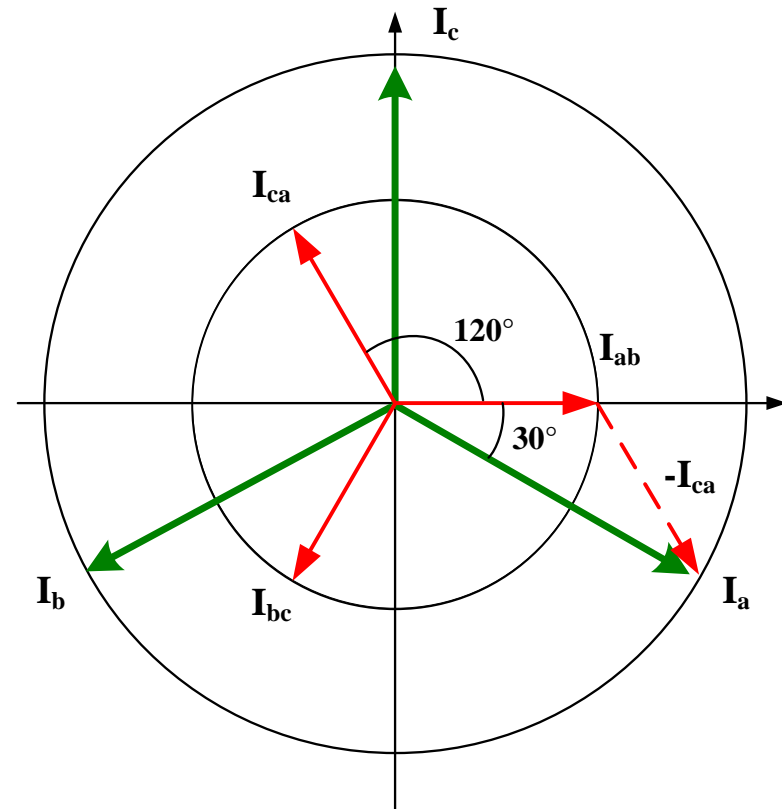Line Current (I_L) lagging current phase (I_{PH}) with 30° .





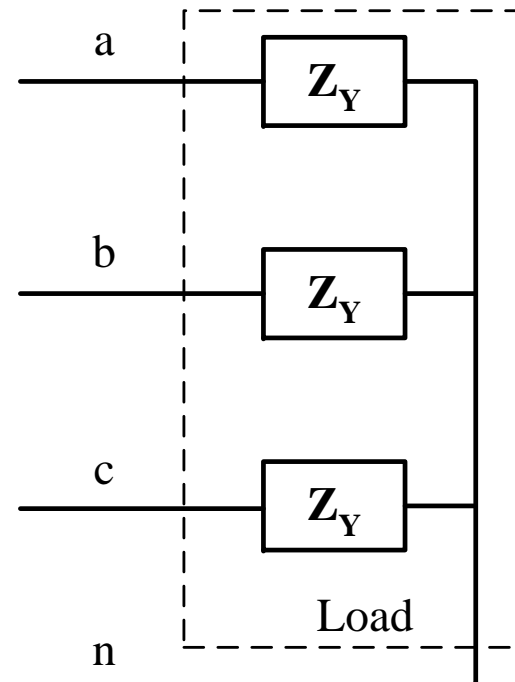
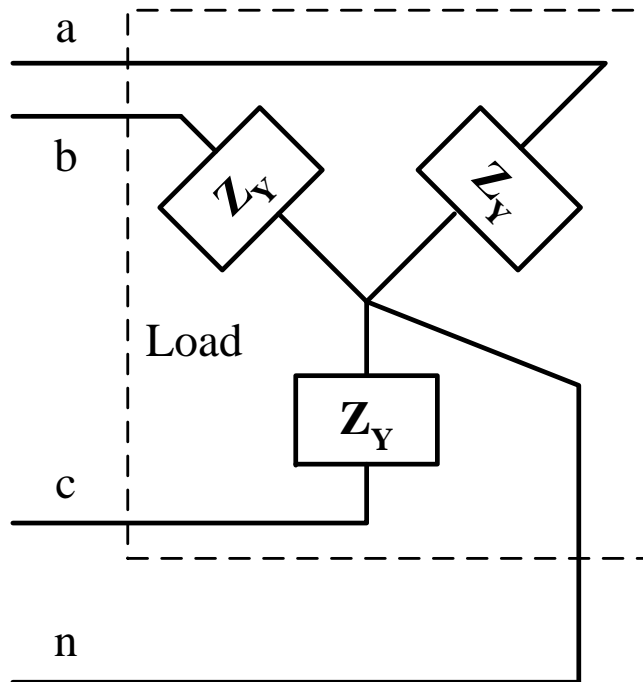
Loads can also be connected in a 3-phase fashion



Star (Wye) connection of Load



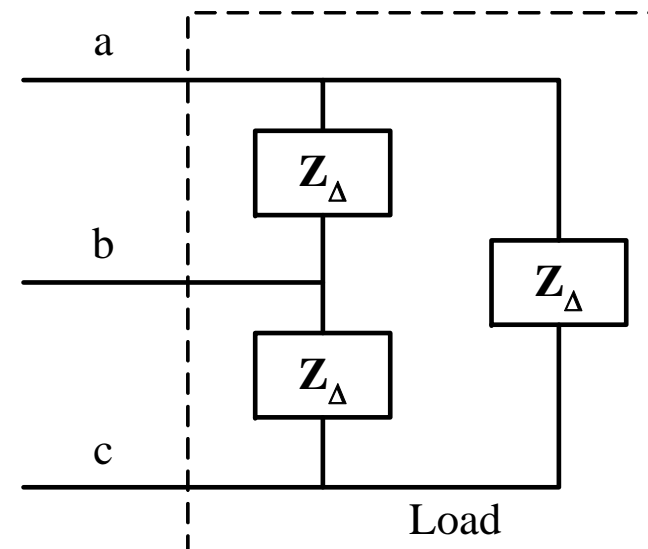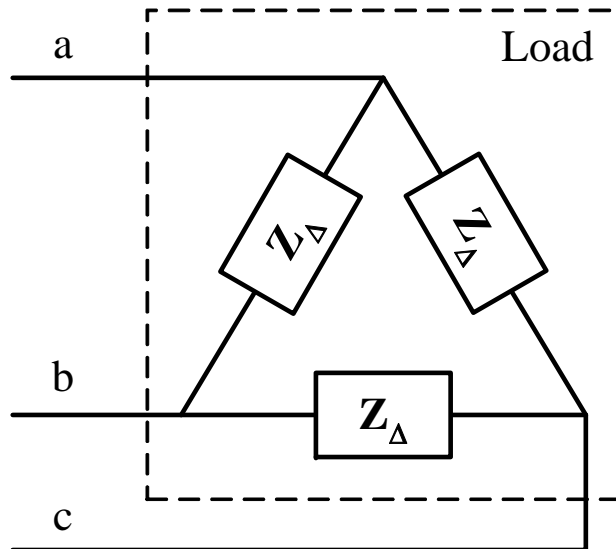Loads can also be connected in a 3-phase fashion



Delta connection at the Load




3-Phase balanced system

A 3-Phase 4 Wire Balanced System consists of a star connected source connected to a star connected load by 3 live wires and one neutral

Such a system will be balanced if all the three loads are equal

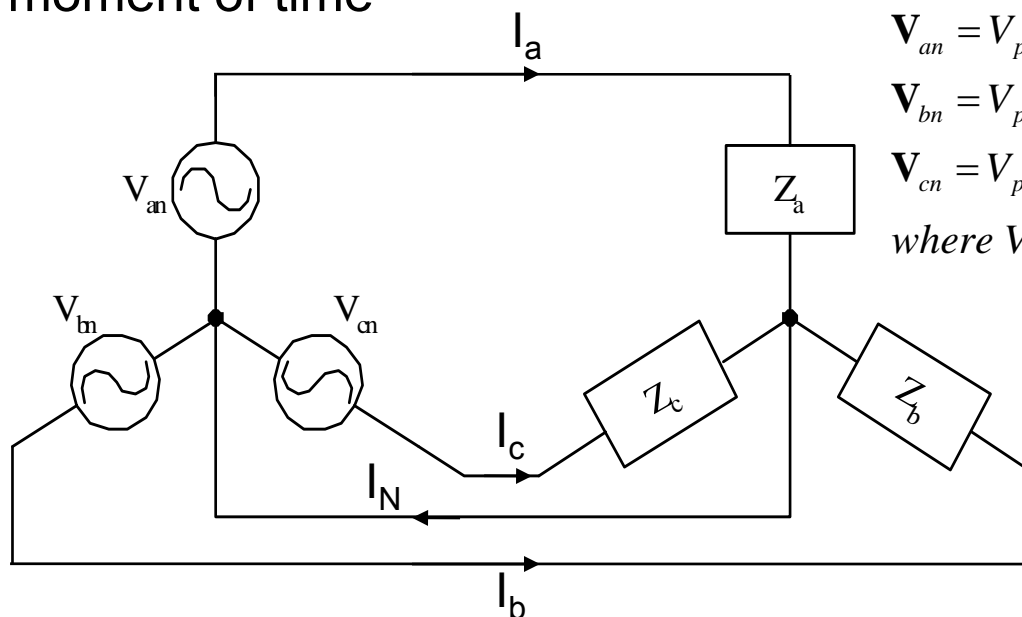In a balanced system, $I_a + I_b + I_c = I_N \rightarrow$ The neutral current is zero at each moment of time



$$V_{an} = V_{phase} \angle 0^\circ$$

$$V_{bn} = V_{phase} \angle -120^\circ$$

$$V_{cn} = V_{phase} \angle -240^\circ$$

$$\text{where } V_{phase} = |V_{an}| = |V_{bn}| = |V_{cn}|$$

$$I_a = \frac{V_{an} \angle 0^\circ}{Z_a}$$

$$I_b = \frac{V_{bn} \angle -120^\circ}{Z_b}$$

$$I_c = \frac{V_{cn} \angle 120^\circ}{Z_c}$$



3-Phase balanced system


Wye-Connected Balanced Loads - Three wire system

$$\mathbf{V}_{as} = V_{phase} \angle 0^\circ$$

$$\mathbf{V}_{bs} = V_{phase} \angle -120^\circ$$

$$\mathbf{V}_{cs} = V_{phase} \angle -240^\circ$$

$$\text{where } V_{phase} = |\mathbf{V}_{as}| = |\mathbf{V}_{bs}| = |\mathbf{V}_{cs}|$$

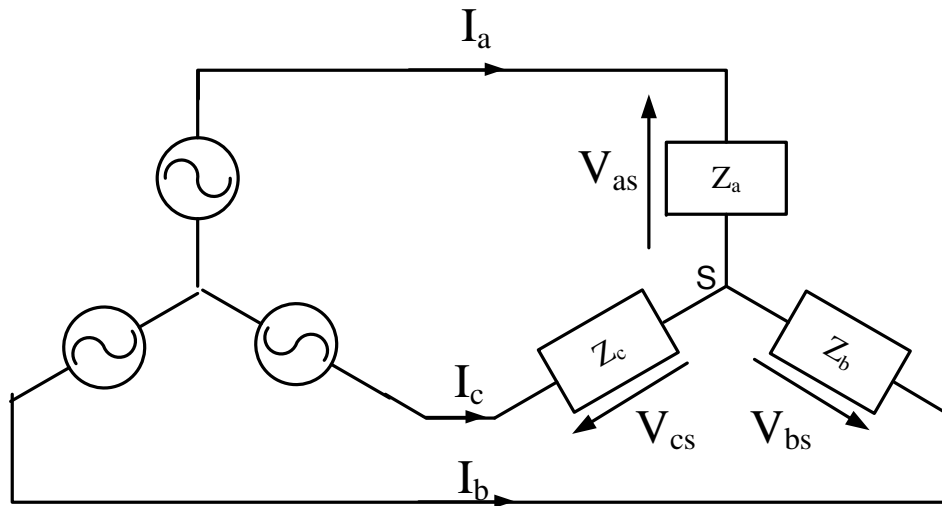

$$I_a = \frac{V_{as} \angle 0^\circ}{Z_a}$$

$$I_b = \frac{V_{bs} \angle -120^\circ}{Z_b}$$


$$I_c = \frac{V_{cs} \angle 120^\circ}{Z_c}$$

06/07/2009



3-Phase balanced system

Delta-Connected Balanced Loads

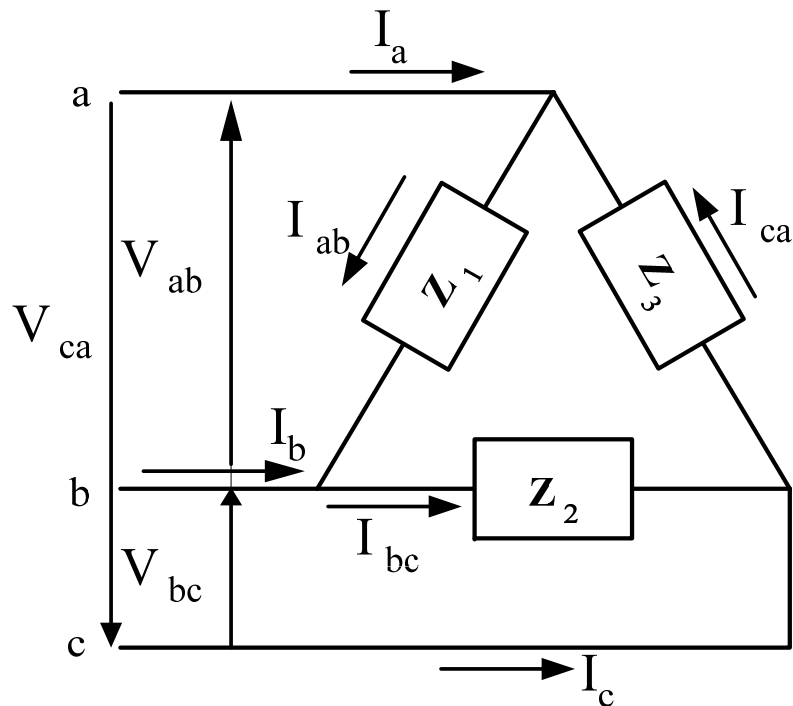

where $|\mathbf{I}_{RY}| = |\mathbf{I}_{YB}| = |\mathbf{I}_{BR}| = \mathbf{I}_{\text{phasa}}$

and $|\mathbf{I}_R| = |\mathbf{I}_Y| = |\mathbf{I}_B| = \mathbf{I}_{\text{line}}$

Phase currents:

$$\mathbf{I}_{ab} = \frac{\mathbf{V}_{ab} \angle 0^\circ}{\mathbf{Z}_1}$$

$$\mathbf{I}_{bc} = \frac{\mathbf{V}_{bc} \angle -120^\circ}{\mathbf{Z}_2}$$

$$\mathbf{I}_{ca} = \frac{\mathbf{V}_{ca} \angle 120^\circ}{\mathbf{Z}_3}$$

Line currents:

$$\mathbf{I}_a = \mathbf{I}_{ab} - \mathbf{I}_{ca}$$

$$\mathbf{I}_b = \mathbf{I}_{bc} - \mathbf{I}_{ab}$$


$$\mathbf{I}_c = \mathbf{I}_{ca} - \mathbf{I}_{bc}$$



Example Problem

Given a balanced three phase four wire system with a wye-connected inductive load whose series impedance is: $Z = 4 + j4$ (per phase), and a 415 V supply,

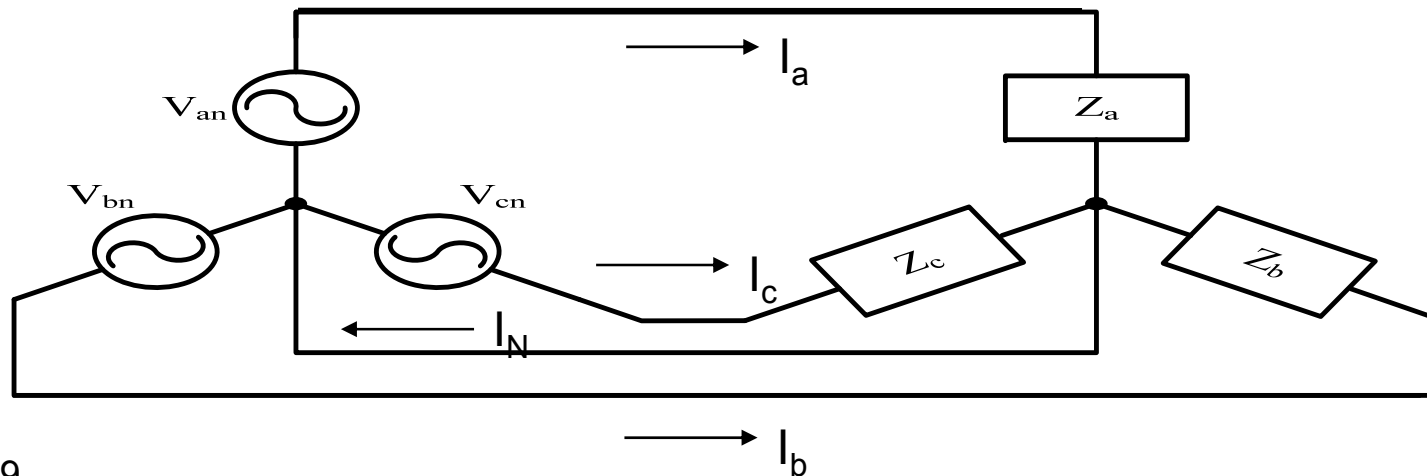
- i) Calculate the phase and line voltages
- ii) Line currents
- iii) Demonstrate that the neutral current is zero





Unbalanced Loads

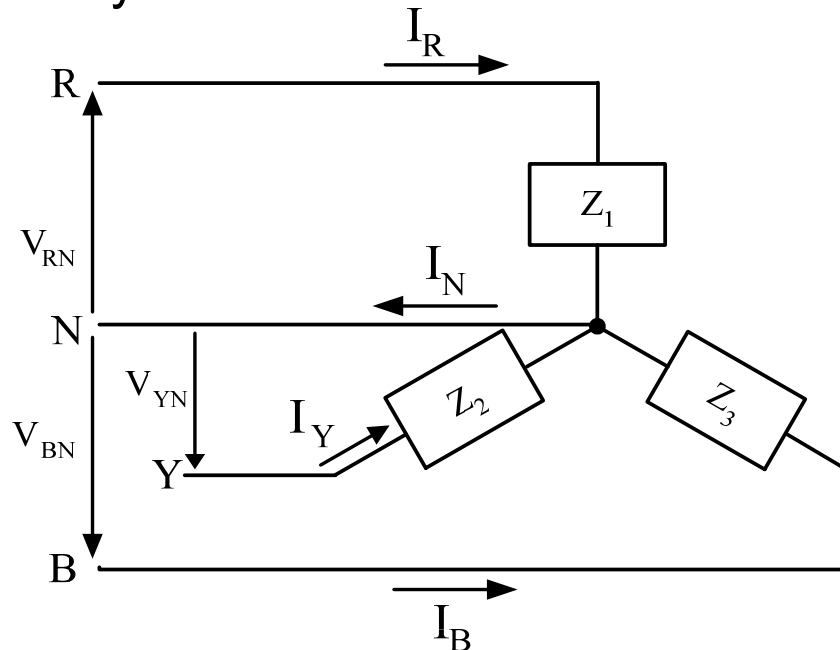Wye-Connected unbalanced Loads - Four wire system



$$\mathbf{I}_N = \mathbf{I}_R + \mathbf{I}_Y + \mathbf{I}_B$$

For unbalanced load system,

$$\mathbf{I}_N \neq 0 \text{ and } Z_1 \neq Z_2 \neq Z_3$$

$$\mathbf{V}_{RN} = \mathbf{V}_{\text{phasa}} \angle 0^\circ$$

$$\mathbf{V}_{YN} = \mathbf{V}_{\text{phasa}} \angle -120^\circ$$

$$\mathbf{V}_{BN} = \mathbf{V}_{\text{phasa}} \angle 120^\circ$$

$$\mathbf{I}_R = \frac{\mathbf{V}_{RN} \angle 0^\circ}{Z_1}$$


$$\mathbf{I}_Y = \frac{\mathbf{V}_{YN} \angle -120^\circ}{Z_2}$$

$$\mathbf{I}_B = \frac{\mathbf{V}_{BN} \angle 120^\circ}{Z_3}$$



Unbalanced Loads

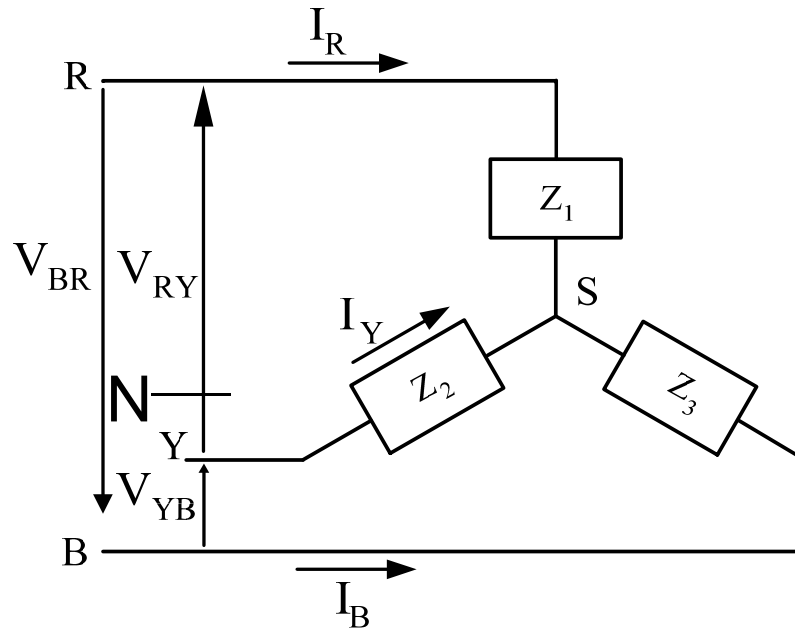Wye-Connected unbalanced Loads - Three wire system



Note:

Point N \neq Point S

Potential between two point,
displacement Neutral voltage,
 V_{SN}




Two methods to solve Wye-Connected unbalanced Loads i.e. three wire/without neutral:

- **Change star connection to delta (Refer: Y- Star to delta transformation)**
 - Calculate I_{PH} from delta
 - Calculate I_L using KCL
 - Phase current (star) = line current (delta) because line I = phase I in Y connection
- **Using loop analysis**
 - ❖ Indicate direction of loop current
 - ❖ Write loop equations
 - ❖ Calculate loop current
 - ❖ Calculate line current = branch current

Unbalanced Loads

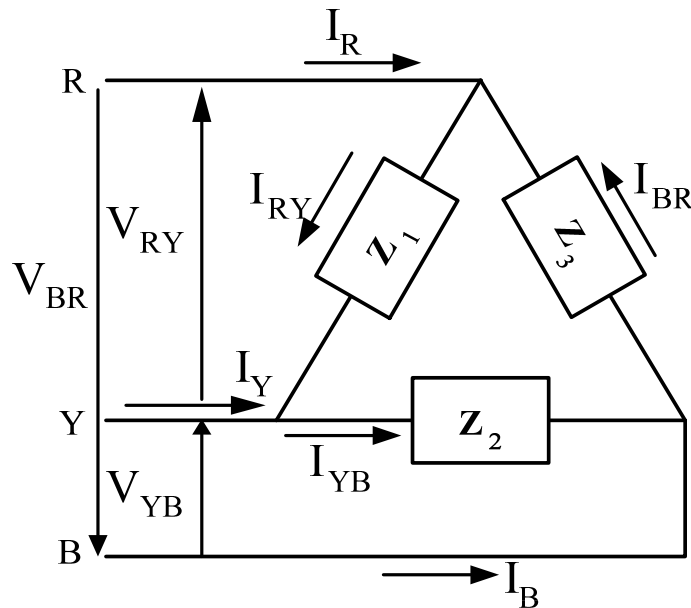Delta-Connected unbalanced Loads - Three wire system



$$V_{RY} = V_{phase} \angle 0^\circ$$

$$V_{YB} = V_{phase} \angle -120^\circ$$

$$V_{BR} = V_{phase} \angle 120^\circ$$

Phase currents:

$$I_{RY} = \frac{V_{RY} \angle 0^\circ}{Z_1}$$

$$I_{YB} = \frac{V_{YB} \angle -120^\circ}{Z_2}$$

$$I_{BR} = \frac{V_{BR} \angle 120^\circ}{Z_3}$$

Line currents:

$$I_R = I_{RY} - I_{BR}$$

$$I_Y = I_{YB} - I_{RY}$$

$$I_B = I_{BR} - I_{YB}$$



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

www.utm.my

Example Problem

Given an unbalanced delta-connected load which is:

$Z_1 = 6 + j8 \, \Omega$ (per phase), $Z_2 = 4 - j3 \, \Omega$, $Z_3 = 8 + j6 \, \Omega$,

Supply=110 V

- i) Calculate the phase and line currents
- ii) Construct the phasor diagram



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

www.utm.my

Example Problem

A 3-Phase 4 Wire unbalanced load is supplied by a three phase 220V.
The impedance per phase are as follows:

$$Z_1 = 10\angle -50^\circ \Omega, Z_2 = 15\angle 25^\circ \Omega, \text{ and } Z_3 = 5\angle -90^\circ \Omega$$

- i) Calculate the line currents and neutral current
- ii) Construct the phasor diagram



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

www.utm.my

Example Problem

A balanced line voltage 415 V is supplied to the three impedance as follows:

$$Z_1 = 10\angle 30^\circ \Omega, Z_2 = 20\angle 60^\circ \Omega, \text{ and } Z_3 = 10\angle -45^\circ \Omega.$$

Note: All the three impedance form Y connected without neutral line.

- i) Calculate the line currents
- ii) Calculate the voltage across each impedance



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

www.utm.my

Example Problem

A 3 phase supply, 4 wire, 415 V, 50Hz supplies power to the loads. The values of loads are given below:

Load 1 : $P_1 = 11 \text{ kW}$, p.f 0.85 lag

Load 2 : $Q_2 = 8 \text{ kVar}$, p.f 0.8 lag

Load 3 : $S_3 = 15 \text{ kVA}$, p.f 0.75 lag

$Z_4 = 10 \angle 15^\circ \Omega$

Calculate the line currents (I_R , I_Y , and I_B)

Hint: Choose V_{RN} as a reference



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

www.utm.my

Example Problem

A factory is supplied by a balanced three phase source. The factory has two plants, each a balanced three phase load as follows:

- i) Load 1: 150 kVA at 0.8 pf leading – Y connected
- ii) Load 2: 80 kW and 95 kVAR (inductive)- delta connected

The loads are connected in parallel. Assume a lossless line, find the current at each load and total current if the source voltage is 415 V.



Example Problem

A 3 phase Y connected load is supplied by a three phase source 346.4 V, 50Hz. The magnitudes of line currents are $I_R = 50$ A, $I_Y = 40$ A and $I_B = 33.33$ A. By using a phasor diagram in figure 1, calculate the each load impedance value. Choose phase R voltage as a reference.

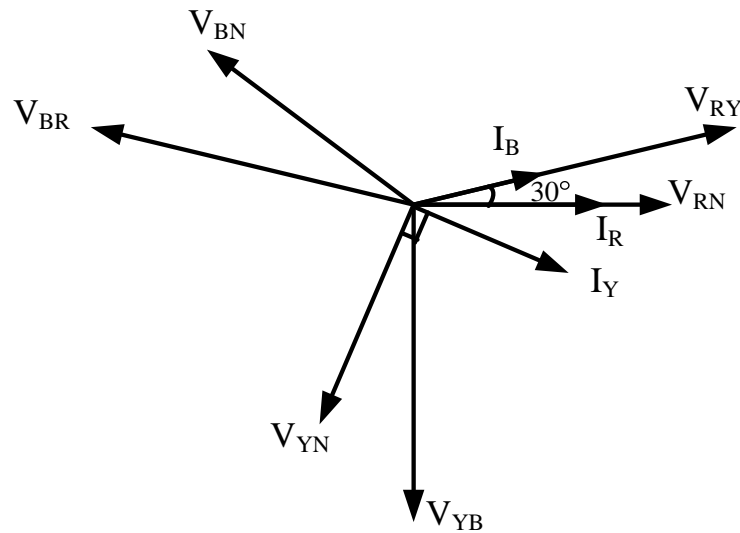


Figure 1



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

www.utm.my

Example Problem

Three similar coils having $20 \, \Omega$ resistance and $0.8 \, \text{H}$ inductance are connected in Y for a three phase supply $400 \, \text{V}$, $50 \, \text{Hz}$.

- I) Calculate per phase impedance
- ii) Total real power of the loads



3-Phase power

The three phase power is equal to the algebraic sum of individual phase powers

If the load is balanced: $P_{3ph} = 3 P_{phase} = 3 V_{phase} I_{phase} \cos \theta$

- Wye connection system**

$$I_{phase} = I_L \quad \text{and} \quad V_{LL} = \sqrt{3} V_{phase}$$

$$\text{Real Power, } P_{3ph} = 3 V_{phase} I_{phase} \cos \theta$$

$$= \sqrt{3} |V_{LL}| |I_L| \cos \theta \text{ Watt}$$



3-Phase power

- Wye connection system

$$I_{\text{phase}} = I_L \quad \text{and} \quad |V_{LL}| = \sqrt{3} |V_{\text{phase}}|$$

$$\begin{aligned} \text{Reactive power, } Q_{3\text{ph}} &= 3 V_{\text{phase}} I_{\text{phase}} \sin \theta \\ &= \sqrt{3} |V_{LL}| |I_L| \sin \theta \text{ VAr} \end{aligned}$$

$$\begin{aligned} \text{Apparent power, } S_{3\text{ph}} &= 3 V_{\text{phase}} I_{\text{phase}} \\ &= \sqrt{3} |V_{LL}| |I_L| \text{ VA} \end{aligned}$$



3-Phase power

- Delta connection system

$$V_{LL} = V_{phase} \quad I_L = \sqrt{3} I_{phase}$$

$$\begin{aligned} \text{Real Power, } P &= 3 V_{phase} I_{phase} \cos \theta \\ &= \sqrt{3} |V_{LL}| |I_L| \cos \theta \text{ Watt} \end{aligned}$$

$$\begin{aligned} \text{Reactive power, } Q_{3ph} &= 3 V_{phase} I_{phase} \sin \theta \\ &= \sqrt{3} |V_{LL}| |I_L| \sin \theta \text{ VAr} \end{aligned}$$

$$\begin{aligned} \text{Apparent power, } S_{3ph} &= 3 V_{phase} I_{phase} \\ &= \sqrt{3} |V_{LL}| |I_L| \text{ VA} \end{aligned}$$



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

www.utm.my

3-Phase power

For connection of wye as well as delta, the formula for calculation of all the 3ϕ powers that are P(real), Q(reactive) and S(apparent) are the same

06/07/2009

INSPIRING CREATIVE AND INNOVATIVE MINDS



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

www.utm.my

Example Problem

A balanced wye-connected load of $(8+j6)\Omega$ per phase is connected to a balanced 3-phase 400V supply. Find:

- i) line currents
- ii) power factor
- iii) Real power, Reactive power and total volt-amperes.



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

www.utm.my

Example Problem

Three impedances each of magnitude $(15-j20)\Omega$ are connected in delta across a 3 phase, 400V supply. Determine the phase current, line current, real power and reactive power drawn from the supply.



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

www.utm.my

Power measurement

- In a four-wire system (3 phases and a neutral) the real power is measured using three single-phase watt-meters.
- In a three-wire system (three phases without neutral) the power is measured using only two single phase watt-meters.
- The watt-meters are supplied by the line current and the line-to-line voltage.


06/07/2009

INSPIRING CREATIVE AND INNOVATIVE MINDS



Power measurement

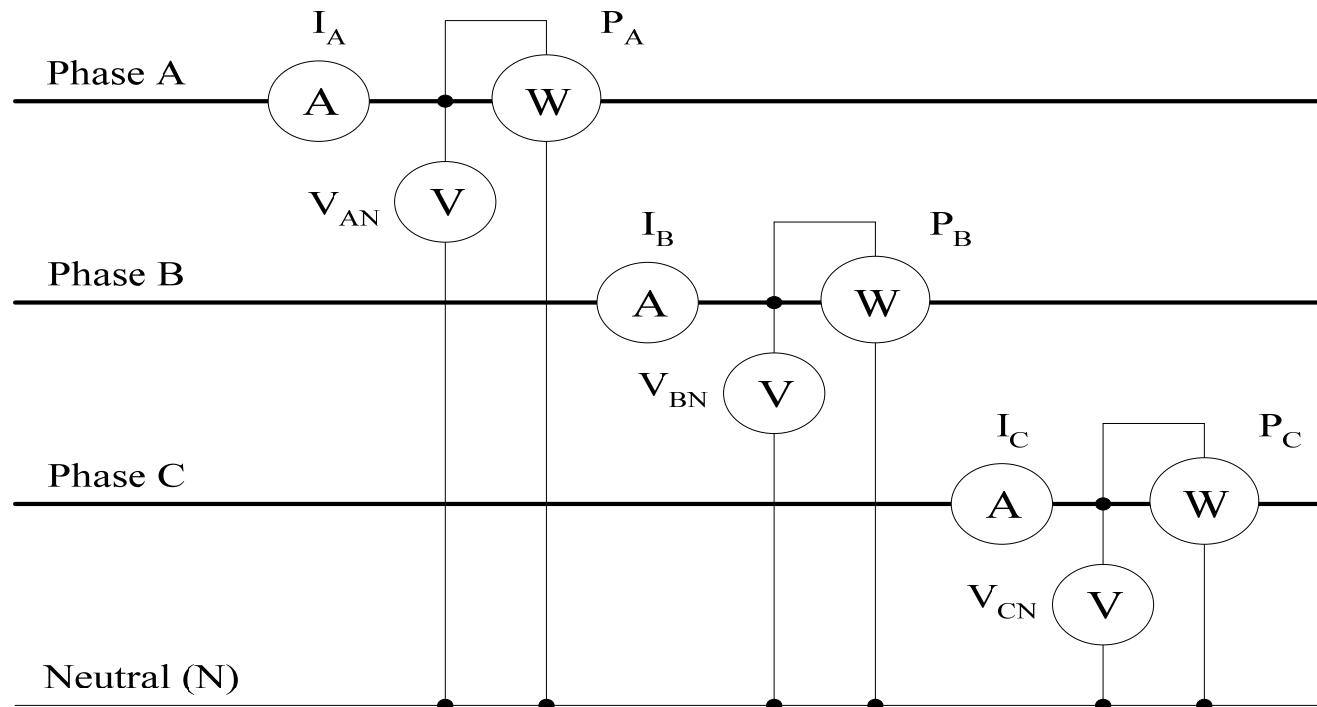Four wire system - Each phase measured separately




06/07/2009



Power measurement

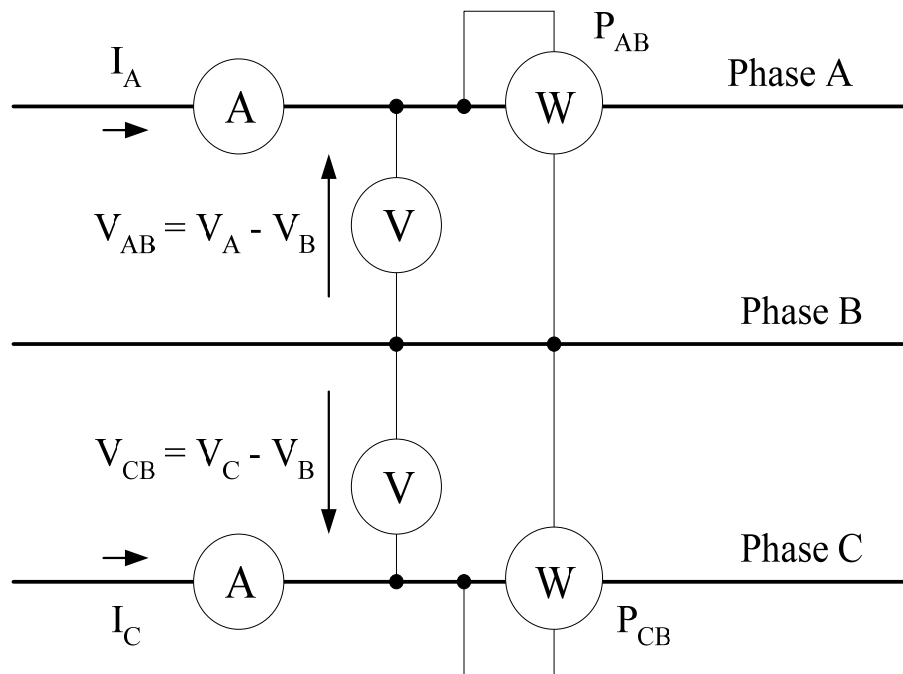Three wire system -The three phase power is the sum of the two watt-meters reading



$$P_{3\phi} = P_{AB} + P_{CB}$$

$$V_{ab} = 110 \angle 0^\circ \text{V}$$

$$I_a = 20 \angle -70^\circ \text{A}$$



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

www.utm.my



06/07/2009

INSPIRING CREATIVE AND INNOVATIVE MINDS