

MODULE 5: TUTORIAL QUESTIONS FOR UNIVERSAL & DUAL SYMBOL

For every circuit, please replace the basic gates with universal gates using the different techniques.

REPLACEMENT TECHNIQUE

- (i) NAND gates
- (ii) NOR gates

BUBBLE TECHNIQUE

- (iii) NAND gates
- (iv) NOR gates



