



Extra

Exercise 8b.3: Design 2-bit synchronous counter that using D flip-flop.
Show all steps clearly.



Extra

Exercise 8b.5: Design 3-bit synchronous counter that using T flip-flop.
Show all steps clearly.




Extra


Exercise 8b.6: Design 4-bit synchronous counter that using J-K flip-flop with negative edge triggered. Show all steps clearly.

Extra

Exercise 8b.7: Design 3-bit synchronous counter that using J-K flip-flop based on the state diagram below. Show all steps clearly.

 


 Exercise 8b.11: Design a counter with the irregular binary count sequence shown in the state diagram below using JK FF.



Extra

 Exercise 8b.12: Design a synchronous counter with the irregular binary count sequence shown in the state diagram below using J-K FF.



K-maps: Exercise 8b.12:



		Q_1Q_0			
XQ_2		00	01	11	10
00		0	X	1	X
01		X	X	X	X
11		X	X	X	X
10		1	X	0	X

$$J_2 = X\bar{Q}_1 + \bar{X}Q_1$$

		Q_1Q_0			
XQ_2		00	01	11	10
00		1	X	X	X
01		0	1	X	X
11		1	1	X	X
10		1	X	X	X

$$J_1 = X + \bar{Q}_2 + Q_0$$

		Q_1Q_0			
XQ_2		00	01	11	10
00		1	X	X	X
01		0	X	X	X
11		1	X	X	X
10		1	X	X	X

$$J_0 = X + \bar{Q}_2$$

		Q_1Q_0			
XQ_2		00	01	11	10
00		X	X	X	X
01		0	0	1	X
11		1	1	0	X
10		X	X	X	X

$$K_2 = X\bar{Q}_1 + \bar{X}Q_1$$

		Q_1Q_0			
XQ_2		00	01	11	10
00		X	X	1	X
01		X	X	1	X
11		X	X	1	X
10		X	X	0	X

$$K_1 = \bar{X} + Q_2$$

		Q_1Q_0			
XQ_2		00	01	11	10
00		X	X	0	X
01		X	0	1	X
11		X	0	0	X
10		X	X	0	X

$$K_0 = \bar{X}Q_2Q_1$$



Extra

Exercise 8b.13: Two type of counters, modulus-4 and modulus-8 need to be used to achieve count up to modulus- n (n CLK).

- a) How to cascade the counters to achieve count until 32 CLK (modulus-32)?
- b) What is the frequency produced by each counter given an initial frequency as 800MHz?

Extra

Exercise 8b.15: Analysis for the following sequential circuit. Use Method 1. Get state diagram for the sequential

