

**CONFIDENTIAL**

**FINAL EXAMINATION SEMESTER I 2013/2014**

**SUBJECT CODE** : **SCSR1013**  
**SUBJECT TITLE** : **DIGITAL LOGIC**  
**YEAR/COURSE** :  
**DURATION** :  
**DATE** :  
**VENUE** :

-----  
-----

## STRUCTURED QUESTIONS (100 MARKS)

(INSTRUCTION: Please answer ALL questions in the space provided.)

### QUESTION 1 (15 Marks)

- (a) Determine the sum generated by the 3-bit parallel adder in Figure 1 by completing the values in Table 1 for input A and B equal to  $101_2$  and  $110_2$  are being added. [4 marks]

 


Figure 1

Table 1

Label	A <sub>1</sub>	A <sub>2</sub>	A <sub>3</sub>	B <sub>1</sub>	B <sub>2</sub>	B <sub>3</sub>	C <sub>0</sub>	C <sub>1</sub>	C <sub>2</sub>	Σ <sub>1</sub>	Σ <sub>2</sub>	Σ <sub>3</sub>	Σ <sub>4</sub>
<b>Value (binary)</b>													

- (b) Identify the comparator inputs and outputs when the binary numbers of A and B are applied as shown in Figure 2. Complete Table 2. [5 marks]

Table 2

Symbol	Value (Binary)
<b>A</b>	
<b>B</b>	
<b>x</b>	
<b>y</b>	
<b>z</b>	

 


Figure 2

(1)

(c) Based on Figure 3, the data-input,  $D_i$  ( $i = 0, 1, 2, 3$ ) and data-select,  $S_j$  ( $j = 0, 1$ ) waveforms are applied to the multiplexer.

 


Figure 3

i. Identify the selection line ( $D_i$ ) at  $t_0$  until  $t_7$  by filling in Table 3. [2 marks]

Table 3

Time	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$
Selection line, $D_i$								

ii. Draw the output waveform Y in Figure 3. [4 marks]

**QUESTION 2 (20 Marks)**

(a) Referring to Figure 4, answer the questions below.

 


Figure 4

- i. What are the possible values of the signals to activate the asynchronous operation?  
[2 marks]
  
- ii. JK flip-flop is a universal flip-flop, which can be configured to work as different flip-flops. What type of flip-flop do FF1 and FF0 represent? Write your answers and provide justification in Table 4. [5 marks]

Table 4

Flip-flop	Type	Justification
FF1		
FF0		

- iii. Fill in Table 5 with the appropriate inputs according to the flip-flop priority operation. [2 marks]

Table 5

Priority	Input(s)
Highest	
Lowest	

- iv. Complete the values in Table 6 after 3 clock cycles for the given conditions. The initial value of  $Q_{FF0}$  is 0. Justify your answer. [5 marks]

Table 6

FF0		FF1		CLOCK	$Q_{FF0}$	$Q_{FF1}$
$\overline{PRE}$	$\overline{CLR}$	$\overline{PRE}$	$\overline{CLR}$			
1	0	1	1			

**Justification:**

- (b) Draw the output, Q of the different latches and flip-flop in Figure 5. Assume positive-edge clock. [6 marks]

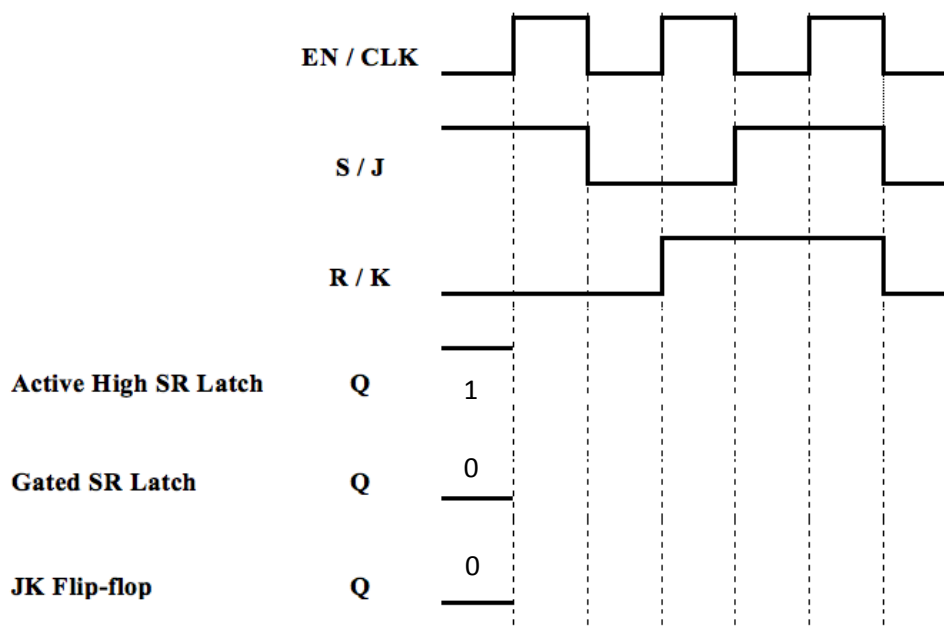


Figure 5

**QUESTION 3 (20 Marks)**

Answer the following questions based on Figure 6.

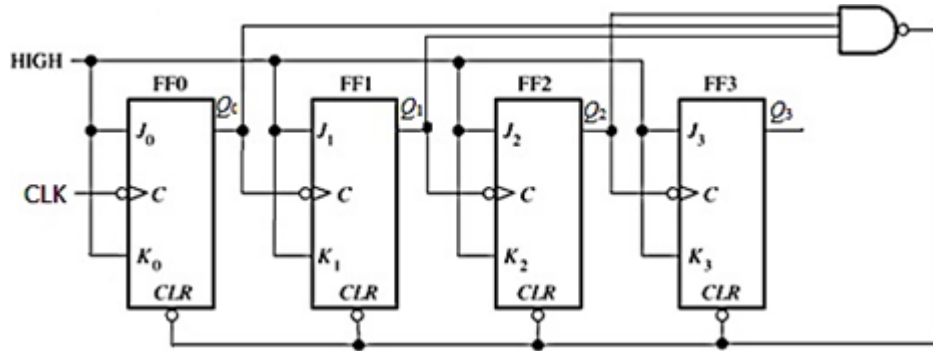


Figure 6

- (a) Draw the complete timing diagram for ten clock pulses in Figure 7. Initial value for  $Q_3 = Q_2 = Q_1 = Q_0 = 0$ . [4 marks]

 


Figure 7

- (b) Determine whether the counter is asynchronous or synchronous. Justify. [3 marks]

**Type of counter:**

**Justification:**

- (c) Is the counter count-up or count-down? [1 mark]

(d) What is the minimum and maximum number that can be counted by the counter based on **ONLY** four flip-flops? [2 marks]

(e) What is the purpose of the NAND gate in Figure 6? [2 marks]

(f) What is the actual modulus (MOD) for the counter? [2 marks]

(g) From your answer in 3(f), draw the state diagram for the counter. [4 marks]

(h) Based on your answers, comment on the efficiency of the counter design. [2 marks]

**QUESTION 4 (30 Marks)**

(a) Give **TWO** characteristics of each counter in Table 7 shown by the state diagram in Figure 8. [2 marks]

 


Figure 8

Table 7

Figure 8	Characteristic 1	Characteristic 2
(a)		
(b)		

(b) Complete the next state table for D and T flip-flops in Table 8 and Table 9. [2 marks]

Table 8

Present State		Next State		D flip-flop transition	
Q <sub>1</sub>	Q <sub>0</sub>	Q <sub>1+</sub>	Q <sub>0+</sub>	D <sub>1</sub>	D <sub>0</sub>
1	0	0	1		
0	1			1	0

Table 9

Present State		Next State		T flip-flop transition	
Q <sub>1</sub>	Q <sub>0</sub>	Q <sub>1+</sub>	Q <sub>0+</sub>	T <sub>1</sub>	T <sub>0</sub>
1	1	0	1		
		0	0	0	1



(c) A two bit sequential circuit counter has an input  $X$ . The characteristic of the counter operates according to the transition state value in Table 10. Answer the following questions based on Table 10.

Table 10

Input $X$	Present State		Next State		JK FF Transition			
	$Q_1$	$Q_0$	$Q_{1+}$	$Q_{0+}$	$J_1$	$K_1$	$J_0$	$K_0$
0	0	0	0	0				
0	0	1	0	1				
0	1	0	1	0				
0	1	1	1	1				
1	0	0	0	1				
1	0	1	1	0				
1	1	0	1	1				
1	1	1	0	0				

i. Draw a complete state diagram. [3 marks]

ii. Complete all the values in Table 10 if JK flip-flops are used in the synchronous counter design. [8 marks]

iii. Using K-map, find the optimized Boolean equations for all the input JK flip-flops. [4 marks]

iv. Draw the final circuit of the counter design. [3 marks]

**(d)** Analyze the cascaded counter circuit in Figure 9. If the input frequency of the counter is 1 KHz, calculate the output frequency of MOD 2 and MOD 10 (i.e.  $f_0$  and  $f_2$ ). [2 marks]

 


Figure 9

(e) Analyze the synchronous counter circuit in Figure 10.

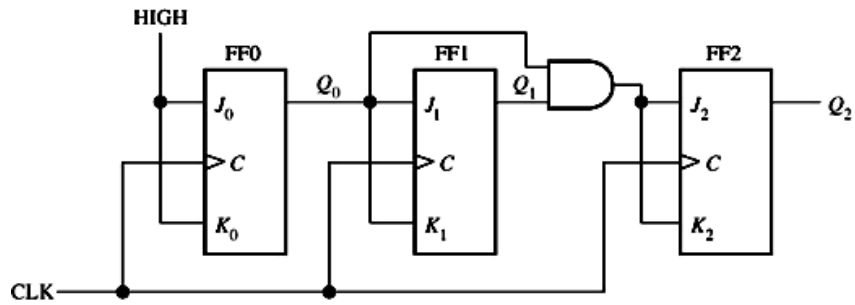


Figure 10

i. Write Boolean equations for all the inputs of JK flip-flops. [1.5 marks]

ii. Based on the Boolean equations in (i), write the Boolean equations for the next state value for  $Q_0$ ,  $Q_1$  and  $Q_2$ . [3 marks]

iii. Calculate the next state for the current state value given in Table 11. Use your answers in question (ii). [1.5 marks]

Table 11

Current State	Next State
$Q_2 Q_1 Q_0 = 100_2$	

**QUESTION 5 (15 Marks)**

(a) Figure 11 shows a shift register using type JK storage element. Answer the following questions.

 


Figure 11

- i. What is the type of the shift register? [1 mark]
  
- ii. Draw the flip-flops output in Figure 12 for the specified data input and clock waveforms. Assume that the register is initially cleared (all 0s). [4 marks]

 


Figure 12

(b) Figure 13 shows a shift register counter. Answer the following questions.

 


Figure 13

- i. Complete the truth table in Table 12 for the operation of the shift register counter. Determine how many states the counter has? [5 marks]

Table 12

Clock	Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
↑	1	0	1	1
↑				
↑				
↑				
↑				

Number of state: .....

- ii. Modify the circuit in Figure 13, so that it becomes a 3-bit *Johnson counter*. Draw the complete circuit. [3 marks]

- iii. What is the MOD of the new modified counter in (ii)? [2 marks]