




**UTM**  
UNIVERSITI TEKNOLOGI MALAYSIA

**FINAL EXAMINATION  
SEMESTER I 2010/2011**

**SUBJECT CODE** : SCR1013  
**SUBJECT NAME** : DIGITAL LOGIC  
**YEAR/COURSE** : SCR / SCV / SCI / SCJ / SCD  
**DURATION** : 2 HOURS 30 MINUTES  
**DATE** :  
**VENUE** :

---

**INSTRUCTIONS TO CANDIDATES:**

1. Please FILL in your particulars in the answer booklet.
2. The paper consists of two parts: PART A and PART B.
3. Part A has 20 questions. Answer ALL questions of PART A in the objective answer sheet on page 14
4. Part B has 3 questions. Question marked with  need to be answered on Part B Answer sheet on page 15 to 17. Answer ALL other questions of PART B in the given answer booklet.

|                        |   |
|------------------------|---|
| <b>Name</b>            |   |
| <b>Matric No.</b>      |   |
| <b>Year/Course</b>     | * 1 2 3 4 / SCR / SCV / SCI / SCJ                     |
| <b>Section</b>         | * 01 02 03 04 05 06                                   |
| <b>Lecturer's Name</b> | * EN. MOHD FO'AD / EN. ABD. BAHRIM / EN. ISMAIL FAUZI |

*This booklet consist of 17 pages including this page*

**PARTB: SUBJECTIVE QUESTIONS**

*Answer all questions on the answer book provided.*

1. a) Two binary numbers A and B are given as,  $A_2 A_1 A_0 = 101$  and  $B_2 B_1 B_0 = 110$ .

a) Draw the block diagram of parallel adder to solve the equation  $X = A + B$ .

[ 4M ]

b) Label the diagram with appropriate value of inputs and output. Indicate the MSB and LSB.


[ 3M ]

c) What is the value of X in binary?

[ 1M ]

*Note: MSB = Most Significant Bit, LSB = Least Significant Bit.*

 b) 74LS151 IC is a 1 of 8 Multiplexer and its symbol is shown in the figure below.



i) What is the purpose of a multiplexer?

[ 1M ]

ii) Pins of the IC are categorised into 4 categories such as Enable Pin, Data Selector Pin, Input Data Pin and Output Data Pin.

Complete the table below by write-in all of 13 pin labels from figure above into its correct category.

[ 3M ]

| Pin Category      | Label           |
|-------------------|-----------------|
| Enable Pin        | $\overline{EN}$ |
| Output Data Pin   |                 |
| Data Selector Pin |                 |
| Input Data Pin    |                 |


iii) Complete the table below.

[ 5M ]


| $\overline{EN}$ | $D_0$ | $D_1$ | $D_2$ | $D_3$ | $D_4$ | $D_5$ | $D_6$ | $D_7$ | $S_2$ | $S_1$ | $S_0$ | $Y$ | $\overline{Y}$ |
|-----------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-----|----------------|
| 0               | 0     | 1     | 0     | 1     | 1     | 1     | 1     | 1     | 0     | 1     | 1     |     |                |
| 0               | 1     | 0     | 1     | 0     | 1     | 1     | 0     | 0     | 1     | 1     | 0     |     |                |
| 0               | 0     | 1     | 1     | 1     | 0     | 1     | 0     | 1     | 1     | 1     | 1     |     |                |
| 1               | 0     | 1     | 1     | 0     | 0     | 1     | 1     | 0     | 0     | 1     | 0     |     |                |
| 0               | 0     | 1     | 1     | 0     | 1     | 1     | 0     | 1     | 1     | 0     | 1     |     |                |

Note: Hi-Z = neither 0 nor 1 logic

 2. a) You are given SR gated latch and SR flip-flop.  $Q_X$  is the output of SR gated latch and  $Q_Y$  is the output of SR flip-flop. If the clock is negative edge triggered, draw  $Q_X$  and  $Q_Y$ . The initial value of  $Q_X$  and  $Q_Y$  are LOW. [ 6M ]



b) You are given IC 74LS76 as follows:

 

i) List the Asynchronous and Synchronous inputs. Arrange the priority execution based on the listed input. [ 3M ]

ii) Using single JK flip-flop, draw the circuit for the following. [ 6M ]

i. D flip-flop


ii. T flip-flop

iii. Complete the following table to show the operation of a D and T flip-flop


| CLK | $\overline{PRE}$ | $\overline{CLR}$ | D | T | $Q_D$ | $Q_T$ |
|-----|------------------|------------------|---|---|-------|-------|
| ↑   | 0                | 1                | 0 | 0 |       |       |
| ↑   | 1                | 1                | 0 | 1 |       |       |
| ↑   | 1                | 0                | 1 | 0 |       |       |
| ↑   | 1                | 1                | 1 | 1 |       |       |



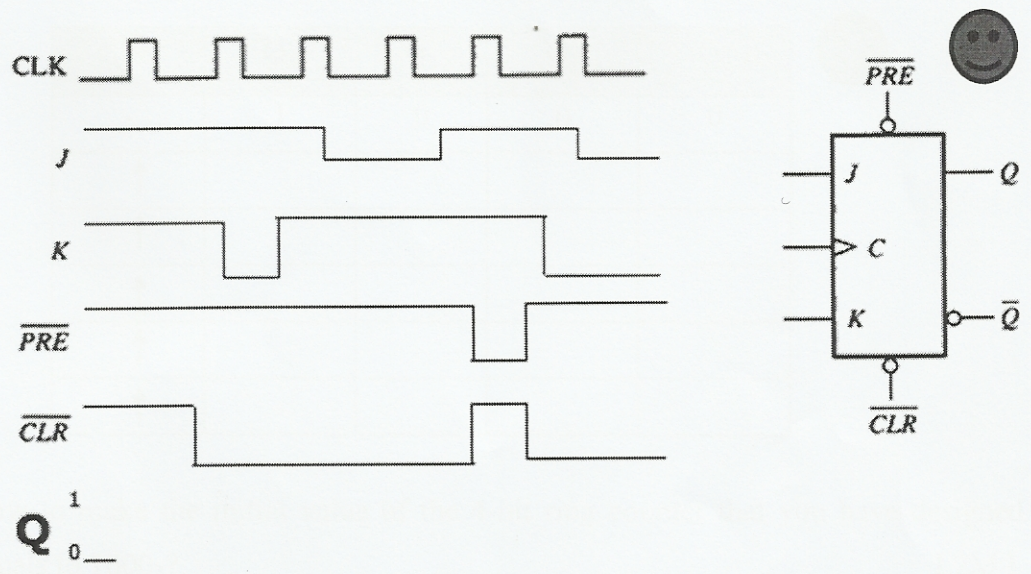iii) Determine the **Q waveform** relative to the clock if the signals shown in the following figure are applied to the inputs of the J-K flip-flop. Assume that Q is initially LOW. [ 5M ]



 3. Questions referring to a shift register below.



- a) What is the name of the shift register? [ 1M ]
- b) If a nibble data 1101 is to be loaded and shifted by the circuit, complete the following table. Initial value of  $Q_3 = 0$ . [4M]

| $SHIFT / \overline{LOAD}$ | CLK | $D_0$ | $D_1$ | $D_2$ | $D_3$ | $Q_3$ |
|---------------------------|-----|-------|-------|-------|-------|-------|
| 0                         | -   |       |       |       |       |       |
| 1                         | ↑   |       |       |       |       |       |
| 1                         | ↑   |       |       |       |       |       |
| 1                         | ↑   |       |       |       |       |       |


4. a) Design a 4-bit ring counter using JK flip-flop. [ 4M ]  
 b) Show the output of the 4-bit ring counter that you have designed in the following table. [ 5M ]

| CLK | Q <sub>3</sub> | Q <sub>2</sub> | Q <sub>1</sub> | Q <sub>0</sub> |
|-----|----------------|----------------|----------------|----------------|
| -   | 1              | 0              | 0              | 0              |
| ↑   |                |                |                |                |
| ↑   |                |                |                |                |
| ↑   |                |                |                |                |
| ↑   |                |                |                |                |
| ↑   |                |                |                |                |



- c) How to make the initial value of the 4-bit ring counter that you have designed equals to 1000<sub>2</sub>? [ 2M ]  
 d) Draw the state diagram of the designed ring counter and determine its MOD. [ 4M ]

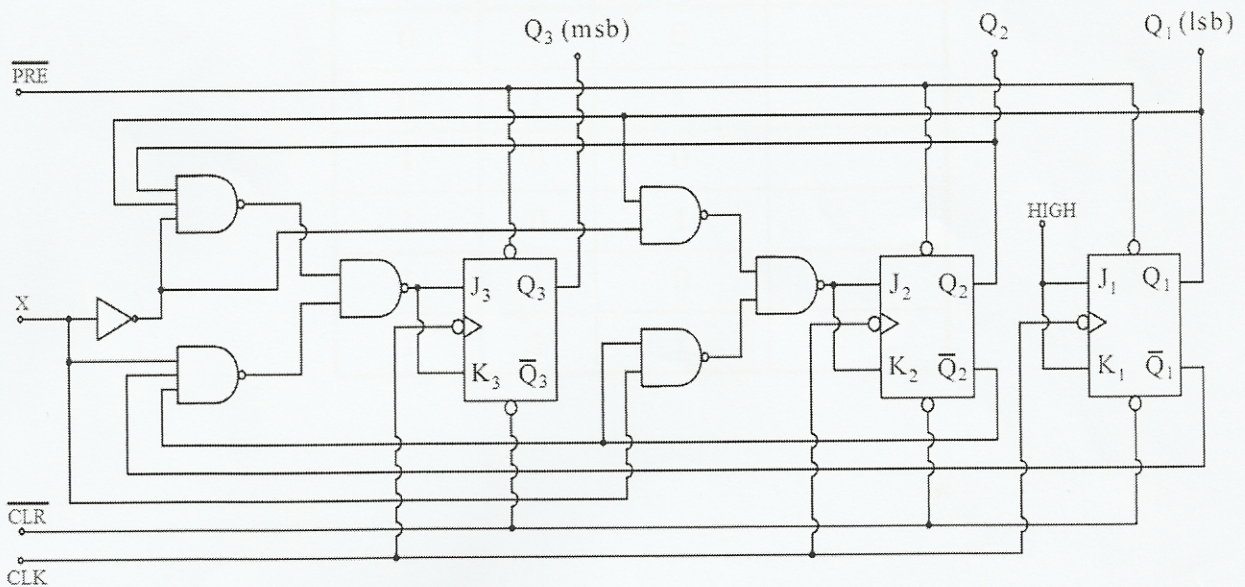5. Questions referring to a circuit in figure below.



- a) How to make the initial value of the output  $Q_3Q_2Q_1$  equals to 0? [ 1M ]
- b) If the propagation delay of a NAND gate is 20ns, an inverter 10ns and JK flip-flop 40ns, determine the maximum frequency of the clock to guarantee the proper counting sequence. [ 3M ]
- c) Draw the state diagram
- i) for **three states only** starting from state  $000_2$  when  $X = 0$ . [ 6M ]
  - ii) for **three states only** starting from state  $101_2$  when  $X = 1$ . [ 6M ]


6 a) Comparing a synchronous counter to an asynchronous counter

- i) What is the difference between a synchronous counter and an asynchronous counter? [ 1M ]
  - ii) Give one advantage of a synchronous counter. [ 1M ]
- b) i) Fill in the Next State column in the table below [ 2M ]
- ii) Use the completed table, produce an Excitation table for JK flip-flop. [ 3M ]

| FF State |   | Present State | Next State |
|----------|---|---------------|------------|
| J        | K | $Q_n$         | $Q_{n+1}$  |
| 0        | 0 | 0             |            |
| 0        | 0 | 1             |            |
| 0        | 1 | 0             |            |
| 0        | 1 | 1             |            |
| 1        | 0 | 0             |            |
| 1        | 0 | 1             |            |
| 1        | 1 | 0             |            |
| 1        | 1 | 1             |            |



 - c) i) Design a synchronous counter using JK flip-flop that will have a state diagram as in figure below. *Show all your design steps.* [ 10M ]



- ii) Add a switch to your designed circuit from (5.c.i) and label it as RESET. Show the connection of the switch so that the counter will move to state  $110_2$  when RESET switch is pressed. [ 3M ]