

**K-MAP TUTORIAL**SOP

	<b>cd</b>				
<b>ab</b>		<b>00</b>	<b>01</b>	<b>11</b>	<b>10</b>
<b>00</b>		0	1	0	0
<b>01</b>		0	1	0	0
<b>11</b>		1	1	1	1
<b>10</b>		0	1	0	0

**X =**  
 $\Sigma_{abcd}()$   
 $\Pi_{abcd}()$   
CIRCUIT

(1)

	<b>cd</b>				
<b>ab</b>		<b>00</b>	<b>01</b>	<b>11</b>	<b>10</b>
<b>00</b>		0	1	1	0
<b>01</b>		1	1	1	0
<b>11</b>		1	X	X	X
<b>10</b>		0	1	1	0

**X =**  
 $\Sigma_{abcd}()$   
 $\Pi_{abcd}()$   
CIRCUIT

(2)

	<b>cd</b>				
<b>ab</b>		<b>00</b>	<b>01</b>	<b>11</b>	<b>10</b>
<b>00</b>		1	1	0	1
<b>01</b>		0	0	0	0
<b>11</b>		1	1	1	1
<b>10</b>		1	1	0	1

**X =**  
 $\Sigma_{abcd}()$   
 $\Pi_{abcd}()$

(3)

POS

<b>ab</b> \ <b>cd</b>	<b>00</b>	<b>01</b>	<b>11</b>	<b>10</b>
<b>00</b>	0	1	1	0
<b>01</b>	1	1	0	0
<b>11</b>	X	X	0	0
<b>10</b>	0	0	X	X

 $X =$  $\Sigma_{abcd}(1, 3, 4, 5)$  $\Pi_{abcd}$ 

CIRCUIT

(4)

<b>ab</b> \ <b>cd</b>	<b>00</b>	<b>01</b>	<b>11</b>	<b>10</b>
<b>00</b>	0	1	0	X
<b>01</b>	0	1	X	X
<b>11</b>	1	1	1	1
<b>10</b>	0	1	0	0

 $X =$  $\Sigma_{abcd}()$  $\Pi_{abcd}()$ 

CIRCUIT

(5)

<b>ab</b> \ <b>cd</b>	<b>00</b>	<b>01</b>	<b>11</b>	<b>10</b>
<b>00</b>	0	0	0	1
<b>01</b>	0	0	1	1
<b>11</b>	1	1	1	1
<b>10</b>	0	1	0	0

 $X =$  $\Sigma_{abcd}()$  $\Pi_{abcd}()$ 

(6)

	<b>BC</b>				<b>X =</b>
<b>A</b>		<b>00</b>	<b>01</b>	<b>11</b>	<b>10</b>
<b>0</b>		0	0	0	1
<b>1</b>		0	0	1	1

$\Sigma_{abc}()$   
 $\Pi_{abc}()$

(7) SOP

	<b>BC</b>				<b>X =</b>
<b>A</b>		<b>00</b>	<b>01</b>	<b>11</b>	<b>10</b>
<b>0</b>		1	0	0	1
<b>1</b>		1	0	1	1

$\Sigma_{abc}()$   
 $\Pi_{abc}()$

(8) SOP

	<b>BC</b>				<b>X =</b>
<b>A</b>		<b>00</b>	<b>01</b>	<b>11</b>	<b>10</b>
<b>0</b>		0	1	0	1
<b>1</b>		0	X	X	1

$\Sigma_{abc}()$   
 $\Pi_{abc}()$

(9) POS

	<b>BC</b>				<b>X =</b>
<b>A</b>		<b>00</b>	<b>01</b>	<b>11</b>	<b>10</b>
<b>0</b>		X	X	X	1
<b>1</b>		0	0	1	1

$\Sigma_{abc}()$   
 $\Pi_{abc}()$

(10) POS

	<b>c</b>		
<b>ab</b>		<b>0</b>	<b>1</b>
<b>00</b>		1	0
<b>01</b>		0	0
<b>11</b>		0	1
<b>10</b>		1	1

X =

 $\Sigma_{abc}()$  $\Pi_{abc}()$ 

(11) SOP

	<b>c</b>		
<b>ab</b>		<b>0</b>	<b>1</b>
<b>00</b>		0	0
<b>01</b>		0	X
<b>11</b>		0	1
<b>10</b>		0	0

X =

 $\Sigma_{abc}()$  $\Pi_{abc}()$ 

(12) SOP

	<b>c</b>		
<b>ab</b>		<b>0</b>	<b>1</b>
<b>00</b>		0	X
<b>01</b>		0	1
<b>11</b>		X	0
<b>10</b>		1	1

X =

 $\Sigma_{abc}()$  $\Pi_{abc}()$ 


(13) POS

INPUT			OUTPUT
A	B	C	X
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


(14)

INPUT				OUTPUT
A	B	C	D	X
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	X
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	X

(15)

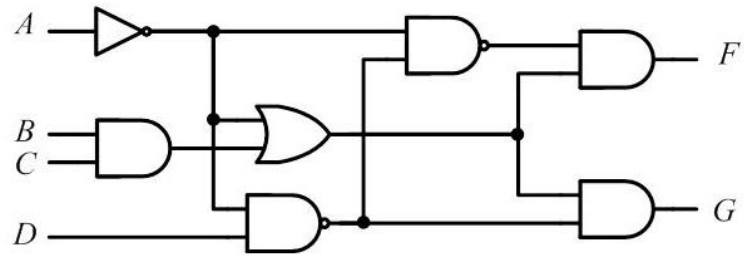

(16)

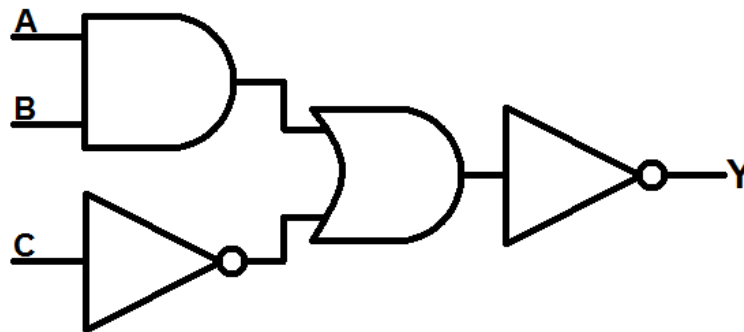

(17)

SIMPLIFIED EQUATION

F =

G =

Y =

STANDARD FORM

F =

G =

Y =

$\Sigma_{abcd}()$

$\Pi_{abcd}()$