



UNIVERSITI
TEKNOLOGI
MALAYSIA
www.utm.my

SCSR1013 DIGITAL LOGIC

MODULE 8b: COUNTERS (SYNC)

2016/2017-1

FACULTY OF COMPUTING



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

www.utm.my

Synchronous Counters:

Synchronous Counter Design

- **Step 1**
Describe a general sequential circuit in terms of its basic parts and its input and outputs.
- **Step 2**
Develop state diagram
- **Step 3**
Create next state table

- **Step 4**
Create flip-flop transition table.
- **Step 5**
Use K-maps to derive the logic equations.
- **Step 6**
Implement counter implementation



excitation table

FF Excitation Table

About creating Next State table

- JK Flip-Flop

FF State			
J	K		
0	0	0	0
0	1	0	0
1	0	0	1
1	1	0	1

NO CHANGE


RESET

SET

TOGGLE

↑
(Refer to JK FF truth table
in module 7: page 228)

Present State	Next State	FF State	
Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

 

(J-K ff state diagram)

Exercise 8b.1:

Construct the
excitation table
for **D flip-flop**

(using its state
diagram)

Exercise 8b.2:

Construct the
excitation table
for **T flip-flop**

(using its state
diagram)

Note:

These excitation tables will be used while filling in the flip-flop transition table in STEP 4 of designing synchronous counter.

Summary

Excitation tables of flip-flops:

NO CHANGE / RESET

SET / TOGGLE

RESET / TOGGLE

NO CHANGE / SET

Present State	Next State	FF State	
Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

J-K flip-flop

Q_{n+1}	D
0	0
1	1

D flip-flop

Q_{n+1}	T
Q_n	0
$\overline{Q_n}$	1


T flip-flop

Design 2-bit Synchronous Counter:

J-K Flip-flop

- **Step 1:**
To design 2-bit synchronous counter using JK FF. There is no input or output element in this design.

- **Step 2:** Draw state diagram

 

- **Step 3:** Create next state table

Present State		Next State	
Q_{1n}	Q_{0n}	Q_{1n+1}	Q_{0n+1}
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0

Note:

While filling in the flip-flop transition table, refer to the excitation table.

Present State	Next State	FF State	
Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

- Step 4:

Construct the flip-flop transition table

FF1

FF0

Present State		Next State		JK Transition			
Q_{1n}	Q_{0n}	Q_{1n+1}	Q_{0n+1}	J_1	K_1	J_0	K_0
0	0	0	1				
0	1	1	0				
1	0	1	1				
1	1	0	0				

Note:

While filling in the flip-flop transition table, refer to the excitation table.

Present State	Next State	FF State	
Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

- Step 4:

Construct the flip-flop transition table

FF1

FF0


Present State		Next State		JK Transition			
Q_{1n}	Q_{0n}	Q_{1n+1}	Q_{0n+1}	J_1	K_1	J_0	K_0
0	0	0	1	0	X	1	X
0	1	1	0	1	X	X	1
1	0	1	1	X	0	1	X
1	1	0	0	X	1	X	1

Present State		Next State		JK Transition			
Q_{1n}	Q_{0n}	Q_{1n+1}	Q_{0n+1}	J_1	K_1	J_0	K_0
0	0			0	X	1	X
0	1			1	X	X	1
1	0			X	0	1	X
1	1			X	1	X	1


• **Step 5:**

Use K-maps to derive the logic equations


(for present state only).

 


$$J_1 = Q_0$$

 

$$K_1 = Q_0$$




 


$$J_0 = 1$$

 

$$K_0 = 1$$

 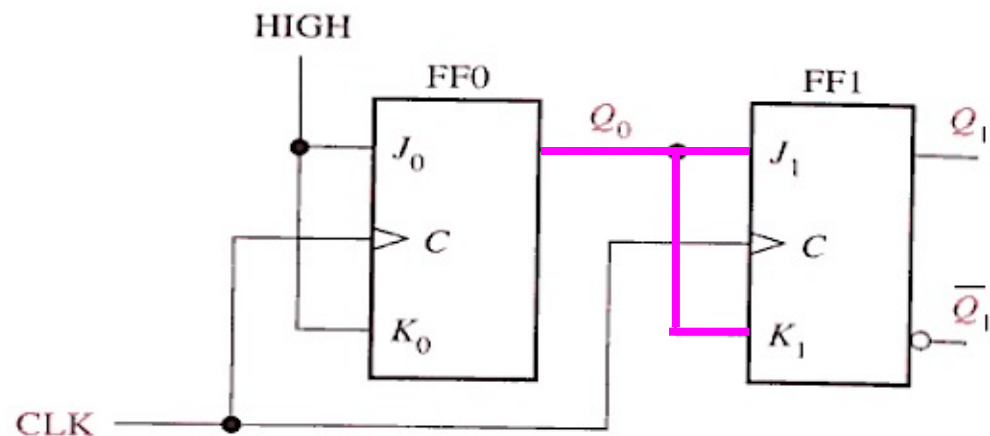  - **Step 6:** Implement counter implementation by drawing the logic symbol connection / counter circuit.



Q_1 toggle when $Q_0=1$

- Q_0 toggle at positive edge (CLK1, CLK2, CLK3, CLK4)
- Q_1 toggle when $Q_0=1$ at positive edge (CLK2, CLK4)



Extra

Exercise 8b.3: Design 2-bit synchronous counter that using D flip-flop.
Show all steps clearly.




Extra

Exercise 8b.4: Design 2-bit synchronous counter that using T flip-flop.
Show all steps clearly.

Design 3-bit Synchronous Counter:

J-K Flip-flop

- Step 2: State diagram

 

- Step 3: Next State table

Present State			Next State		
Q_2	Q_1	Q_0	Q_{2+}	Q_{1+}	Q_{0+}
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

Note:
While filling in the flip-flop transition table, refer to the excitation table.

Present State	Next State	FF State	
Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

- Step 4:

FF transition table

FF2

FF1

FF0

Present State			Next State			JK Transition Table					
Q_2	Q_1	Q_0	Q_{2+}	Q_{1+}	Q_{0+}	J_2	K_2	J_1	K_1	J_0	K_0
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	0	1	1	0	X	X	0	1	X
0	1	1	1	0	0	1	X	X	1	X	1
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	1	1	1	X	0	X	0	1	X
1	1	1	0	0	0	X	1	X	1	X	1

- Step 5:

Create K-map to determine the Boolean expression

Present State			Next State			JK Transition Table					
Q_2	Q_1	Q_0	Q_{2+}	Q_{1+}	Q_{0+}	J_2	K_2	J_1	K_1	J_0	K_0
0	0	0				0	X	0	X	1	X
0	0	1				0	X	1	X	X	1
0	1	0				0	X	X	0	1	X
0	1	1				1	X	X	1	X	1
1	0	0				X	0	0	X	1	X
1	0	1				X	0	1	X	X	1
1	1	0				X	0	X	0	1	X
1	1	1				X	1	X	1	X	1

		Q_1Q_0			
		00	01	11	10
Q_2	0	0	0	1	0
	1	X	X	X	X

$$J_2 = Q_1Q_0$$

		Q_1Q_0			
		00	01	11	10
Q_2	0	0	1	X	X
	1	0	1	X	X

$$J_1 =$$

		Q_1Q_0			
		00	01	11	10
Q_2	0	1	X	X	1
	1	1	X	X	1

$$J_0 =$$

		Q_1Q_0			
		00	01	11	10
Q_2	0				
	1				

$$K_2 =$$

		Q_1Q_0			
		00	01	11	10
Q_2	0				
	1				

$$K_1 =$$

		Q_1Q_0			
		00	01	11	10
Q_2	0				
	1				

$$K_0 =$$

- Step 5:

Create K-map to determine the Boolean expression

		Q_1Q_0			
		00	01	11	10
Q_2	0	0	0	1	0
	1	X	X	X	X

$$J_2 = Q_1Q_0$$

		Q_1Q_0			
		00	01	11	10
Q_2	0	0	1	X	X
	1	0	1	X	X

$$J_1 = Q_0$$

		Q_1Q_0			
		00	01	11	10
Q_2	0	1	X	X	1
	1	1	X	X	1

$$J_0 = 1$$

		Q_1Q_0			
		00	01	11	10
Q_2	0	X	X	X	X
	1	0	0	1	0

$$K_2 = Q_1Q_0$$

		Q_1Q_0			
		00	01	11	10
Q_2	0	X	X	1	0
	1	X	X	1	0



$$K_1 = Q_0$$

		Q_1Q_0			
		00	01	11	10
Q_2	0	X	1	1	X
	1	X	1	1	X

$$K_0 = 1$$


- Step 6:

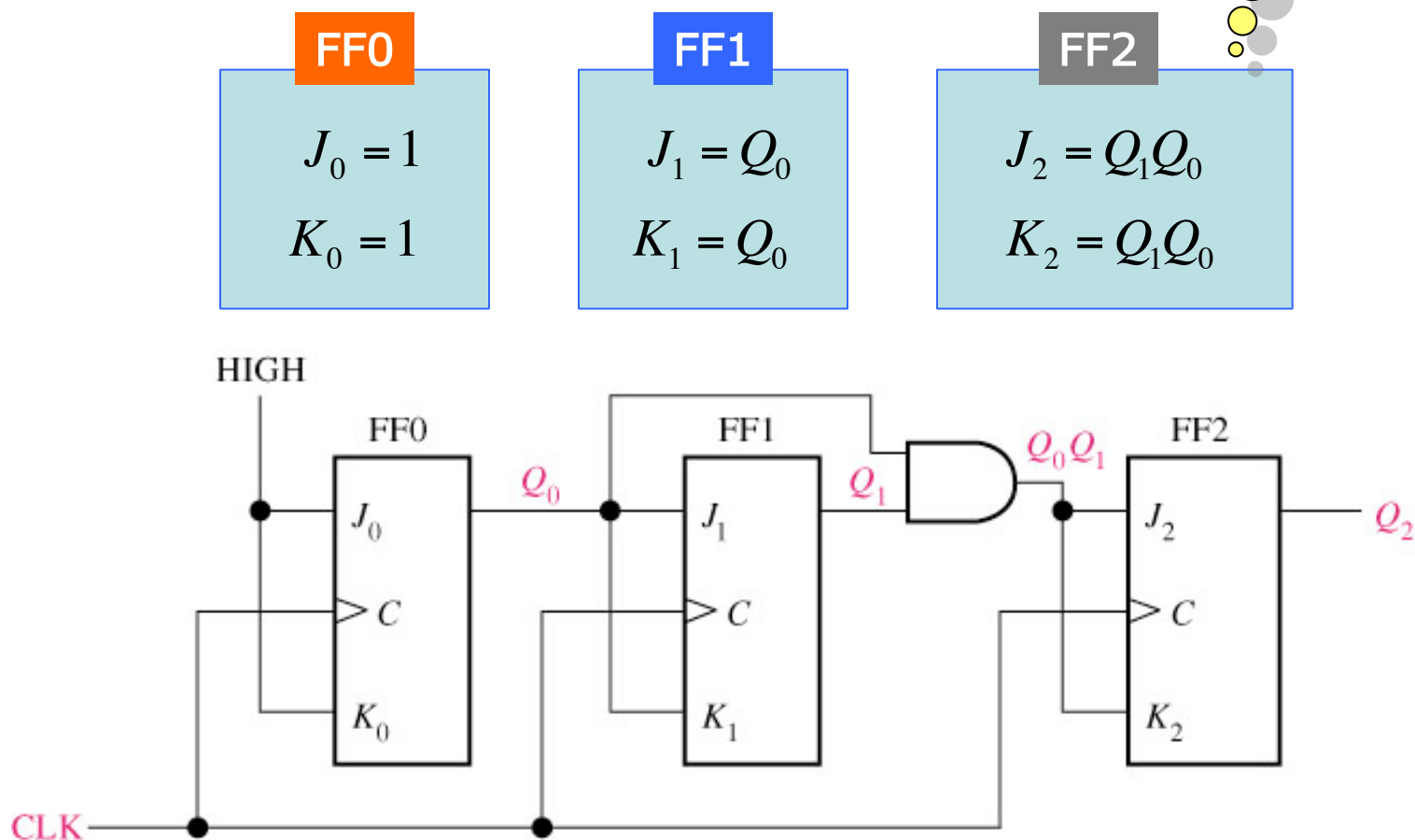 The implementation of 3-bit synchronous counter



Q_1 toggle when $Q_0=1$

Q_2 toggle when $Q_0=Q_1=1$

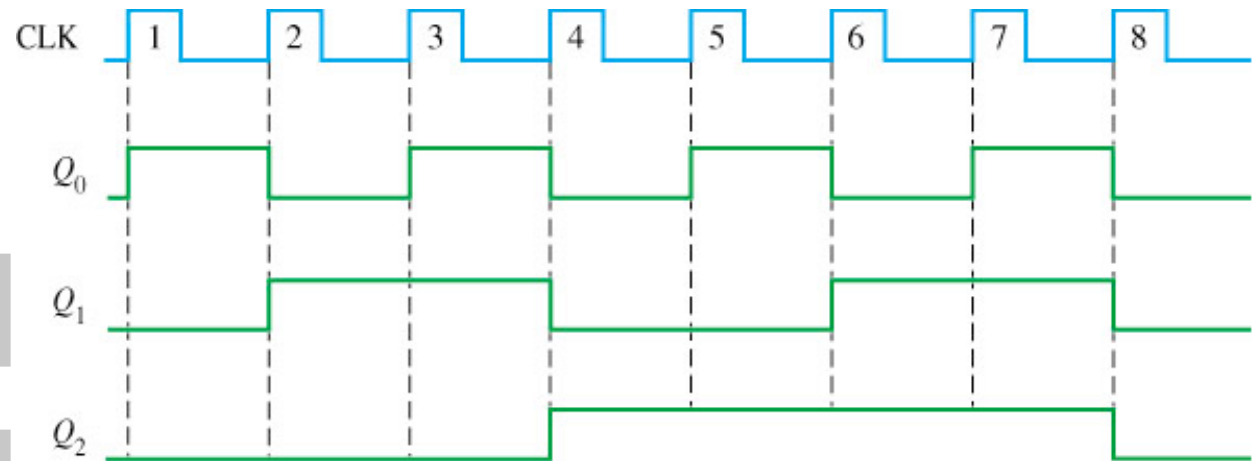

Note:

Actually we can design a synchronous counter by observing its timing diagram, based on the above timing diagram:

Q_0 always toggle. To achieve this, we have to operate FF0 in toggle mode by connecting J_0 and K_0 to HIGH
 Q_1 goes to opposite state every time Q_0 is HIGH (at the positive edge of clock CLK2, CLK4, CLK6 and CLK8).

From the observation we can achieve this by connecting Q_0 to the J_1 and K_1 inputs of FF1

Q_2 changes state when both Q_0 and Q_1 is HIGH. (at the positive edge of clock CLK4 and CLK8).

From the observation we can achieve this by 'AND'ing Q_0 and Q_1 to the J_2 and K_2 inputs of FF2



Extra

Exercise 8b.5: Design 3-bit synchronous counter that using T flip-flop.
Show all steps clearly.




Extra

Exercise 8b.6: Design 4-bit synchronous counter that using J-K flip-flop with negative edge triggered. Show all steps clearly.

Extra

 Exercise 8b.7: Design 3-bit synchronous counter that using J-K flip-flop based on the state diagram below. Show all steps clearly.





Extra

Exercise 8b.7b: Continue exercise 8b.7 by drawing the counter design.


2-bit Down Synchronous Counter:

D Flip-flop

- **Step 1:**

To design 2-bit down synchronous counter using D FF. There is no input or output element in this design.

- **Step 2:** Draw state diagram

 

- **Step 3:** Create next state table

Present State		Next State	
Q_1	Q_0	Q_{1+}	Q_{0+}
0	0	1	1
0	1	0	0
1	0	0	1
1	1	1	0

Q_{n+1}	D
0	0
1	1

- Step 4:

Draw flip-flop transition table. For D FF, D input is the same as the next state values.

Present State		Next State		D Transition	
Q_1	Q_0	Q_{1+}	Q_{0+}	D_1	D_0
0	0	1	1	1	1
0	1	0	0	0	0
1	0	0	1	0	1
1	1	1	0	1	0

- Step 5: K-Map.

		Q_0	
		0	1
Q_1	0	1	0
	1	1	0

$$D_0 = Q_0$$

		Q_0	
		0	1
Q_1	0	1	0
	1	0	1

$$D_1 = \bar{Q}_1 \bar{Q}_0 + Q_1 Q_0$$

$$D_1 = Q_0 \odot Q_1$$

Exercise 8b.8: Draw the circuit for of 2-bit down synchronous counter using D FF with $D1 = Q0 \odot Q1$ and $D0 = \overline{Q0}$

(Refer previous example: module page 262)


2-bit UP/DOWN Synchronous Counter: D Flip-flop

- Step 1:

To design 2-bit up down synchronous counter using D FF based on input X. When $X=0 \rightarrow$ Counter UP and $X=1 \rightarrow$ Counter DOWN

- Step 2:

Given the state diagram.

 

- Step 3: Create next state table

Input, X	Present State		Next State	
	$Q1_n$	$Q0_n$	$Q1_{n+1}$	$Q0_{n+1}$
0	0	0	0	1
0	0	1	1	0
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	0	1
1	1	1	1	0

Count up
Count down

- Step 4:

D FF transition table and determine Boolean expression.

Input, X	Present State		Next State		D FF	
	$Q1_n$	$Q0_n$	$Q1_{n+1}$	$Q0_{n+1}$	D1	D0
0	0	0	0	1	0	1
0	0	1	1	0	1	0
0	1	0	1	1	1	1
0	1	1	0	0	0	0
1	0	0	1	1	1	1
1	0	1	0	0	0	0
1	1	0	0	1	0	1
1	1	1	1	0	1	0

- Step 5:

Implement the circuit.

Q_1Q_0		00	01	11	10
X	0				
	1				

$D_1 =$

Q_1Q_0		00	01	11	10
X	0				
	1				

$D_0 =$

a checker board pattern

ab \ cd	00	01	11	10
00		1		1
01	1		1	
11		1		1
10	1		1	

$$X = A \oplus B \oplus C \oplus D$$

- Step 4:
D FF transition table.

Input, X	Present State		Next State		D FF	
	$Q1_n$	$Q0_n$	$Q1_{n+1}$	$Q0_{n+1}$	D1	D0
0	0	0	0	1	0	1
0	0	1	1	0	1	0
0	1	0	1	1	1	1
0	1	1	0	0	0	0
1	0	0	1	1	1	1
1	0	1	0	0	0	0
1	1	0	0	1	0	1
1	1	1	1	0	1	0

- Step 5:
Define logic equation.

Q_1Q_0	00	01	11	10
X				
0	0	1	0	1
1	1	0	1	0

$$D_1 = X \oplus Q_1 \oplus Q_0$$

Q_1Q_0	00	01	11	10
X				
0	1	0	0	1
1	1	0	0	1


$$D_0 = \overline{Q_0}$$

Exercise 8b.9: Draw the circuit for of 2-bit up-down synchronous counter using D FF with $D_1 = X \oplus Q_1 \oplus Q_0$ and $D_0 = \overline{Q_0}$


(Refer previous example: module page 261)

Counter for Arbitrary Sequences

 - Design the counter base on the given state diagram using T FF.



 - The counter is 3-bit counter
- The total number state = $2^3 = 8$
- Only 4 state (1, 2, 5, 7)
→ **Valid State**
- Other states (0, 3, 4, 6)
→ **Invalid State**
(never occur / **don't care**)




- State table and T FF transition table.

Present State			Next State			T FF		
$Q2_n$	$Q1_n$	$Q0_n$	$Q2_{n+1}$	$Q1_{n+1}$	$Q0_{n+1}$	T2	T1	T0
0	0	0	X	X	X	X	X	X
0	0	1	0	1	0	0	1	1
0	1	0						
0	1	1						
1	0	0						
1	0	1						
1	1	0						
1	1	1						

- Derive the Boolean expression and draw the circuit diagram.

**Fill in the next state and T FF transition column

Q_{n+1}	T
Q_n	0
$\overline{Q_n}$	1

 

- State table and T FF transition table.

FF2

FF1

FF0


Present State			Next State			T FF		
$Q2_n$	$Q1_n$	$Q0_n$	$Q2_{n+1}$	$Q1_{n+1}$	$Q0_{n+1}$	T2	T1	T0
0	0	0	X	X	X	X	X	X
0	0	1	0	1	0	0	1	1
0	1	0	1	0	1	1	1	1
0	1	1	X	X	X	X	X	X
1	0	0	X	X	X	X	X	X
1	0	1	1	1	1	0	1	0
1	1	0	X	X	X	X	X	X
1	1	1	0	0	1	1	1	0

- Derive the Boolean expression and draw the circuit diagram.

**Fill in the next state and T FF transition column


Exercise 8b.10: Derive the Boolean expression and draw the circuit diagram from the previous example.

 Exercise 8b.11: Design a counter with the irregular binary count sequence shown in the state diagram below using JK FF.



Synchronous BCD Decade Counter

 - Synchronous decade counter counts from 0 to 9 and then recycles to 0 again.
- 4 FF is required and the unused states ie 10 to 15 are taken as don't care terms.



**Fill in the
T0 column

Present State				Next State				T FF Transition			
Q3	Q2	Q1	Q0	Q3 ₊	Q2 ₊	Q1 ₊	Q0 ₊	T3	T2	T1	T0
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	1	0	0	1	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	1
0	0	1	1	0	1	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	1
0	1	0	1	0	1	1	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	1
0	1	1	1	1	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	1
1	0	0	1	0	0	0	0	1	0	0	1
1	0	1	0	X	X	X	X	X	X	X	X
1	0	1	1	X	X	X	X	X	X	X	X
1	1	0	0	X	X	X	X	X	X	X	X
1	1	0	1	X	X	X	X	X	X	X	X
1	1	1	0	X	X	X	X	X	X	X	X
1	1	1	1	X	X	X	X	X	X	X	X

**Fill in the K-maps

Self-Test:

Fill in the k-map
to simplify the
equations.

		Q1Q0			
		00	01	11	10
Q3Q2	00				
	01				
	11				
	10				

T3 =

		Q1Q0			
		00	01	11	10
Q3Q2	00				
	01				
	11				
	10				

T1 =


		Q1Q0			
		00	01	11	10
Q3Q2	00				
	01				
	11				
	10				

T2 =

		Q1Q0			
		00	01	11	10
Q3Q2	00				
	01				
	11				
	10				

T0 =

 Exercise 8b.12: Design a synchronous counter with the irregular binary count sequence shown in the state diagram below using J-K FF.





UTM
UNIVERSITI TEKNOLOGI MALAYSIA

www.utm.my

Cascaded Counter

Recap: Modulus


- The **modulus** → number of unique states through which the counter will sequence.
- Maximum possible number of states = 2^N , N is the number of flip-flops in the counter.
 - Example : Modulus 8 = 2^3 (Need 3 flip flops)
- Counter can be designed to have less number of states in their sequence → **Truncated sequence**.
 - One common modulus for counters → ten (Modulus 10).
 - It called BCD decade counters (as explained in previous slides).

Cascaded Counter

- Counter can be connected to achieve higher modulus operation.
- **Cascading** means that the last-stage output of one counter drives the input of the next counter.

 
Example:

- Two counters, modulus-4 and modulus-8 connected in cascade, can achieve count until 32 CLK (modulus-32). (i.e 4 x 8)



Cascaded Counter: Modulus-100 Counter

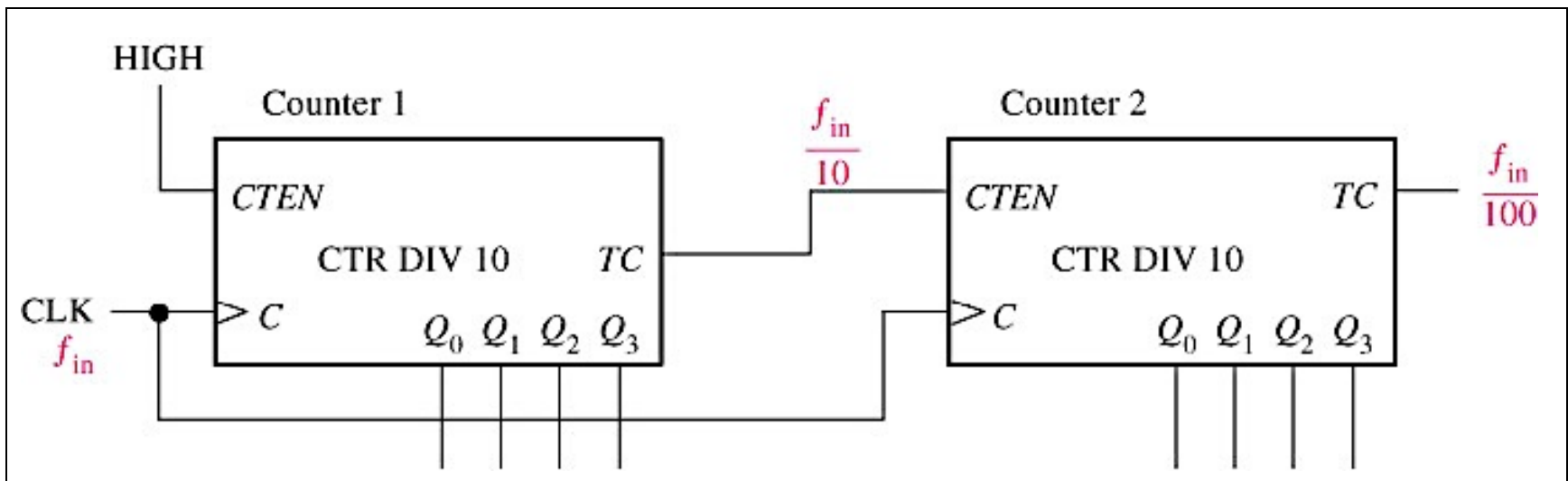
- Modulus-100 counter using 2 cascaded decade counters.
- This counter can be viewed as a **frequency divider**.
- It **divides the input clock frequency by 100**.



(Total MOD = 10 x 10 = 100)

Cascaded Counter: Modulus-1000 Counter

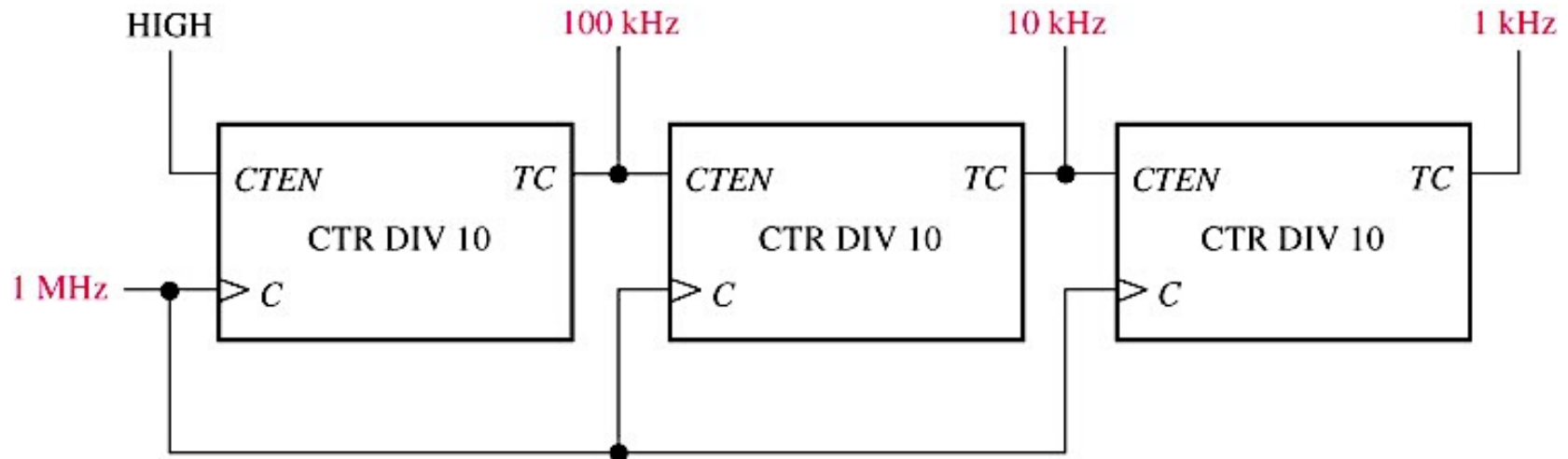- Three cascaded decade counters forming a divide-by-1000 frequency divider.



Basis clock frequency of 1 MHz and you wish to obtain 100kHz, 10Hz, and 1kHz, a series of cascaded decade counters can be used. If 1 MHz signal is divided by 10, the output is 100kHz. Then if the 100 kHz signal is divided by 10, the output is 10kHz. Further division by 10 gives the 1 kHz frequency.

$$\begin{aligned}\text{Total MOD} &= 10 \times 10 \times 10 \\ &= 1000\end{aligned}$$



Extra

Exercise 8b.13: Two type of counters, modulus-4 and modulus-8 need to be used to achieve count up to modulus- n (n CLK).


- a) How to cascade the counters to achieve count until 32 CLK (modulus-32)?
- b) What is the frequency produced by each counter given an initial frequency as 800MHz?



74HC163:


4-Bit Synchronous Binary Counter

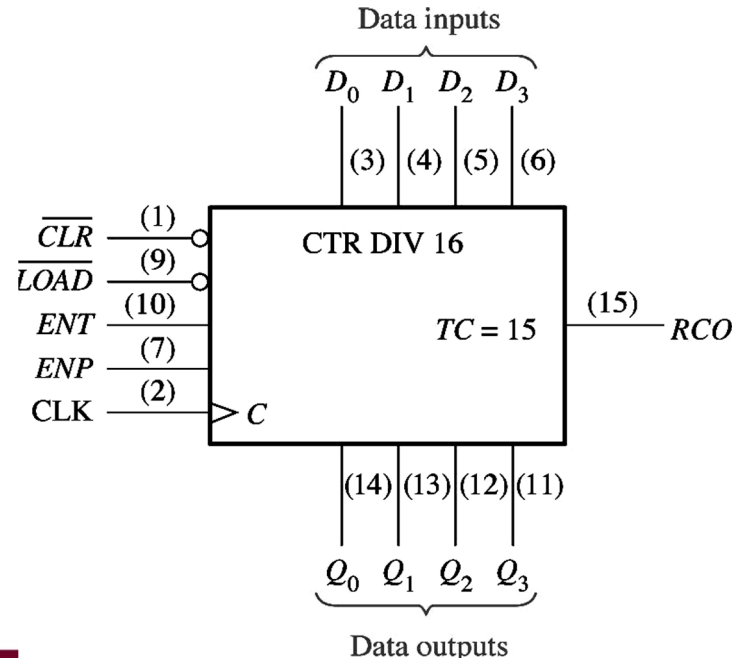- There is a dedicated counter IC, e.g 74HC163 which is a MOD 16 counter IC
- The starting counting sequence can be change by setting the initial value at $D_3D_2D_1D_0$
 - To load the initial value, LOAD' must be 0



Cascaded Counter with Truncated Sequence

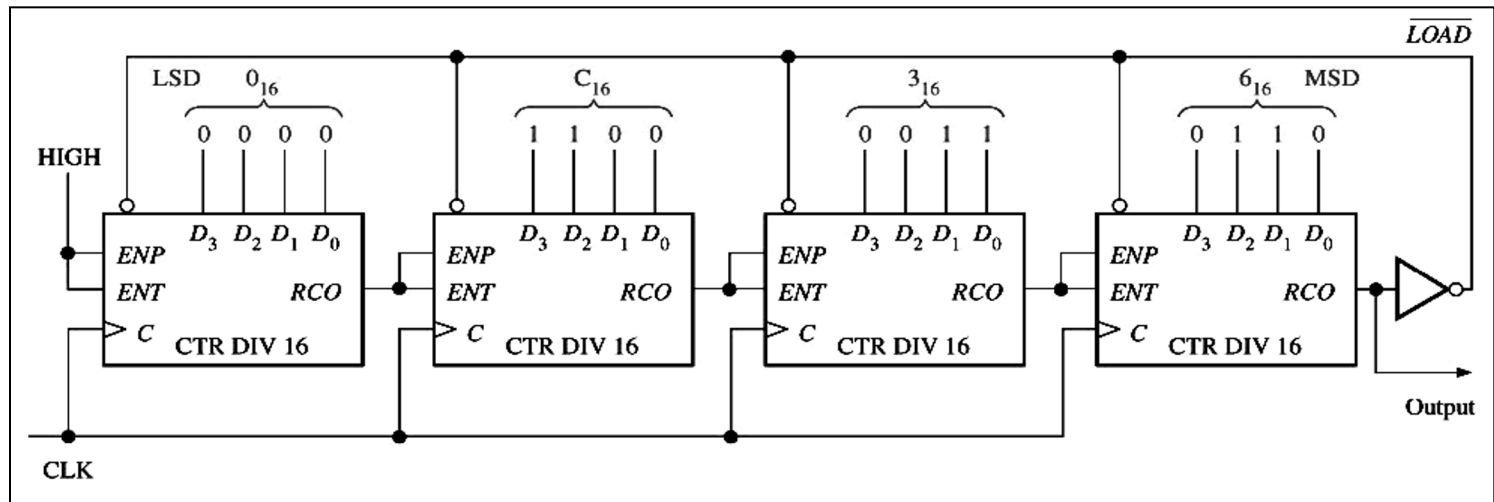- The cascaded counter below has $16^4 = 65,536$ states (full modulus for four cascaded CTR DIV 16).
- If we need a modulus 40,000 counter only. So, how?
 - Determine the initial value : $65536 - 40000 = 25536$ ($63C0_{16}$) make the counter starts at this count.
 - Therefore preset the cascaded counter to $63C0_{16}$ by setting the value of $D_3D_2D_1D_0$ as shown below.






UTM
UNIVERSITI TEKNOLOGI MALAYSIA

www.utm.my

Analysis of Sequential Circuits

Analysis of Sequential Circuits

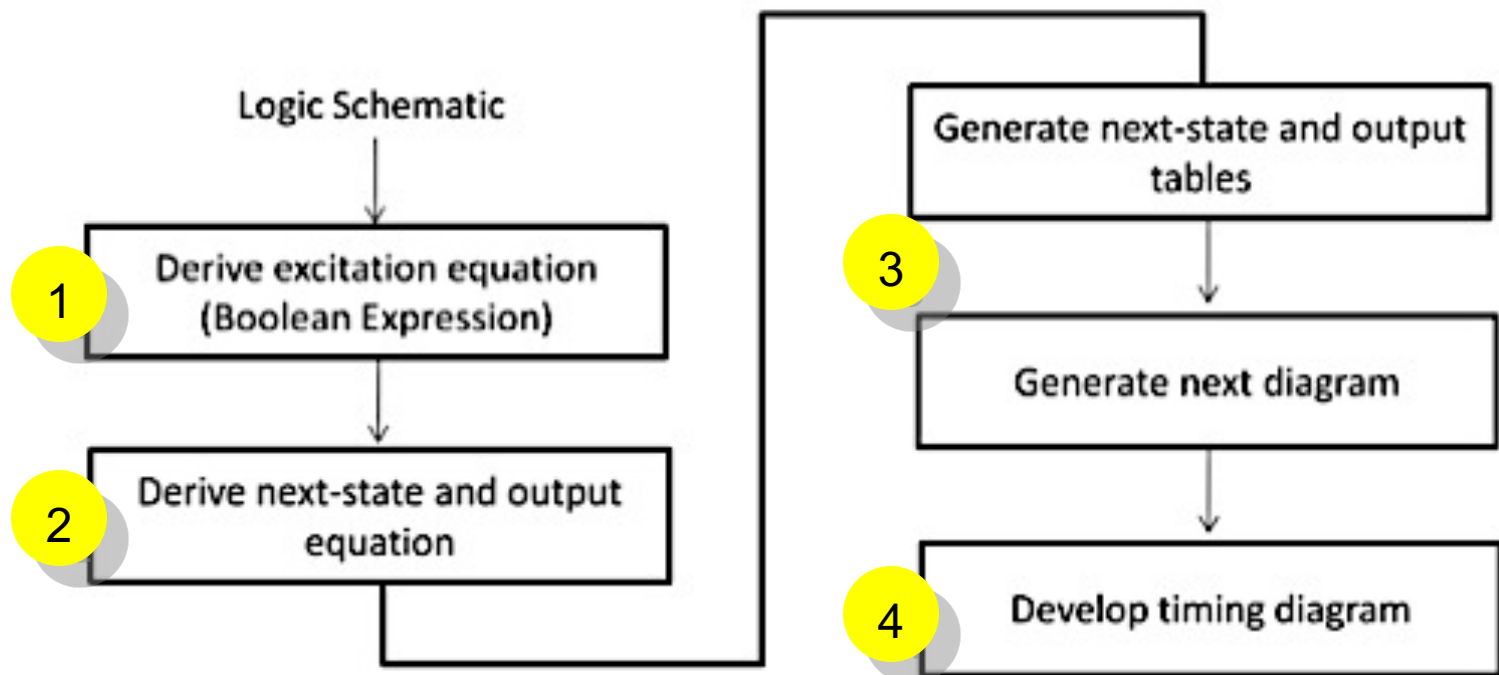- Behavior of a sequential circuit is determined from the **inputs**, the **outputs** and the **states** of its flip-flops.
- Both the **output and the next state** are a function of the **inputs and the present state**.



- **Step 1:**

Start with the logic schematic from which we can derive **excitation equations** for each flip-flop input.

- **Step 2:**

To obtain **next-state equations**, we insert the excitation equations into the characteristic equations. The **output equations** can be derived from the schematic:

Flip-flop characteristic equation:

$$\text{active HIGH SR : } Q_{\text{next}} = S + \bar{R}Q, \text{ SR} = 0$$

$$\text{JK : } Q_{\text{next}} = J\bar{Q} + \bar{K}Q$$

$$\text{D : } Q_{\text{next}} = D$$

$$\text{T : } Q_{\text{next}} = T\bar{Q} + \bar{T}Q$$

- **Step 3:**

Once we have our output and next-state equations, we can generate the **next-state and output tables** as well as **state diagrams**.


- **Step 4:**

When we reach this stage, we use either the table or the state diagram to develop a **timing diagram** which can be verified through simulation.

Analysis of Sequential Circuits:

 Example:

Derive the state table and state diagram for the sequential circuit below. Use Method 1



active HIGH SR : $Q_{next} = S + \overline{R}Q, SR = 0$
JK : $Q_{next} = J\overline{Q} + \overline{K}Q$
D : $Q_{next} = D$
T : $Q_{next} = T\overline{Q} + \overline{T}Q$

- **Step 1: Boolean expressions** for the inputs of each flip-flops in the schematic.

$$D_0 = Cnt \oplus Q_0 = \overline{Cnt} \cdot Q_0 + Cnt \cdot \overline{Q_0}$$

$$D_1 = \overline{Cnt} \cdot Q_1 + Cnt \cdot \overline{Q_1} \cdot Q_0 + Cnt \cdot Q_1 \cdot Q_0$$

- **Step 2:** Derive the **next-state equations** by converting these excitation equations into flip-flop characteristic equations. In the case of D flip-flops, $Q_+ = D$.

$$Q_{0+} = D_0 = Cnt \oplus Q_0 = \overline{Cnt} \cdot Q_0 + Cnt \cdot \overline{Q_0}$$

$$Q_{1+} = D_1 = \overline{Cnt} \cdot Q_1 + Cnt \cdot \overline{Q_1} \cdot Q_0 + Cnt \cdot Q_1 \cdot Q_0$$


$$Q_{0+} = D_0 = Cnt \oplus Q_0 = \overline{Cnt} \cdot Q_0 + Cnt \cdot \overline{Q_0}$$

$$Q_{1+} = D_1 = \overline{Cnt} \cdot Q_1 + Cnt \cdot \overline{Q_1} \cdot Q_0 + Cnt \cdot Q_1 \cdot Q_0$$

- **Step 3:**
Construct the
next-state table.



Input, Cnt	Present State		Next State	
	Q_1	Q_0	$Q_{1+} = D_1$	$Q_{0+} = D_0$
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	1
1	0	0	0	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	0

 
- Step 4:
- The **state diagram** is generated directly from the next-state table.



Input, Cnt	Present State		Next State	
	Q_1	Q_0	$Q_{1+} = D_1$	$Q_{0+} = D_0$
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	1
1	0	0	0	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	0

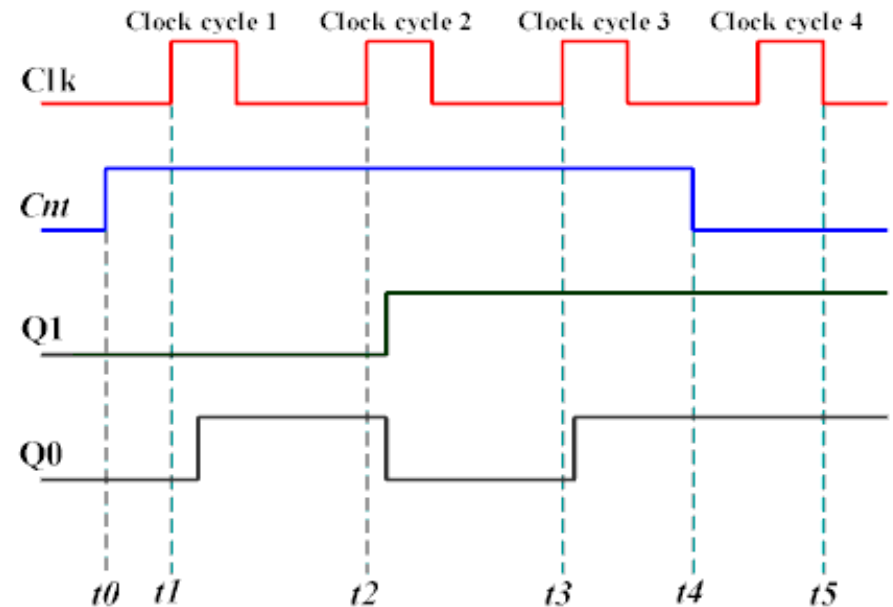 - **Step 4:**
- The **state diagram** is generated directly from the next-state table.
- Next get the **timing diagram**



 

We can conclude:

a) From the counter circuit:

- 2- bit counter because there are 2 FFs in the design.
- Synchronous counter because the FFs have a common clock.


b) From the counter state diagram:

- MOD 4 because has 4 state (i.e. $2^2=4$), not a truncated counter.
- Count Up counter when $Cnt=1$, and stay in the previous state when $Cnt=0$.

Analysis of Sequential Circuits:

Method 2: JK Circuit Analysis

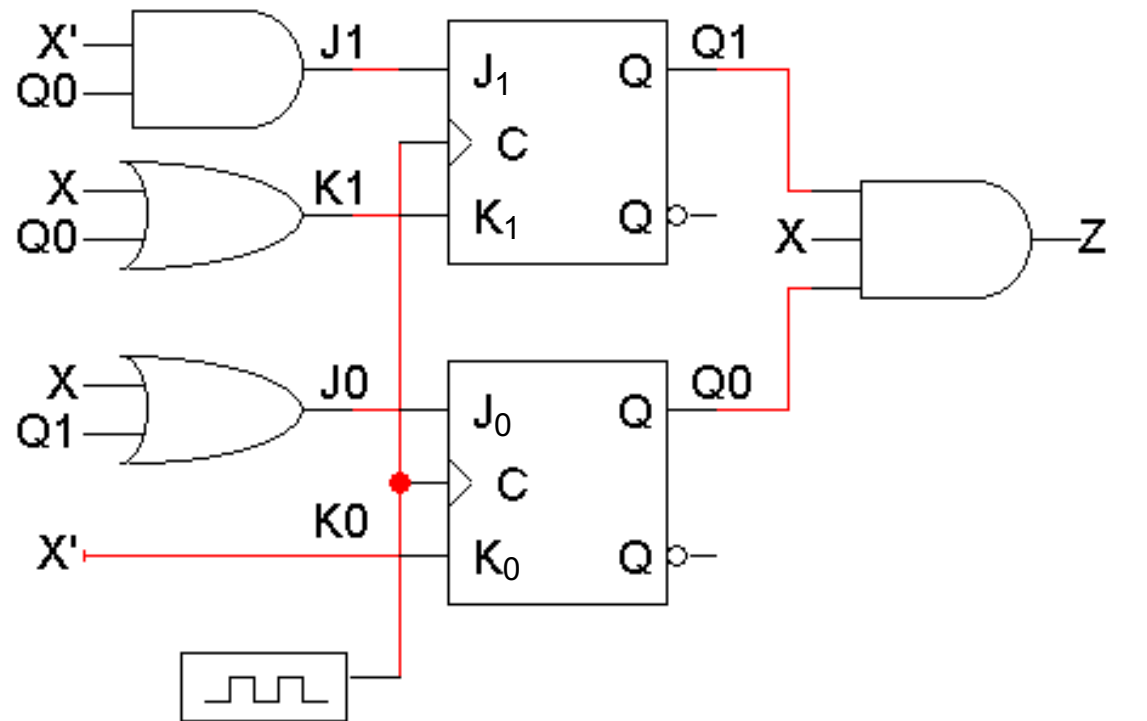- Sequential circuit with two JK flip-flops. There is one input, X, and one output, Z. Use Method 2



$$J_1 = X' Q_0$$

$$K_1 = X + Q_0$$

$$J_0 = X + Q_1$$

$$K_0 = X'$$

$$Z = Q_1 Q_0 X$$

$$J_1 = X' Q_0$$

$$K_1 = X + Q_0$$

$$J_0 = X + Q_1$$

$$K_0 = X'$$

$$Z = Q_1 Q_0 X$$

Input, X	Present State		Next State		JK FF Transition				Output, Z
	Q ₁	Q ₀	Q ₁₊	Q ₀₊	J ₁	K ₁	J ₀	K ₀	
0	0	0			0	0	0	1	0
0	0	1			1	1	0	1	0
0	1	0			0	0	1	1	0
0	1	1			1	1	1	1	0
1	0	0			0	1	1	0	0
1	0	1			0	1	1	0	0
1	1	0			0	1	1	0	0
1	1	1			0	1	1	0	1


**Fill in the JK FF transition column

Input, X	Present State		Next State		JK FF Transition				Output, Z
	Q ₁	Q ₀	Q ₁₊	Q ₀₊	J ₁	K ₁	J ₀	K ₀	
0	0	0	0	0	0	0	0	1	0
0	0	1	1	0	1	1	0	1	0
0	1	0	1	1	0	0	1	1	0
0	1	1	0	0	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0
1	0	1	0	1	0	1	1	0	0
1	1	0	0	1	0	1	1	0	0
1	1	1	0	1	0	1	1	0	1

**Fill in the next state column

Draw the state diagram for the example in previous slide.


Present state

 

Next state

Extra


Exercise 8b.15: Analysis for the following sequential circuit. Use Method 1.

 

Exercise 8b.15: Draw the state diagram for the example in previous slide.



Present state

 

Next state

Input, X	Present State		Next State		Output, Y
	A	B	A ₊	B ₊	
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	1	1	0
1	0	0	0	1	1
1	0	1	0	1	0
1	1	0	1	1	1
1	1	1	0	0	0

Extra

Exercise 8b.16:

Derive the state table and state diagram for the sequential circuit below. Use Method 2

