



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

DIGITAL LOGIC

SEMESTER I 2020/2021

SECR1013-05

LAB 1

NAME OF STUDENTS	MATRIC NO.
ARIF SUFFIAN BIN MUHAMAD ZAILI	A20EC0184
MOHAMAD HAZIQ ZIKRY BIN MOHAMMAD RAZAK	A20EC0079

LECTURER: RASHIDAH BINTI KADIR

SUBMISSION DATE: 26TH NOVEMBER 2020

E. Laboratory Work

Part 1

1. Construct Circuit 1 on the breadboard. Connect all inputs (A, B) to a switches and output F to LEDs.

Truth Table 5



Circuit 1

Input		Output
A	B	F
1	1	1
1	0	0
0	1	0
0	0	0

2. Test Circuit 1 and fill in Truth Table 5 for the circuit response to all possible input combinations. The Truth Table 5 should match the Truth Table 1 prepared in the Preliminary Work.



Fully Completed ☐


Partially Completed ☐

Checked by: _____

Part 2

3. Construct Circuit 2 on the breadboard. Connect all inputs (A, B) to a switches and output C and F to LEDs.

Truth Table 6

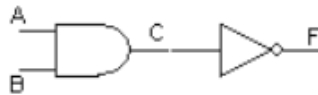

Circuit 2

A	B	C	F
1	1	1	0
1	0	0	1
0	1	0	1
0	0	0	1

4. Test Circuit 2; fill in Truth Table 6, for the circuit response to all possible input combinations.
5. Compare Truth Table 6 to Truth Table 2. What conclusion can you make?

I can conclude that the NOT gate acts as an inverter.




Fully Completed ☐

Partially Completed ☐

Checked by: _____

Part 3

6. Construct circuit 3 on the breadboard. Connect all inputs (A, B) to a switches and output C, D and F to LEDs.

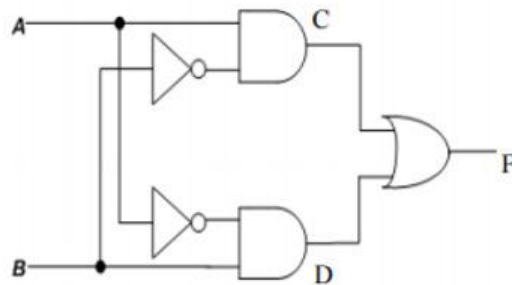

Circuit 3

Truth Table 7

A	B	C	D	F
1	1	0	0	0
0	1	0	1	1
1	0	1	0	1
0	0	0	0	0

7. Test Circuit 3; fill in Truth Table 7 for the circuit outputs (C, D, and F) for all possible input combinations.
8. What single gate does Circuit 3 represent?

XOR GATE