

D. Lab Activities

Part 1

Simulating logic circuit, construct truth table and timing diagram with Deeds.

Given Boolean expression as follow:

$$Y = AB + BC + AC$$

1. Convert the non-standard Boolean expression into standard form.

$$Y = AB + BC + AC$$

$$T_3 = AC(B + \bar{B})$$

$$= ABC + \bar{A}BC$$

$$T_1 = AB(C \text{ missing})$$

$$T_2 = BC(A \text{ missing})$$

$$T_3 = AC(B \text{ missing})$$

$$Y = ABC + \bar{A}BC + ABC + \bar{A}BC + ABC + \bar{A}BC$$

$$= ABC + \bar{A}BC + \bar{A}BC + \bar{A}BC \text{ (standard form)}$$

$$T_1 = AB(C + \bar{C})$$

$$= ABC + \bar{A}BC$$

$$T_2 = BC(A + \bar{A})$$


$$= ABC + \bar{A}BC$$

2. Based on standard form expression, complete the following truth table.

INPUT			OUTPUT
A	B	C	Y
1	1	1	1
1	1	0	1
1	0	1	1
1	0	0	0
0	1	1	1
0	1	0	0
0	0	1	0
0	0	0	0


3. Using Deeds Simulator, draw the following circuits:

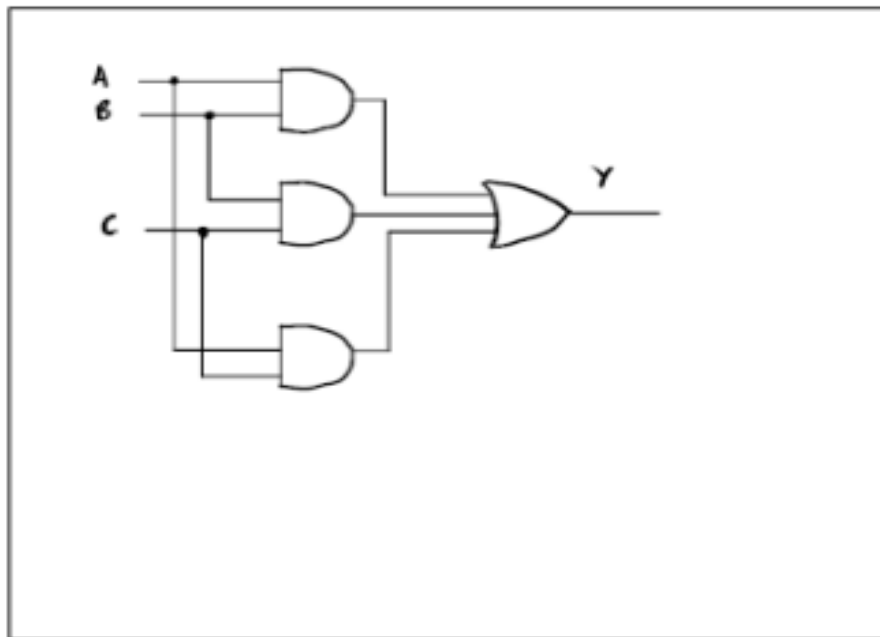a) Circuit (i) for non-standard form (based on the given expression).



Circuit (i)

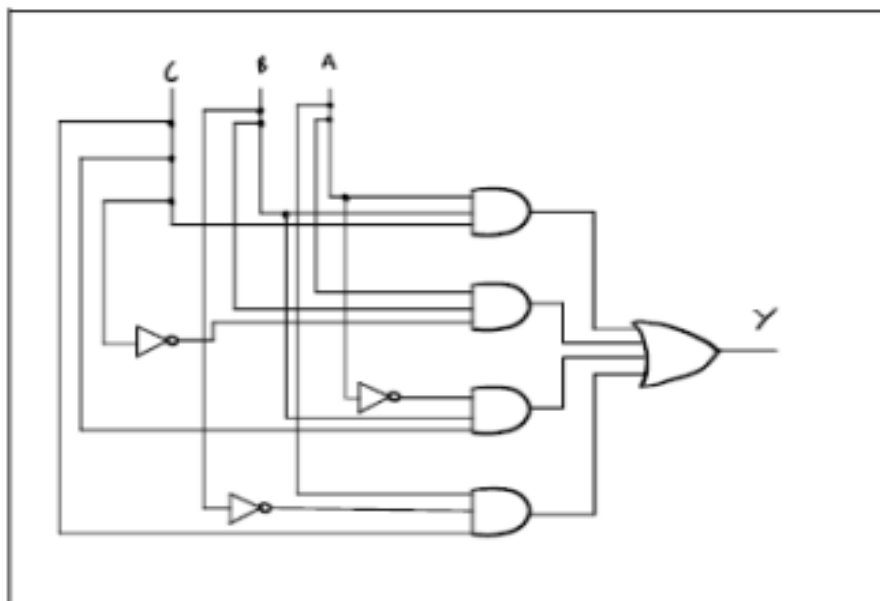b) Circuit (ii) for standard form (from your answer in question (1)).



Circuit (ii)

4. Simulate these two circuits in step (3) and complete their truth table.

Compare the simulation result for these two truth tables. What is your conclusion?

Circuit (i)

INPUT			OUTPUT
A	B	C	Y
1	1	1	1
1	1	0	1
1	0	1	1
1	0	0	0
0	1	1	1
0	1	0	0
0	0	1	0
0	0	0	0

Circuit (ii)

INPUT			OUTPUT
A	B	C	Y
1	1	1	1
1	1	0	1
1	0	1	1
1	0	0	0
0	1	1	1
0	1	0	0
0	0	1	0
0	0	0	0

Conclusion:

the outputs for both circuits are the same because both expressions are same and the difference is expression in circuit (i) is simpler compared to circuit (ii).

5. Simulate output of circuit (ii) with Timing Diagram. Illustrate some examples of different inputs and output.



Experimental Steps

1. Complete Truth Table 1 for Digital Fault Diagnose Circuit. Use variables A, B, C and D as inputs; E1, E2, E3 and E4 as outputs.

Truth Table 1

INPUTS				OUTPUTS			
A	B	C	D	E1	E2	E3	E4
0	0	0	0	0	1	0	0
0	0	0	1	1	0	0	0
0	0	1	0	0	1	0	0
0	0	1	1	x	x	x	x
0	1	0	0	0	1	0	0
0	1	0	1	x	x	x	x
0	1	1	0	x	x	x	x
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	0	1	x	x	x	x
1	0	1	0	x	x	x	x
1	0	1	1	0	0	1	0
1	1	0	0	x	x	x	x
1	1	0	1	0	0	1	0
1	1	1	0	0	0	1	0
1	1	1	1	0	0	0	1
1	1	1	1	0	0	1	0

2. Using K-MAP, get minimized SOP Boolean expressions for E1, E2, E3 and E4 circuits.

E1

cd \ ab	00	01	11	10
00	0	1	x	0
01	0	x	0	x
11	x	0	0	0
10	0	x	0	x

$$E1 = \bar{A}\bar{B}D$$

E3

cd \ ab	00	01	11	10
00	0	0	x	0
01	0	x	0	x
11	x	1	1	0
10	0	x	1	x

$$E3 = AD$$

E2

cd \ ab	00	01	11	10
00	1	0	x	1
01	1	x	0	x
11	x	0	0	0
10	0	x	0	x


$$E2 = \bar{A}\bar{D}$$

E4

cd \ ab	00	01	11	10
00	0	0	x	0
01	0	x	0	x
11	x	0	0	1
10	0	x	0	x

$$E4 = B\bar{C}\bar{D}$$

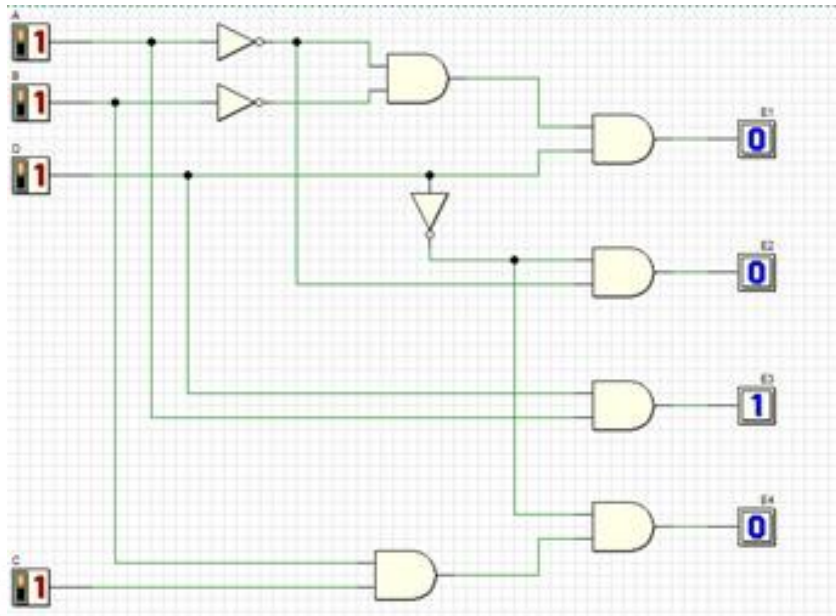3. From the Boolean expression in the step (2), draw your final E1, E2, E3 and E4 circuits using 2 input basic gates (AND, OR, NOT). Use Deeds Simulator.



4. Simulate the Deeds circuit in step (3):

a) Update Truth Table 2 based on the simulation result.


Truth Table 2

INPUTS				OUTPUTS			
A	B	C	D	E1	E2	E3	E4
0	0	0	0	0	1	0	0
0	0	0	1	1	0	0	0
0	0	1	0	0	1	0	0
0	0	1	1	1	0	0	0
0	1	0	0	0	1	0	0
0	1	0	1	0	0	0	0
0	1	1	0	0	1	0	1
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	0	0	0
1	0	1	1	0	0	1	0
1	1	0	0	0	0	0	0
1	1	0	1	0	0	1	0
1	1	1	0	0	0	0	1
1	1	1	1	0	0	1	0

Compare the output results in Truth Table 2 with Truth Table 1. What is your conclusion?


It have the same output

b) Timing Diagram

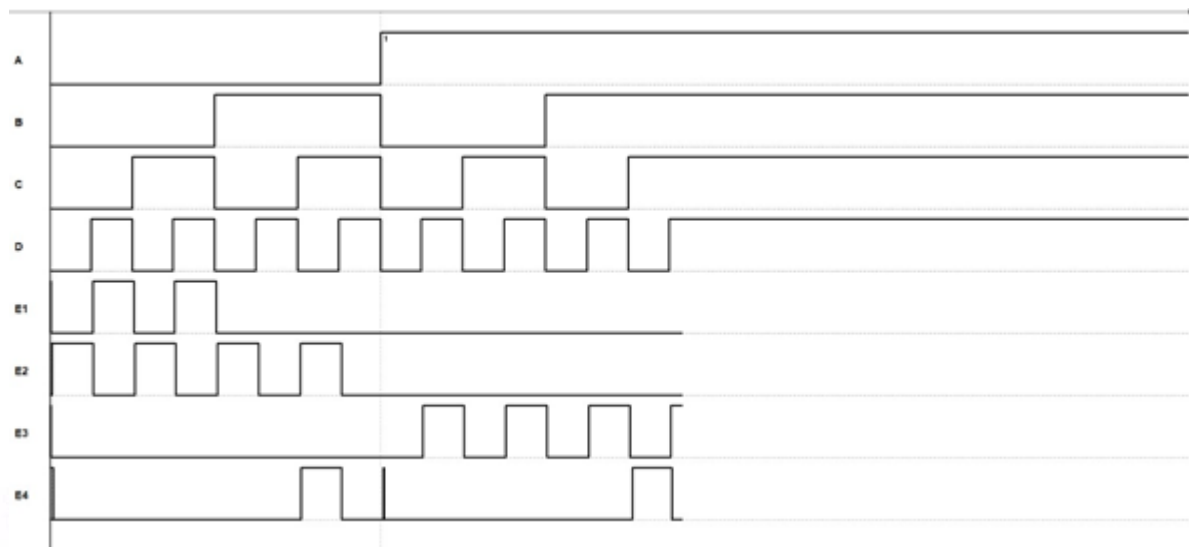

Explain some analysis values based on your timing diagram:

1
2
3
840
84

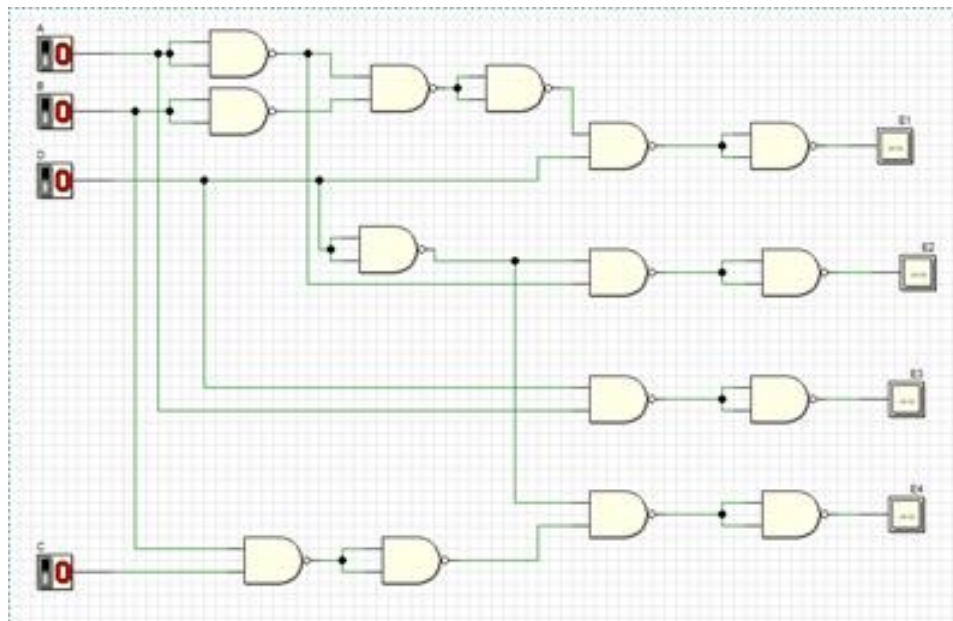

6. Simulate the Deeds circuit in step (5):

a) Update Truth Table 3 based on the simulation result.


Truth Table 3

INPUTS				OUTPUTS			
A	B	C	D	E1	E2	E3	E4
0	0	0	0	0	1	0	0
0	0	0	1	1	0	0	0
0	0	1	0	0	1	0	0
0	0	1	1	1	0	0	0
0	1	0	0	0	1	0	0
0	1	0	1	0	0	0	0
0	1	1	0	0	1	0	1
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	0	0	0
1	0	1	1	0	0	1	0
1	1	0	0	0	0	0	0
1	1	0	1	0	0	1	0
1	1	1	0	0	0	0	0
1	1	1	1	0	0	0	1
1	1	1	1	0	0	1	0

Compare the output results in Truth Table 3 with Truth Table 2. What is your conclusion?

It have the exact output from truth table 2 .

b) Timing Diagram

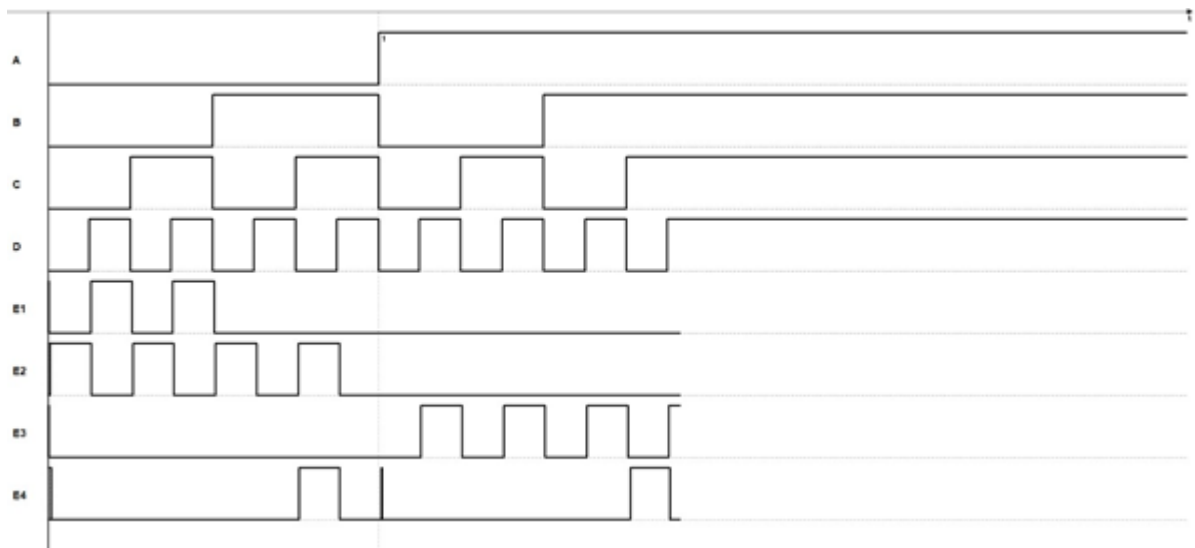

Explain some analysis values based on your timing diagram:

the outcome is the same due to how NAND gates works
thus the timing diagram is similar to the ones before



Fully
Completed ☐

Partially
Completed ☐

Checked by: _____