



Department of Computer Science  
Faculty of Computing  
UNIVERSITI TEKNOLOGI MALAYSIA

SUBJECT : SCSR1013 DIGITAL LOGIC

SESSION/SEM : 1

.....

**LAB 1 : COMBINATIONAL LOGIC**

NAME 1 : AHMAD MUHAJIMIN BIN AHMAD HAMBALI

NAME 2 :

.....  
.....

DATE : 17/11/2020

.....

REMARKS :

MARKS:

## Lab # 1

### Introduction to Logic Circuits

#### A. Objectives

The objectives of this laboratory are to introduce the student to:

- basic bread boarding and wiring techniques
- the use of input switches and output LEDs in generating truth tables for a combinational logic circuit
- to verify the characteristic of the basic gates

#### B. Materials

- Breadboard
- 7408 Quad 2-input AND - 1
- 7404 Hex Inverter - 1
- 7400 Quad 2-input NAND - 1
- 7432 Quad 2 –input OR - 1
- ETS-5000 Digital Training kit

#### C. Introduction

This lab focuses on several practical issues related to bread boarding and testing combinational logic circuits. Several helpful points are made below.

**Wire gauge** - Use only 22 gauge wire. The breadboard may be damaged by forcing smaller gauge (larger diameter) wire into the holes.

**Wire color** - Use organized color schemes when wiring circuits. For example, use RED wire for all  $V_{cc}$  connections, BLACK wire for all ground connections, BLUE wire for all input switches, and YELLOW wire for all intermediate signal connections.

**Wire length and placement** - Use wires that are the appropriate length so that they can lie flat on the breadboard. Avoid running wires over IC's in case the IC's need to be removed.

**Testing IC's** - Chip tester is available in lab, always check your IC's before you begin wiring the circuit.

**Inserting IC's** - IC's are not difficult to insert in the socket strips once they have been properly adjusted. Brand new IC's are shipped with their pins bent apart from the vertical (typically 15° outward) in order to facilitate handling by automatic insertion equipment. Therefore, before an IC is used for the first time its pins must be bent back so that their spacing is vertical.

**IC Orientation** - Arrange all IC's in the same direction. This will facilitate connecting  $V_{cc}$  on each IC to a 5V strip on the breadboard and GND on each IC to a ground strip. If an IC is reversed (thus  $V_{cc}$  and ground are reversed), it may be destroyed. It is recommended that you begin wiring by making all  $V_{cc}$  and ground connections.

**IC Removal** - It is recommended that you use some sort of extraction tool for removing IC's. Attempts to remove IC's by hand may result in bent pins.

### **Monitoring the logic level of the circuit**

Use the LED (at the top right of the digital kit) to monitor the logic level of the digital circuit. A GREEN indicates that the logic level is LOW (0) and a RED means the logic level is HIGH (1). If the LED does not lit, there is something wrong with the circuit. Switch off the power supply and recheck the circuit.

**Note: Please be certain that the MODE switch is flip to TTL not CMOS.**

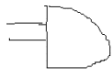

You can use a logic probe (at the bottom right of the digital circuit) to monitor the logic level of any node (point) of the circuit. **H** indicates logic HIGH (1), **L** means LOW (0) and **P** means pulse (the signal keeps on changing between HIGH and LOW).

### **Switches**


There are 8 toggle switches at the bottom row of the digital circuit. These switches will provide a logic input of HIGH (1) and LOW (0) to the circuit.

#### D. Preliminary Work

1. Draw a symbol, determine the IC number and produce a truth table for the following gate.

<b><u>AND</u></b>	<b><u>NAND</u></b>																																				
Symbol: 	Symbol: 																																				
7408	7400																																				
IC Number: .....	IC Number: .....																																				
Truth Table 1	Truth Table 2																																				
<table border="1" style="margin: auto; border-collapse: collapse;"><thead><tr><th colspan="2" style="background-color: #cccccc;">Input</th><th style="background-color: #cccccc;">Output</th></tr><tr><th style="width: 30px;">A</th><th style="width: 30px;">B</th><th style="width: 30px;">F</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></tbody></table>	Input		Output	A	B	F	0	0	0	1	0	0	0	1	0	1	1	1	<table border="1" style="margin: auto; border-collapse: collapse;"><thead><tr><th colspan="2" style="background-color: #cccccc;">Input</th><th style="background-color: #cccccc;">Output</th></tr><tr><th style="width: 30px;">A</th><th style="width: 30px;">B</th><th style="width: 30px;">F</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></tbody></table>	Input		Output	A	B	F	0	0	1	1	0	1	0	1	1	1	1	0
Input		Output																																			
A	B	F																																			
0	0	0																																			
1	0	0																																			
0	1	0																																			
1	1	1																																			
Input		Output																																			
A	B	F																																			
0	0	1																																			
1	0	1																																			
0	1	1																																			
1	1	0																																			

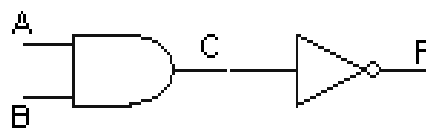
2. Complete the truth table for the following circuit.



Truth Table 3

A	B	C	F
0	0	0	1
1	0	0	1
0	1	0	1
1	1	1	0

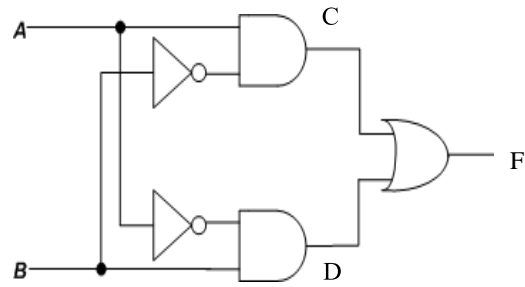3. Write the Boolean expression for output C, D and F the following circuit.



$$C = A \cdot \bar{B}$$

$$D = \bar{A} \cdot B$$

$$F = A \cdot \bar{B} + \bar{A} \cdot B$$

4. Complete the truth table for the circuit in (3) based on the Boolean expression produced for C, D and F.

Truth Table 4

A	B	C	D	F
0	0	0	0	0
1	0	1	0	1
0	1	0	1	1
1	1	0	0	0

## E. Laboratory Work

### Part 1

1. Construct Circuit 1 on the breadboard. Connect all inputs (A, B) to a switches and output F to LEDs.

Truth Table 5



Circuit 1

Input		Output
A	B	F
0	0	0
1	0	0
0	1	0
1	1	1

2. Test Circuit 1 and fill in Truth Table 5 for the circuit response to all possible input combinations. The Truth Table 5 should match the Truth Table 1 prepared in the Preliminary Work.



Fully  
Completed

☐

Partially  
Completed


☐

Checked by: \_\_\_\_\_

### Part 2

3. Construct Circuit 2 on the breadboard. Connect all inputs (A, B) to a switches and output C and F to LEDs.

Truth Table 6

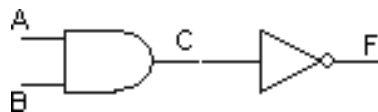

Circuit 2

A	B	C	F
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

4. Test Circuit 2; fill in Truth Table 6, for the circuit response to all possible input combinations.
5. Compare Truth Table 6 to Truth Table 2. What conclusion can you make?

-The truth table 6 and the truth table 2 have the same output. Therefore, the circuit 2 represent NAND gate.



Fully  
Completed

☐


Partially  
Completed

☐

Checked by: \_\_\_\_\_

### Part 3

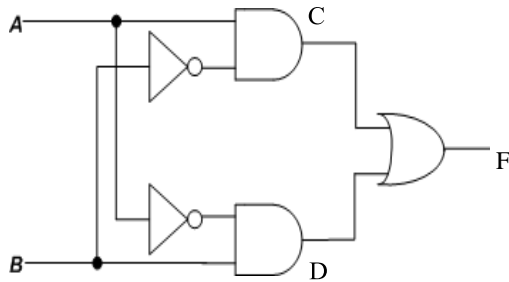6. Construct circuit 3 on the breadboard. Connect all inputs (A, B) to a switches and output C, D and F to LEDs.



Truth Table 7

A	B	C	D	F
0	0	0	0	0
1	0	1	0	1
0	1	0	1	1
1	1	0	0	0

Circuit 3

7. Test Circuit 3; fill in Truth Table 7 for the circuit outputs (C, D, and F) for all possible input combinations.
8. What single gate does Circuit 3 represent?
- Exclusive OR gate



Fully  
Completed

☐

Partially  
Completed

☐

Checked by: \_\_\_\_\_