



**School of Computing
Faculty of Engineering
UNIVERSITI TEKNOLOGI MALAYSIA**

SUBJECT : SECR1013 DIGITAL LOGIC

SESSION/SEM : 02/Semester 1

LAB 3 : SYNCHRONOUS DIGITAL COUNTER

NAME : AFIF HAZMIE ARSYAD BIN AGUS

DATE : January 29, 2021

Lab #3

Identifying the Properties of a Synchronous Counter

A. Aims

- 1) Expose the student with experience on constructing synchronous counter circuit using Flip-Flop IC, Basic Gate ICs, Breadboard and ETS-5000 Digital Kit.
- 2) Promote critical thinking among students by analyzing the given circuit and identifying the behavior of the digital circuit.

B. Objectives

The objectives of this lab activity are to:

- 1) Implement a synchronous counter circuit into physical circuit using Breadboard, Flip-Flops, Basic Gates and Switches.
- 2) Completing the next-state table of the counter circuit.
- 3) Sketch the state diagram of the counter circuit.
- 4) Identify the properties of the counter.

C. Materials and Equipment

Materials and equipment required for this lab are as follows:

Item Name	Number of Item
1. Breadboard	1
2. 7408 Quad 2-Input AND	1
3. 7404 Hex Inverter	1
4. 7432 Quad 2-input OR	1
5. 7476 Dual J-K Flip Flop	1
6. ETS-5000 Digital Kit	1

D. Preliminary Works

- 1) Determine the logic level for each input combinations in Table 1 so that the desired result can be realized.

Table 1

Desired Result	\overline{PRE}	\overline{CLR}	J	K	CLK	Q
Set initial value Q = 1	0	1	X	X	--	1
Output Q stays the same	1	1	0	0	↓	1
Output Q become 0, no change in asynchronous input	1	1	1	1	↓	0
Output Q is not the previous Q	1	1	1	1	↓	1
RESET Q	1	1	0	1	↓	0
SET Q	1	1	1	0	↓	1

- 2) Answer all questions.

- a) Which state that JK flip-flop has, but not on SR flip-flop.
Toggle state
-

- b) Identify whether the JK flip flop in 7476, is a positive-edge triggered or negative-edge triggered flip flop.

Negative-edge triggered flip-flop because to clock shows downward arrow

E. Lab Activities

1) You are given a counter circuit as shown in Figure 4.


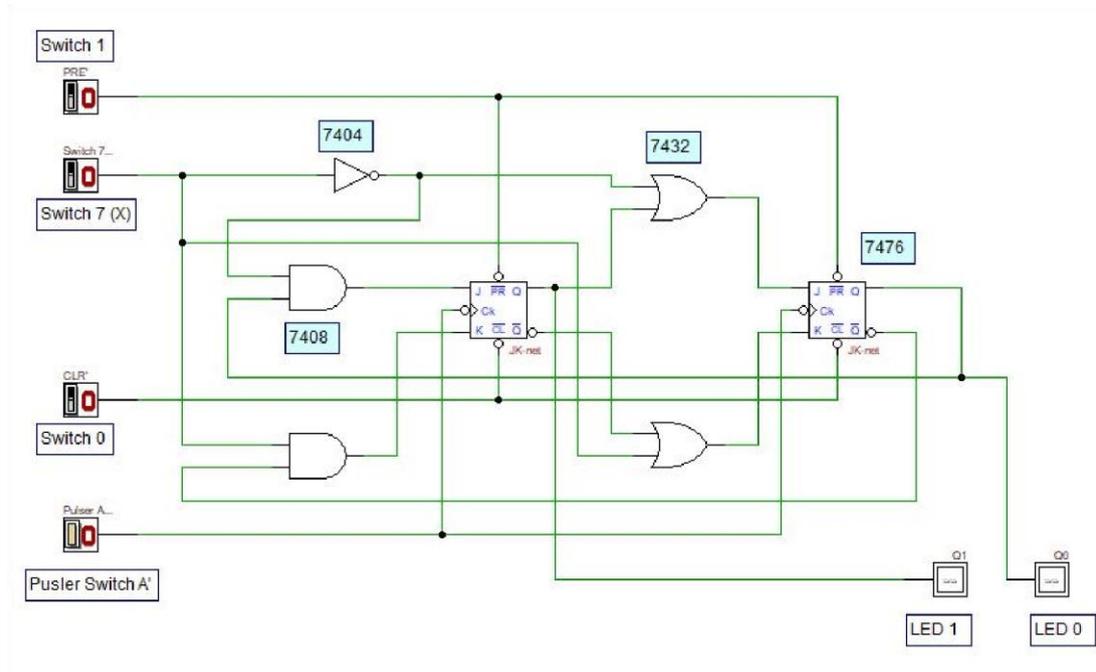


Figure 4: A Synchronous Counter Circuit

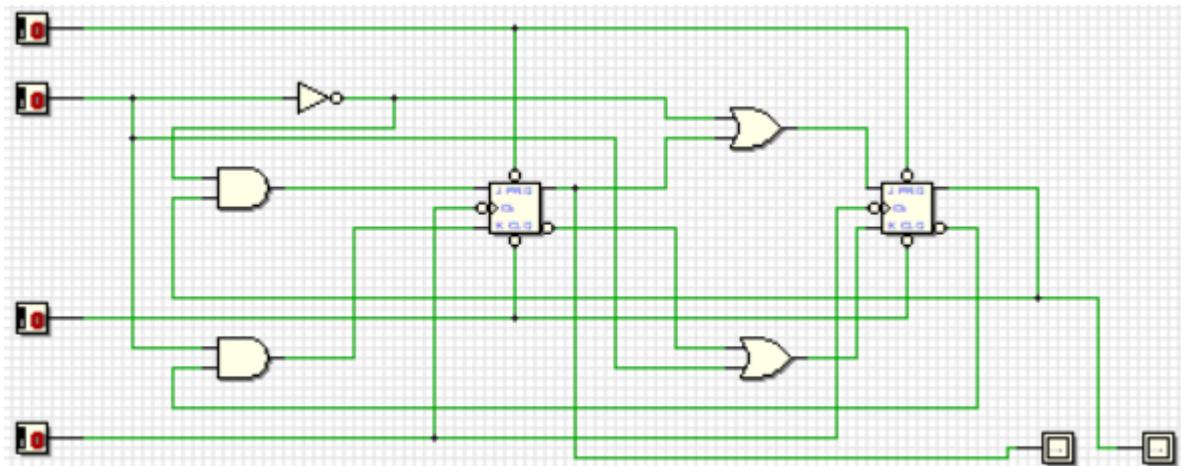2) By using all materials and equipment's listed in section C, construct the physical circuit of Figure 4. (Make sure all ICs are connected to Vcc and GND).




- 3) Investigate the behavior of the counter by observing the next state of the counter for all combination of *Present State* and *X* values. Complete the *NextState* table of the counter in Table 2. Ensure the Switch 0 is in HIGH state.
(0=LOW, 1=HIGH)

Table 2

Switch 7	Present State		Next State	
X	Q1 LED 1	Q0 LED 0	Q1 LED 1	Q0 LED 0
0	0	0	0	1
0	0	1	1	0
0	1	0	1	1
0	1	1	1	1
1	0	0	0	0
1	0	1	0	0
1	1	0	0	1
1	1	1	1	0

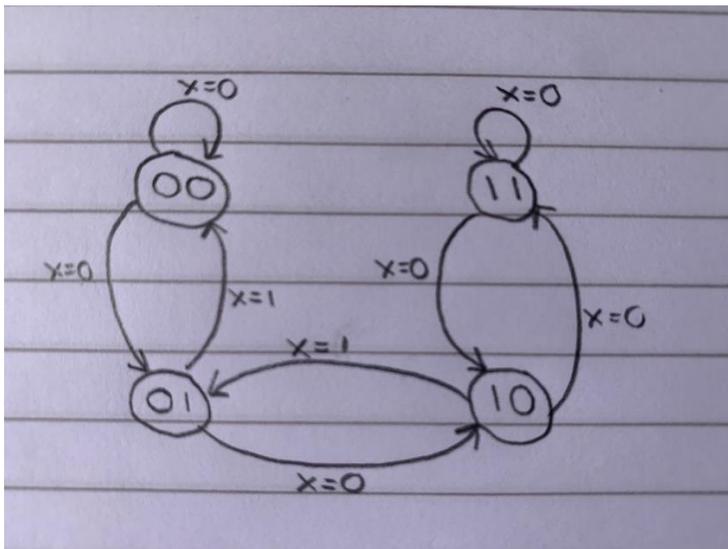- 4) By referring to the *Next-State* in Table 2, sketch the state diagram of the counter.



- 5) By referring to the *Next-State* in Table 2 and the state diagram in (4), answer all questions.

- a) What is the main indicator to decide that the counter is a synchronous counter?

All FF are connected to the same source.

- b) How many states are available for the counter and what are they?

4 states which are 00, 01, 10, 11

- c) What is the function of Switch 7 (X) in the circuit?

Function as Indicator whether it is count up or count down.

- d) What is the function of Switch 0 and Switch 1 in the circuit?

Switch 1 act as Preset input while switch 2 acts as Clear/Reset input.

- e) Is the counter a saturated counter or recycle counter?

Saturated counter. Because the counter repeats the maximum count for count up and minimum count for count down.

6) Referring to state diagram in 4, draw and built a synchronous counter using D flip-flop.

a) Built the next state and transition table using the header in Table 3

Table 3

Input X	Present State		Next State		D FF Transition	
	Q1	Q0	Q1+	Q0+	D1	D0
0	0	0	0	1	0	1
0	0	1	1	0	1	0
0	1	0	1	1	1	1
0	1	1	1	1	1	1
1	0	0	0	0	0	0
1	0	1	0	0	0	0
1	1	0	0	1	0	1
1	1	1	1	0	1	0

b) Get the optimized Boolean expression.

Handwritten Karnaugh maps and Boolean expressions for D1 and D0:

For D1:

x \ Q ₁ Q ₀	00	01	11	10
0	0	1	1	1
1	0	0	1	0

$$D1 = \bar{x}Q_0 + \bar{x}Q_1 + Q_1Q_0$$

$$= \bar{x}(Q_0 + Q_1) + Q_1Q_0$$


For D0:

x \ Q ₁ Q ₀	00	01	11	10
0	1	0	1	1
1	0	0	0	1

$$D0 = \bar{x}\bar{Q}_0 + \bar{x}Q_1 + Q_1\bar{Q}_0$$

$$= \bar{x}(\bar{Q}_0 + Q_1) + Q_1\bar{Q}_0$$

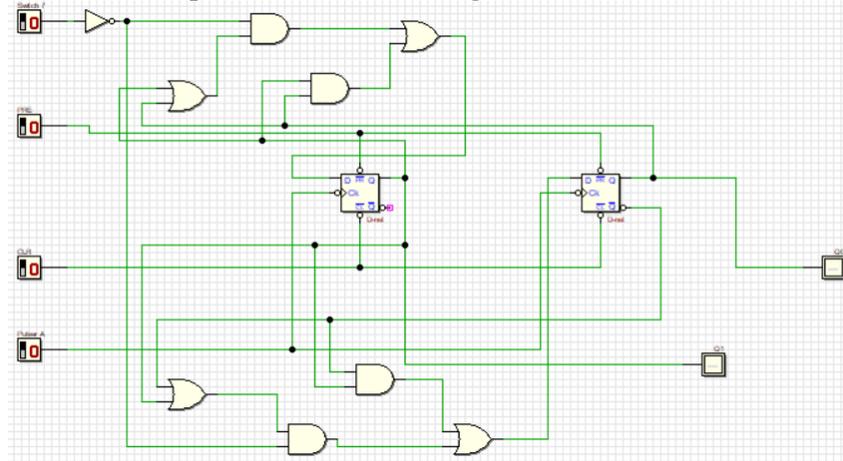c) Draw the complete final circuit design in Deeds.



d) Simulate the circuit to prove that your Table 3 is correct.


7) Repeat steps in Q (6) using T flip-flop.

a) Built the next state and transition table using the header in Table 3

Table 3

Input X	Present State		Next State		D FF Transition	
	Q1	Q0	Q1+	Q0+	D1	D0
0	0	0	0	1	0	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	0	0
1	0	0	0	0	0	0
1	0	1	0	0	0	1
1	1	0	0	1	1	1
1	1	1	1	0	0	1

b) Get the optimized Boolean expression.

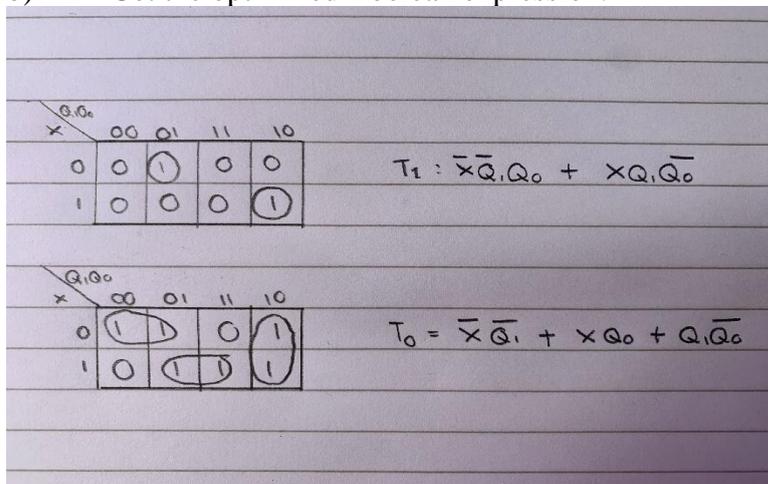

c) Draw the complete final circuit design in Deeds.

