



**Department of Computer Science  
Faculty of Computing  
UNIVERSITI TEKNOLOGI MALAYSIA**

**SUBJECT : SCSR1013 DIGITAL LOGIC**

**SESSION/SEM : 02/1**

**LAB 1 : COMBINATIONAL LOGIC**

**NAME 1 : Luqman Ariff Bin Noor Azhar**

**DATE : 17 November 2020**

**REMARKS :**

**Lab # 1****Introduction to Logic Circuits****A. Objectives**

The objectives of this laboratory are to introduce the student to:

- basic bread boarding and wiring techniques
- the use of input switches and output LEDs in generating truth tables for a combinational logic circuit
- to verify the characteristic of the basic gates

**B. Materials**

- Breadboard
- 7408 Quad 2-input AND - 1
- 7400 Quad 2-input NAND - 1
- 7432 Quad 2 -input OR - 1
- ETS-5000 Digital Training kit

**C. Introduction**

This lab focuses on several practical issues related to bread boarding and testing combinational logic circuits. Several helpful points are made below.

**Wire gauge** - Use only 22-gauge wire. The breadboard may be damaged by forcing smaller gauge (larger diameter) wire into the holes.

**Wire color** - Use organized color schemes when wiring circuits. For example, use RED wire for all  $V_{cc}$  connections, BLACK wire for all ground connections, BLUE wire for all input switches, and YELLOW wire for all intermediate signal connections.

**Wire length and placement** - Use wires that are the appropriate length so that they can lie flat on the breadboard. Avoid running wires over IC's in case the IC's need to be removed.

**Testing IC's** - Chip tester is available in lab, always check your IC's before you begin wiring the circuit.

**Inserting IC's** - IC's are not difficult to insert in the socket strips once they have been properly adjusted. Brand new IC's are shipped with their pins bent apart from the vertical (typically 15° outward) in order to facilitate handling by automatic insertion equipment. Therefore, before an IC is used for the first time its pins must be bent back so that their spacing is vertical.

**IC Orientation** - Arrange all IC's in the same direction. This will facilitate connecting  $V_{cc}$  on each IC to a 5V strip on the breadboard and GND on each IC to a ground strip. If an IC is reversed (thus  $V_{cc}$  and ground are reversed), it may be

destroyed. It is recommended that you begin wiring by making all  $V_{cc}$  and ground connections.

**IC Removal** - It is recommended that you use some sort of extraction tool for removing IC's. Attempts to remove IC's by hand may result in bent pins.

### **Monitoring the logic level of the circuit**

Use the LED (at the top right of the digital kit) to monitor the logic level of the digital circuit. A GREEN indicates that the logic level is LOW (0) and a RED means the logic level is HIGH (1). If the LED does not light, there is something wrong with the circuit. Switch off the power supply and recheck the circuit.

**Note: Please be certain that the MODE switch is flip to TTL not CMOS.**

You can use a logic probe (at the bottom right of the digital circuit) to monitor the logic level of any node (point) of the circuit. **H** indicates logic HIGH (1), **L** means LOW (0) and **P** means pulse (the signal keeps on changing between HIGH and LOW).

### **Switches**


There are 8 toggle switches at the bottom row of the digital circuit. These switches will provide a logic input of HIGH (1) and LOW (0) to the circuit.

## **D. Preliminary Work**

1. Draw a symbol, determine the IC number and produce a truth table for the following gate.

### AND

Symbol:

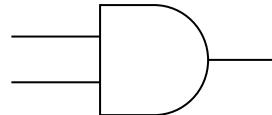


IC Number: 7408

Truth Table 1

Input		Output
A	B	F
1	1	1
1	0	0
0	1	0
0	0	0

### NAND

Symbol:

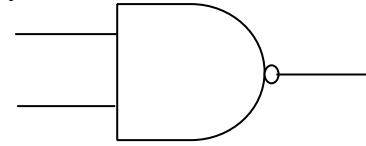


IC Number: 7400

Truth Table 2

Input		Output
A	B	F
1	1	0
1	0	1
0	1	1
0	0	1

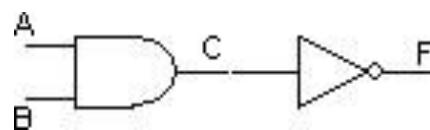
2. Complete the truth table for the following circuit.



Truth Table 3

A	B	C	F
1	1	1	0
1	0	0	1
0	1	0	1
0	0	0	1

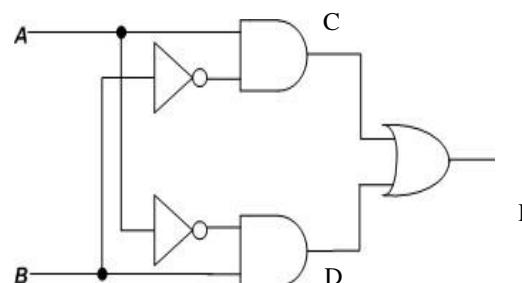3. Write the Boolean expression for output C, D and F the following circuit.



$$C = (A \wedge \neg B)$$

$$D = (\neg A \wedge B)$$

$$F = (A \wedge \neg B) \vee (\neg A \wedge B)$$

4. Complete the truth table for the circuit in (3) based on the Boolean expression produced for C, D and F.


Truth Table 4

A	B	C	D	F
1	1	0	0	0
1	0	1	0	1
0	1	0	1	1
0	0	0	0	0


## E. Laboratory Work

### Part 1

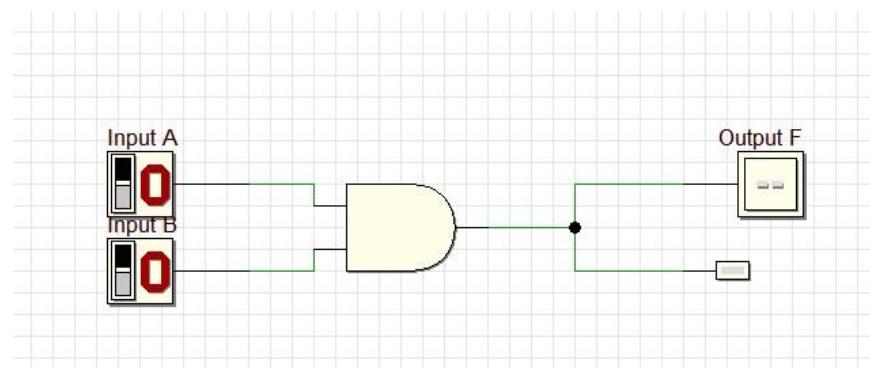1. Construct Circuit 1 on the breadboard. Connect all inputs (A, B) to a switches and output F to LEDs.



Truth Table 5

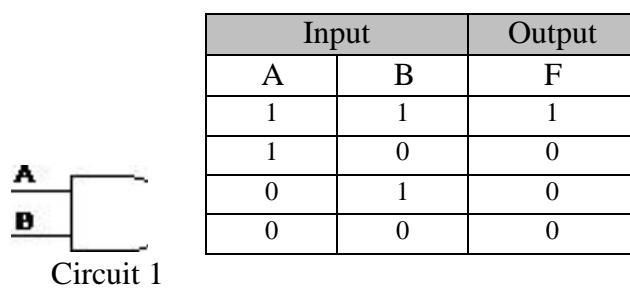

2. Test Circuit 1 and fill in Truth Table 5 for the circuit response to all possible input combinations. The Truth Table 5 should match the Truth Table 1 prepared in the Preliminary Work.



*Fully*

*Completed*




*Partially*




*Checked by:* \_\_\_\_\_

## Part 2

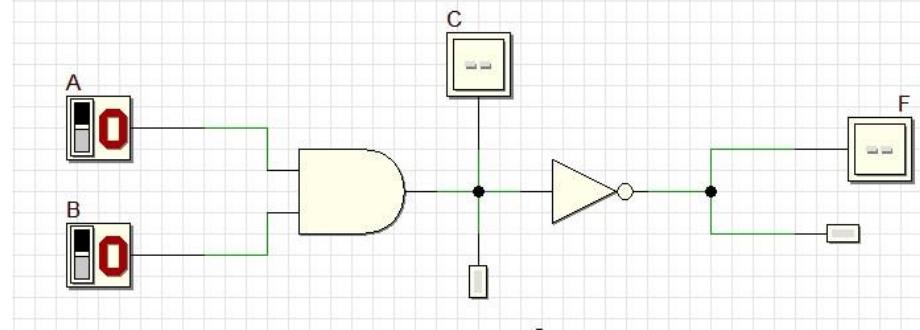3. Construct Circuit 2 on the breadboard. Connect all inputs (A, B) to a switches and output C and F to LEDs.



Truth Table 6

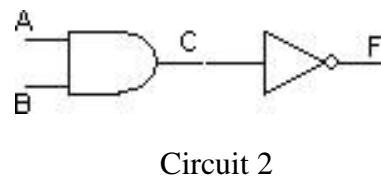

A	B	C	F
1	1	1	0
1	0	0	1
0	1	0	1
0	0	0	1

4. Test Circuit 2; fill in Truth Table 6, for the circuit response to all possible input combinations.
5. Compare Truth Table 6 to Truth Table 2. What conclusion can you make?

Conclusion that I can make is AND gate combine with NOT gate will produce NAND gate.



*Fully*



*Partially*




*Checked by: \_\_\_\_\_*


*Completed*

### Part 3

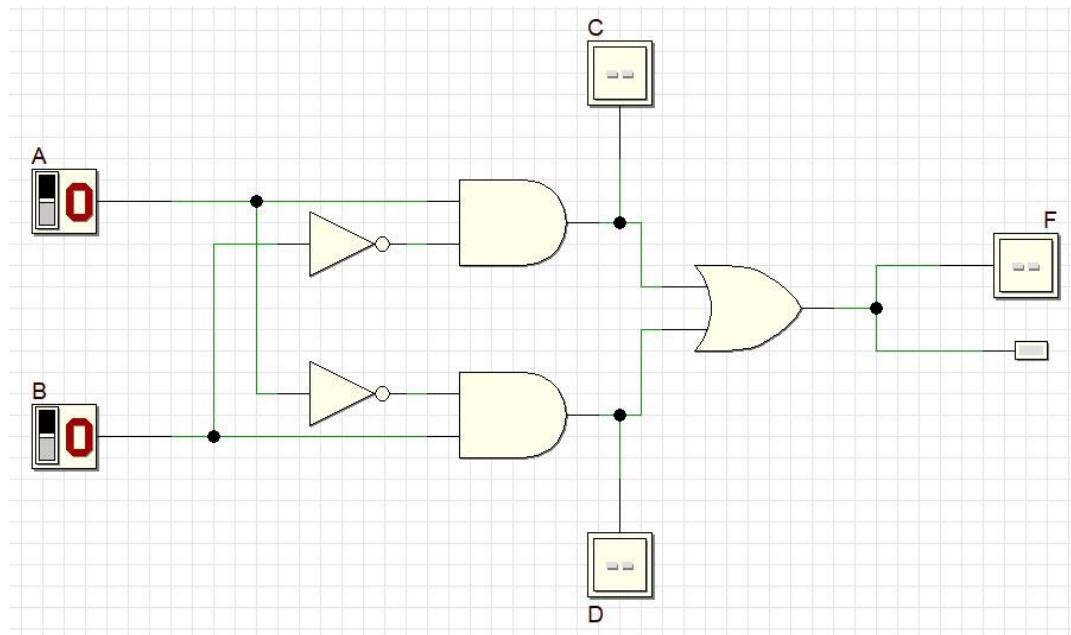6. Construct circuit 3 on the breadboard. Connect all inputs (A, B) to a switches and output C, D and F to LEDs.



### Truth Table 7

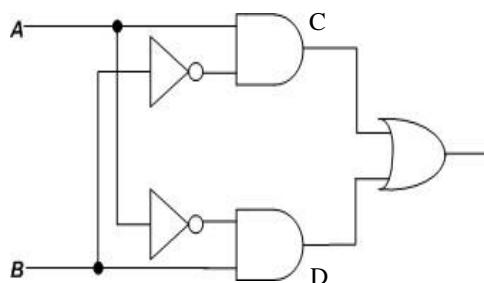

A	B	C	D	F
1	1	0	0	0
1	0	1	0	1
0	1	0	1	1
0	0	0	0	0

### Circuit 3

7. Test Circuit 3; fill in Truth Table 7 for the circuit outputs (C, D, and F) for all possible input combinations.
8. What single gate does Circuit 3 represent?
  - EXOR Gate



*Partially*



*Checked by:* \_\_\_\_\_