

SUBJECT: SCSR1013 DIGITAL LOGIC

SESSION/SEM: SEM-1


LAB-1: COMBINATION LOGIC

NAME: NABIL RAYHAN-(A20EC9107)

NAME: NAZMUL ALAM KHAN

D. Preliminary work

1. AND GATE

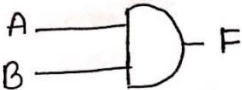Symbol : 


IC Numbers: 7408

Truth table : 1


A	B	$F = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1




* D.1 WITH DEEDS SIMULATOR

AND GATE

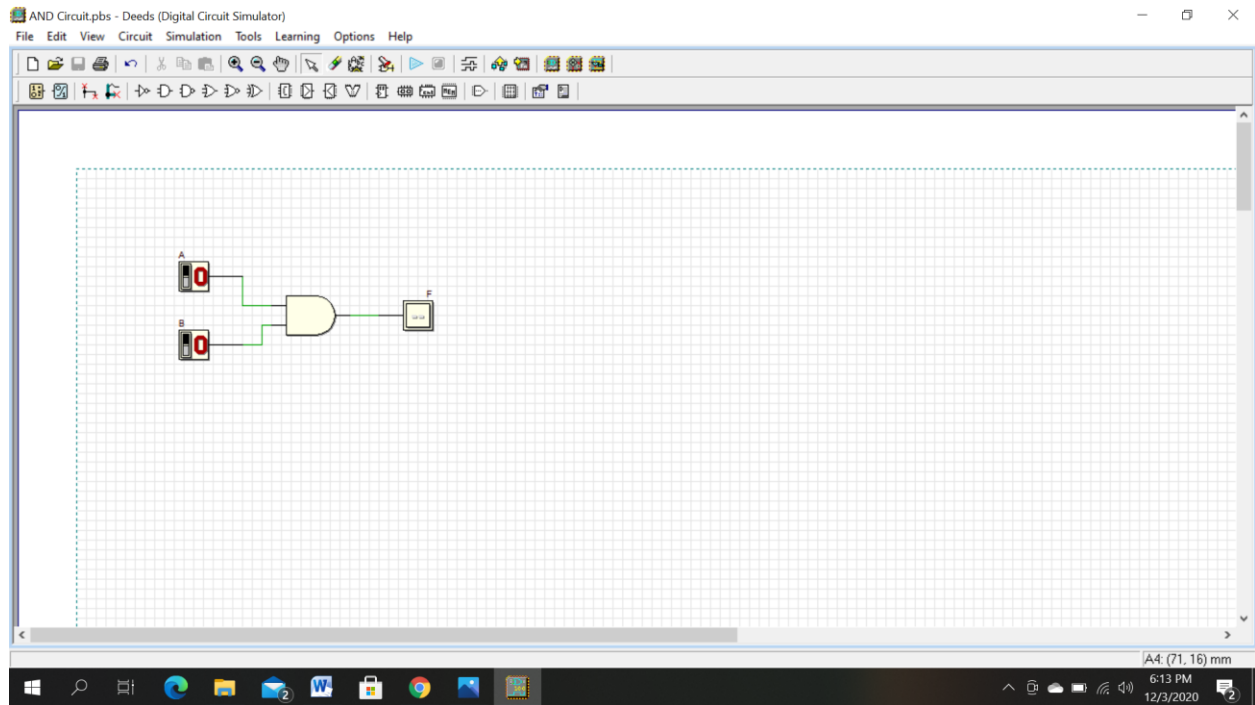

*TRUTH TABLE WITH DEEDS SIMULATOR

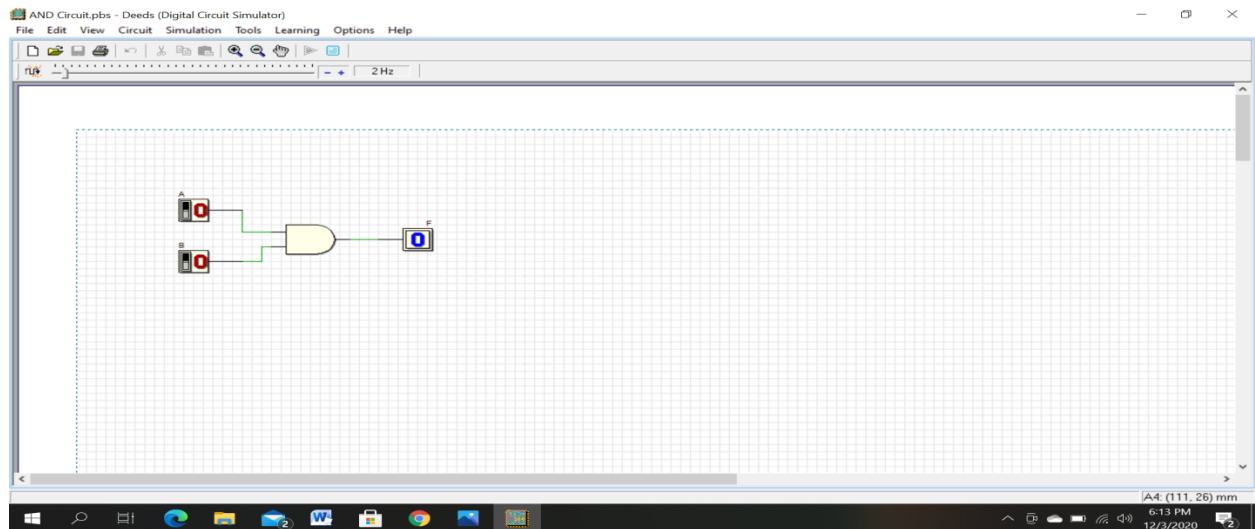

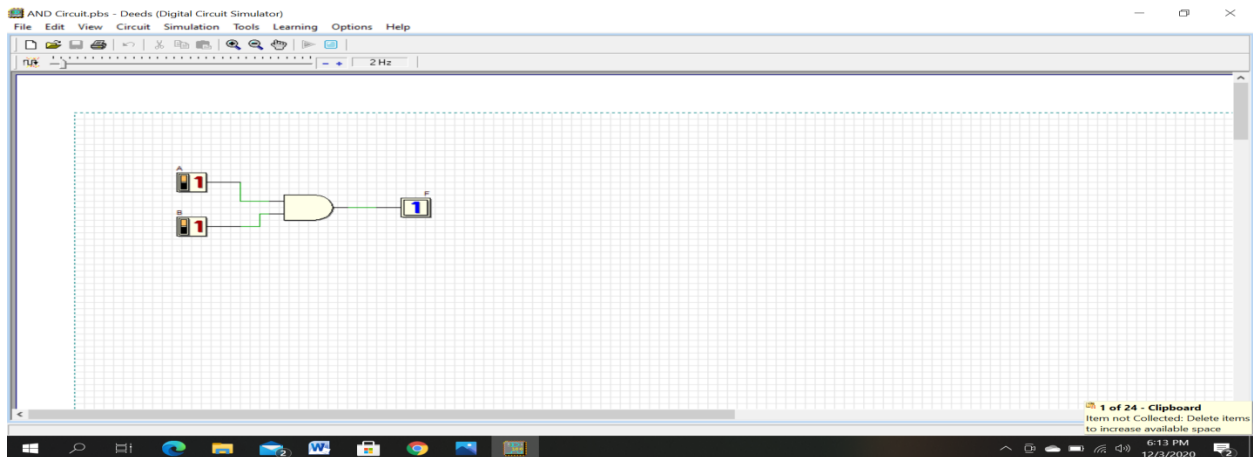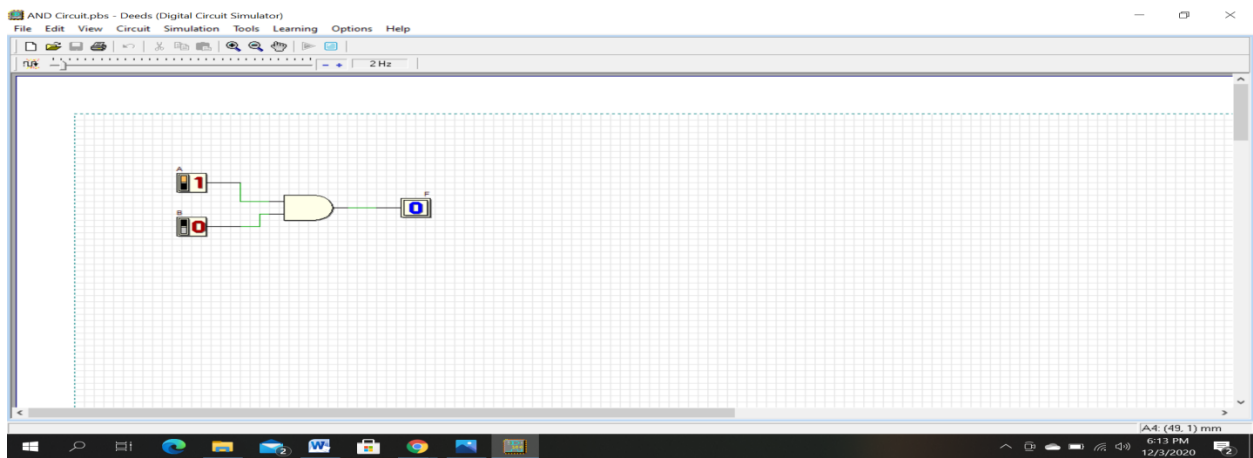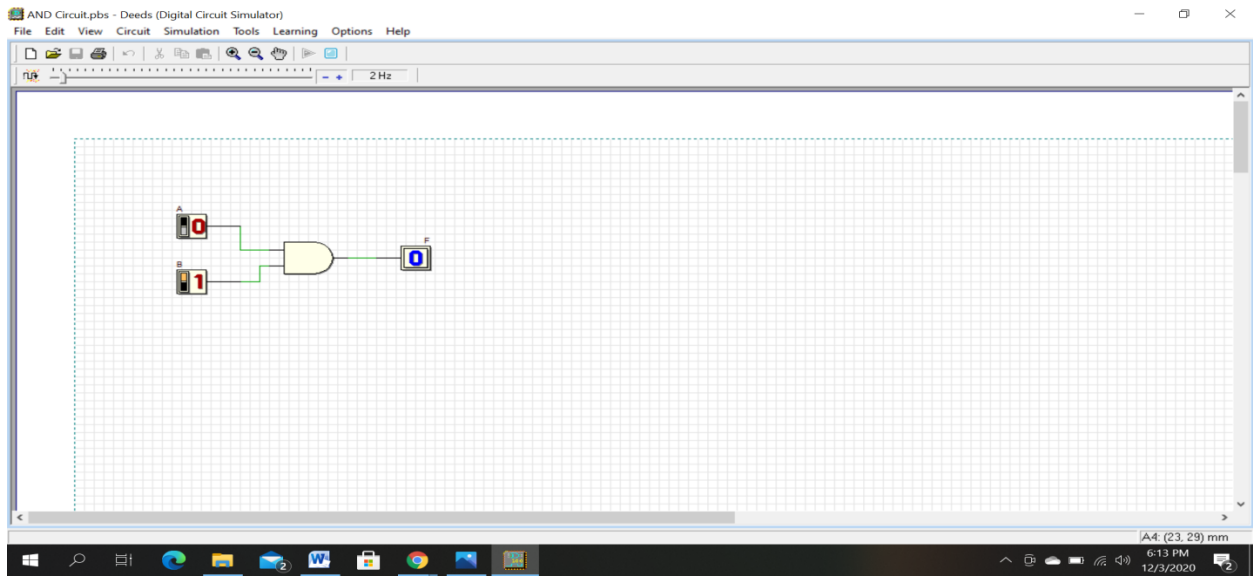


D.1.

NAND GATE

D.1

NAND GATE

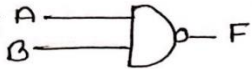Symbol : 

IC Numbers : 7400

Truth-table : 02

A	B	$A \cdot B$	$F = \overline{A \cdot B}$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

Hence,

$$\overline{A \cdot B} = \overline{A \cdot B}$$

$$0 \cdot 0 = \overline{0} = 1$$


$$\overline{0 \cdot 1} = \overline{0} = 1$$

$$\overline{1 \cdot 0} = \overline{0} = 1$$


$$\overline{1 \cdot 1} = \overline{1} = 0$$




D.1 WITH DEEDS SIMULATOR

NAND GATE

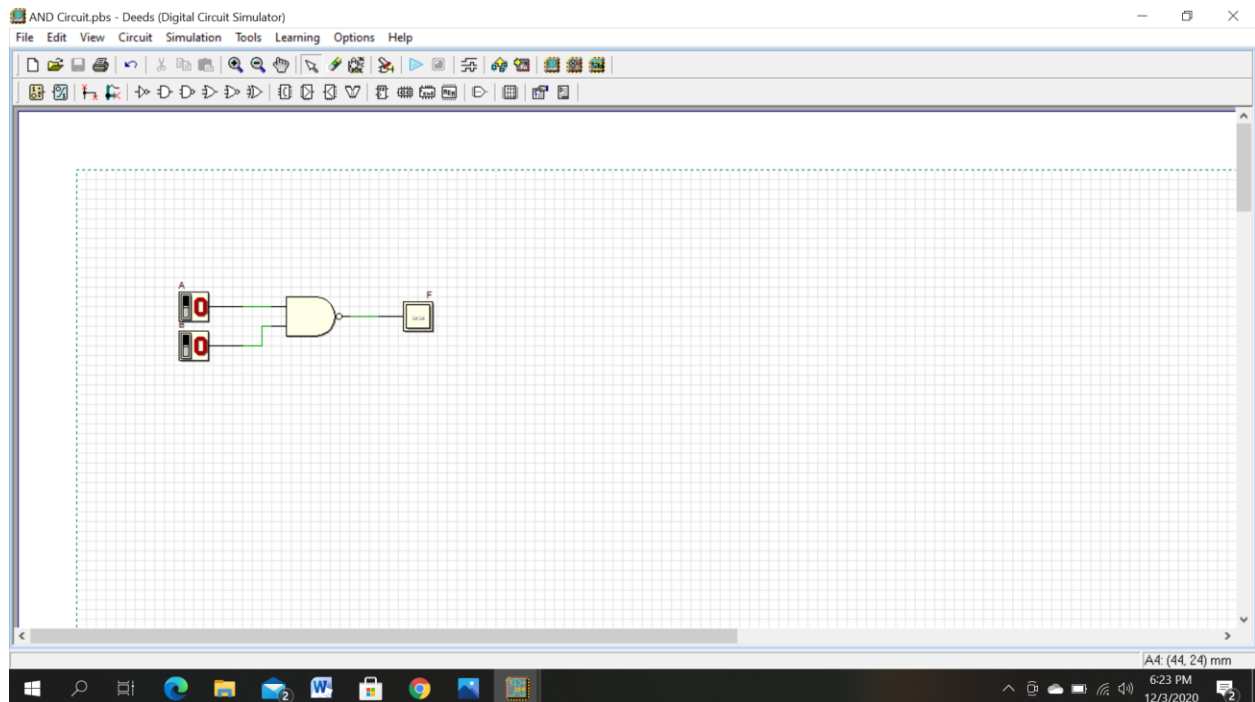


*TRUTH TABLE WITH DEEDS SIMULATOR

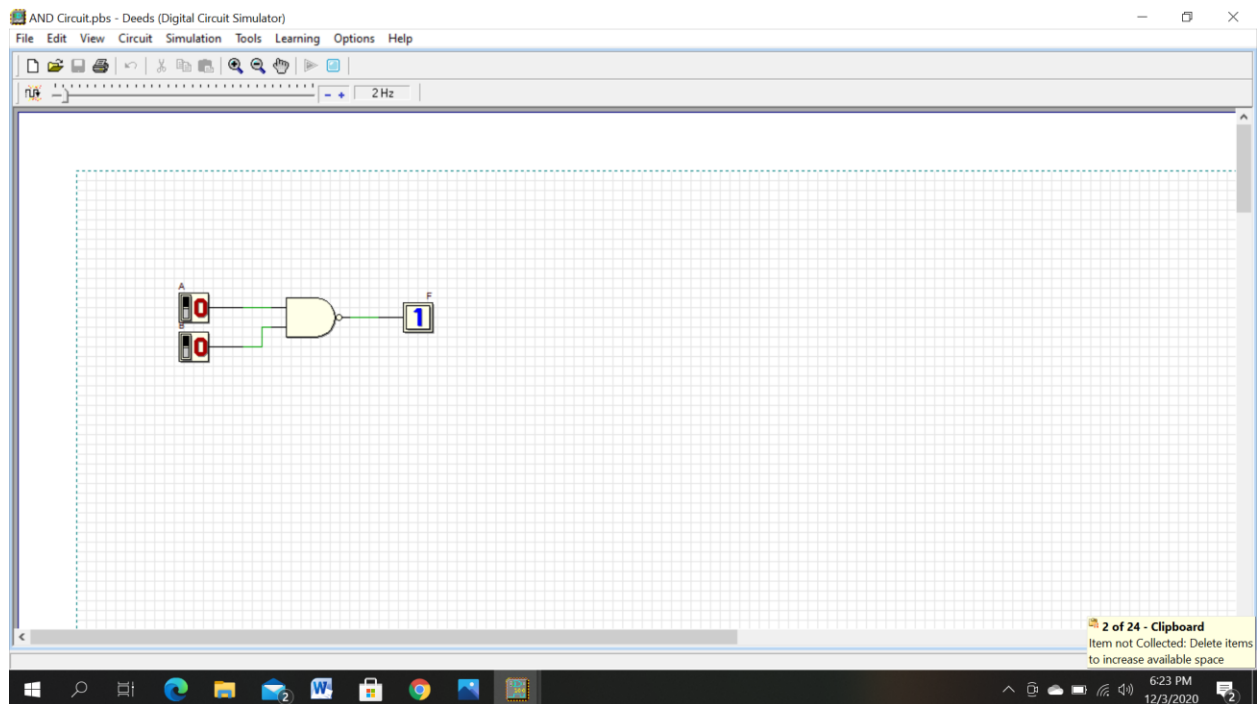

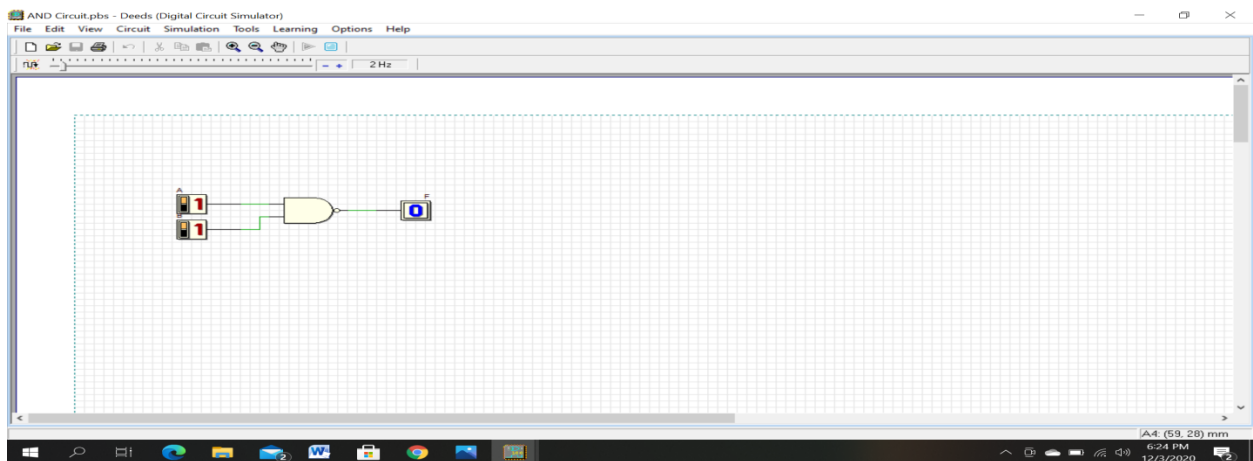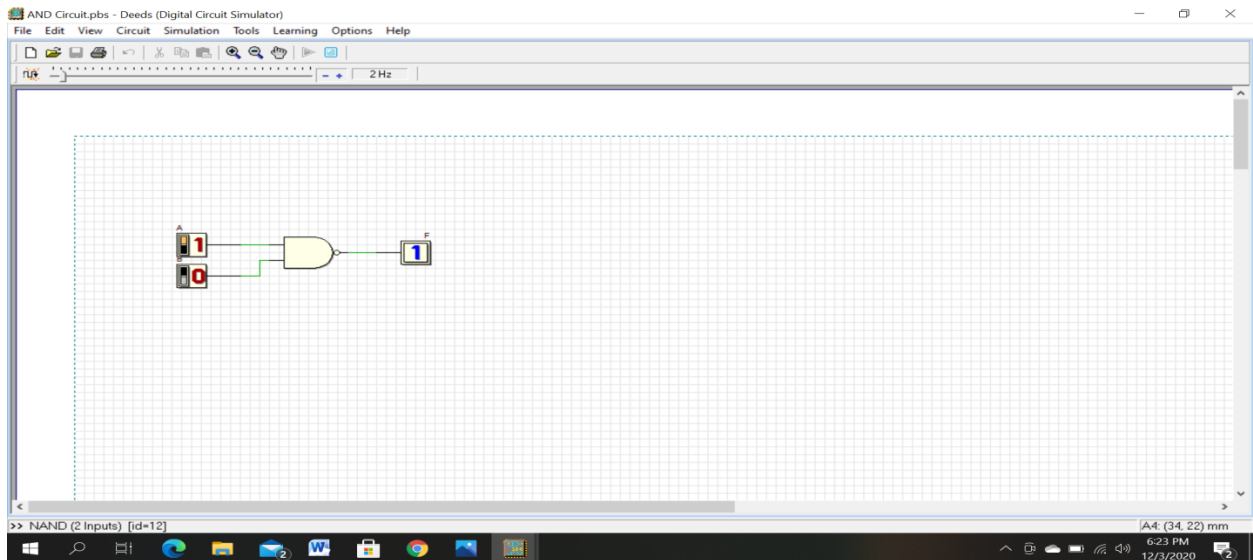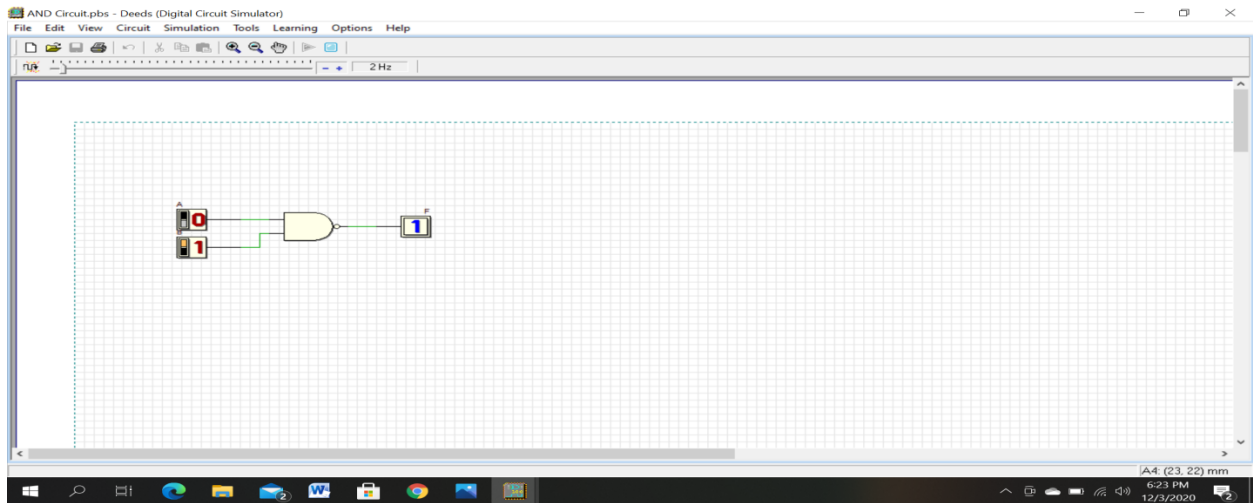


D.2

D.2

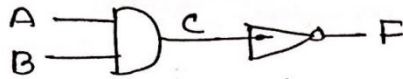





A	B	$C = A \cdot B$	$F = \overline{A \cdot B}$
0	0	0	$\bar{0} = 1$
0	1	0	$\bar{0} = 1$
1	0	0	$\bar{0} = 1$
1	1	1	$\bar{1} = 0$

D.2 WITH DEEDS SIMULATOR

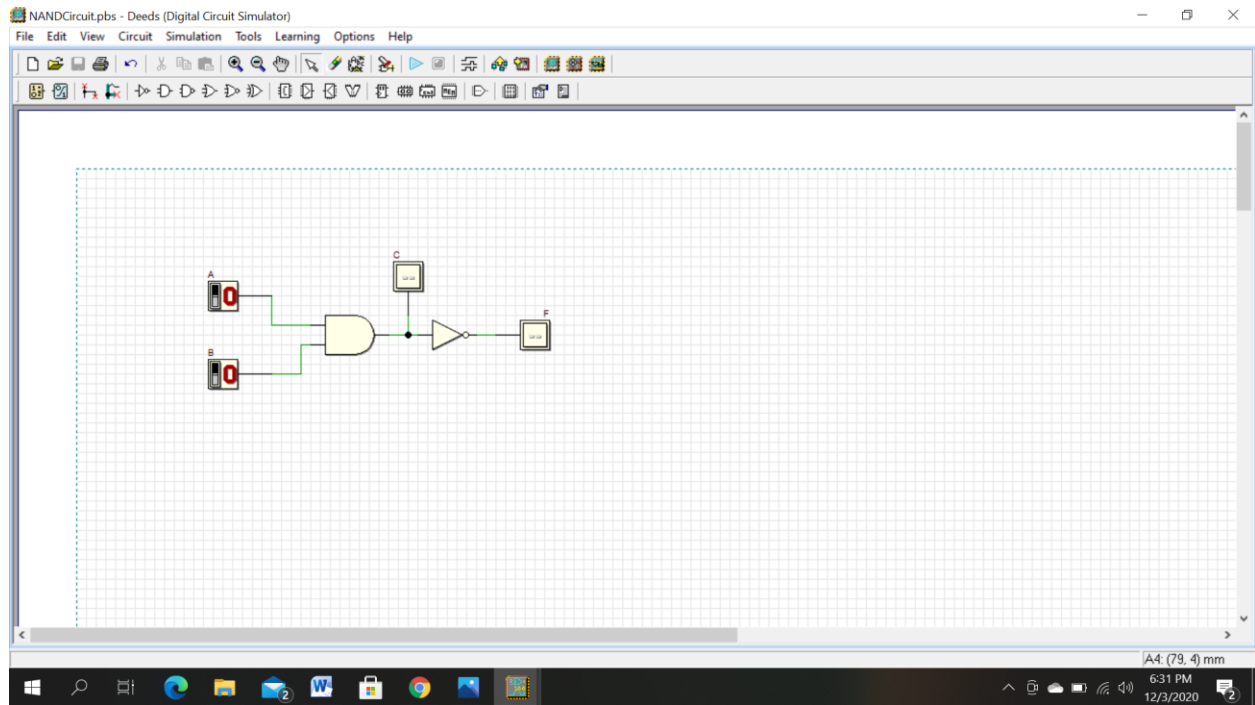


*TRUTH TABLE WITH DEEDS SIMULATOR

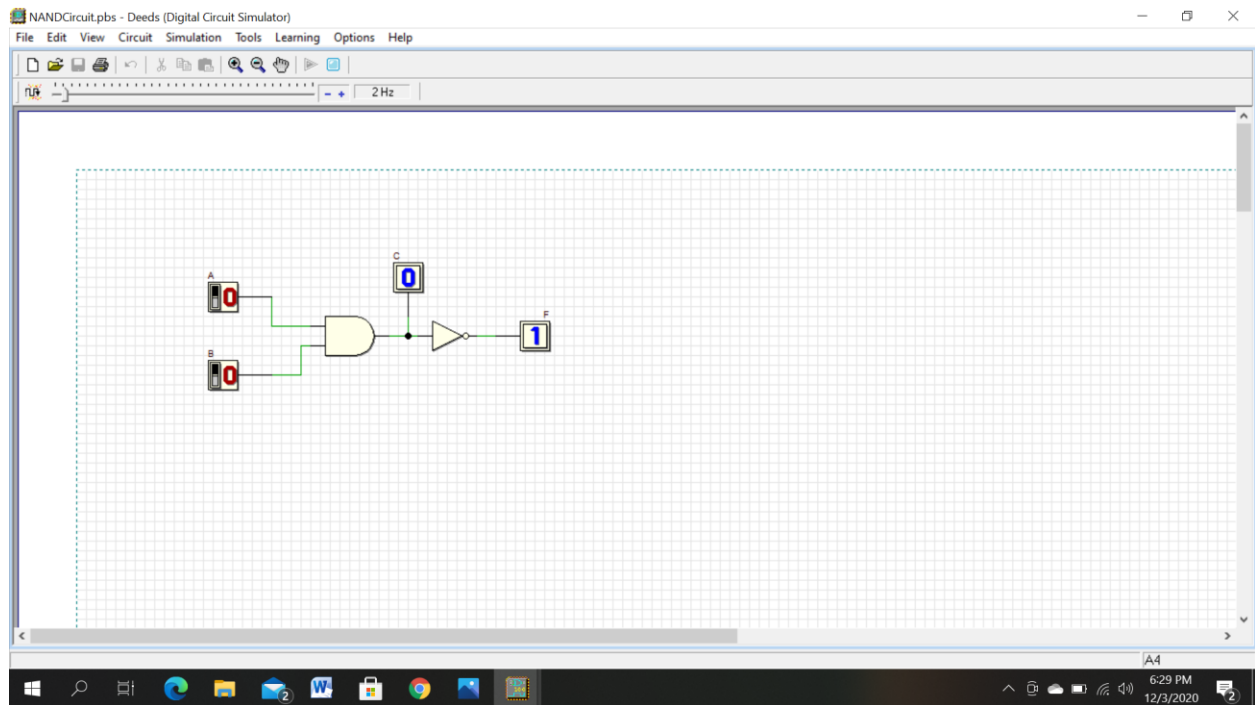

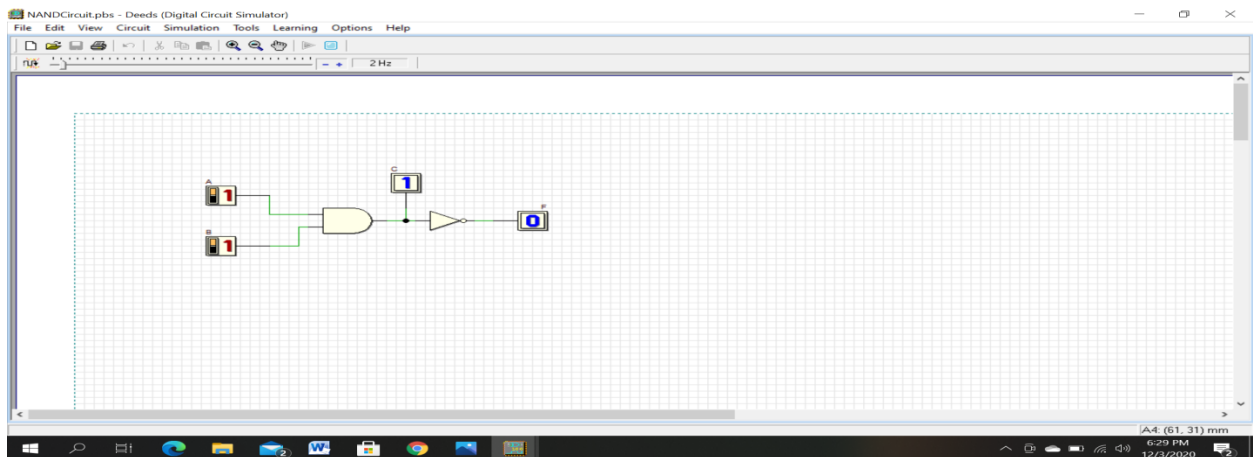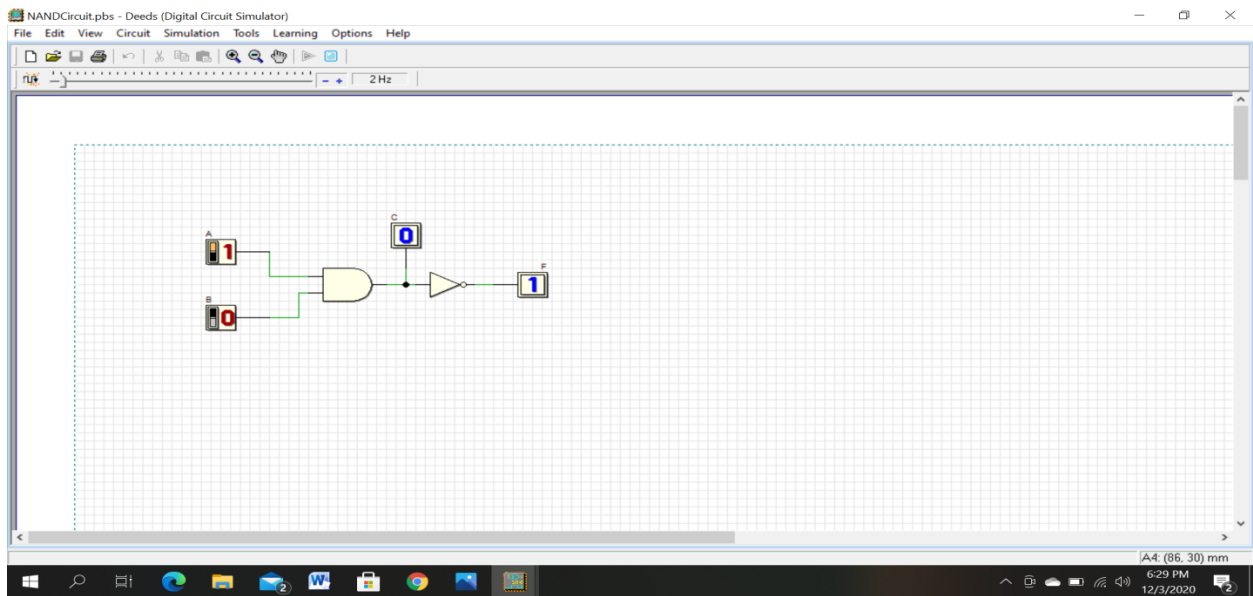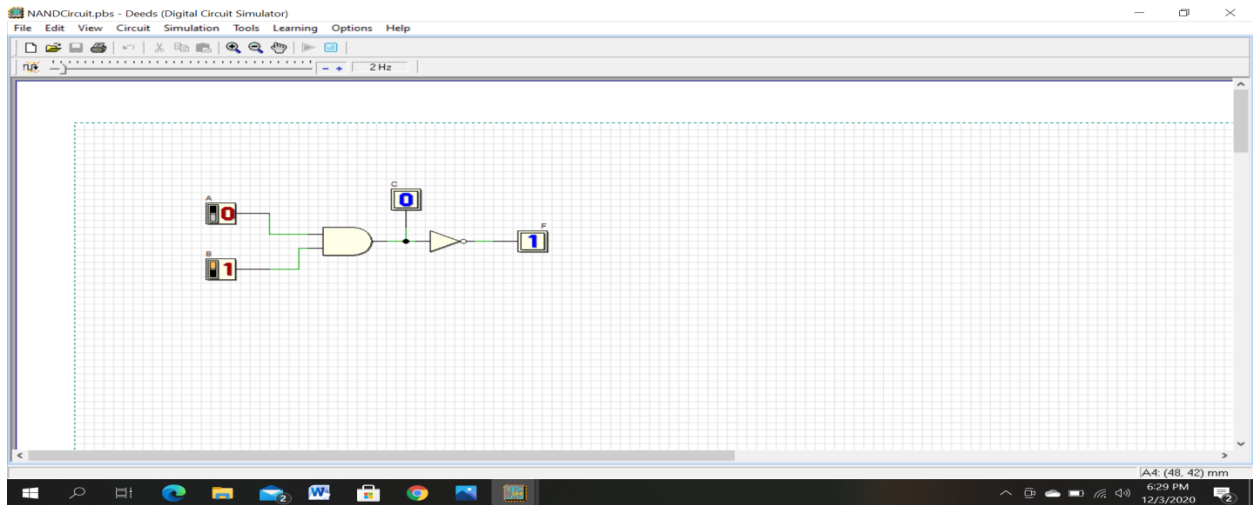

D.3

8.

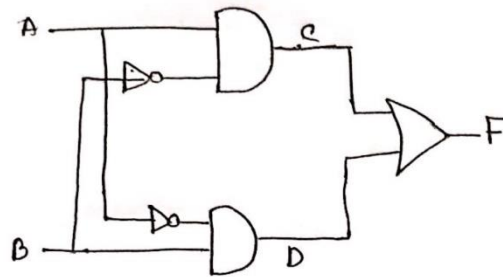

$$c = A \cdot \bar{B}$$

$$D = B \cdot \bar{A}$$


$$F = A \cdot \bar{B} + B \cdot \bar{A}$$

4

Truth table


A	B	$c = A \cdot \bar{B}$	$D = B \cdot \bar{A}$	$F = A \cdot \bar{B} + \bar{A} \cdot B$
0	0	$0 \cdot 1 = 0$	$0 \cdot \bar{0} = 0 \cdot 1 = 0$	$0 + 0 = 0$
0	1	$0 \cdot \bar{1} = 0 \cdot 0 = 0$	$1 \cdot \bar{0} = 1 \cdot 1 = 1$	$0 + 1 = 1$
1	0	$1 \cdot \bar{0} = 1 \cdot 1 = 1$	$0 \cdot \bar{1} = 0 \cdot 0 = 0$	$1 + 0 = 1$
1	1	$1 \cdot \bar{1} = 1 \cdot 0 = 0$	$1 \cdot \bar{1} = 1 \cdot 0 = 0$	$0 + 0 = 0$




D.3 WITH DEEDS SIMULATOR

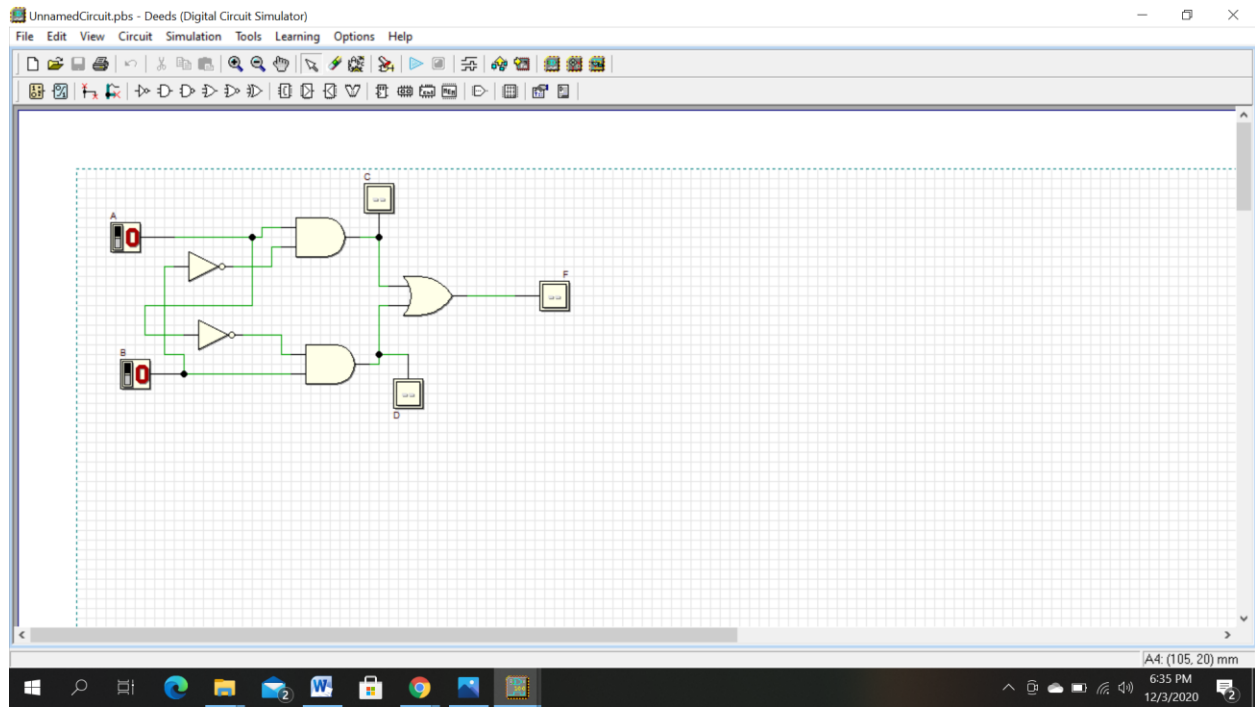

D.4

*TRUTH TABLE WITH DEEDS SIMULATOR

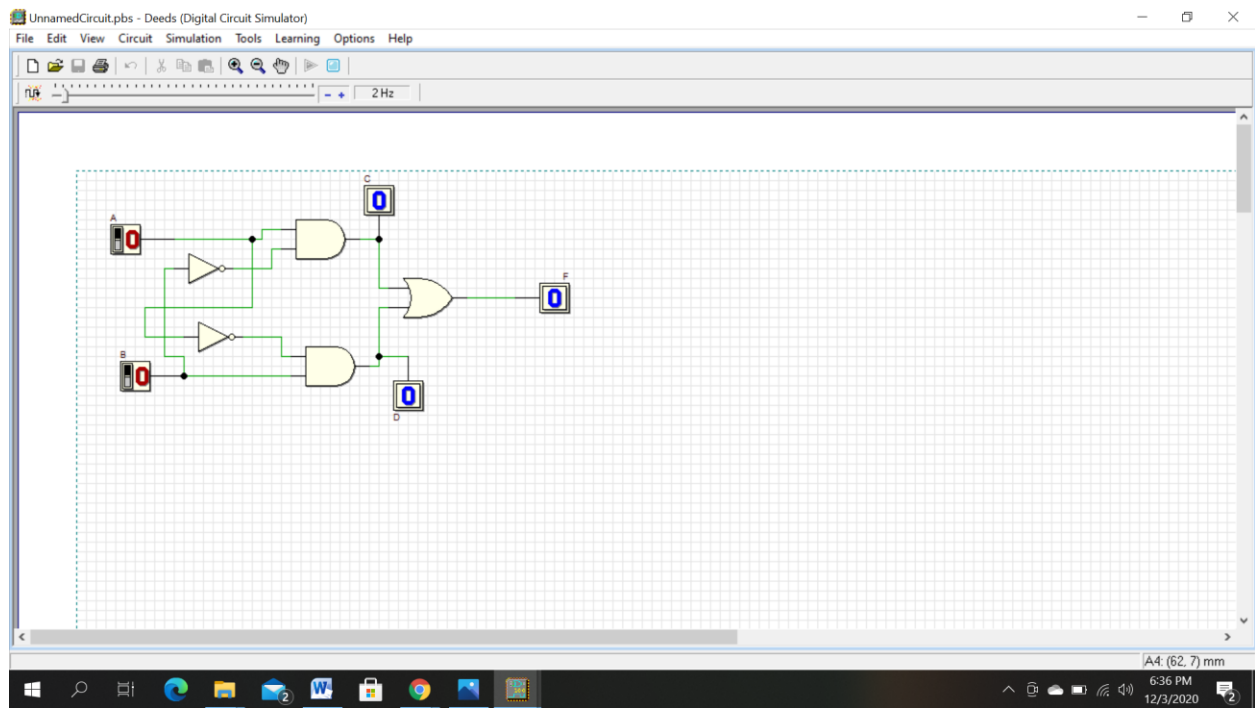

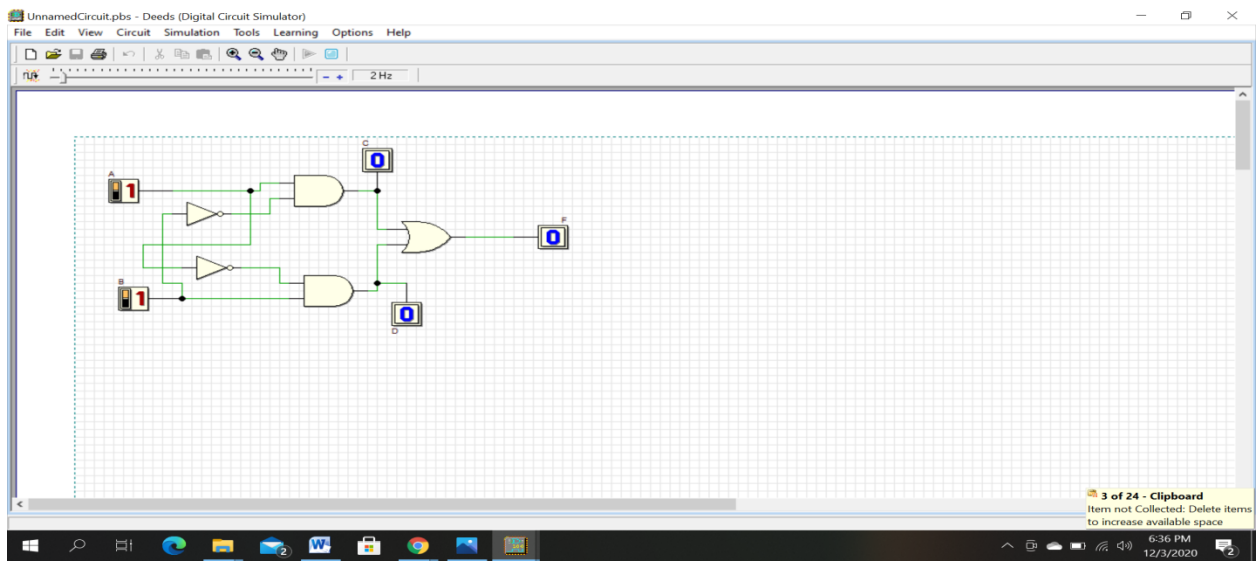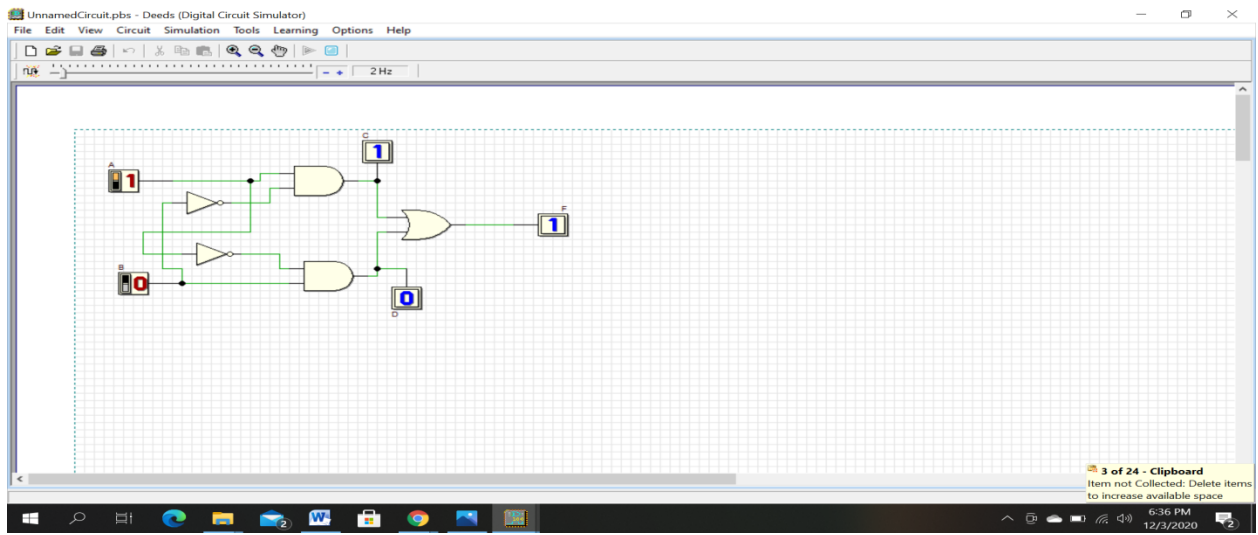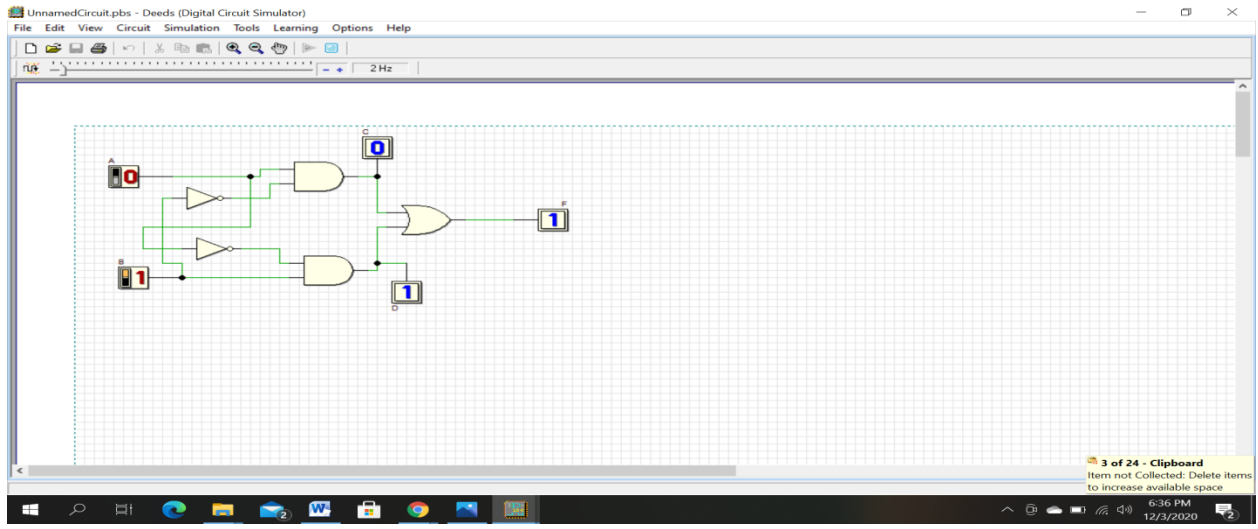


E-LABTORY WORK

PART-1

E- Laboratory work

Part 1

①

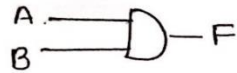

A	B	$F = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1


Truth table-5

②


The truth table 5 should match the truth table 1 prepared in the preliminary work.




So,
After use deeds, we can tell that,
The truth table 5 and table 1, both
are match. Both are same.

E.PART 1.1 WITH DEEDS SIMULATOR

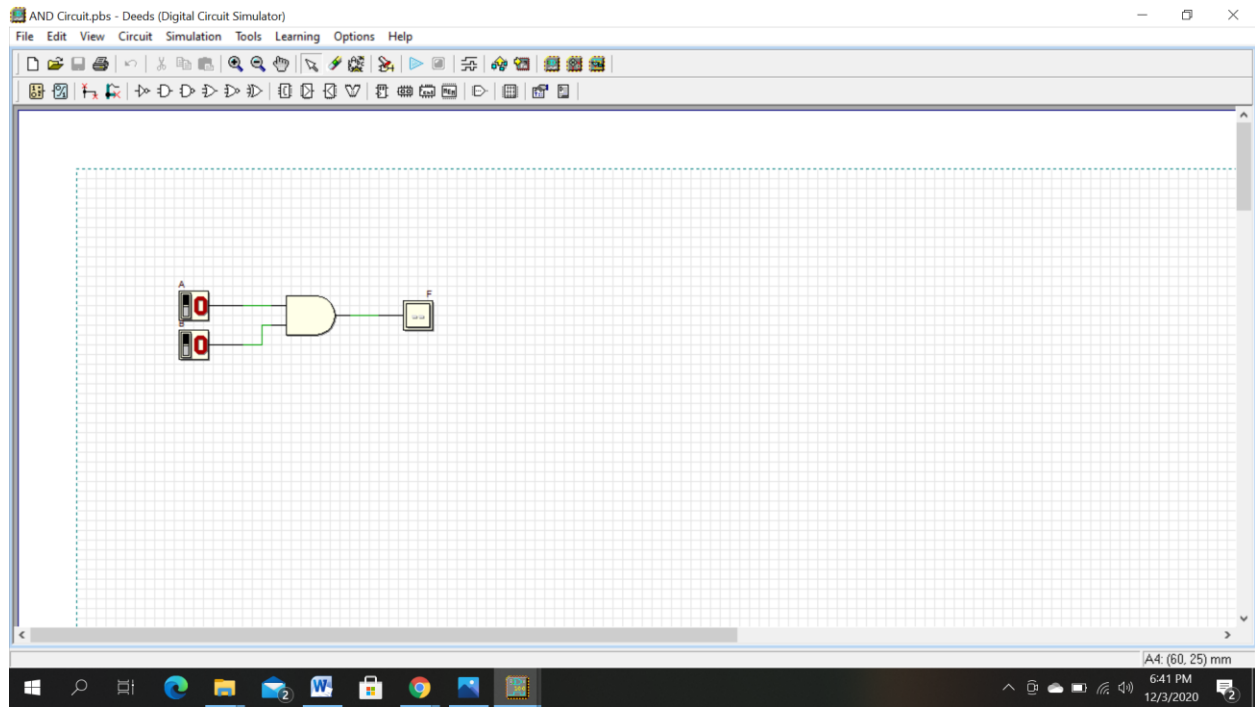

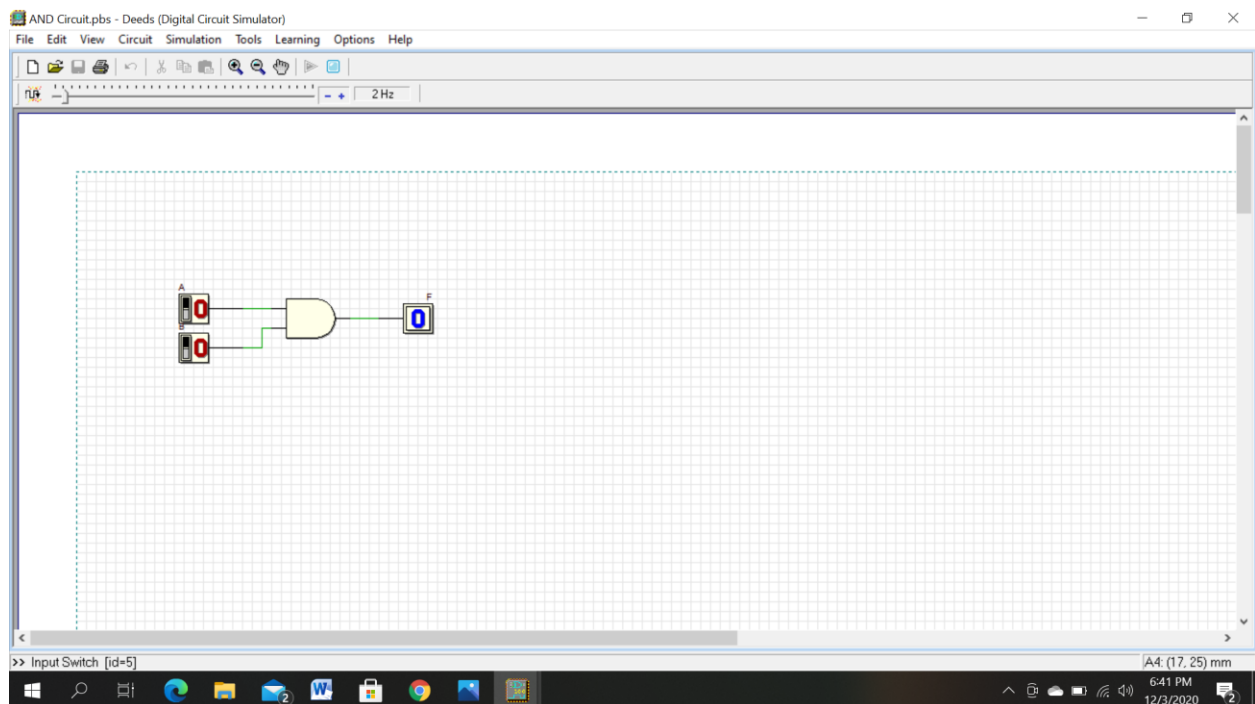- E-PART 1.2 TRUTH TABLE WITH DEEDS SIMULATOR




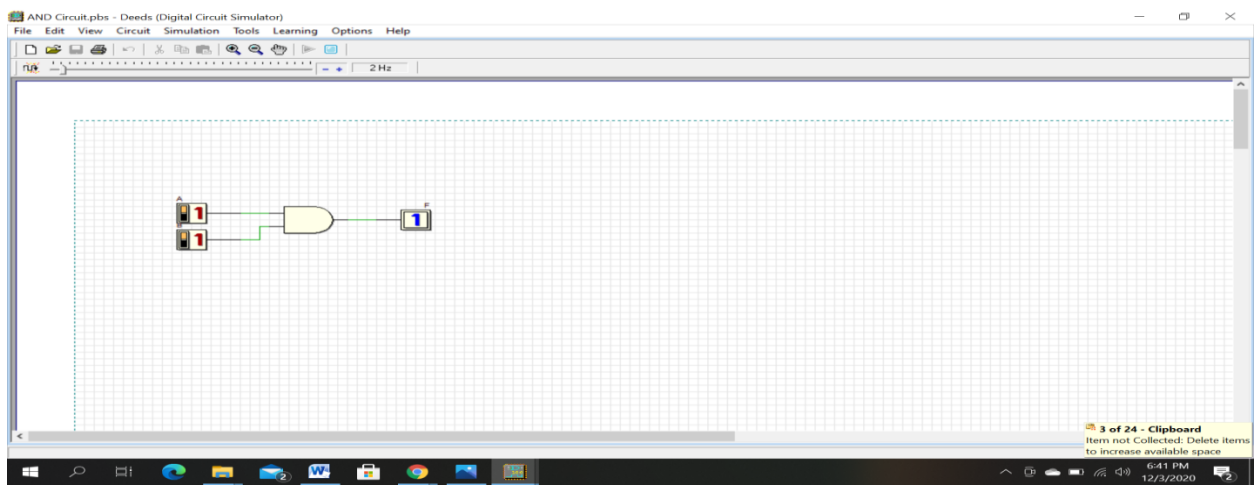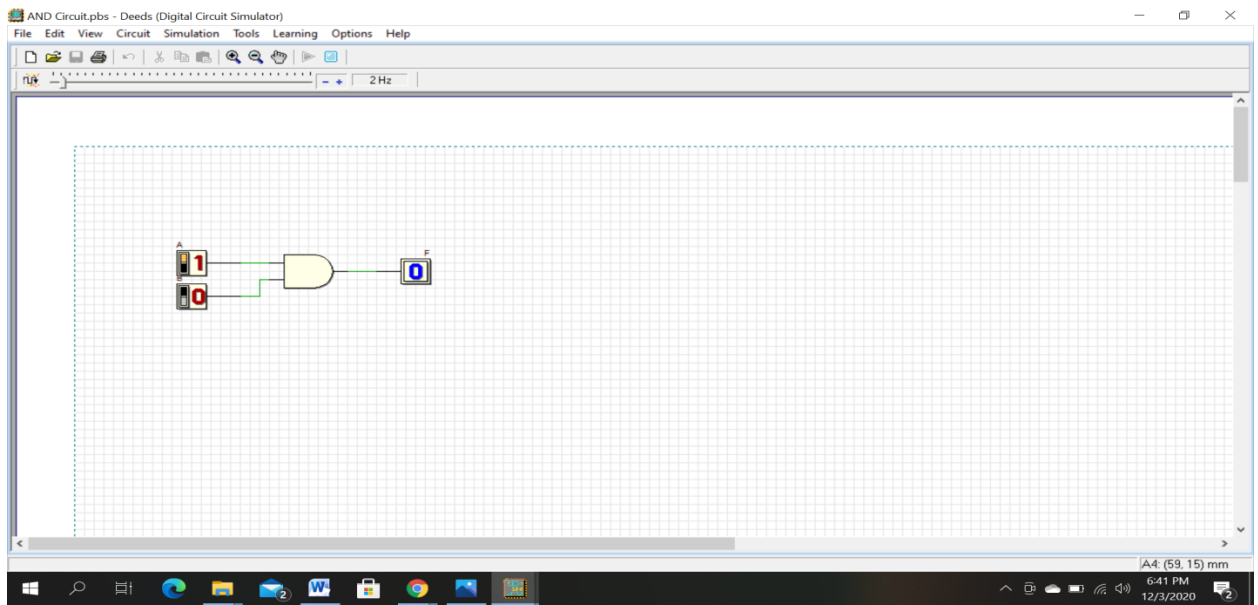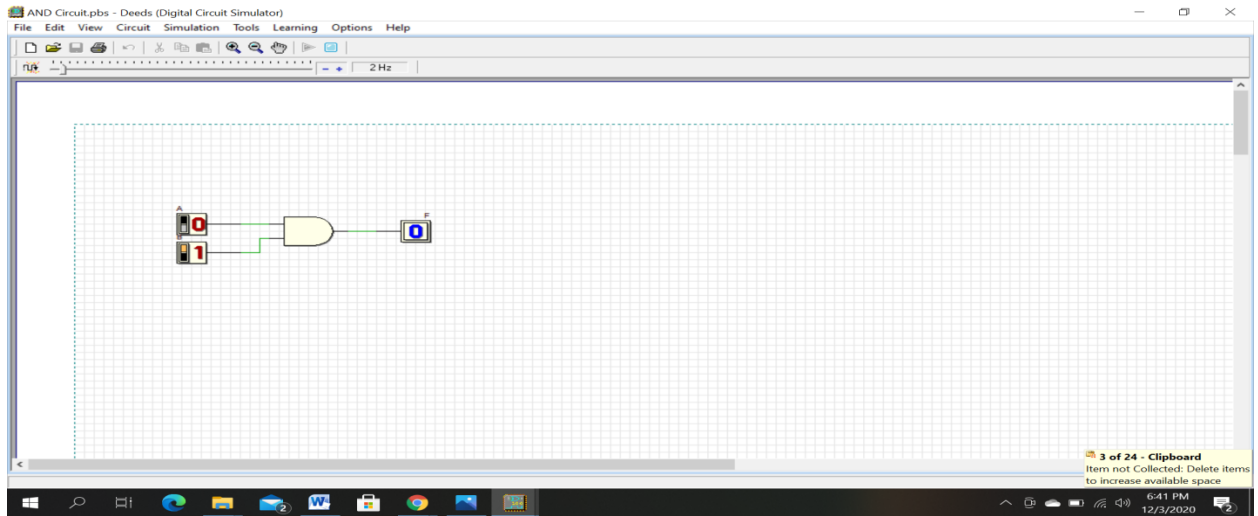

E.PART 2

Part-2

③.

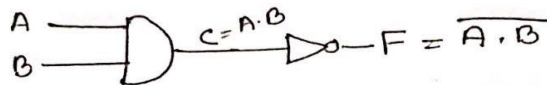

4


A	B	$C = A \cdot B$	$F = \overline{A \cdot B}$
0	0	0	$\overline{0} = 1$
0	1	0	$\overline{0} = 1$
1	0	0	$\overline{0} = 1$
1	1	1	$\overline{1} = 0$

Truth table-6


5




compare Truth table 6 to Truth table 2
both are same. both are NAND gate.

E.PART 2.3 WITH DEEDS SIMULATOR

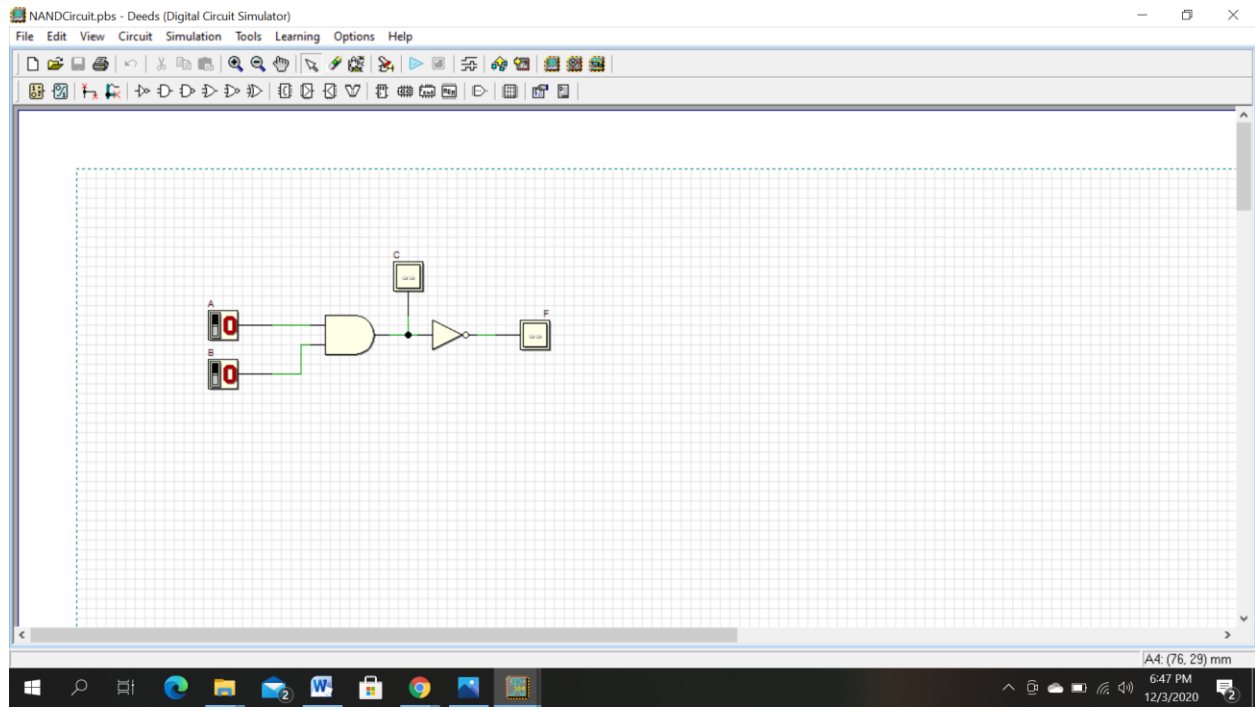

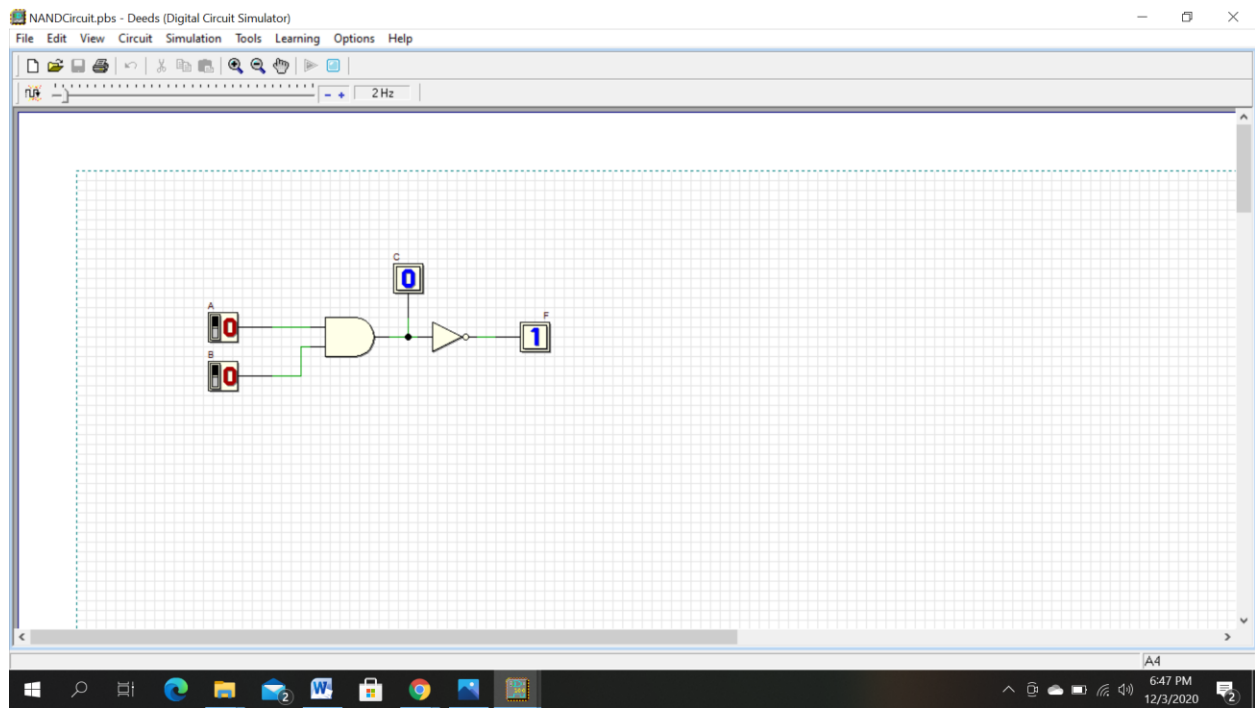
E.PART 2.4 *TRUTH TABLE WITH DEEDS SIMULATOR



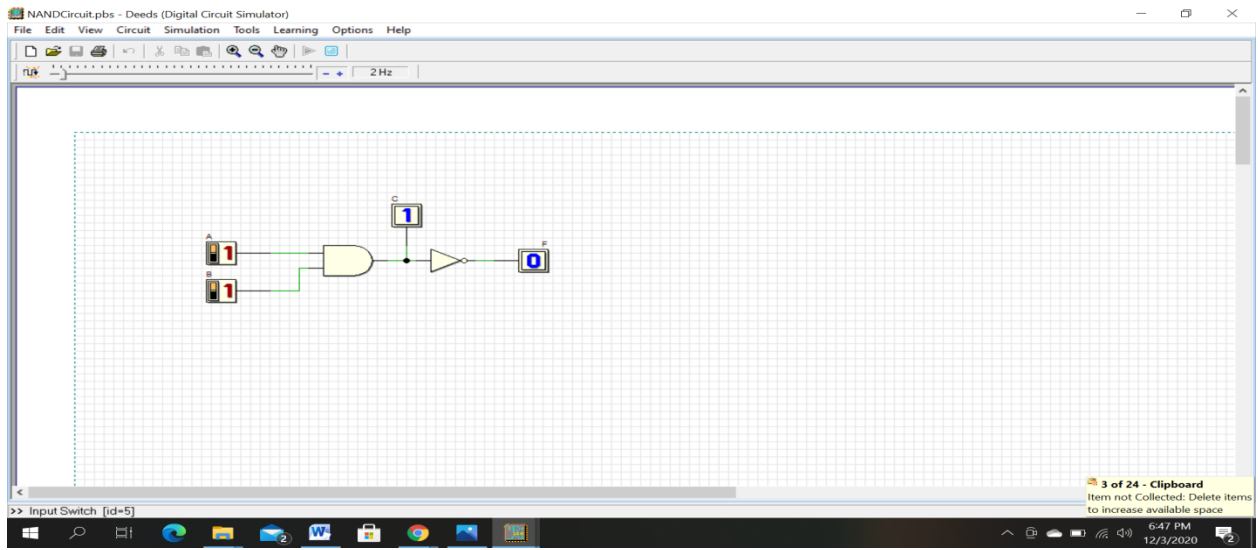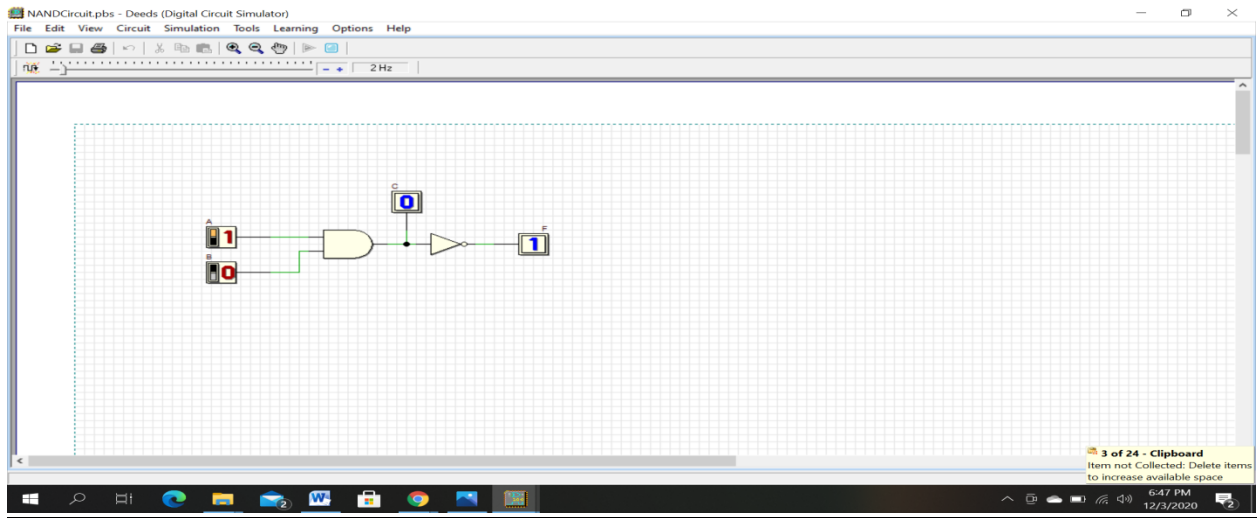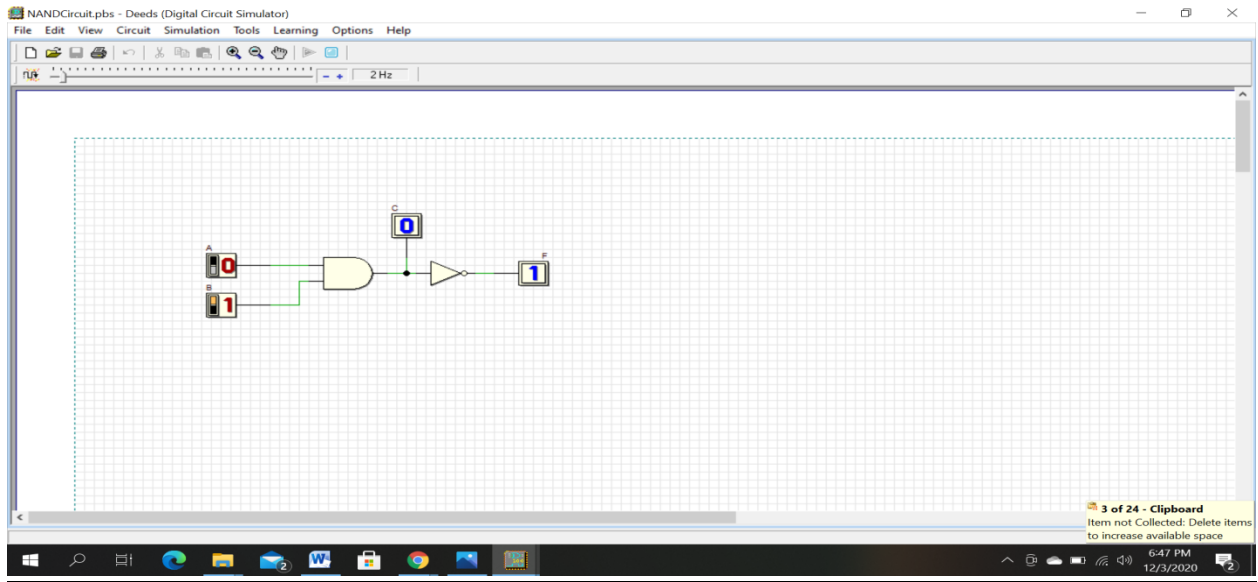

E.PART 3

Part-3

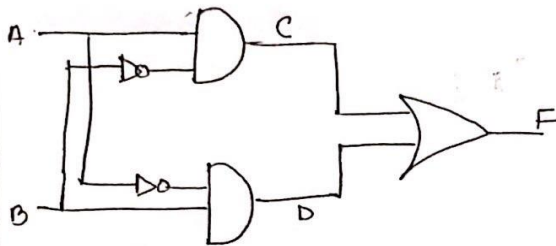

⑥

$$C = A \cdot \bar{B}$$

$$D = \bar{A} \cdot B$$


$$F = A \cdot \bar{B} + \bar{A} \cdot B$$

⑦

A	B	$C = A \cdot \bar{B}$	$D = \bar{A} \cdot B$	$F = A \cdot \bar{B} + \bar{A} \cdot B$
0	0	0	0	0
0	1	0	1	1
1	0	1	0	1
1	1	0	0	0

⑧ The single gate does circuit 3 represent "OR GATE".

E.PART 3.6 WITH DEEDS SIMULATOR

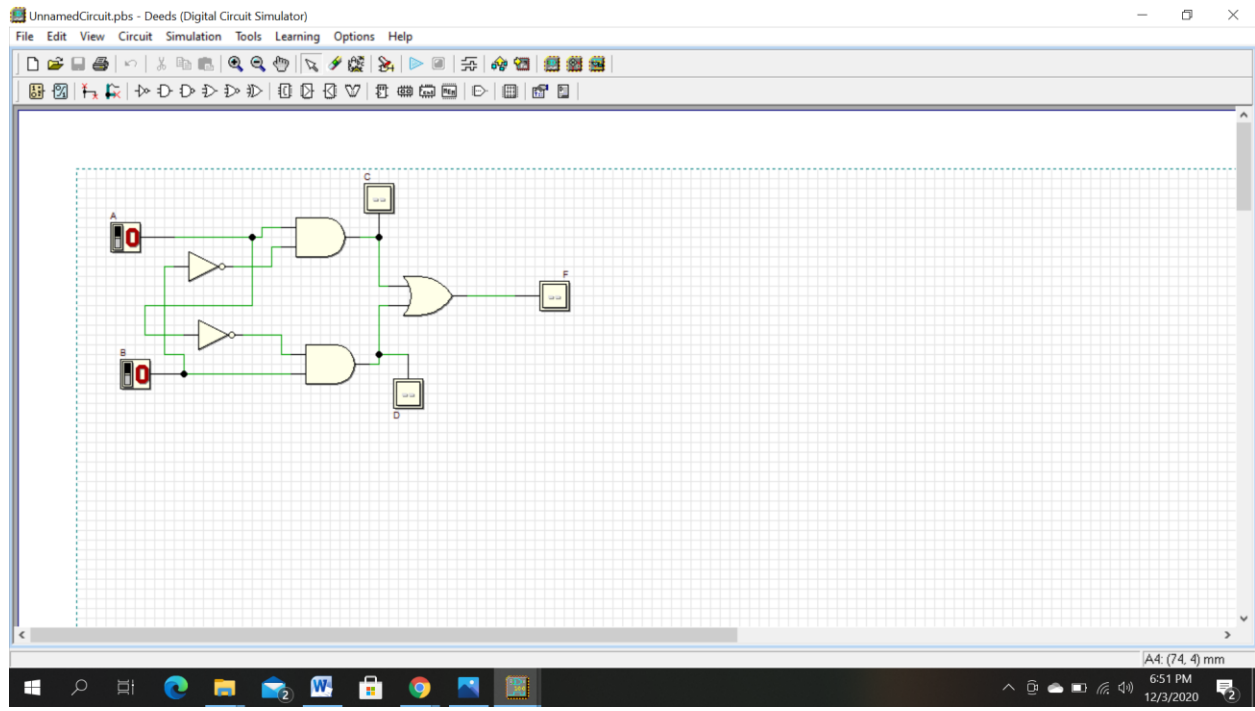

E.PART 3.7 *TRUTH TABLE WITH DEEDS SIMULATOR

