



UTM

UNIVERSITI TEKNOLOGI MALAYSIA

Semester 2020/2021

Subject : Digital logic

Section : 06

Task : Lab 1

Submission : 21/12/2020

Group member

Toya Lazmin Khan

A20EC0284

G M SHAHEEN SHAH SHIMON


A20EC0266

Lecturer: Dr. Yousuf

Preliminary work

1) AND

Symbol:

 


IC Number:7408

Truth table 1

Input		Output
A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

NAND

Symbol:

 

IC Number:7400

Truth table 2

Input		Output
A	B	F
0	0	1
0	1	1
1	0	1
0	0	0

2)

Truth table 3

A	B	C	F
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

- 3) $C = A.B'$
 $D = A'.B$
 $F = A.B' + A'.B$

4)


Truth table 4

A	B	C	D	F
0	0	0	0	0
0	1	0	1	1
1	0	1	0	1
1	1	0	0	0

Laboratory Work

Part 1

1)

 


2)

Truth table 5

Input		Output
A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

Part 2

3)

 

4)


Truth table 6


A	B	C	F
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

5) They have the same output

Part 3

6)

 

 

7)

Truth table 7

A	B	C	D	F
0	0	0	0	0
0	1	0	1	1
1	0	1	0	1
1	1	0	0	0

8) Inventor gate: negotiation of input.

AND gate: output is high when both inputs are high.

OR gate: output is false when both inputs are false.

