



Department of Computer Science
Faculty of Computing
UNIVERSITI TEKNOLOGI MALAYSIA

SUBJECT: SECR1013 DIGITAL LOGIC


SESSION/SEMESTER: 01/2020 2021

LAB 1: COMBINATIONAL LOGIC

NAME 1: YASSER EHAB MOHIELDIN FAHMY (A17CS3013)

NAME 2: SAYANG ELYIANA AMIERA BINTI HELMEY (A20EC0143)

3.

 

$$C = A \cdot \bar{B}$$

$$D = \bar{A} \cdot B$$

$$F = C + D$$


4. Truth Table 4

A	B	C	D	F
0	0	0	0	0
0	1	0	1	1
1	0	1	0	1
1	1	0	0	0


Laboratory Work:

Part 1:

1. Circuit 1

 

2.

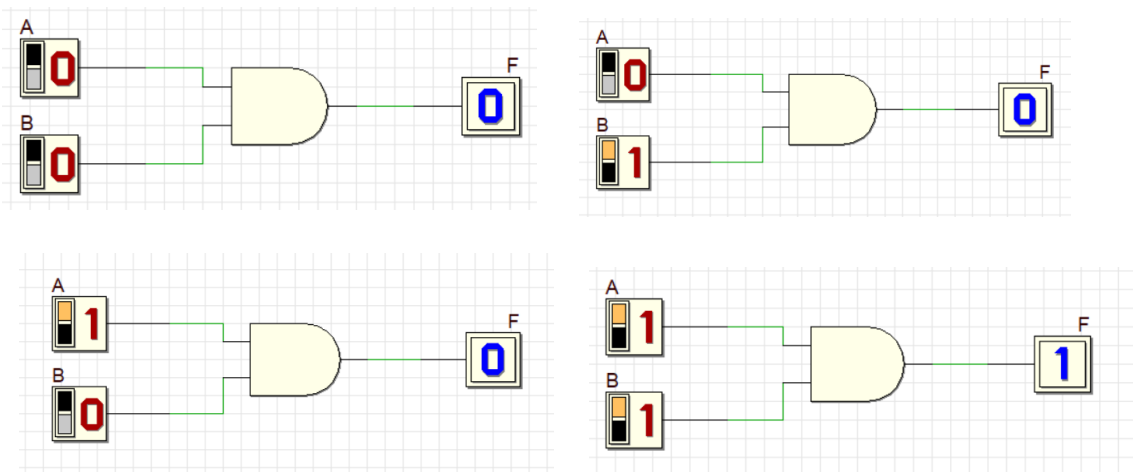


Truth Table 5





Input		Output
A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

Part 2:

3. Circuit 2

 

4. .

   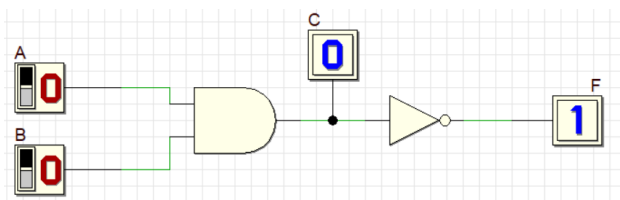


Truth Table 6

A	B	C	F
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0





5. Truth table 6 shows the inputs and outputs of the AND gate that is then connected to a NOT inverter (NOT-AND), this is the same as the outputs of truth table 2 which is a NAND gate. Thus, we can conclude that NOT-AND could be simplified as NAND.

Part 3:

6. Circuit 3

 


7.

    

Truth Table 7

A	B	C	D	F
0	0	0	0	0
0	1	0	1	1
1	0	1	0	1
1	1	0	0	0

8. Circuit 3 represents XOR gate

 

Truth table for XOR:

Input		Output
A	B	F
0	0	0
0	1	1
1	0	1
1	1	0