



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

SCHOOL OF COMPUTING
Faculty of Engineering

UNIVERSITI TEKNOLOGI MALAYSIA

SEMESTER 1, 2020/2021

LAB 2: COMBINATIONAL LOGIC CIRCUIT DESIGN SIMULATION

SUBJECT : SECR1013 DIGITAL LOGIC
SECTION : 02
NAME : ONG HAN WAH
MATRIC NO : A20EC0129
SCHOOL : SCHOOL OF COMPUTING
FACULTY : FACULTY OF ENGINEERING
LECTURER'S NAME : DR. NUR HALIZA BINTI ABDUL WAHAB

Lab Activities


Part 1

1.
$$Y = AB + BC + CA$$
$$= AB(C + \bar{C}) + BC(A + \bar{A}) + CA(B + \bar{B})$$
$$= ABC + AB\bar{C} + ABC + \bar{A}BC + ABC + A\bar{B}C$$
$$= ABC + AB\bar{C} + \bar{A}BC + A\bar{B}C$$


2.

Input			Output
A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

3. a)

 

3. b)

 

4.

Circuit (i)



Input			Output
A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Circuit (ii)

Input			Output
A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

The results are the same. Circuit (i) is equivalent to Circuit (ii).

5.

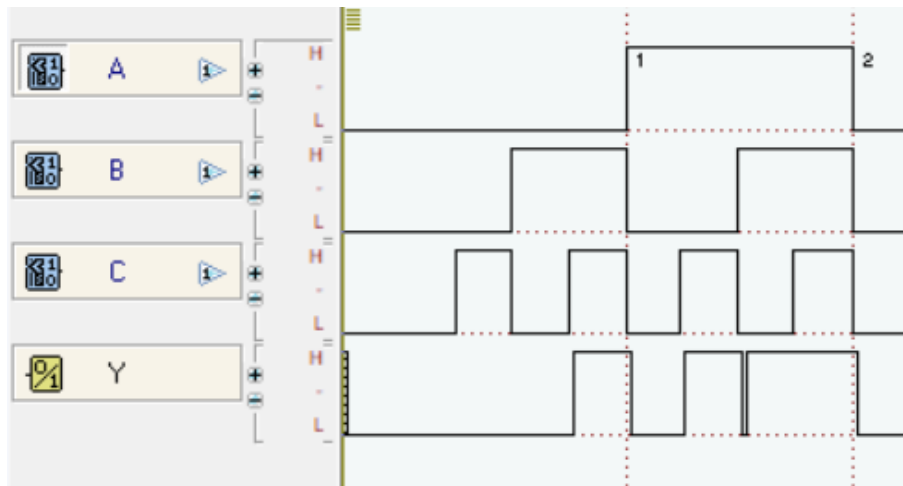 

Part 2

1. Truth Table 1

INPUTS				OUTPUTS			
A	B	C	D	E1	E2	E3	E4
0	0	0	0	0	1	0	0
0	0	0	1	1	0	0	0
0	0	1	0	0	1	0	0
0	0	1	1	X	X	X	X
0	1	0	0	0	1	0	0
0	1	0	1	X	X	X	X
0	1	1	0	X	X	X	X
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	0	1	X	X	X	X
1	0	1	0	X	X	X	X
1	0	1	1	0	0	1	0
1	1	0	0	X	X	X	X
1	1	0	1	0	0	1	0
1	1	1	0	0	0	0	1
1	1	1	1	0	0	1	0

2.

AB \ CD	CD			
	00	01	11	10
00		1	X	
01		X		X
11	X			
10		X		X

$$E1 = \bar{A}\bar{B}D$$

AB \ CD	CD			
	00	01	11	10
00	1		X	1
01	1	X		X
11	X			
10		X		X

$$E2 = \bar{A}\bar{D}$$


AB \ CD	CD			
	00	01	11	10
00			X	
01		X		X
11	X	1	1	
10		X	1	X

$$E3 = AD$$

AB \ CD	CD			
	00	01	11	10
00			X	
01		X		X
11	X			1
10		X		X

$$E4 = AC\bar{D}$$

3.

 


4. a) Truth Table 2

INPUTS				OUTPUTS			
A	B	C	D	E1	E2	E3	E4
0	0	0	0	0	1	0	0
0	0	0	1	1	0	0	0
0	0	1	0	0	1	0	0
0	0	1	1	1	0	0	0
0	1	0	0	0	1	0	0
0	1	0	1	0	0	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	0	0	1
1	0	1	1	0	0	1	0
1	1	0	0	0	0	0	0
1	1	0	1	0	0	1	0
1	1	1	0	0	0	0	1
1	1	1	1	0	0	1	0


The output results are the same except for don't cares. It can be used to represent the circuit.

4. b)

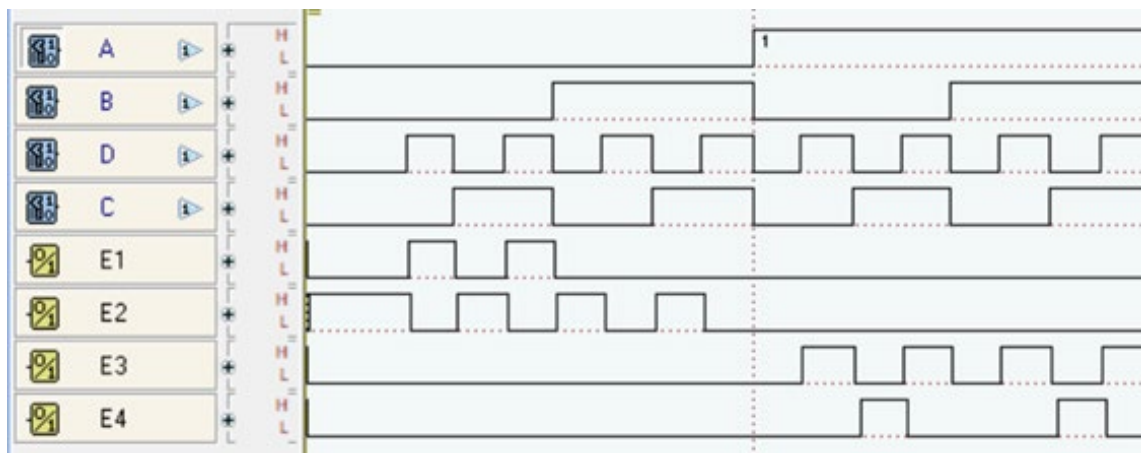

E1 and E2 are high only when A is high. E3 and E4 are high only when A is low.

5.

 


6. a) Truth Table 3

INPUTS				OUTPUTS			
A	B	C	D	E1	E2	E3	E4
0	0	0	0	0	1	0	0
0	0	0	1	1	0	0	0
0	0	1	0	0	1	0	0
0	0	1	1	1	0	0	0
0	1	0	0	0	1	0	0
0	1	0	1	0	0	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	0	0	1
1	0	1	1	0	0	1	0
1	1	0	0	0	0	0	0
1	1	0	1	0	0	1	0
1	1	1	0	0	0	0	1
1	1	1	1	0	0	1	0

The output results are the same. NAND gate is a universal gate which can perform the function of basic gates and used to implement any logic circuits.

6. b)

 

When ABCD=0001, it is equivalent to 1, thus E1 is high because it is positive odd and the majority of the bits is '0'.

When ABCD=1110, it is equivalent to -1, thus E4 is high because it is negative even and the majority of the bits is '1'.