



**School of Computing**  
**Faculty of Engineering**  
**UNIVERSITI TEKNOLOGI MALAYSIA**

**SUBJECT** : **SECR1013** **DIGITAL** **LOGIC**

**SESSION/SEM** : **20202021/1**

**LAB 3** : **SYNCHRONOUS** **DIGITAL** **COUNTER**

**NAME** : YASSER EHAB MOHIELDIN

SAYANG ELYIANA AMIERA BINTI HELMEY

### Lab #3

#### A. Preliminary Works

- 1) Determine the logic level for each input combinations in Table 1 so that the desired result can be realized.

Table 1

Desired Result	$\overline{PRE}$	$\overline{CLR}$	J	K	CLK	Q
Set initial value Q = 1	0	1	X	X	--	1
Output Q stays the same	1	1	0	0	↓	1
Output Q become 0, no change in asynchronous input	1	1	0	1	↓	0
Output Q is not the previous Q	1	1	1	1	↓	1
RESET Q	1	1	0	1	↓	0
SET Q	1	1	1	0	↓	1

- 2) Answer all questions.

- a) Which state that JK flip-flop has, but not on SR flip-flop.


When both the input J & K are 1, Jk flip-flop has a toggle state which Sr flip-flop does not have.

- b) Identify whether the JK flip flop in 7476, is a positive-edge triggered or negative-edge triggered flip flop.

It is a negative edge triggered flip-flop.


## B. Lab Activities

1) You are given a counter circuit as shown in Figure 4.

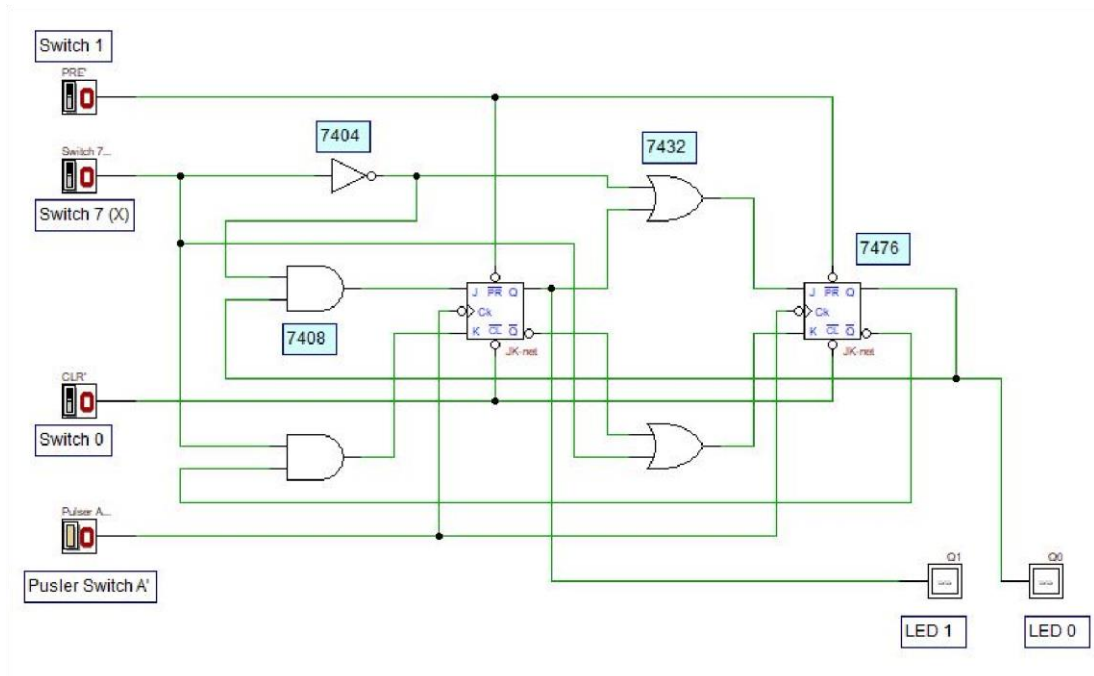

**Figure 4: A Synchronous Counter Circuit**

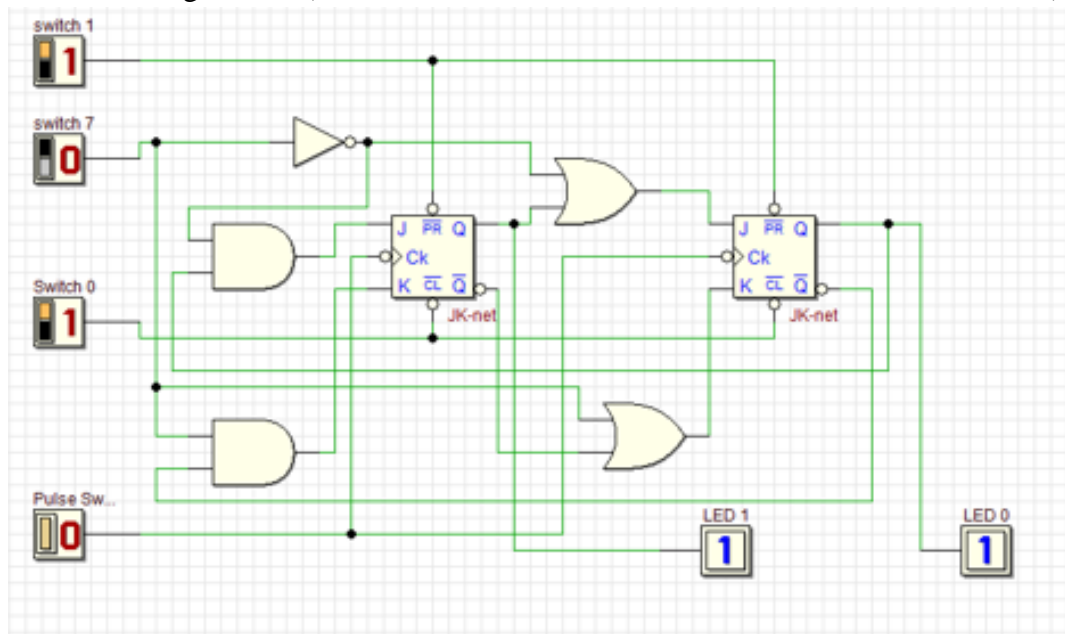2) By using all materials and equipment's listed in section C, construct the physical circuit of Figure 4. (Make sure all ICs are connected to Vcc and GND).




- 3) Investigate the behavior of the counter by observing the next state of the counter for all combination of *Present State* and *X* values. Complete the *NextState* table of the counter in Table 2. Ensure the Switch 0 is in HIGH state.  
(0=LOW, 1=HIGH)

**Table 2**

Switch 7	Present State		Next State	
X	Q1 LED 1	Q0 LED 0	Q1 LED 1	Q0 LED 0
0	0	0	0	1
0	0	1	1	0
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	0	1
1	1	1	1	0

 - 4) By referring to the *Next-State* in Table 2, sketch the state diagram of the counter.



- 5) By referring to the *Next-State* in Table 2 and the state diagram in (4), answer all questions.

- a) What is the main indicator to decide that the counter is a synchronous counter?

It uses clock inputs to synchronize the circuit operation and all clock are from the same source.

- b) How many states are available for the counter and what are they?

4 states : 00, 01, 11, 01

- c) What is the function of Switch 7 (X) in the circuit?

As clock input

- d) What is the function of Switch 0 and Switch 1 in the circuit?

As positive or negative edge (CLK)

- e) Is the counter a saturated counter or recycle counter?

Saturated counter

6) Referring to state diagram in 4, draw and built a synchronous counter using D flip-flop.

a) Built the next state and transition table using the header in Table 3

Table 3

Input X	Present State		Next State		D FF Transition	
	Q1	Q0	Q1+	Q0+	D1	D0
0	0	0	0	1	0	1
1	0	0	0	0	0	0
0	0	1	1	0	1	0
1	0	1	0	0	0	0
0	1	0	1	1	1	1
1	1	0	0	1	0	1
0	1	1	1	1	1	1
1	1	1	1	0	1	0

b) Get the optimized Boolean expression.

D1:

Q1 \ Q0X	00	01	11	10
0				1
1	1		1	1

$$D1 = Q1Q0 + Q1\bar{X} + Q0\bar{X}$$

$$D1 = Q1(Q0 + \bar{X}) + Q0\bar{X}$$


D0:

Q1 \ Q0X	00	01	11	10
0	1			
1	1	1		1

$$D0 = Q1\bar{Q0} + \bar{Q1}\bar{X} + \bar{Q0}\bar{X}$$

$$D0 = Q1(\bar{Q0} + \bar{X}) + \bar{Q0}\bar{X}$$

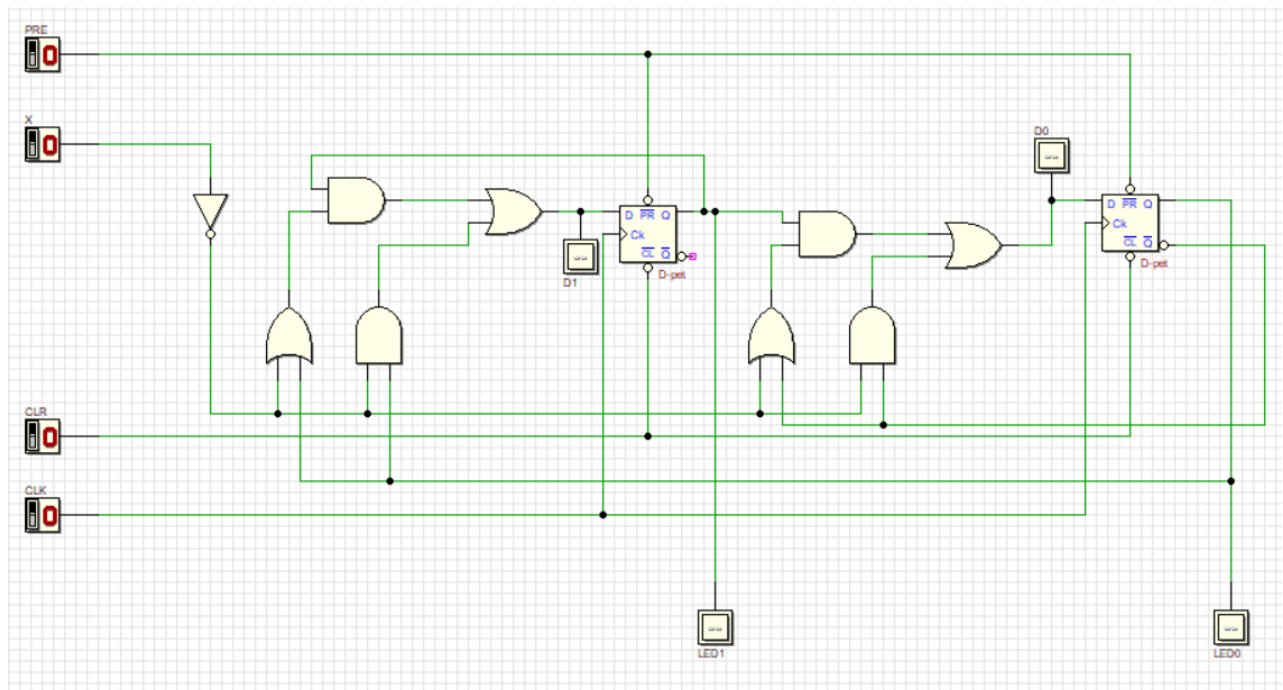- c) Draw the complete final circuit design in Deeds.  
d) Simulate the circuit to prove that your Table 3 is correct.



7) Repeat steps in Q(6) using T flip-flop.

Input X	Present State		Next State		T FF Transition	
	Q1	Q0	Q1+	Q0+	T1	T0
0	0	0	0	1	0	1
1	0	0	0	0	0	0
0	0	1	1	0	1	1
1	0	1	0	0	0	1
0	1	0	1	1	0	1
1	1	0	0	1	1	1
0	1	1	1	1	0	0
1	1	1	1	0	0	1

T1:

Q1 \ Q0X	00	01	11	10
0	0	0	0	1
1	0	1	0	0

$$T1 = \overline{Q0}XQ1 + Q0\overline{X}Q1$$

T0:

Q1 \ Q0X	00	01	11	10
0	1	0	1	1
1	1	1	1	0

$$T0 = \overline{Q1}\overline{X} + Q1Q0 + Q0X$$

