
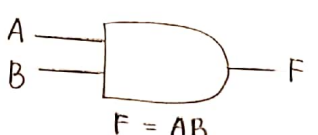
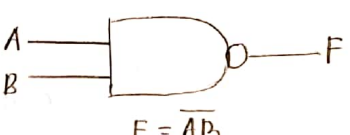


**D. Preliminary Work**

1. Draw a symbol, determine the IC number and produce a truth table for the following gate.

<u>AND</u>	<u>NAND</u>																																				
<p>Symbol:</p>  <p style="text-align: center;"><math>F = AB</math></p> <p>IC Number: ..... 7408 .....</p> <p style="text-align: center;">Truth Table 1</p> <table border="1" style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th colspan="2">Input</th> <th>Output</th> </tr> <tr> <th>A</th> <th>B</th> <th>F</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	Input		Output	A	B	F	0	0	0	0	1	0	1	0	0	1	1	1	<p>Symbol:</p>  <p style="text-align: center;"><math>F = \overline{AB}</math></p> <p>IC Number: ..... 7400 .....</p> <p style="text-align: center;">Truth Table 2</p> <table border="1" style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th colspan="2">Input</th> <th>Output</th> </tr> <tr> <th>A</th> <th>B</th> <th>F</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	Input		Output	A	B	F	0	0	1	0	1	1	1	0	1	1	1	0
Input		Output																																			
A	B	F																																			
0	0	0																																			
0	1	0																																			
1	0	0																																			
1	1	1																																			
Input		Output																																			
A	B	F																																			
0	0	1																																			
0	1	1																																			
1	0	1																																			
1	1	0																																			

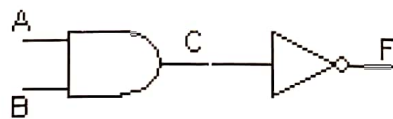
2. Complete the truth table for the following circuit.



Truth Table 3

A	B	C	F
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

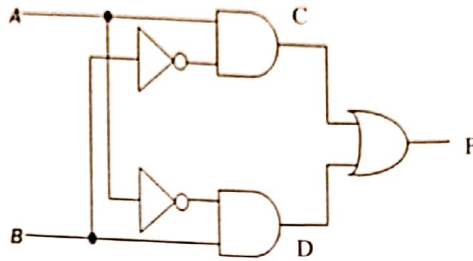3. Write the Boolean expression for output C, D and F the following circuit.



$$C = A \text{ and NOT } B$$

$$D = B \text{ and NOT } A$$

$$F = (A \text{ and NOT } B) \text{ or } (B \text{ and NOT } A)$$

4. Complete the truth table for the circuit in (3) based on the Boolean expression produced for C, D and F.

Truth Table 4

A	B	C	D	F
0	0	0	0	0
0	1	0	1	1
1	0	1	0	1
1	1	0	0	0


## E. Laboratory Work

### Part 1

- Construct Circuit 1 on the breadboard. Connect all inputs (A, B) to a switches and output F to LEDs.

Truth Table 5

Input		Output
A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

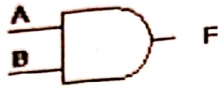

Circuit 1

- Test Circuit 1 and fill in Truth Table 5 for the circuit response to all possible input combinations. The Truth Table 5 should match the Truth Table 1 prepared in the Preliminary Work.



Fully Completed


Partially Completed

Checked by: \_\_\_\_\_

### Part 2

- Construct Circuit 2 on the breadboard. Connect all inputs (A, B) to a switches and output C and F to LEDs.

Truth Table 6

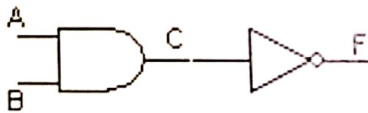

Circuit 2

A	B	C	F
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

- Test Circuit 2; fill in Truth Table 6, for the circuit response to all possible input combinations.

- Compare Truth Table 6 to Truth Table 2. What conclusion can you make?

Table 2 invert the output in one way, but in table 6 there are two output, which is before invert and after inverted.




Fully Completed

Partially Completed

Checked by: \_\_\_\_\_

**Part 3**

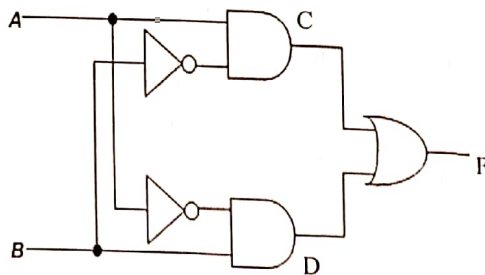6. Construct circuit 3 on the breadboard. Connect all inputs (A, B) to a switches and output C, D and F to LEDs.



Truth Table 7

A	B	C	D	F
0	0	0	0	0
0	1	0	1	1
1	0	1	0	1
1	1	0	0	0

Circuit 3

7. Test Circuit 3; fill in Truth Table 7 for the circuit outputs (C, D, and F) for all possible input combinations.
8. What single gate does Circuit 3 represent?

NAND gate.



Fully Completed

Partially Completed

Checked by: \_\_\_\_\_