


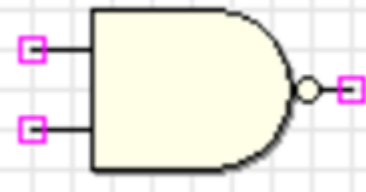
Digital Logic Lab 1

Huda Najihah binti Ahmad Asri (A20EC0045)


Saidah binti Saiful Bahari (A20EC0141)

D. Preliminary Work

1. Draw a symbol, determine the IC number and produce a truth table for the following gate.

<u>AND</u>			<u>OR</u>		
Symbol:			Symbol:		
					
IC Number: 7408			IC Number: 7400		
Truth Table 1			Truth table 2		
INPUT		OUTPUT	INPUT		OUTPUT
A	B	F	A	B	F
0	0	0	0	0	0
0	1	0	0	1	1
1	0	0	1	0	1
1	1	1	1	1	1

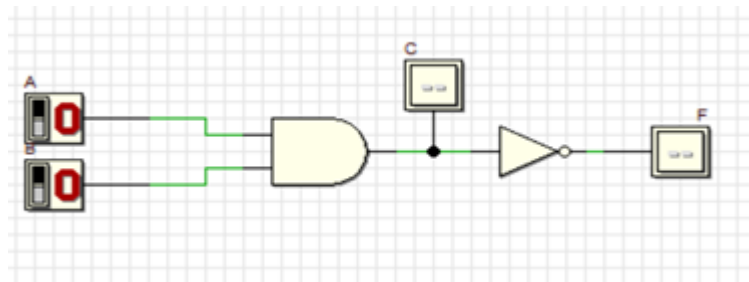2. Complete the truth table for the following circuit




<p>1.</p>	<p>2.</p>
<p>3.</p>	<p>4.</p>

Truth Table 3

A	B	C	F
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

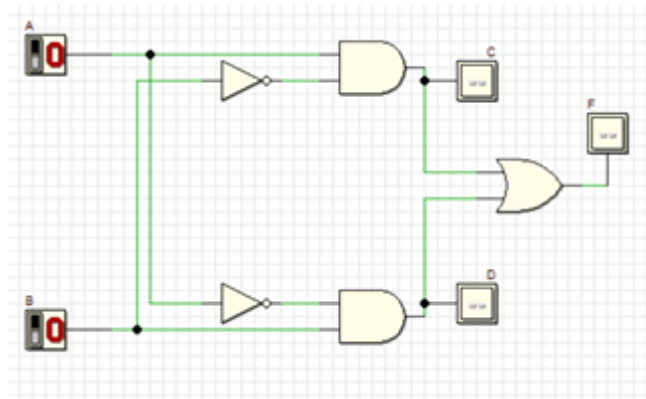3. Write the Boolean expression for output C, D and F the following circuit.




$$C = A * B'$$

$$D = A' * B$$

$$F = C + D$$

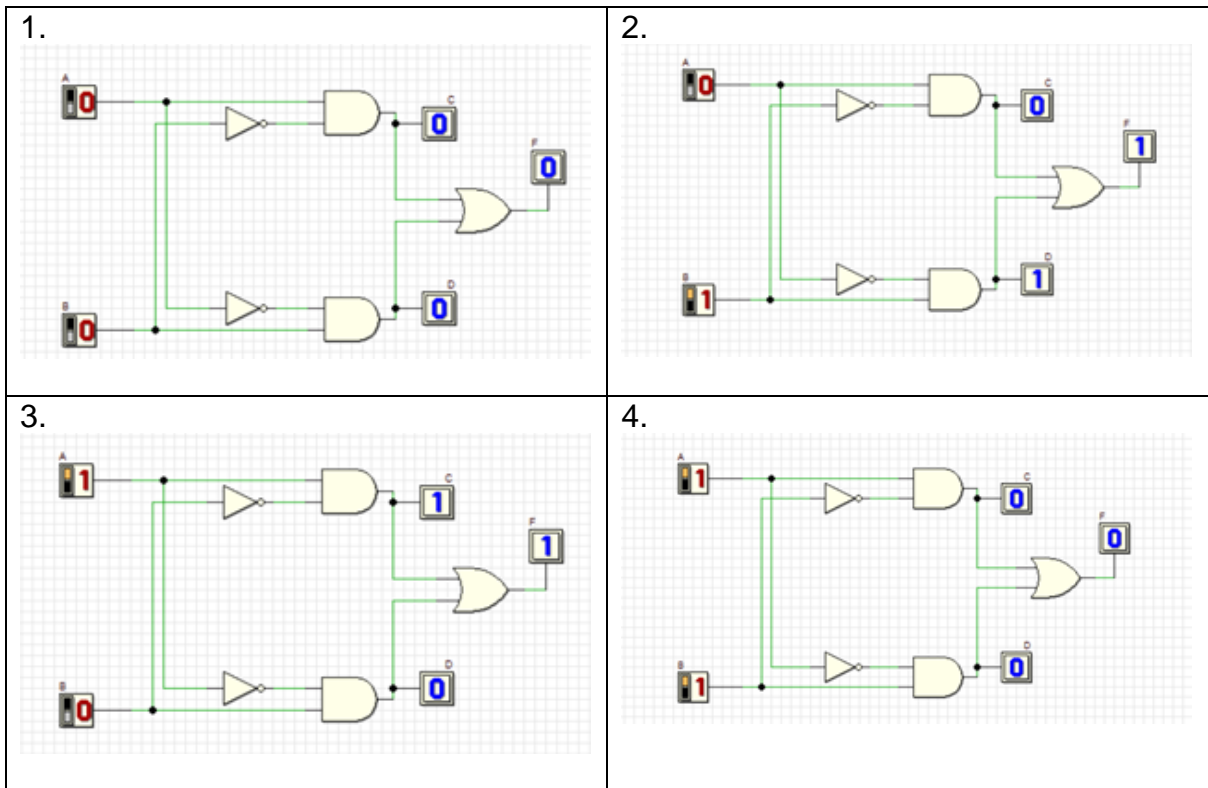4. Complete the truth table for the circuit in (3) based on the Boolean expression produced for C, D and F.




Truth Table 4

A	B	C	D	F
0	0	0	0	0
0	1	0	1	1
1	0	1	0	1
1	1	0	0	0

E. Laboratory Work

Part 1

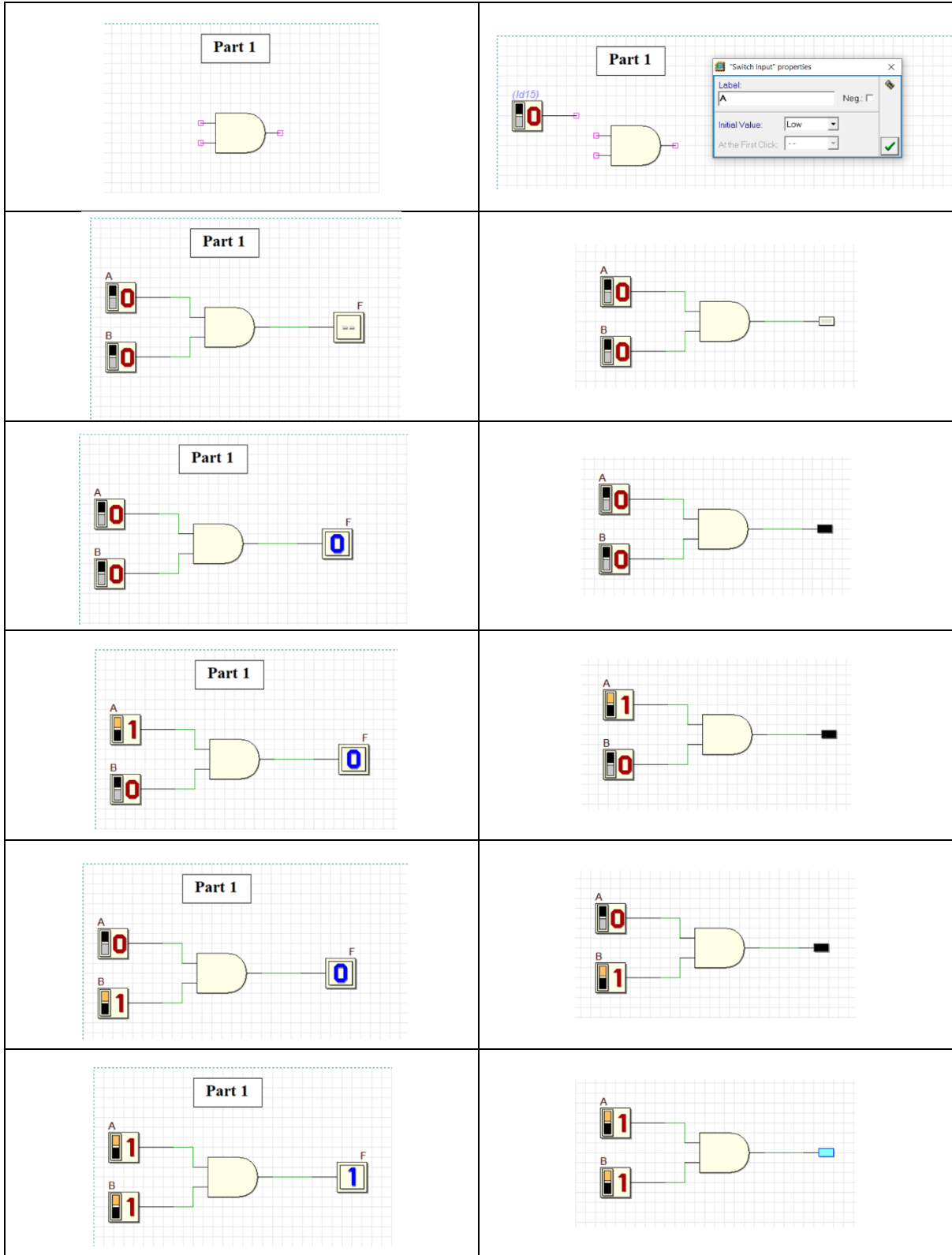1. Construct Circuit 1 on the breadboard. Connect all inputs (A, B) to a switches and output F to LEDs.




2. Test Circuit 1 and fill in Truth table 5 for the circuit response to all possible input combinations. The Truth Table 5 should match the Truth Table 1 prepared in the Preliminary Work.


Input		Output
A	B	C
0	0	F
0	1	F
1	0	F
1	1	F

Truth Table 5

Part 2

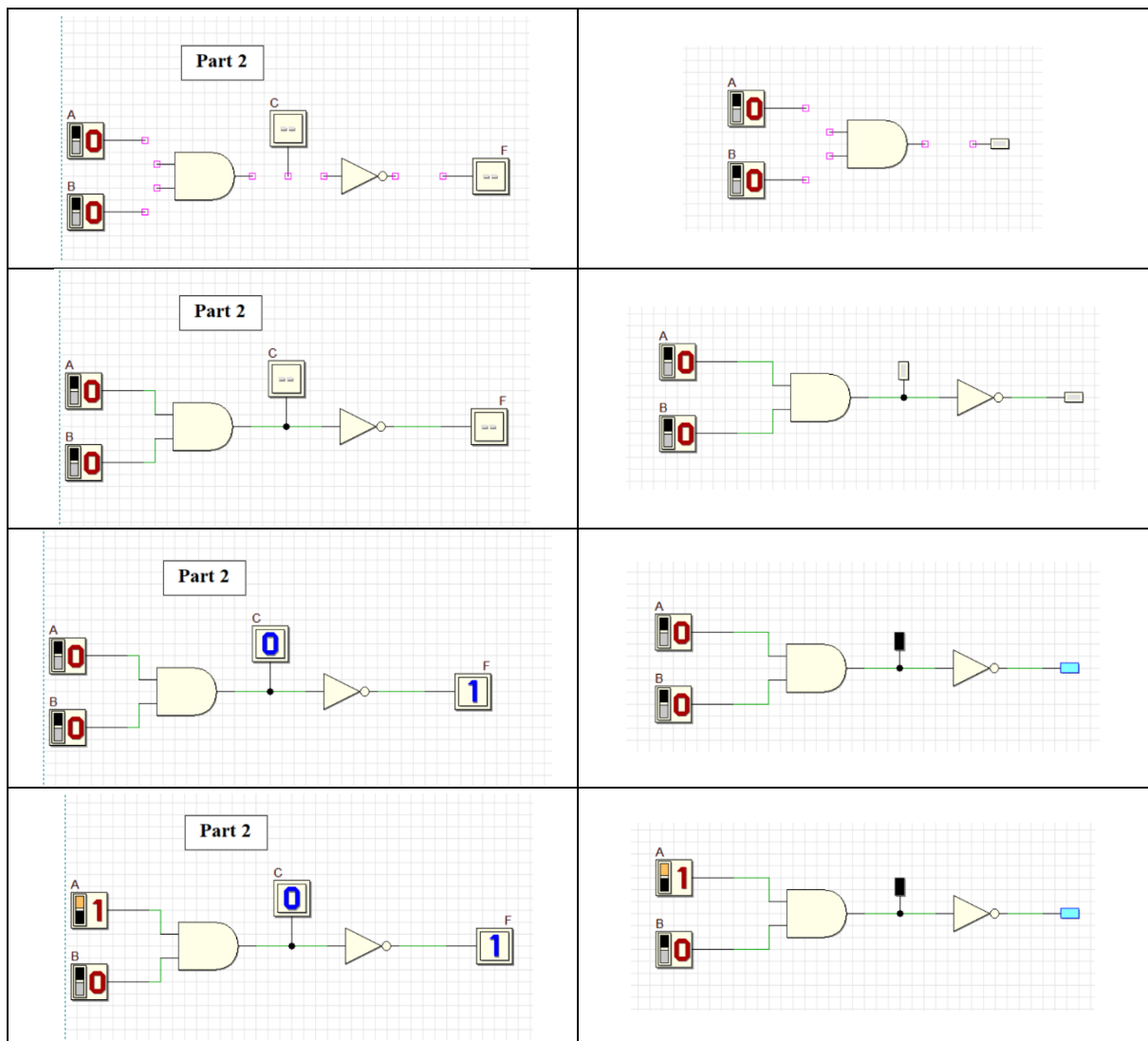3. Construct Circuit 2 on the breadboard. Connect all inputs (A, B) to a switches and output C and F to LEDs.



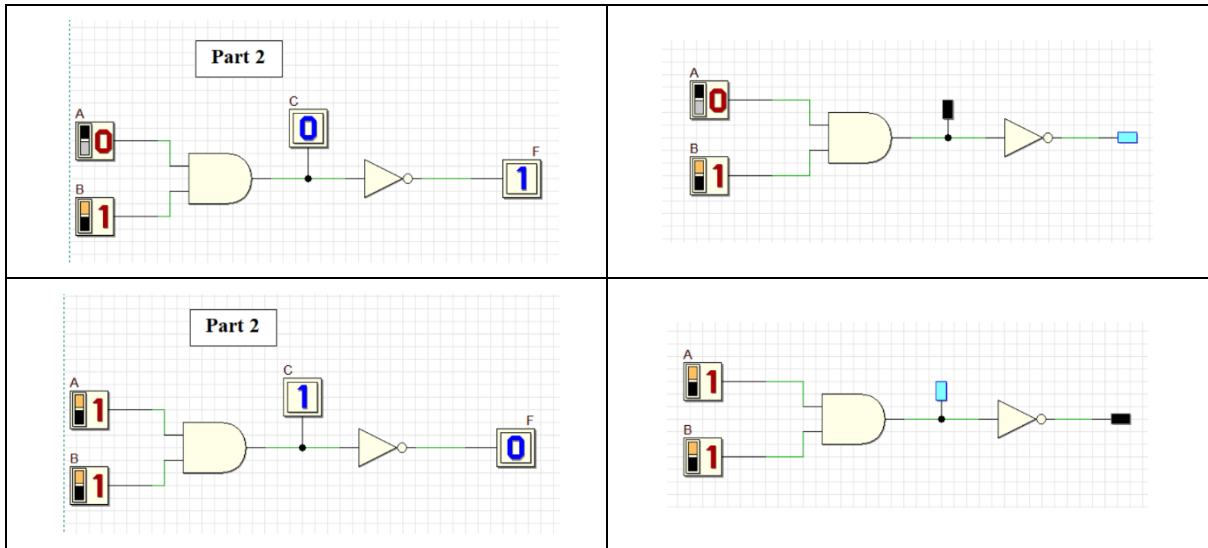

4. Test Circuit 2; fill in Truth Table 6, for the circuit response to all possible input combinations.


Input		Output	
A	B	C	F
0	0	F	T
0	1	F	T
1	0	F	T
1	1	T	F


Truth Table 6

5. Compare Truth Table 6 to Truth Table 2. What conclusion can you make?

Part 3

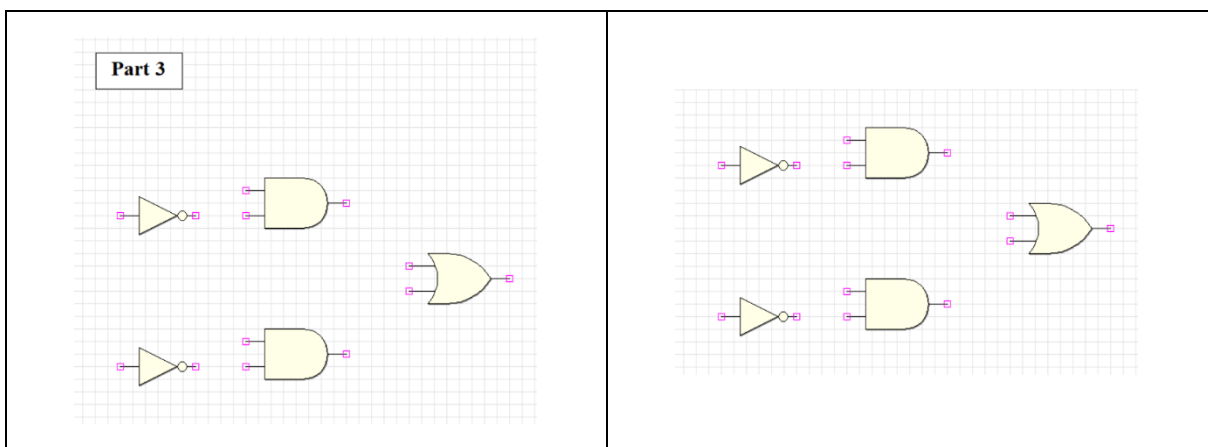6. Construct circuit 3 on the breadboard. Connect all inputs (A, B) to a switches and output C, D and F to LEDs.



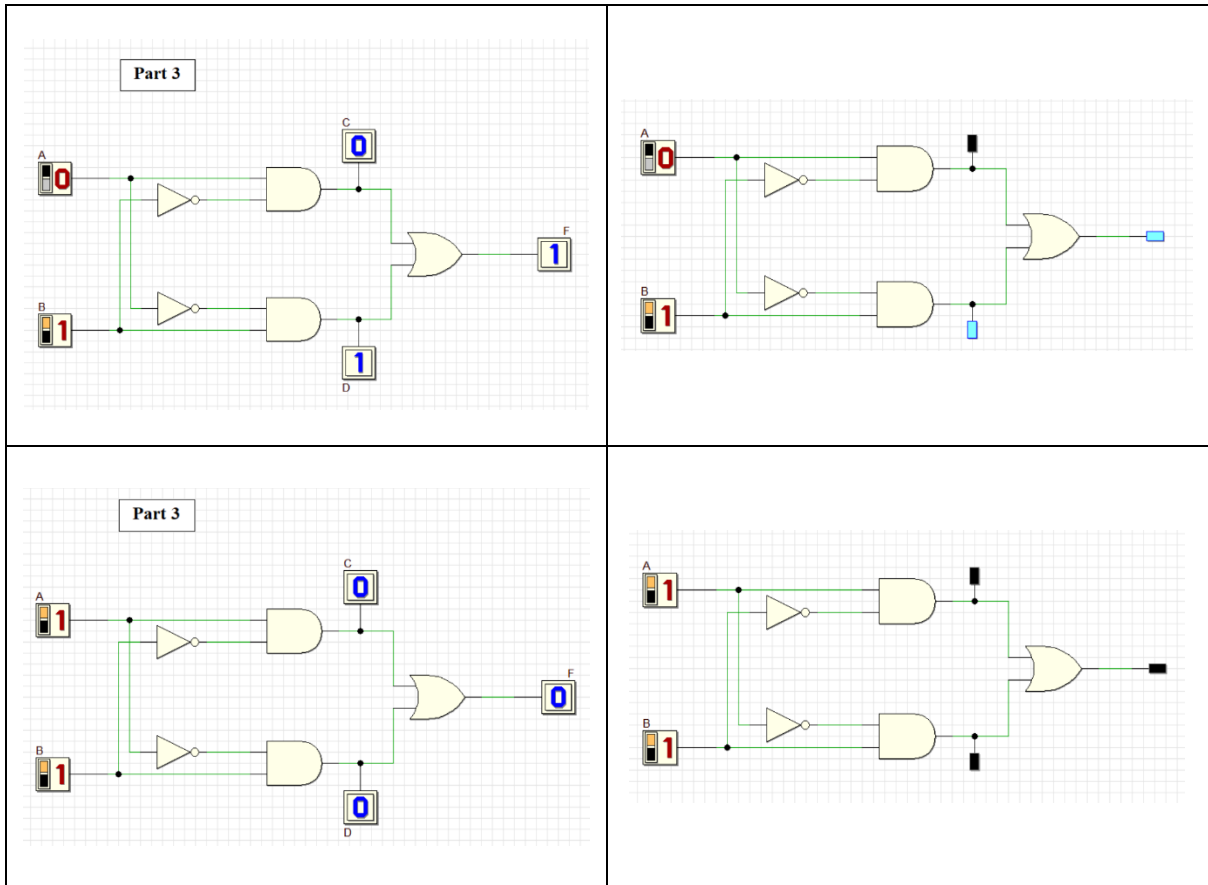

7. Test Circuit 3; fill in the truth Table 7 for the circuit outputs (C, D, and F) for all possible input combinations.

Input		Output		
A	B	C	D	F
0	0	F	F	F
0	1	T	F	T
1	0	F	T	T
1	1	F	F	F

Truth Table 7

8. What single gate does Circuit 3 represent?

Circuit 3 represent XOR gate