



**School of Computing
Faculty of Engineering
UNIVERSITI TEKNOLOGI MALAYSIA**

SUBJECT : SECR1013 DIGITAL LOGIC

SESSION/SEM : 2020/2021 / SEM1

LAB 3 : SYNCHRONOUS DIGITAL COUNTER

NAME : Lee Jia Xian A20EC0200

DATE : 28/1/2021

D. Preliminary Works

- 1) Determine the logic level for each input combinations in Table 1 so that the desired result can be realized.

Table 1

Desired Result	$\overline{PRE}$	$\overline{CLR}$	J	K	CLK	Q
Set initial value Q = 1	0	1	X	X	--	1
Output Q stays the same	1	1	0	0	↓	1
Output Q become 0, no change in asynchronous input	1	1	1	1	↓	0
Output Q is not the previous Q	1	1	1	1	↓	1
RESET Q	1	1	0	1	↓	0
SET Q	1	1	1	0	↓	1

- 2) Answer all questions.

- a) Which state that JK flip-flop has, but not on SR flip-flop.

In JK flip-flop when both input is equal to 1, the output Q will be toggle. But on SR flip-flop when both input state is equal 1 it is an invalid state. So, we can say that JK flip-flop has a toggle state when both input is equal to 1, but SR flip-flop don't have because it is an invalid state.

- b) Identify whether the JK flip flop in 7476, is a positive-edge triggered or negative-edge triggered flip flop.

Negative-edge triggered flip-flop because the synchronous input change when meet the negative clock edge.

E. Lab Activities

- 1) You are given a counter circuit as shown in Figure 4.


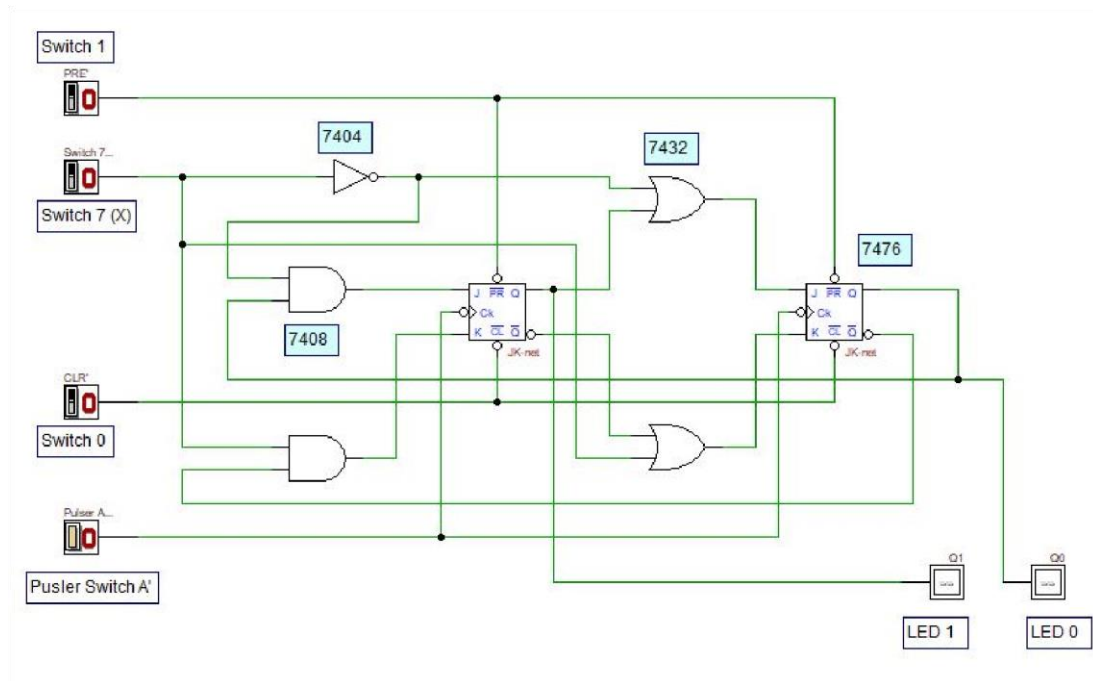


Figure 4: A Synchronous Counter Circuit

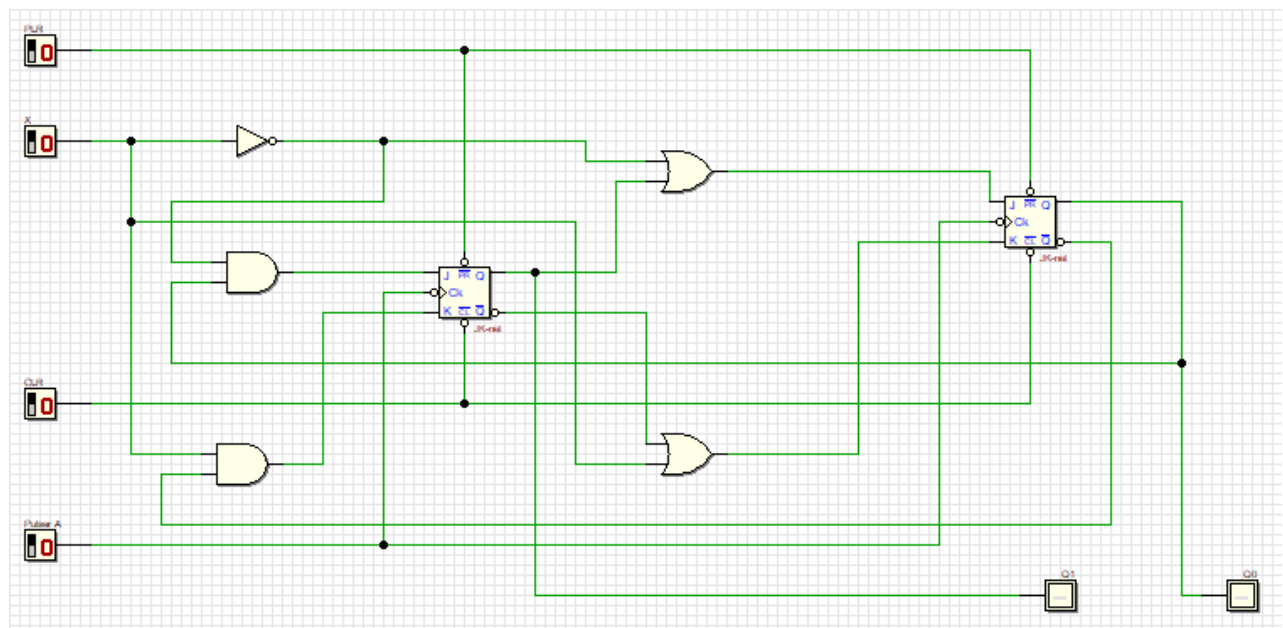- 2) By using all materials and equipment's listed in section C, construct the physical circuit of Figure 4. (Make sure all ICs are connected to Vcc and GND).




- 3) Investigate the behaviour of the counter by observing the next state of the counter for all combination of *Present State* and *X* values. Complete the *NextState* table of the counter in Table 2. Ensure the Switch 0 is in HIGH state.
(0=LOW, 1=HIGH)

Table 2

Switch 7	Present State		Next State	
X	Q1 LED 1	Q0 LED 0	Q1 LED 1	Q0 LED 0
0	0	0	0	1
0	0	1	1	0
0	1	0	1	1
0	1	1	1	1
1	0	0	0	0
1	0	1	0	0
1	1	0	0	1
1	1	1	1	0

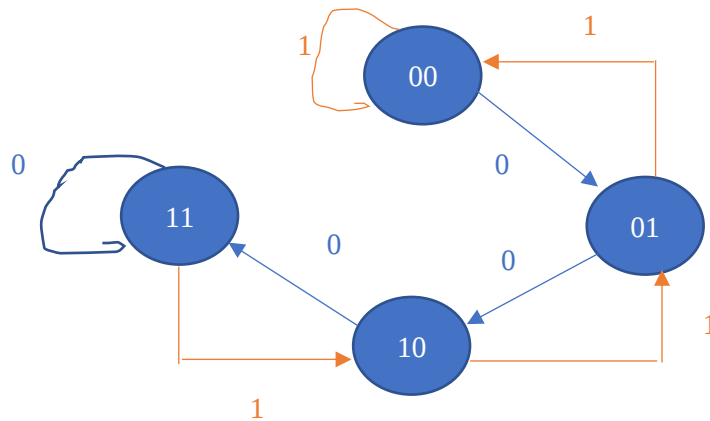4) By referring to the *Next-State* in Table 2, sketch the state diagram of the counter.



5) By referring to the *Next-State* in Table 2 and the state diagram in (4), answer all questions.

a) What is the main indicator to decide that the counter is a synchronous counter?

The state of PLE' and CLR'. When the state of PLE' and CLR' is equal to 1 then the counter will be a synchronous counter.

b) How many states are available for the counter and what are they?

4 states : 00, 01, 10, 11

c) What is the function of Switch 7 (X) in the circuit?

Act as an input mode selector to select the counter to be up counter (when $x=0$) or down counter (when $x=1$)

d) What is the function of Switch 0 and Switch 1 in the circuit?

Switch 1 act as preset, PRE' to set initial value of 1 to the output.
Switch 0 act as clear, CLR' to reset the output to 0.

e) Is the counter a saturated counter or recycle counter?

Saturated counter

6) Referring to state diagram in 4, draw and built a synchronous counter using D flip-flop.

a) Built the next state and transition table using the header in Table 3

Table 3

Input X	Present State		Next State		D FF Transition	
	Q1	Q0	Q1+	Q0+	D1	D0
0	0	0	0	1	0	1
0	0	1	1	0	1	0
0	1	0	1	1	1	1
0	1	1	1	1	1	1
1	0	0	0	0	0	0
1	0	1	0	0	0	0
1	1	0	0	1	0	1
1	1	1	1	0	1	0

b) Get the optimized Boolean expression.

K-map for D1:

		Q1Q0			
		00	01	11	10
X	0	0	1	1	1
	1	0	0	1	0


$$D1 = X'Q0 + X'Q1 + Q1Q0$$

K-map for D0:

		Q1Q0			
		00	01	11	10
X	0	1	0	1	1
	1	0	0	0	1

$$D0 = X'Q0' + X'Q1 + Q1Q0'$$

 - c) Draw the complete final circuit design in Deeds.



- d) Simulate the circuit to prove that your Table 3 is correct.

Table 4

Input X	Present State		Next State		D FF Transition	
	Q1	Q0	Q1+	Q0+	D1	D0
0	0	0	0	1	0	1
0	0	1	1	0	1	0
0	1	0	1	1	1	1
0	1	1	1	1	1	1
1	0	0	0	0	0	0
1	0	1	0	0	0	0
1	1	0	0	1	0	1
1	1	1	1	0	1	0

Since Table 3 and Table 4 show the same output, we proved that Table 3 is correct

- 7) Repeat steps in Q(6) using T flip-flop.
 a) Built the next state and transition table.

Table 5

Input X	Present State		Next State		T FF Transition	
	Q1	Q0	Q1+	Q0+	T1	T0
0	0	0	0	1	0	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	0	0
1	0	0	0	0	0	0
1	0	1	0	0	0	1
1	1	0	0	1	1	1
1	1	1	1	0	0	1

- b) Get the optimized Boolean expression.

K-map for T1:

		Q1Q0			
		00	01	11	10
X	0	0	1	0	0
	1	0	0	0	1


$$T1 = X'Q1'Q0 + XQ1Q0'$$

K-map for T0:

		Q1Q0			
		00	01	11	10
X	0	1	1	0	1
	1	0	1	1	1

$$T0 = (X' + Q1 + Q0)(X + Q1' + Q0')$$

 c) Draw the complete final circuit design in Deeds.



d) Simulate the circuit to prove that your Table is correct.

Table 6

Input X	Present State		Next State		T FF Transition	
	Q1	Q0	Q1+	Q0+	T1	T0
0	0	0	0	1	0	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	0	0
1	0	0	0	0	0	0
1	0	1	0	0	0	1
1	1	0	0	1	1	1
1	1	1	1	0	0	1

Since Table 5 and Table 6 show the same output, we proved the table 5 is correct.